

EECS 242: BJT High Frequency Distortion


**Professor Ali M Niknejad
Advanced Communication Integrated Circuits**

University of California, Berkeley




High Frequency Distortion in BJTs

Meyer:

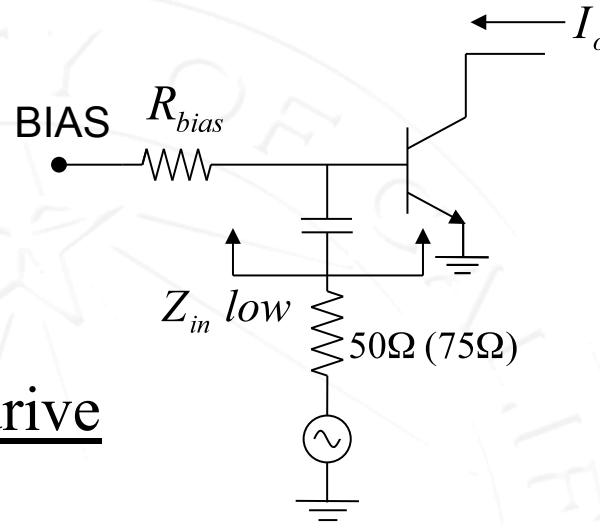

Assume current drive

Large Circuit Equivalent Circuit:

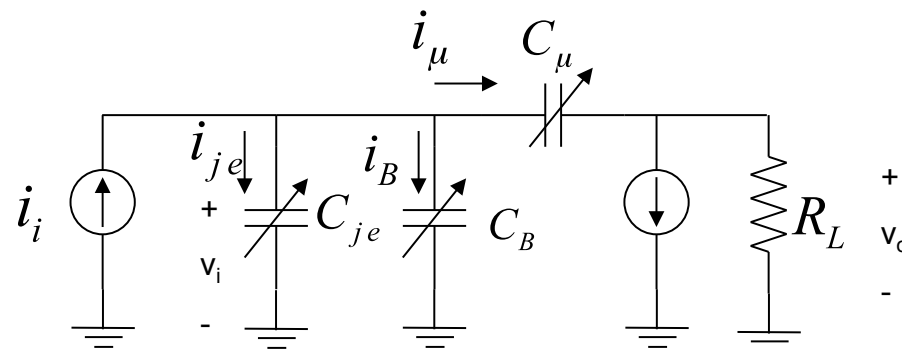

$$i_c = I_Q \left(e^{v_1/V_T} - 1 \right)$$

neglect


$$r_\pi, r_b, r_o$$

Distortion Due to Diffusion Capacitor

C_B is a non-linear diffusion capacitor

$$C_B = C_\pi - C_{je}$$
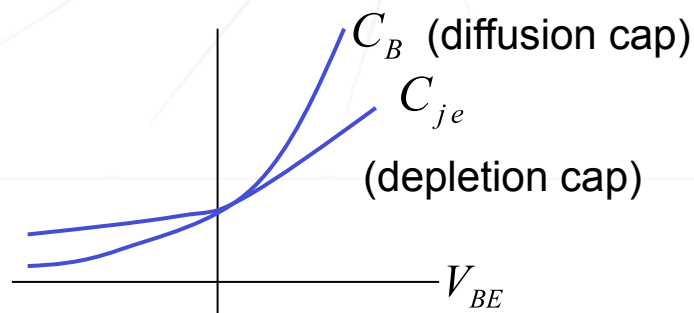
$$Q_B = \tau_F I_C \quad C_B = \frac{dQ_B}{dV_{BE}} = \tau_F \frac{dI_C}{dV_{BE}} = \tau_F \frac{qI_C}{kT} = \tau_F \frac{I_S}{V_T} e^{V_{BE}/V_T}$$



C_{je} is emitter -base depletion capacitor

Assume constant


$$C_{je} \propto \frac{1}{(\varphi + V_{BE})^n}$$

If f_T of a BJT is constant with I_C , then we have no high frequency distortion in the device for current drive and $C_B \gg C_{je}$

$$i_i = \tau_F \frac{di_c}{dt}$$

\Rightarrow Linear Differential Equation
 f_T constant $\Rightarrow \tau_F$ constant

Kirk Effect

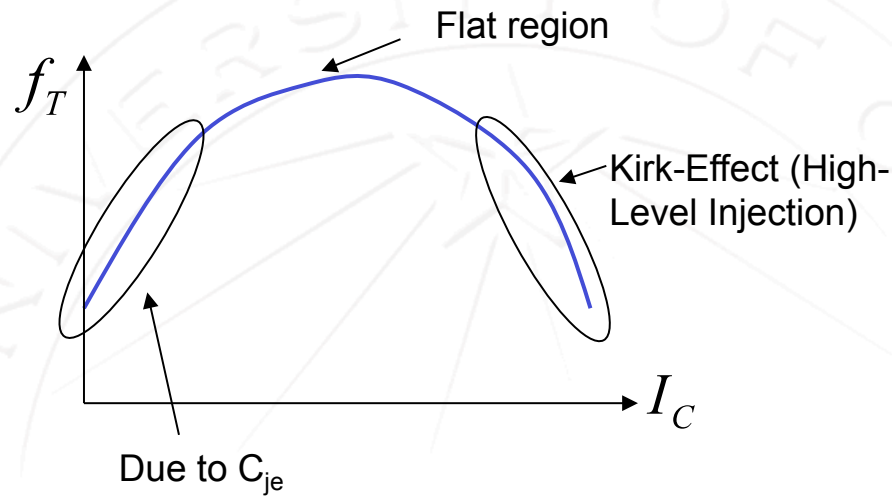

$$i_C = I_C - I_Q = I_Q (e^{v_1/V_T} - 1)$$

$$i_i = i_x + i_b + i_\mu$$

$$= C_{je} \frac{dv_1}{dt} + \frac{dQ_B}{dt} + \frac{dQ_\mu}{dt}$$

0

$$\frac{dQ_\mu}{dt} = \frac{dQ_\mu}{\underbrace{d(v_1 - v_o)}_{C_\mu(v)}} \frac{d(v_1 - v_o)}{dt} = C_\mu \frac{dv_1}{dt} - C_\mu \frac{dv_o}{dt}$$

$$C_\mu = \frac{k}{(\phi + V_{CB})^{\frac{1}{n}}} = \frac{k}{(\phi + V_{CBQ} + V_{CB})^{\frac{1}{n}}}$$

Governing Differential Eq.

$$\frac{dQ_B}{dt} = \tau_F \frac{dI_c}{dt} = \tau_F \frac{di_c}{dt}$$

$$i_i = C_{je} \frac{dv_1}{dt} + \tau_F \frac{di_c}{dt} - C_{\mu} \frac{dv_o}{dt}$$

$$v_1 = V_T \ln \left(\frac{i_c + I_Q}{I_Q} \right)$$

$$\frac{dv_1}{dt} = \frac{dv_1}{di_c} \frac{di_c}{dt} = \frac{V_T}{I_Q} \frac{I_Q}{i_c + I_Q} \frac{di_c}{dt} = \frac{V_T}{i_c + I_Q} \frac{di_c}{dt}$$

$$\therefore i_i = C_{je} \frac{V_T}{i_c + I_Q} \frac{di_c}{dt} + \tau_F \frac{di_c}{dt} - C_{\mu} \frac{dv_o}{dt}$$

BJT Series Expansion

$$v_o = -i_c R_L \quad i_i = -\left\{ \frac{1}{R_L} \left(\tau_F + \frac{C_{je} V_T}{I_Q + i_c} \right) + C_\mu \right\} \frac{dv_o}{dt}$$

$$= -\frac{1}{R_L} \left[\tau_F + \frac{C_{je} V_T}{\underbrace{I_Q + i_c}} + C_\mu R_L \right] \frac{dv_o}{dt}$$

$$\frac{1}{I_Q \left(1 + \frac{i_c}{I_Q} \right)} \Rightarrow \frac{1}{1+x} = 1 - x + x^2 + \dots$$

$$C_\mu = \frac{C_{\mu_o}}{\left(1 + \frac{v_o}{V_Q} \right)^{\frac{1}{n}}} = C_{\mu_o} \left(1 - \frac{1}{n} \frac{v_o}{V_Q} + \frac{1}{2n} \left(\frac{1}{n} + 1 \right) \left(\frac{v_o}{V_Q} \right)^2 + \dots \right)$$

BJT Series Expansion (cont)

$$\therefore i_i \cong -\frac{1}{R_L} \left[\tau_F + \frac{C_{je} V_T}{I_Q} - \frac{C_{je} V_T}{I_Q} \frac{i_c}{I_Q} + \frac{C_{je} V_T}{I_Q} \left(\frac{i_c}{I_Q} \right)^2 + \right. \\ \left. C_{\mu_o} R_L - C_{\mu_o} R_L \frac{1}{n} \frac{v_o}{V_Q} + C_{\mu_o} R_L \frac{1}{2n} \left(1 + \frac{1}{n} \right) \left(\frac{v_o}{V_Q} \right)^2 \right] \times \frac{dv_o}{dt}$$

Substitute $v_o = -i_c R_L$

$$i_i \cong \left(a_1 + a_2 v_o + a_3 v_o^2 \right) \frac{dv_o}{dt} \quad (*)$$

$$\cong a_1 \frac{dv_o}{dt} + \frac{1}{2} a_2 \frac{dv_o^2}{dt} + \frac{1}{3} a_3 \frac{dv_o^3}{dt} \quad (**)$$


Memoryless Terms

Non-linear differential equation for v_o vs. i_i where

$$a_1 = -\frac{1}{R_L} \left(\tau_F + \frac{C_{je} V_T}{I_Q} + C_{\mu_o} R_L \right)$$

$$a_2 = -\frac{1}{R_L} \left(\frac{C_{je} V_T}{R_L I_Q^2} - C_{\mu_o} R_L \frac{1}{n} \frac{1}{V_Q} \right)$$

null

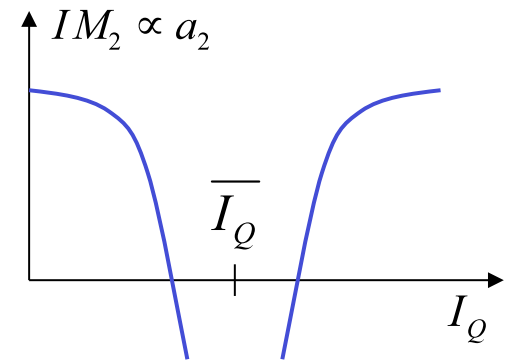

$$a_3 = -\frac{1}{R_L} \left(\frac{C_{je} V_T}{R_L^2 I_Q^3} + C_{\mu_o} R_L \frac{1}{2n} \left(1 + \frac{1}{n} \right) \frac{1}{V_Q^2} \right)$$

always add

Memory Terms

In (**), put

$$v_o = A_1(j\omega_a) \circ i_i + A_2(j\omega_a, j\omega_b) \circ i_i^2 + \dots$$
$$i_i = a_1 \frac{dv_o}{dt} + \frac{1}{2} a_2 \frac{dv_o^2}{dt} + \frac{1}{3} a_3 \frac{dv_o^3}{dt}$$

First Order:

$$i_i = a_1 j\omega A_1(j\omega) \circ i_i$$

$$\therefore A_1(j\omega) = \frac{1}{j\omega a_1}$$

Second Order Memory

Second Order:

$$0 = a_1 j(\omega_a + \omega_b) A_2(j\omega_a, j\omega_b) + \frac{1}{2} a_2 (j\omega_a + j\omega_b) A_1(j\omega_a) A_1(j\omega_b)$$

$$\therefore A_2(j\omega_a, j\omega_b) = -\frac{1}{2} \frac{a_2}{a_1} A_1(j\omega_a) A_1(j\omega_b)$$

$$A_2(j\omega_a, j\omega_b) = -\frac{1}{2} \frac{a_2}{a_1} \frac{1}{j\omega_a a_1} \frac{1}{j\omega_b a_1}$$

$$= \frac{1}{2} \frac{a_2}{a_1^3} \frac{1}{\omega_a \omega_b}$$

Third Order Memory

Third Order:

$$0 = [a_1 A_3 + \frac{1}{2} a_2 \overline{2A_1 A_2} + \frac{1}{3} a_3 A_1 A_1 A_1] (j\omega_a + j\omega_b + j\omega_c)$$

$$\therefore A_3 = \frac{-\frac{1}{2} a_2 \overline{2A_1 A_2} + \frac{1}{3} a_3 A_1 A_1 A_1}{a_1}$$


$$A_3 = \frac{\frac{a_3}{3} - \frac{a_2^2}{2a_1}}{j\omega_a \omega_b \omega_c a_1^4}$$

No null because a_3 is negative

IM₂ in BJT at High Frequency

$$i_i = I_1 \cos \omega_1 t + I_2 \cos \omega_2 t$$

$$IM_2 = \frac{|A_2| I_1 I_2}{\hat{v}_o} \frac{2!}{1!1!} \frac{1}{2}$$

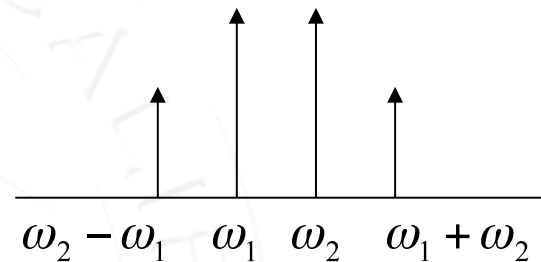

$$\hat{v}_o = |A_1(j\omega_1)| I_1 = |A_1(j\omega_2)| I_2$$

$$\therefore IM_2 = \frac{|A_2(j\omega_1, \pm j\omega_2)|}{|A_1(j\omega_1)| |A_1(j\omega_2)|} \hat{v}_o$$

$$IM_2 = \frac{1}{2} \frac{a_2}{a_1^3} \frac{1}{\omega_1 \omega_2} a_1 \omega_1 a_1 \omega_2 \hat{v}_o = \frac{1}{2} \frac{a_2}{a_1} \hat{v}_o$$

Independent of frequency at high frequency

IM3 in BJT at High Frequency

$$IM_3 = \frac{3!}{2!!} \frac{1}{2^2} \frac{I_1 I_o^2 |A_3|}{\hat{v}_o}$$

Again $|A_1(j\omega_1)|I_1 = |A_1(j\omega_2)|I_2 = \hat{v}_o$

$$IM_3 = \frac{3}{4} \frac{|A_3(j\omega_2, j\omega_2, -j\omega_1)|}{|A_1(j\omega_1)||A_1(j\omega_2)||A_1(j\omega_2)|} \hat{v}_o^2 = \frac{3}{4} \hat{v}_o^2 \frac{\frac{a_3}{3} - \frac{a_3^2}{2a_1}}{a_1} \approx \frac{3}{4} \hat{v}_o^2 \frac{a_3}{3a_1}$$

$$a_1 = -\frac{1}{R_L} \left(\tau_F + \frac{C_{je}}{g_m Q} + C_{\mu_o} R_L \right)$$

$$a_3 = -\frac{1}{R_L} \left(\frac{C_{je} V_T}{R_L^2 I_Q^3} + C_{\mu_o} R_L \frac{1}{2n} \left(\frac{1}{n} + 1 \right) \frac{1}{V_Q^2} \right)$$

Example: 2 GHz LNA Front End

$$\tau_F = 12 \text{ ps}$$

$$C_{\mu_o} = 37 \text{ fF}$$

$$r_b = 10 \Omega$$


$$I_C = 3 \text{ mA}$$

$$C_{je} = 416 \text{ fF}$$

$$R_L = 50 \Omega$$

$$\eta = 3$$

$$V_Q = 2 \text{ V}$$

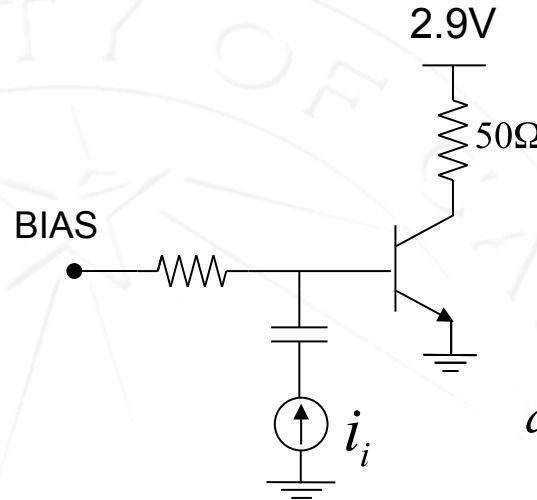

$$\begin{aligned} \text{Supply} &\approx \overbrace{V_{BE} + V_Q}^{750 \text{ mA}} + \underbrace{3 \text{ mA} \times 50 \Omega}_{150 \text{ mA}} \\ &= 2.9 \text{ V} \end{aligned}$$

$$a_3 = -\frac{1}{R_L} (1.6 \times 10^{-10} + 1 \times 10^{-13})$$

$$a_1 = -\frac{1}{R_L} (12 + 3.6 + 1.9) \times 10^{-12}$$

$$IM_3 = \frac{3}{4} \hat{v}_o^2 \frac{a_3}{3a_1} = 1 \quad \text{for intercept point}$$

$$\hat{v}_o = 0.66 \text{ V} \quad \text{into } 50 \Omega$$

$$= +6 \text{ dBm output } IP_3$$

→ Very close to SPICE
and measurements

LNA Example (cont)

Note:

$$r_{\pi} = \frac{\beta}{g_m} = \frac{150}{g_m} \approx 1.3k\Omega$$

$$C_{\pi} = C_{je} + C_B \quad C_B = \tau_F g_m = 1.38pF$$

$$C_{je} = 0.416pF$$

$$\frac{1}{\omega C_{\pi}} = 44\Omega \longleftarrow \text{Low compared to } r_{\pi}$$

LNA with Emitter Degen

IEEE JOURNAL OF SOLID-STATE CIRCUITS, VOL. 33, NO. 4, APRIL 1998

High-Frequency Nonlinearity Analysis of Common-Emitter and Differential-Pair Transconductance Stages

Keng Leong Fong, *Member, IEEE*, and Robert G. Meyer, *Fellow, IEEE*



- Analysis of BJT transconductor as a non-linear Gm cell
- Include emitter degeneration.

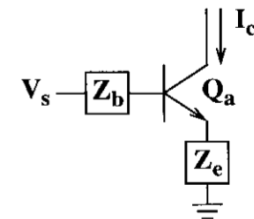


Fig. 1. Common-emitter transconductance stage.

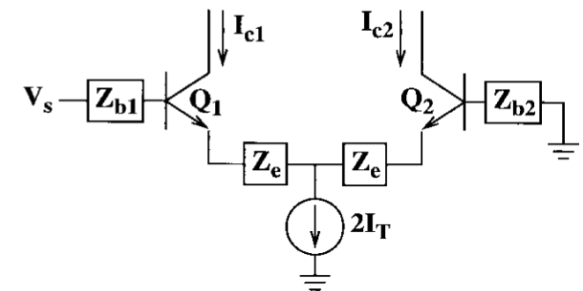


Fig. 2. Differential-pair transconductance stage.

KCL Equations

$$V_s = (sC_{je}V_\pi + s\tau_F I_c + I_c/\beta_0)(Z_b + Z_e) + I_c Z_e + V_\pi \quad (1)$$

$$I_c = A_1(s) \circ V_s + A_2(s_1, s_2) \circ V_s^2 + A_3(s_1, s_2, s_3) \circ V_s^3 + \dots$$

$$V_\pi$$

$$= C_1(s_1) \circ V_s + C_2(s_1, s_2) \circ V_s^2 + C_3(s_1, s_2, s_3) \circ V_s^3 + \dots$$

$$A_1(s) = g_m C_1(s)$$

$$A_2(s_1, s_2) = g_m c_2(s_1, s_2) + \frac{I_Q}{2V_T^2} C_1(s_1) C_1(s_2) \quad C_1(s)$$

$$A_3(s_1, s_2, s_3) = g_m C_3(s_1, s_2, s_3)$$

$$+ \frac{I_Q}{6V_T^3} C_1(s_1) C_1(s_2) C_1(s_3)$$

$$+ \frac{I_Q}{V_T^2} \overline{C_1 C_2}$$

$$C_2(s_1, s_2) = -C_1(s_1 + s_2) C_1(s_1) C_1(s_2) \frac{I_Q}{2V_T^2} \times \left[(s_1 + s_2) \tau_F Z(s_1 + s_2) + \frac{Z(s_1 + s_2)}{\beta_0} + Z_e(s_1 + s_2) \right]$$

$$C_3(s_1, s_2, s_3) = -\frac{A_1(s_1 + s_2 + s_3) I_Q}{6V_T^3} \times [A_1(s_1) A_1(s_2) A_1(s_3) + 6V_T \overline{A_1 A_2}] \times \left[(s_1 + s_2 + s_3) \tau_F Z(s_1 + s_2 + s_3) + \frac{Z(s_1 + s_2 + s_3)}{\beta_0} + Z_e(s_1 + s_2 + s_3) \right]$$

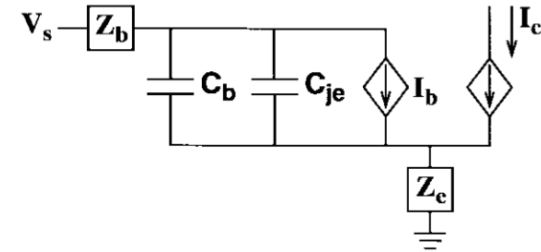


Fig. 4. Model of common-emitter transconductance stage.

IM3 Calculation

$$\begin{aligned}
 |IM_3| &= \left| \frac{3}{4} \frac{A_3(s_a, s_a, -s_b)}{A_1(2s_a - s_b)} \right| |V_s|^2 \\
 &\approx \left| \frac{A_1(s)}{I_Q} \right|^3 \left| \frac{V_T}{4} [1 + sC_{je}Z(s)] \right. \\
 &\quad \times \left\{ -1 + \frac{A_1(\Delta s)}{g_m} [1 + \Delta s C_{je} Z(\Delta s)] \right. \\
 &\quad \left. \left. + \frac{A_1(2s)}{2g_m} [1 + 2s C_{je} Z(2s)] \right\} \right| |V_s|^2
 \end{aligned}$$

These terms can resonate:

$$[1 + sC_{je}Z_b(s) + sC_{je}Z_e(s)].$$

For small offset frequencies:

$$[1 + \Delta s C_{je} Z(\Delta s)] \approx 1$$

$$Z(s) = Z_b(s) + Z_e(s)$$

$$\begin{aligned}
 |IM_3| &\approx \left| \frac{A_1(s)}{I_Q} \right|^3 \left| \frac{V_T}{4} [1 + sC_{je}Z(s)] \right. \\
 &\quad \times \left\{ -1 + \frac{A_1(\Delta s)}{g_m} \right. \\
 &\quad \left. \left. + \frac{A_1(2s)}{2g_m} [1 + 2s C_{je} Z(2s)] \right\} \right| |V_s|^2
 \end{aligned}$$

Typical Example

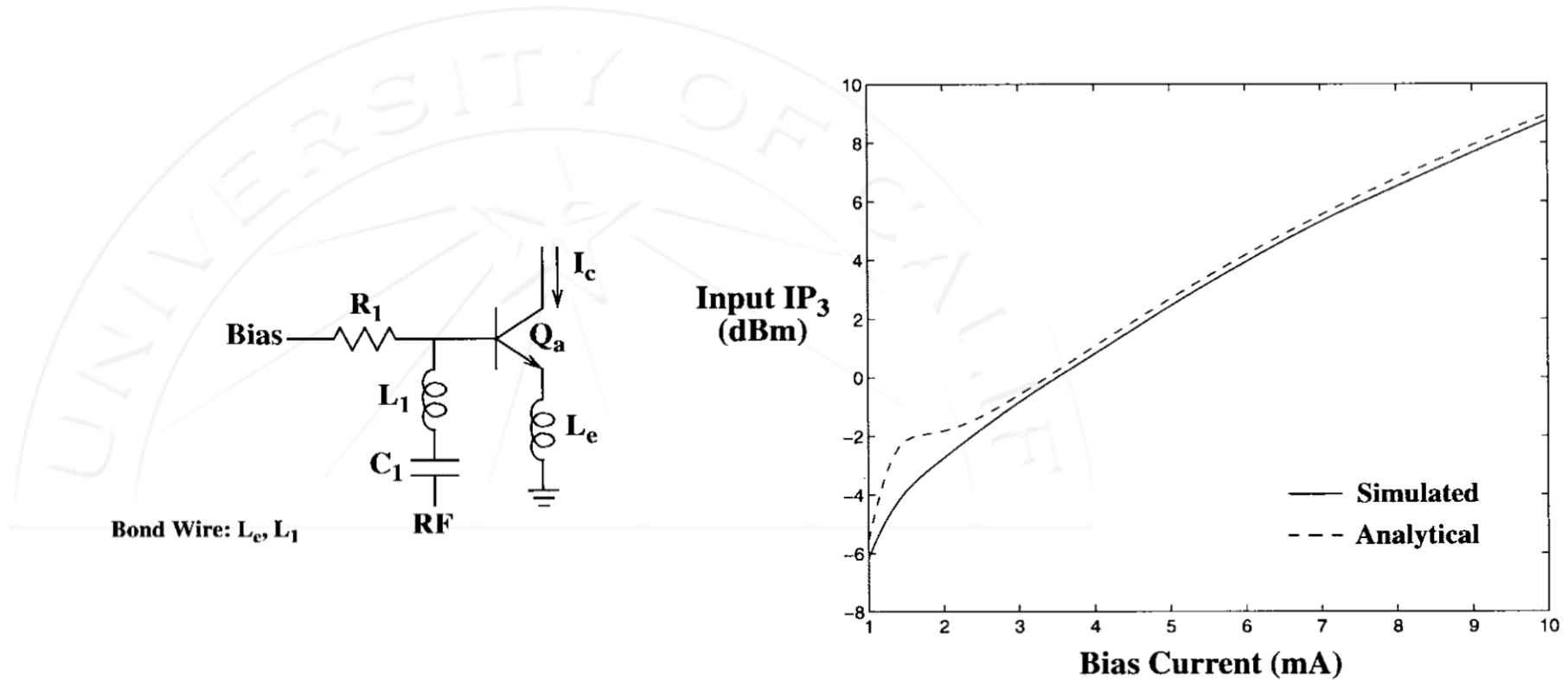


Fig. 6. Input IP3 versus bias current.

significant errors. The two RF sinusoidal signals used are at 900 and 910 MHz, respectively. The component values used are: $\tau_F = 10.5$ ps, $C_{je} = 1.17$ pF, $\beta = 73$, $L_e = 2.4$ nH, $L_1 = 3.5$ nH, $C_1 = 20$ pF, and $R_1 = 150$ Ω .

References

- **UCB EECS 242 Class Notes**, Robert G. Meyer, Spring 1995
- K. L. Fong and R. G. Meyer, “High-Frequency Nonlinearity Analysis of Common-Emitter and Differential Pair Transconductance Stages,” *JSSC*, pp. 548-555, vol. 33, no. 4, April 1998.