

1

Wideband Amplifiers

3,2109



EE 242

Topics:

- 1- Broad band vs. wideband
Open circuit time constants O.C.T
Bootstrapping the capacitors
- 2- F.B. Amplifiers
- 3- Increasing the gain by inserting zeros in the T.F.
shunt peaking Amplifiers
- 4- distributed Amplifiers
- 5- Tuned Amplifiers G.BW.
Effect of C_{gd} and cancelling it
- 6- Multi section Matching Networks
Andrea's Amplifier example
Fano's S_{11} -BW relation
- 7- Transformer Matching Networks


2

Broad band & wide band

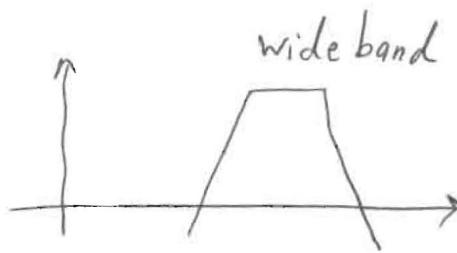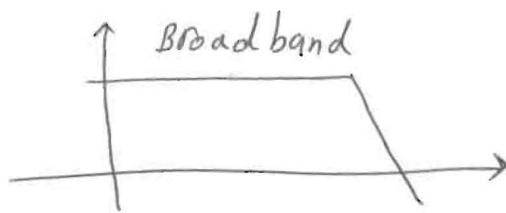

- O.C.T : - good for B.W. estimating of an all-Pole system
With one dominant Pole
 - approximation fails when several Poles are close or on top of each other

- example

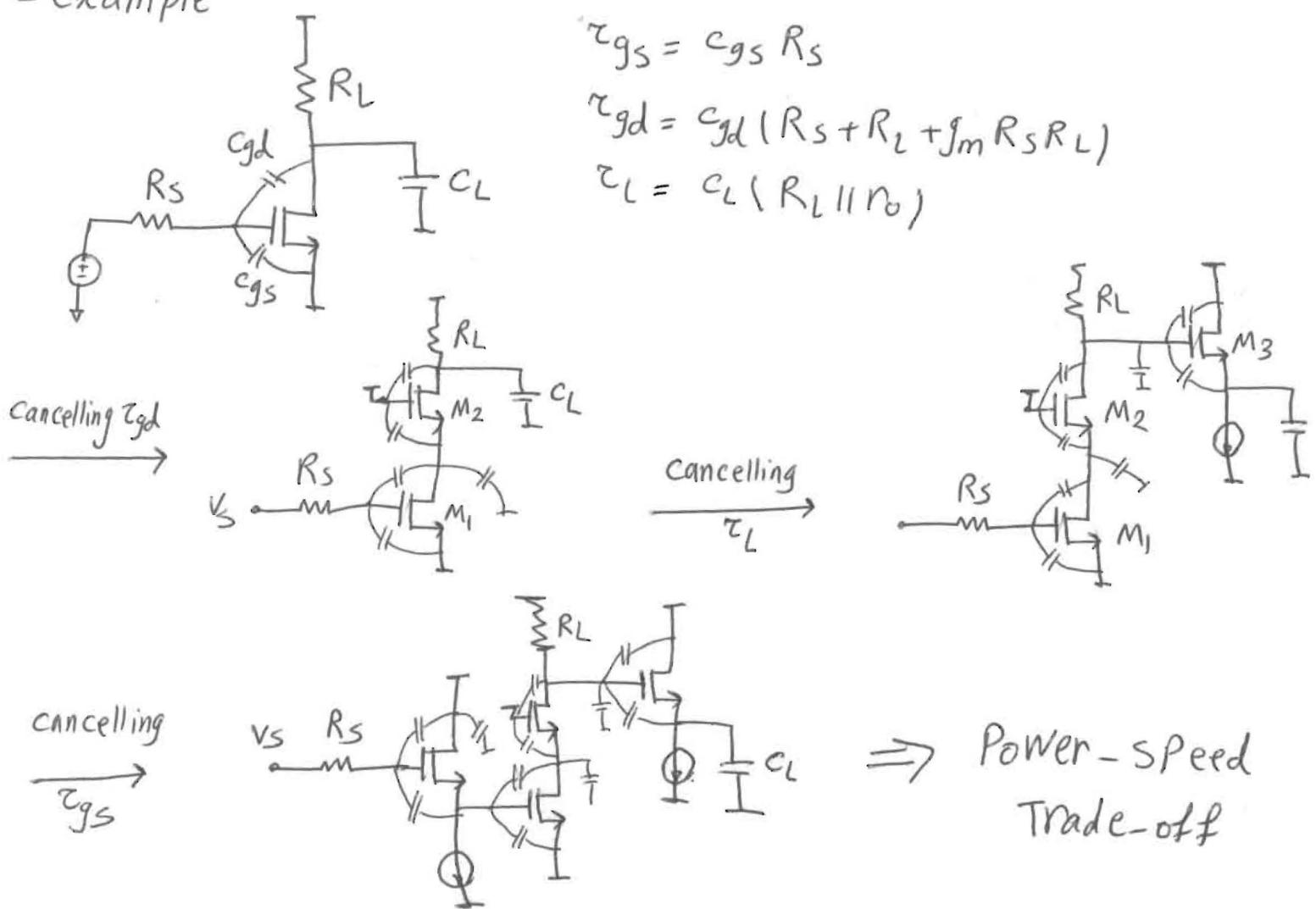


3

Feed back Amplifiers :


For low order systems [systems with one dominant Pole]

Product of Gain \times B.W. is constant

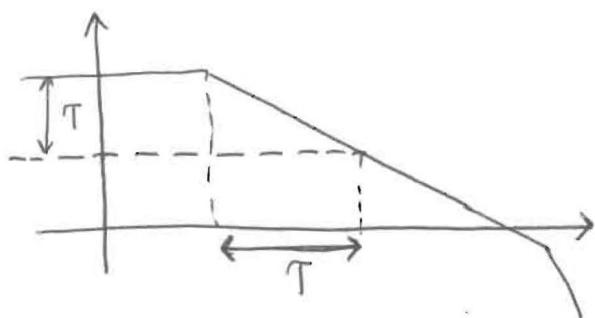

Shunt-series Amplifier

After using F.B.

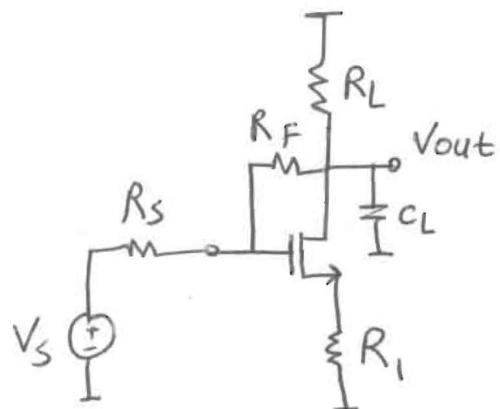

$G \downarrow$

$R_i, R_o \downarrow \Rightarrow$ matching acquired

B.W. \uparrow

$$A_N = -\frac{R_L}{R_E} \frac{R_F - R_E}{R_F + R_E} \quad R_E = \frac{g_m}{1 + g_m R_i}$$

$$R_{in} = \frac{R_E (R_F + R_L)}{R_E + R_L}$$



$$R_{out} = \frac{R_E (R_F + R_S)}{R_E + R_S}$$

$$BW = 1 / \left(A_N \left(\frac{C_S}{g_m} + \frac{R_L C_D}{2} \right) \right)$$

4


Addition of Zeros to the T.F.

concept :

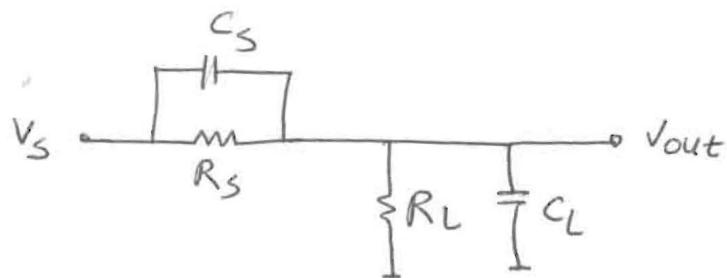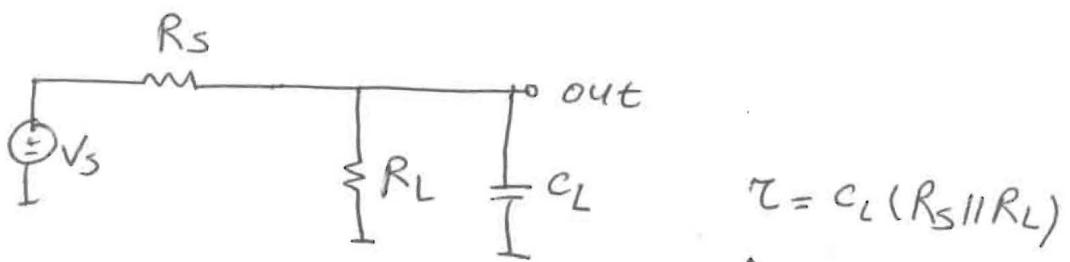

$$\text{at } t=0^+ \quad N_{out} = \frac{C_S}{C_L + C_S} N_s$$
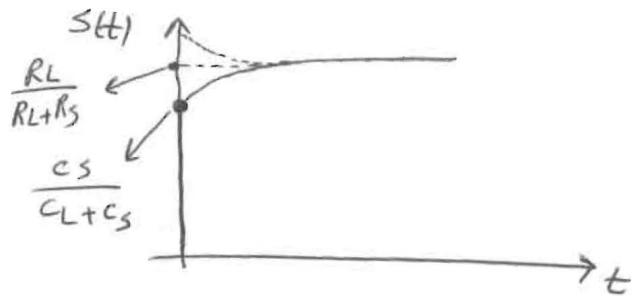
$$t=\infty \quad N_{out} = \frac{R_L}{R_L + R_s} N_s$$




$$\tau = (R_L || R_s)(C_L + C_S)$$

$$\frac{N_{out}}{N_s} = \frac{\frac{R_L}{1 + R_L C_L s}}{\frac{R_L}{1 + R_L C_L s} + \frac{R_s}{1 + R_s C_S s}} = \frac{R_L}{R_L + R_s} \frac{1 + R_s C_S s}{1 + (R_L || R_s)(C_L + C_S)s}$$


$$Z = \frac{-1}{R_s C_S}, \quad P = \frac{-1}{(R_L || R_s)(C_L + C_S)}$$
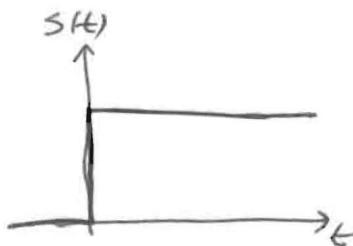
$$\text{if } P = Z \rightarrow R_s C_S = R_L C_L \Rightarrow$$



5)



- Application

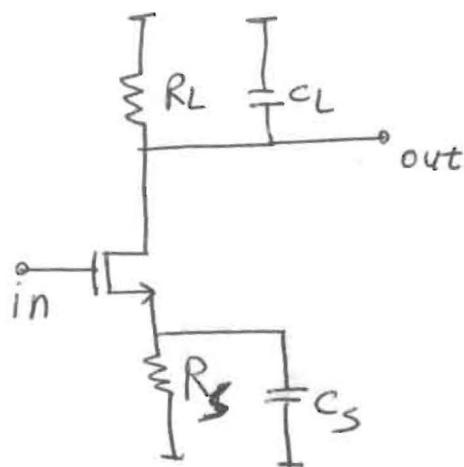

$$\text{if } R_s C_s = R_L C_L$$

$$\frac{V_{\text{out}}}{V_{\text{in}}} \approx \frac{Z_{\text{out}}}{Z_{\text{in}}} \rightarrow \text{constant over frequency up to a fraction of}$$

- Shunt Peaking Amplifier

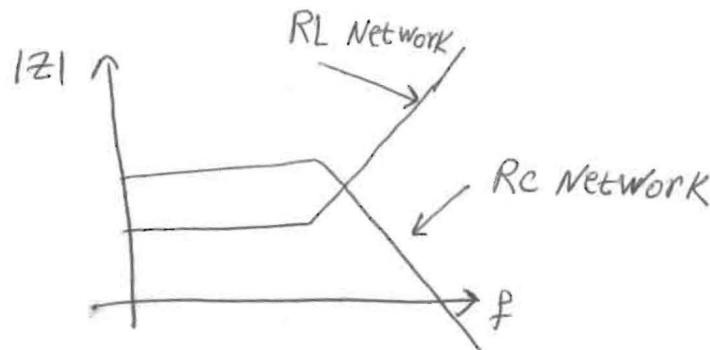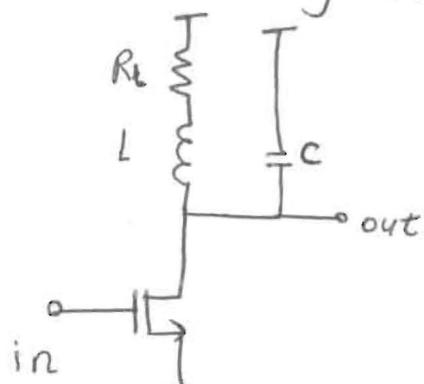

$$Z = (R + jLs) \parallel \frac{1}{jCs} = \frac{R \left[s \left[\frac{L}{R} \right] + 1 \right]}{s^2 LC + sRC + 1}$$


$$m = \frac{Rc}{L/R}, \quad \zeta = L/R$$

$$\Rightarrow \frac{|Z|}{R} = \sqrt{\frac{1 + (w\zeta)^2}{(1 - w^2\zeta^2 m^2) + (w\zeta m)^2}}$$


	m	Normalized B.W.	Normalized Peak
Max B.W.	$\sqrt{2}$	1.85	1.19
$ Z = R @ w = 1/Rc$	2	1.8	1.03
Maximally flat	$1 + \sqrt{2}$	1.72	1
Best group delay	3.1	1.6	1
No shunt peaking	∞	1	1

6/


Shunt Peaking cont'd

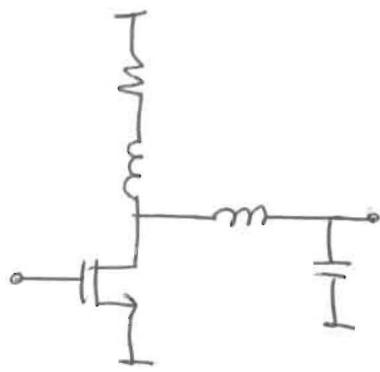

shunt and series
Peaking

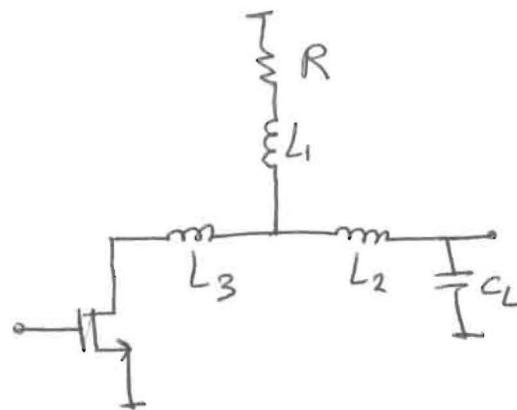

shunt- and double series Peaking

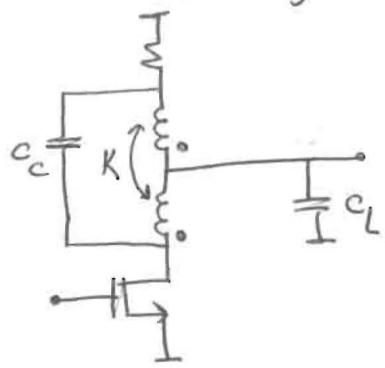


\Rightarrow basically the order of matching network is increasing and it's resembling a synthesized TL.

T-coil B.W. enhancement

In above structures Parasitic caps are charged and discharge serially so the current available to charge a cap is more and hence the risetime is shorter at the expense of delay

\Rightarrow the ultimate case : A distributed amplifier


7 - Distributed Amplifier

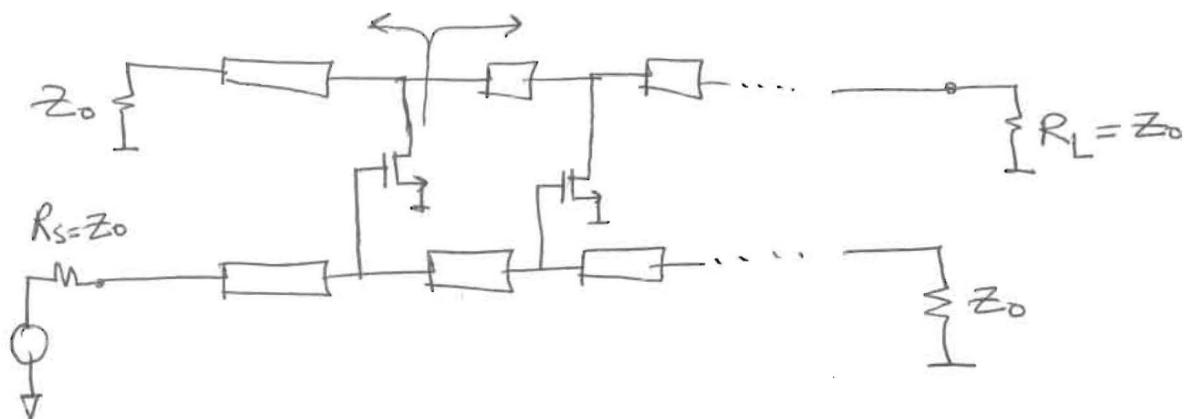

$$A_N = n g_m \left(\frac{Z_0}{2} \right) e^{-t_d W}$$


Additive gain, very high B.W. up to $\frac{f_T}{2}$

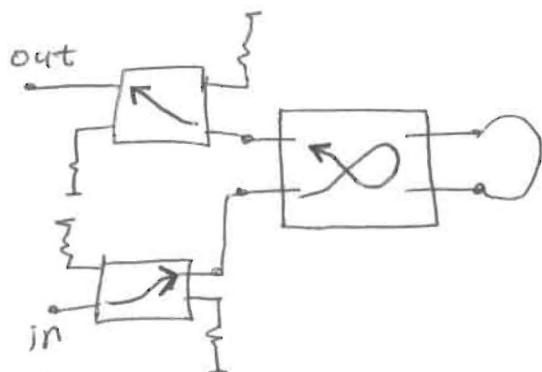- to reuse the signal going into the isolated termination



A. Arbabian, A.M. Niknejad (ISSCC 2008)


or

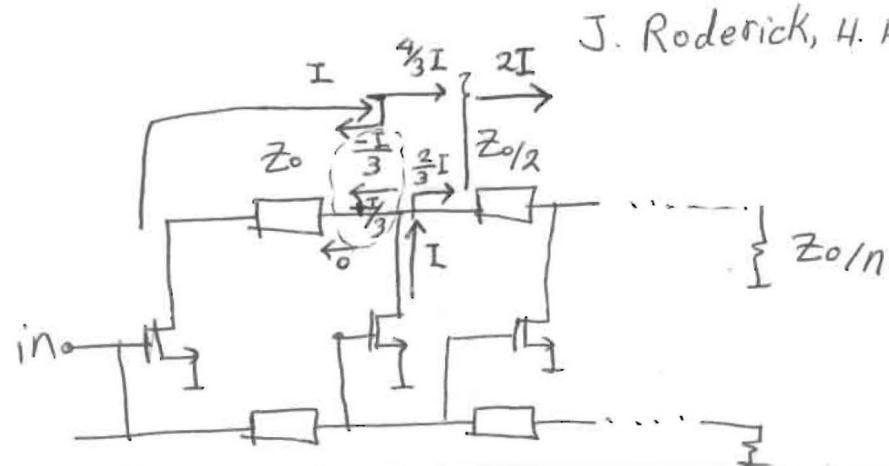

J. Roderick, H. Hashemi (ISSCC 2009)


8 - Wideband Amplifiers

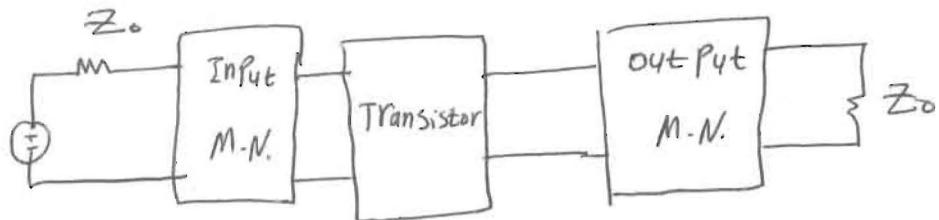- Increasing the B.W. through Matching Network:




$$G_{Tu,\max} = \frac{1}{1 - |S_{11}|^2} |S_{21}|^2 \frac{1}{1 - |S_{22}|^2}$$

$$G_{S\max} = \frac{1}{1 - |S_{11}|^2} \quad G_{L\max} = \frac{1}{1 - |S_{22}|^2}$$

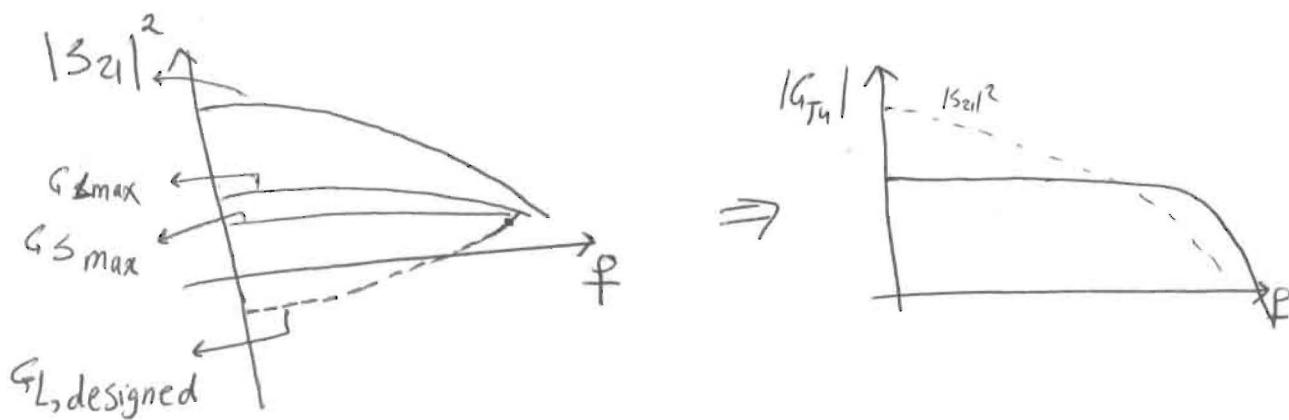


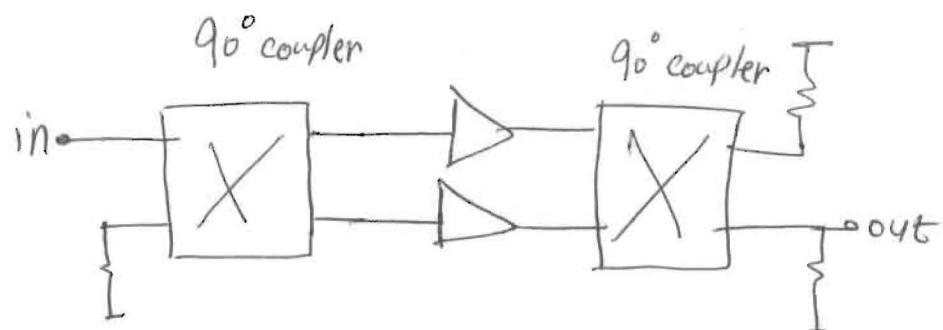\Rightarrow To fix the mismatch (Balanced Amplifiers)



9- High order Matching Networks

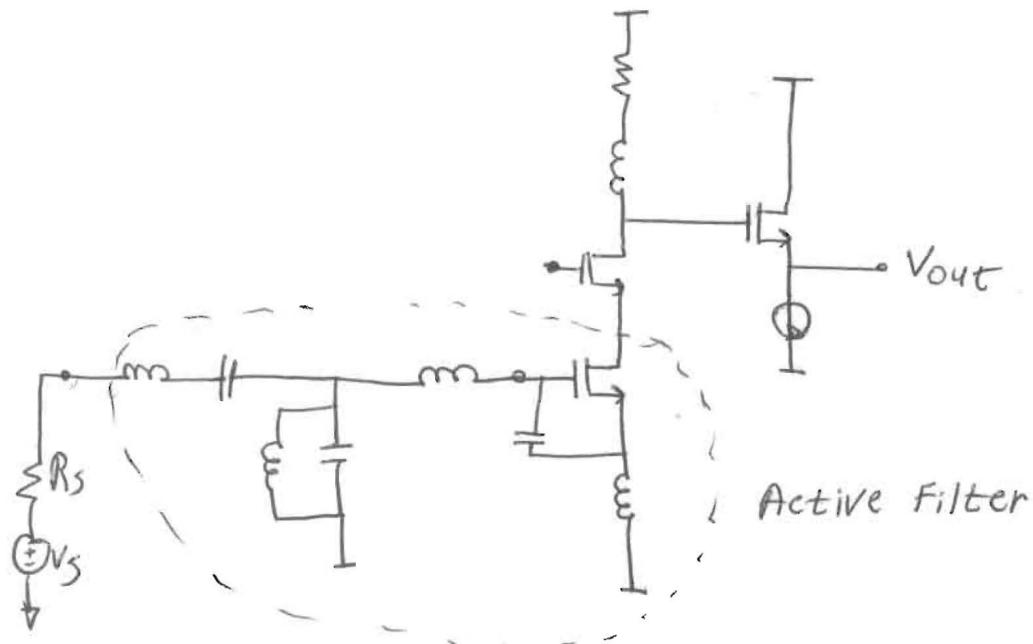A. Bevilacqua , A.M. Niknejad (ISSCC 2004)






- mitigating the effect of C_{gd}

→ unilateralization (cascode, ~~source-coupled~~ pair,


→ Neutralization

10- Transformer Matching

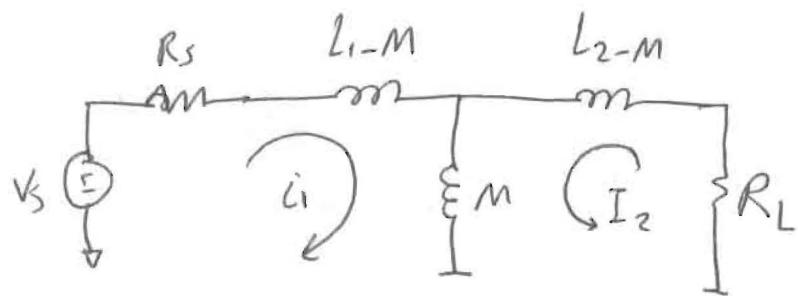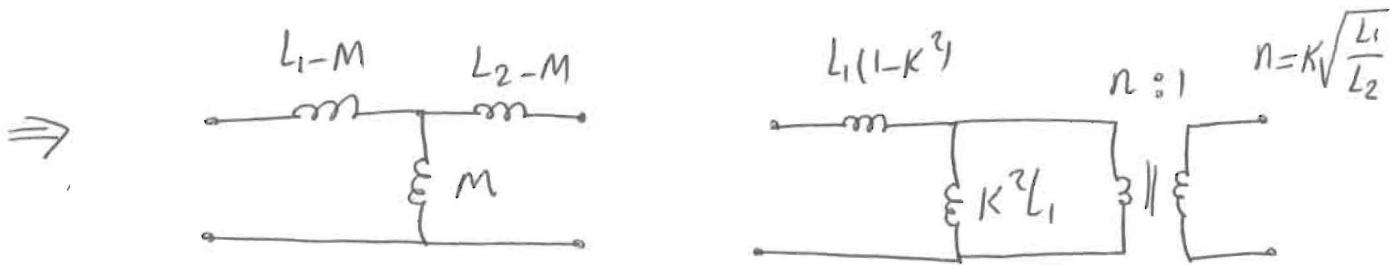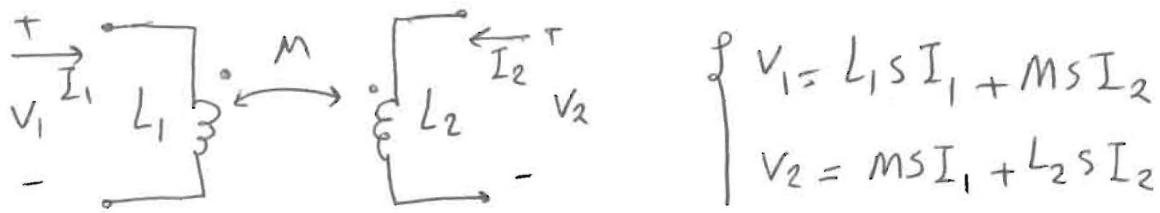

Mesh Analysis $\rightarrow \frac{V_{out}}{V_s} = \frac{R_L M s}{s^2(L_1 L_2 - M^2) + s(R_s L_2 + R_L L_1) + R_s R_L}$
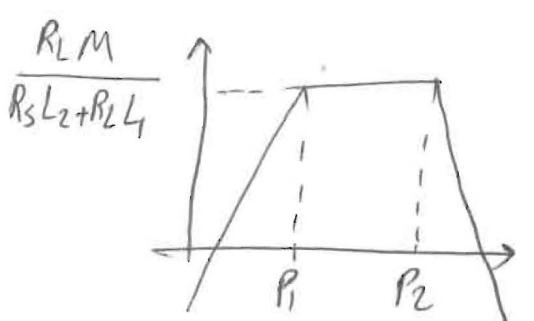
$$\frac{V_{out}}{V_s} = \frac{R_L M}{L_1 L_2 - M^2} \frac{s}{(s - P_1)(s - P_2)} \quad \text{if } P_2 \gg P_1 \Rightarrow P_1 = -\frac{R_s R_L}{R_s L_2 + R_L L_1}$$



$$R_s \rightarrow \infty \Rightarrow A = K \sqrt{\frac{L_2}{L_1}} = K \left(\frac{N_2}{N_1} \right)$$

$$P_2 \approx P_1 + P_2 \Rightarrow P_2 = -\frac{R_s L_2 + R_L L_1}{L_1 L_2 - M^2}$$

mid-band $\frac{V_{out}}{V_s} = \frac{R_L M}{R_s L_2 + R_L L_1}$