

***On the Phase Noise
and Noise Factor in
Circuits and Systems -
New Thoughts on an Old
Subject***

Aleksandar Tasic

QCT - Analog/RF Group

Qualcomm Incorporated, San Diego

A. Tasic © 2009

Outline


- **Spectral Analysis of Noise in LC-Oscillators**
 - LC-tank, g_m -cell, bias current source noise
 - (Phase-) Noise factor
- **Bipolar vs. CMOS LC-Oscillators**
- **LC-Oscillators Noise Reduction Methods**
- **Mixer Noise Factor from VCO Noise Factor**
- **Oscillator Phase Noise in Receiver's SNR**
- **LNA and Mixer Noise Factors in a Receiver**
- **BBFilter Noise Transfer vs. LO/Mix Duty**

***Phase Noise Model
of Bipolar and
CMOS
LC-Oscillators***

Outline

- Oscillation Condition
- LC-Tank Noise Folding
- g_m -Cell Noise Folding
- Bias-Current Source Noise Folding
- Phase-Noise Model of Bipolar LC-Oscillators
- Phase-Noise Model of CMOS LC-Oscillators
- Bipolar vs. CMOS LC-Oscillators

LC-Oscillator Noise Sources

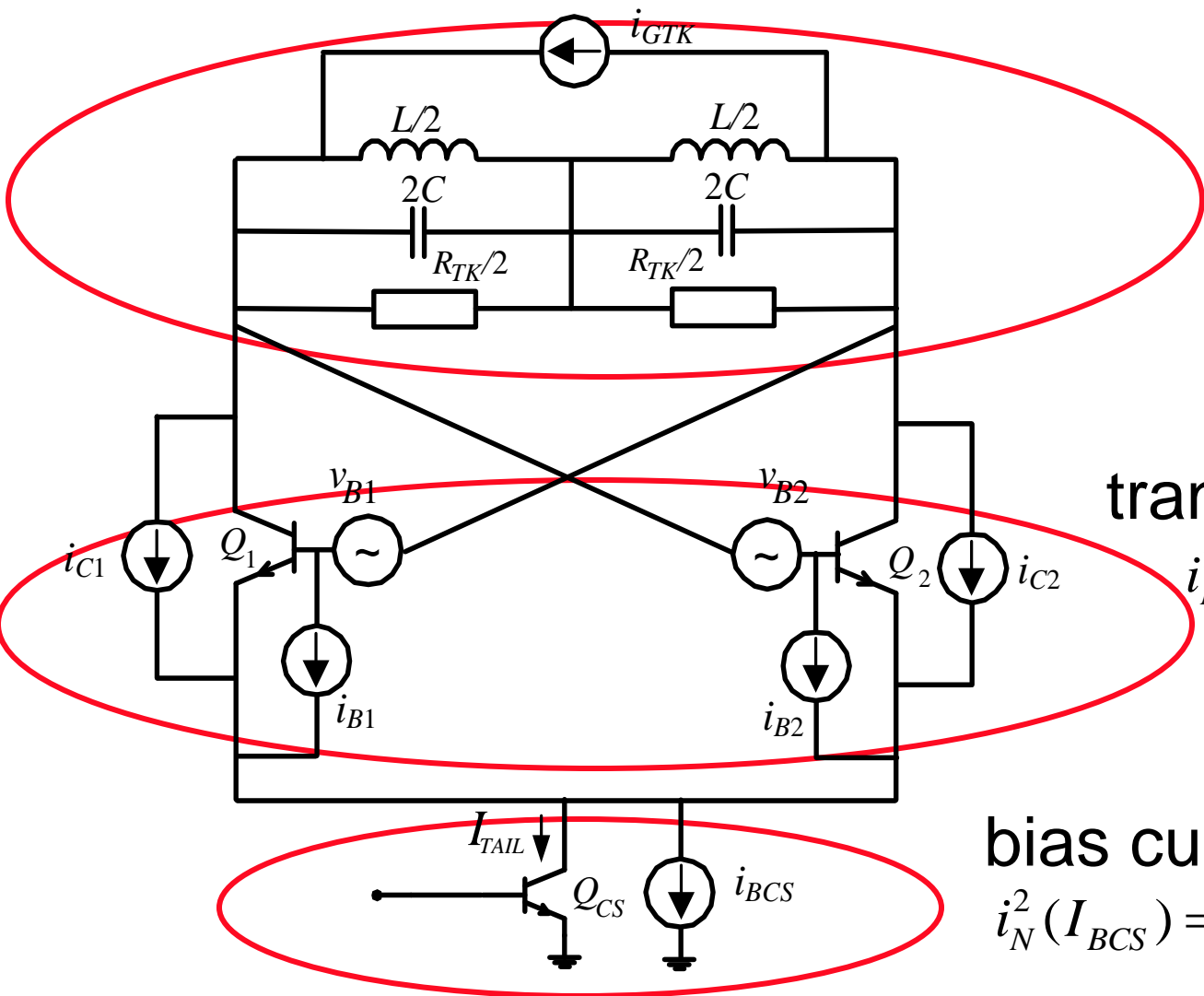

LC-tank noise

$$i_N^2(G_{TK}) = 2KTG_{TK}$$

transconductor noise


$$i_N^2(I_C) = qI_C = 2KTg_m / 2$$

$$v_N^2(r_B) = 2KTr_B$$

bias current source noise

$$i_N^2(I_{BCS}) = KTg_{m,CS} (1 + 2r_{B,CS}g_{m,CS})$$

Oscillator and Phase-Noise Model

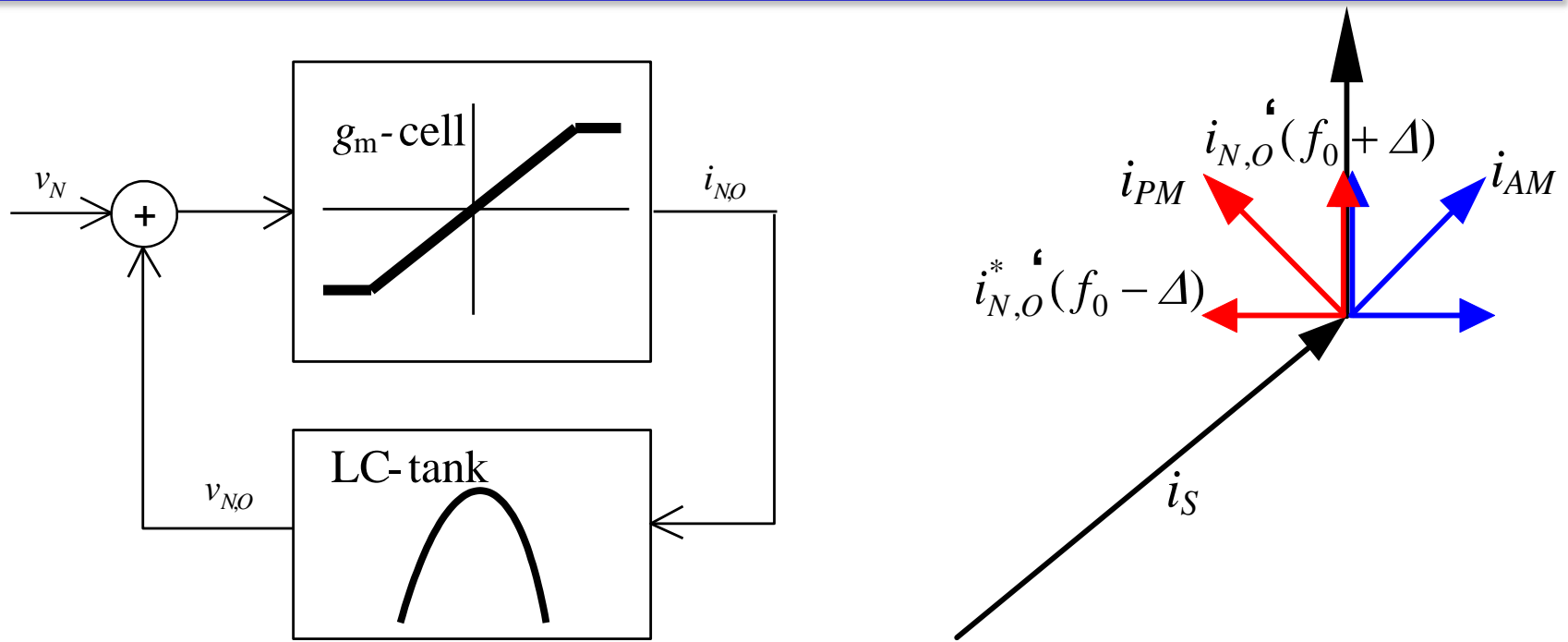

- phase-modulating noise component (double-sided)

$$i_{PM}(f_0 + \Delta) = \frac{1}{2} \left[i_{N,O}(f_0 + \Delta) + i_{N,O}^*(f_0 - \Delta) \right]$$


$$i_{PM}(-f_0 - \Delta) = \frac{1}{2} \left[i_{N,O}(-f_0 - \Delta) + i_{N,O}^*(-f_0 + \Delta) \right]$$

- phase-related noise power (single-sided)


$$v_{PM,TOT}^2 = \frac{1}{2} \left[i_{PM}(f_0 + \Delta) + i_{PM}(-f_0 - \Delta) \right]^2 |Z(f_0 + \Delta)|^2 = \frac{i_{PM,TOT}^2}{4\pi C_{TOT} \Delta^2}$$

g_m -Cell Transfer Function

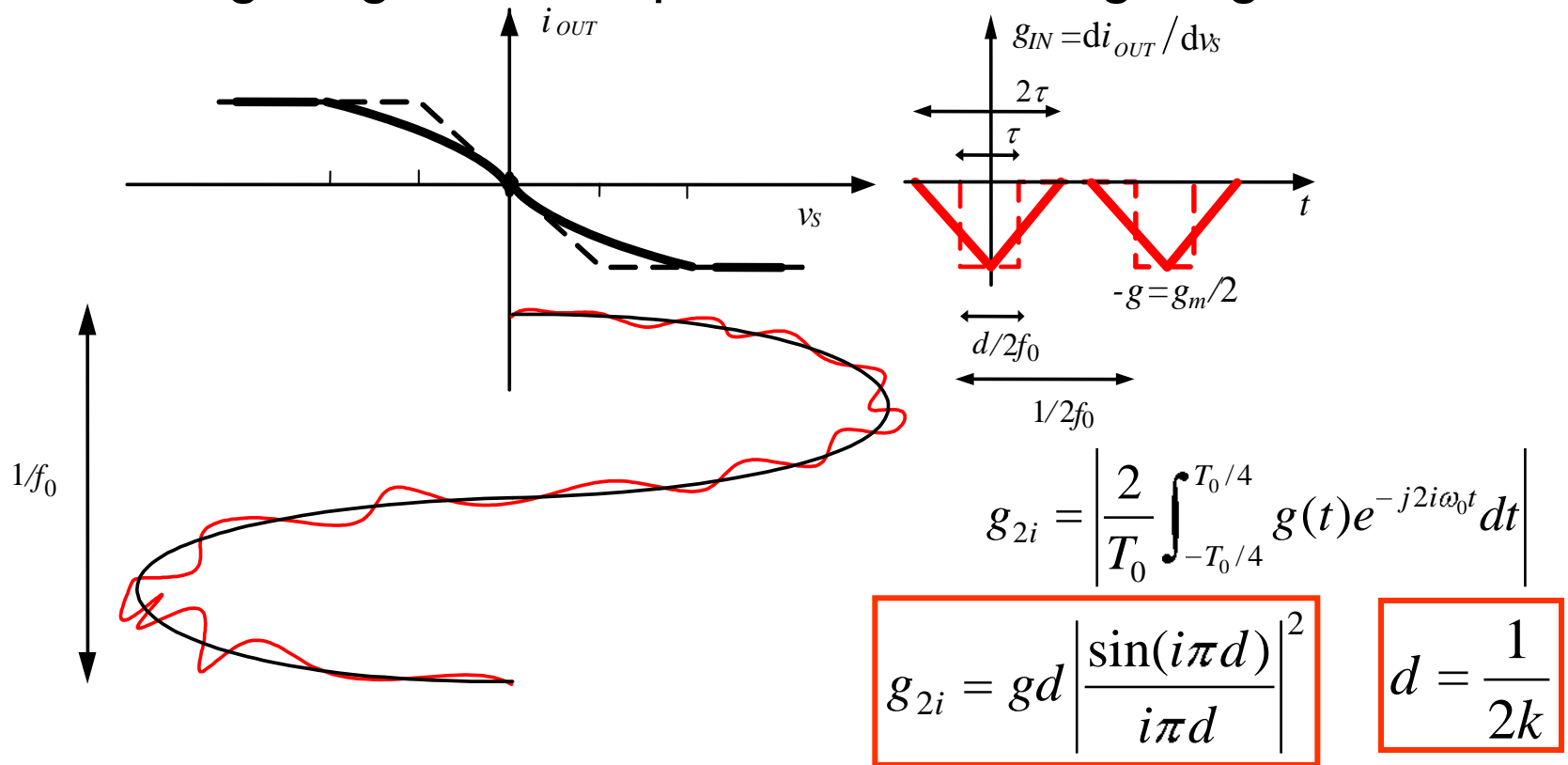- small-signal gain in the presence of a large signal




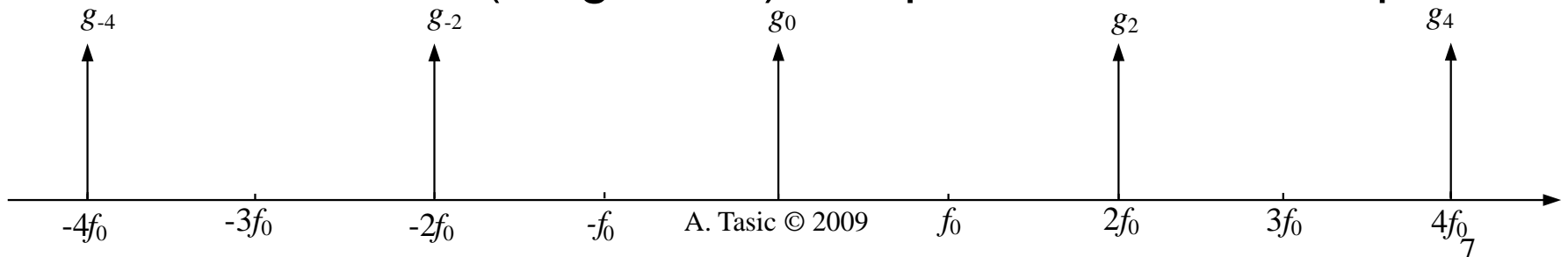- Fourier domain – (magnitude) complex harmonic components




Oscillation Condition

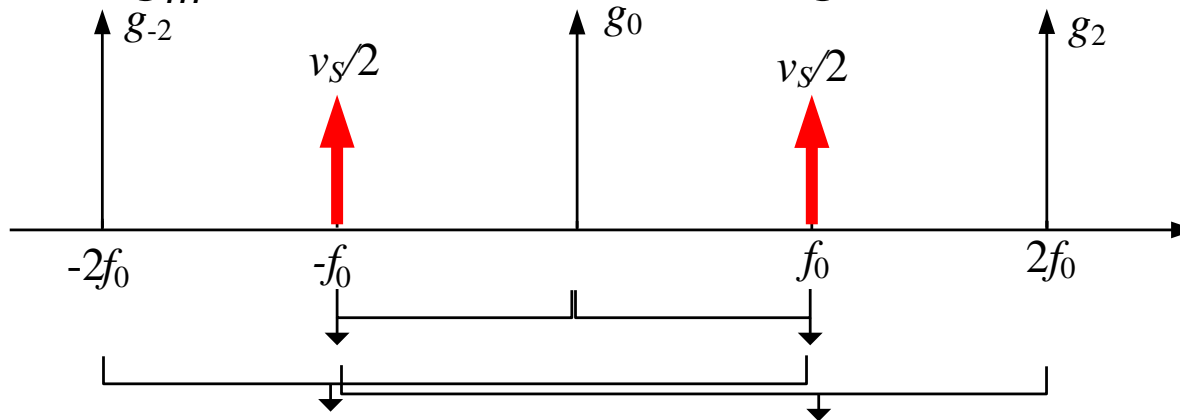- harmonics: g_m -cell and oscillation signal



- convolution:

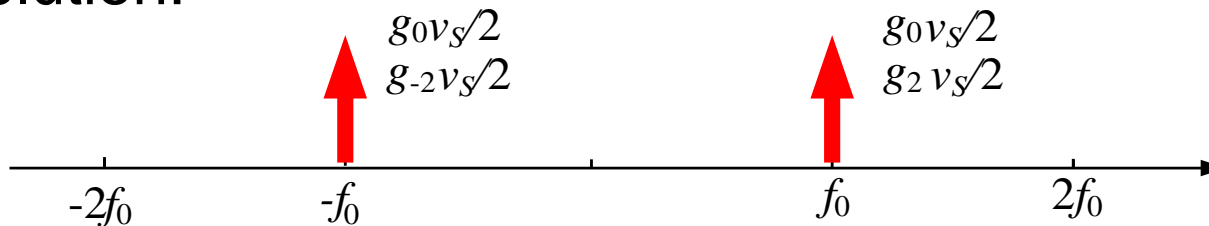

- oscillation signal:

$$v_S = \left(\frac{v_S(-f_0)}{2} g_0 + \frac{v_S(+f_0)}{2} g_0 + \frac{v_S(-f_0)}{2} g_2 + \frac{v_S(+f_0)}{2} g_{-2} \right) R_{TK} = (g_0 + g_2) v_S R_{TK}$$

- oscillation condition: small-signal loop gain: duty cycle:


$$g_0 + g_2 = G_{TK}$$

$$k = R_{TK} g_m / 2$$

$$d = 1 / (2k)$$


LC-Tank Noise Folding

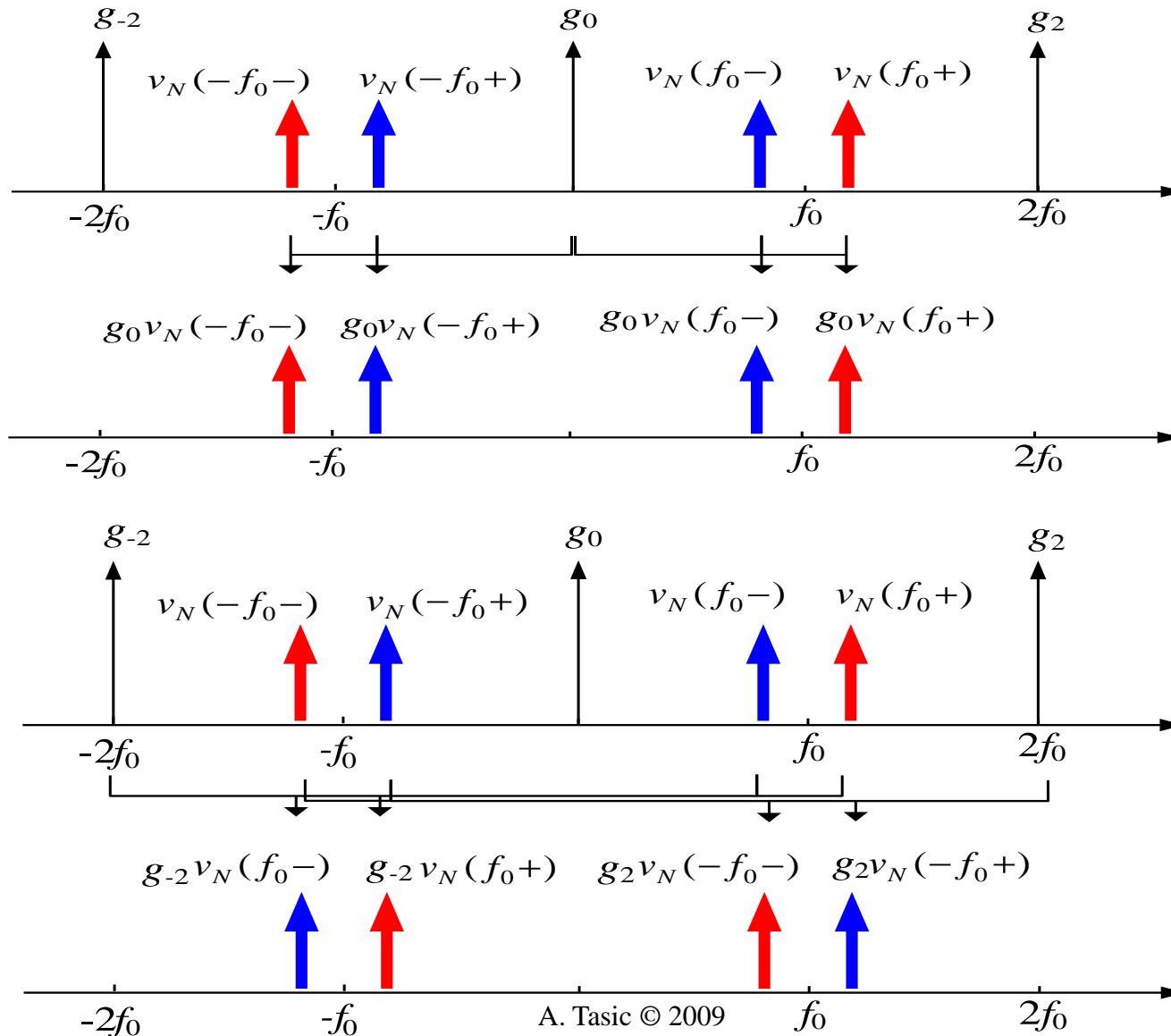- convolution: g_0 and g_2 harmonics and LC-tank noise



LC-Tank Noise Folding

- LC-tank noise contribution:

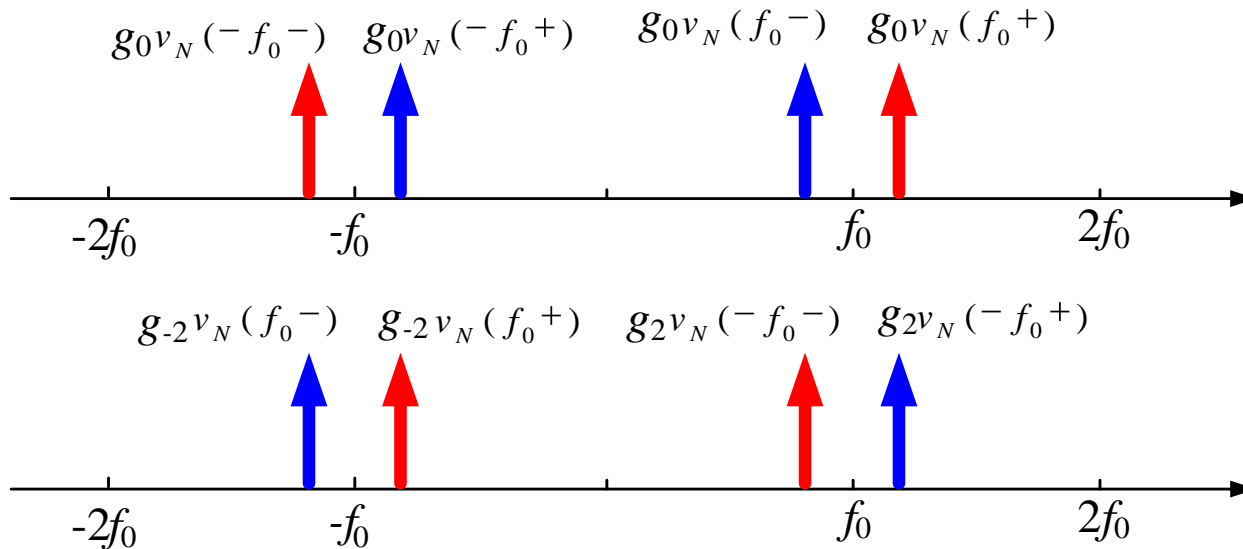

$$i_{N,o}(f_0 - \Delta) = g_0 v_N(f_0 - \Delta) + g_{-2} v_N(-f_0 - \Delta)$$

$$i_{N,o}(-f_0 + \Delta) = g_0 v_N(-f_0 + \Delta) + g_{-2} v_N(f_0 + \Delta)$$

$$i_{N,o}(f_0 + \Delta) = g_0 v_N(f_0 + \Delta) + g_{-2} v_N(-f_0 + \Delta)$$

$$i_{N,o}(-f_0 - \Delta) = g_0 v_N(-f_0 - \Delta) + g_{-2} v_N(f_0 - \Delta)$$

LC-Tank Noise Contribution

- phase-modulating noise component:

$$i_{PM} = \frac{1}{2} \left[i_{N,O}(f_0 + \Delta) + i_{N,O}(-f_0 + \Delta) + i_{N,O}(-f_0 - \Delta) + i_{N,O}(f_0 - \Delta) \right]$$

$$i_{PM} = (g_0 + g_2)v_N(f_0 + \Delta) + (g_0 + g_2)v_N(f_0 - \Delta)$$

- phase-related noise power ($k \gg 1$, $g = g_0 = g_2$):

$$i_{PM}^2(R_{TK}) = (g_0 + g_2)^2 v_N^2(R_{TK})$$

- LC-tank noise transfer function:


$$g^2(R_{TK}) = (g_0 + g_2)^2 = G_{TK}^2$$

- LC-tank noise factor:

$$F(R_{TK}) = \frac{2i_{PM}^2(R_{TK})}{4KTG_{TK}} = \frac{2(g_0 + g_2)^2 v_N^2(R_{TK})}{4KTG_{TK}} = \frac{2G_{TK}^2 v_N^2(R_{TK})}{4KTG_{TK}} = \frac{4KTG_{TK}}{4KTG_{TK}} = 1$$

g_m -Cell Noise Folding

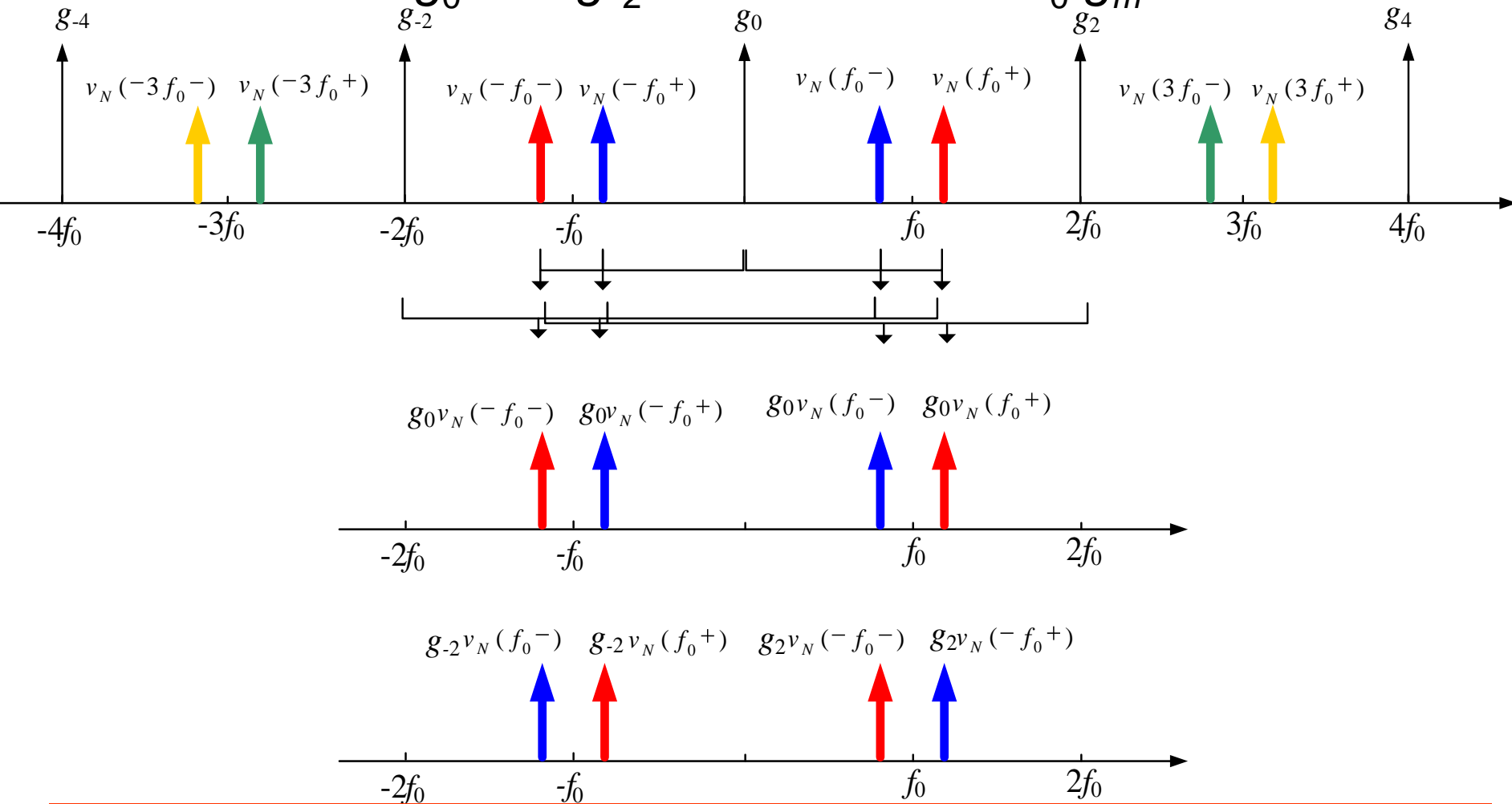- convolution: g_0 and g_2 harmonics and f_0 g_m -cell noise



- g_m -cell noise around odd multiples of the oscillation frequency is folded to the LC-tank noise around the oscillation frequency

g_m -Cell Noise Contribution

- phase-modulating noise component:

$$i_{PM} = (g_0 + g_2)v_N(f_0 + \Delta) + (g_0 + g_2)v_N(f_0 - \Delta) + \\ + (g_2 + g_4)v_N(3f_0 + \Delta) + (g_2 + g_4)v_N(3f_0 - \Delta) + \dots \\ + (g_{2i-2} + g_{2i})v_N((2i-1)f_0 + \Delta) + (g_{2i-2} + g_{2i})v_N((2i-1)f_0 - \Delta)$$

- phase-related noise power ($k \gg 1$, $g = g_0 = g_2 = \dots$):


$$i_{PM}^2(g_{m-IN}) = \left[(g_0 + g_2)^2 + (g_2 + g_4)^2 + \dots + (g_{2i-2} + g_{2i})^2 \right] v_N^2(g_{m-IN})$$

- number of g_{2i} harmonic components:

$$\frac{2f_0}{d} \frac{1}{2f_0} = \frac{1}{d}$$

- number of $(g_{2i-2} + g_{2i})$ folding pairs:

$$\frac{1}{2d} = \frac{2k}{2} = k$$

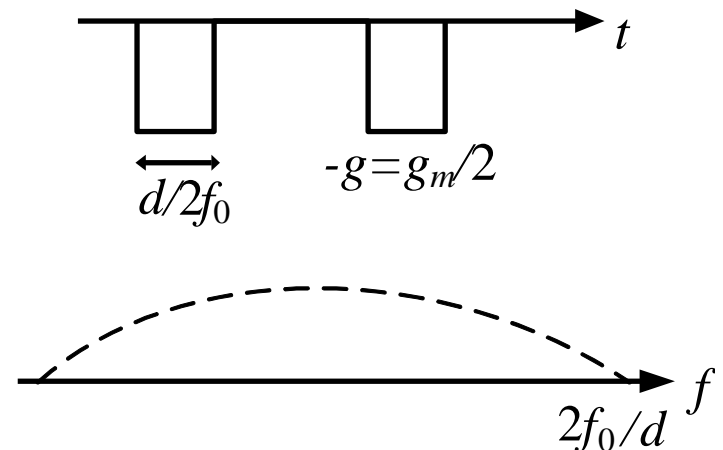

g_m -Cell Noise Contributions

- phase-related noise power:

$$i_{PM}^2(g_{m-IN}) = \frac{1}{2d}(g_{2i-2} + g_{2i})^2 v_N^2(g_{m-IN}) = \frac{2g_{2i}^2}{d} v_N^2(g_{m-IN}) = 2dg^2 v_N^2(g_{m-IN})$$

- g_m -cell noise transfer function:

$$g^2(g_{m-IN}) = 2dg^2 = 2d\left(\frac{g_m}{2}\right)^2 = 2\frac{1}{2k}(kG_{TK})^2 = kG_{TK}^2$$

- g_m -cell noise factors:

$$F(2r_B) = \frac{2i_{PM}^2(2r_B)}{4KTG_{TK}} = \frac{2kG_{TK}^2 4KTr_B}{4KTG_{TK}} = 2kr_B G_{TK} = kc$$

$$F(2I_C) = \frac{2i_{PM}^2(2I_C)}{4KTG_{TK}} = \frac{2kG_{TK}^2 2KT / g_m}{4KTG_{TK}} = kG_{TK} / g_m = \frac{1}{2}$$

r_B Noise Contribution – Be Precise

- phase-related noise power ($k \gg 1$):

$$i_{PM}^2(r_B) = \left[2g_0^2 + 4g_2^2 + 4g_4^2 + \dots + 4g_{2i-2}^2 \right] v_N^2(r_B)$$

- Parseval's Theorem:

$$g^2(r_B) = 2 \left(g_0^2 + 2 \sum_{i=1}^{\infty} |g_{2i}|^2 \right) = \frac{2}{T_2} \int_{-T_2/2}^{T_2/2} g_{\nabla}^2(t) dt = \frac{4}{T_2} \int_0^{\tau} g^2 \left(1 - \frac{t}{\tau}\right)^2 dt = \frac{4}{3} g^2 d$$


- r_B noise factor:

$$F(2r_B) = 2 \frac{2i_{PM}^2(r_B)}{4KTG_{TK}} = \frac{2}{3} kC$$


Bias Current-Source Noise

Transfer Function

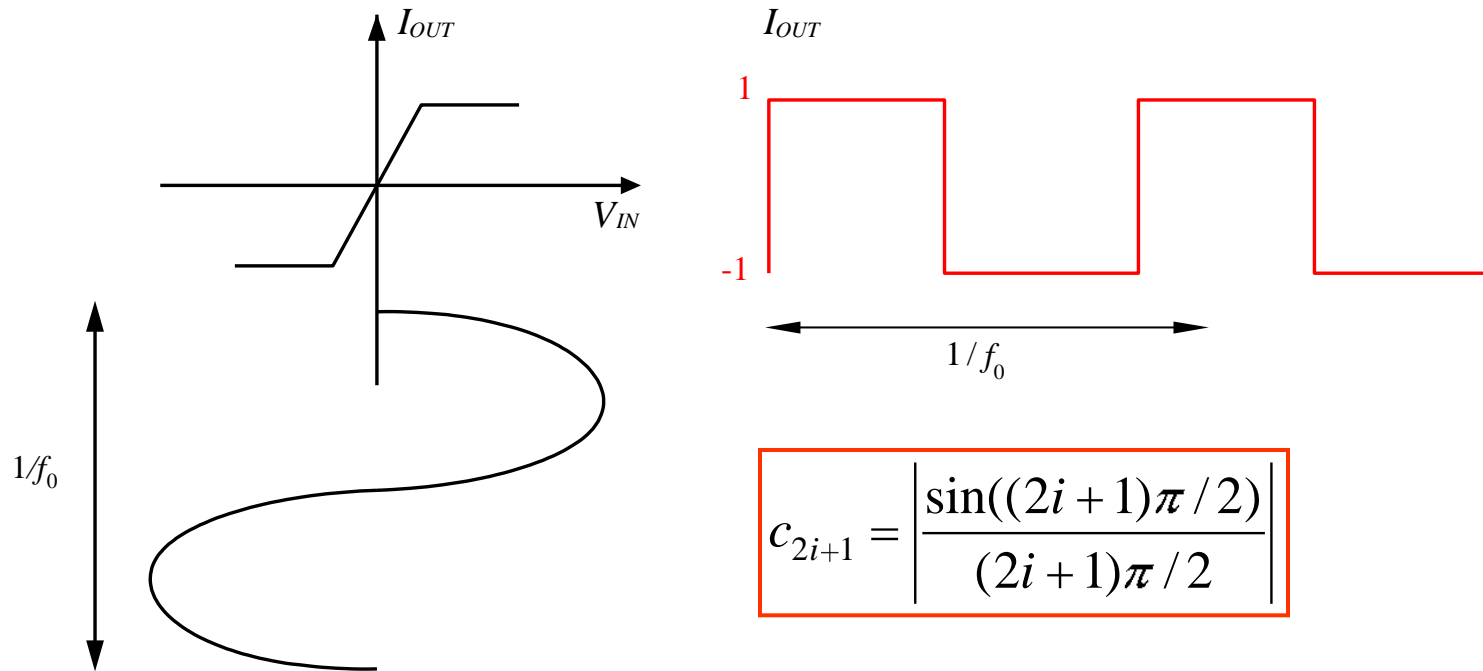- g_m -cell large-signal V-to-I transfer function



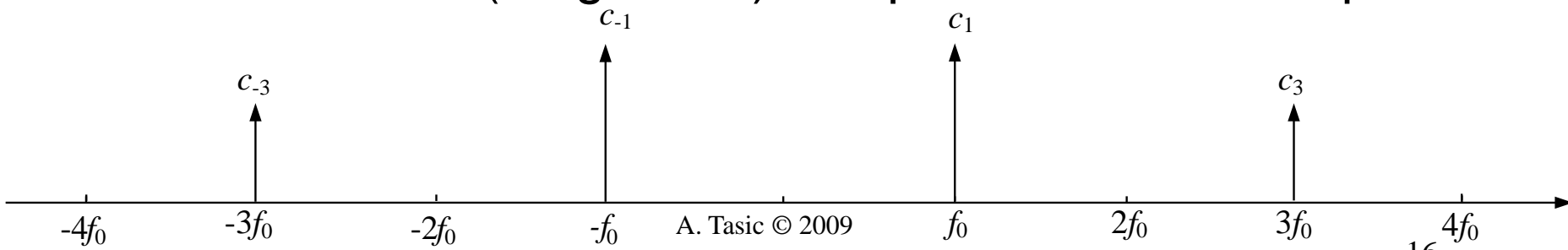- Fourier domain – (magnitude) complex harmonic components



BCS Noise Contribution

BCS noise around even multiples of the oscillation frequency is folded to the LC-tank noise around the oscillation frequency

- phase-related noise power:

$$i_{PM}^2(I_{BCS}) = \frac{i_{PM,DIFF}^2(I_{BCS})}{4} = \frac{1}{4} i_N^2(I_{BCS})$$

- BCS noise transfer function:

$$g^2(I_{BCS}) = \frac{1}{4}$$

- BCS noise factor:

$$F(I_{BCS}) = \frac{2i_{PM}^2(I_{BCS})}{4KTG_{TK}} = \frac{KTg_m(1+2r_Bg_m)}{4KTG_{TK}} = \frac{KT2kG_{TK}(1+2kc)}{4KTG_{TK}} =$$

$$= \frac{1}{2}k(1+2kc) = k\left(\frac{1}{2} + kc\right) \cong k F(2I_C) + F(2r_B)$$

Phase-Noise Model of Bipolar Switching LC-Oscillators

- Noise factor:

$$F = F(R_{TK}) + F(2I_C) + F(2r_B) + F(I_{BCS})$$

$$F = 1 + \frac{1}{2} + \frac{2}{3}kc + k\left(\frac{1}{2} + kc\right) = 1 + \frac{1}{2}(1+k) + kc\left(\frac{2}{3} + k\right)$$

- Phase noise:

$$\mathcal{L} = \frac{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_C) + \mathcal{L}(2r_B) + \mathcal{L}(I_{BCS})}{(4\pi C_{TOT}\Delta)^2} = \frac{4KTG_{TK}F}{v_s^2(4\pi C_{TOT}\Delta)^2} \quad v_s = \frac{8}{\pi}kV_T$$

$$\mathcal{L} = \frac{4KTG_{TK}}{(4\pi C_{TOT}\Delta)^2} \left(\frac{\pi}{8V_T}\right)^2 \frac{1 + \frac{1}{2}(1+k) + kc\left(\frac{2}{3} + k\right)}{k^2}$$

Phase Noise Model of Bipolar Switching LC-Oscillators

$$F = 1 + \frac{1}{2} + \frac{2}{3}kc + k\left(\frac{1}{2} + kc\right)$$

- **Constant phase-noise contributions**
 - LC-tank noise contribution ~ 1
 - g_m -cell current shot noise contribution $\sim \frac{1}{2}$
- **Small-signal loop-gain related contributions**
 - g_m -cell base-resistance noise contribution $\sim 0.66ck$
 - phase-noise contribution of the bias current source is k -times larger than the noise contribution of the g_m -cell $\sim k(\frac{1}{2}+ck)!$

Low/High-Performance VCO Designs

- high ss loop-gain, high quality LC-tank, BCS noise eliminated:

e.g., $k \gg 1 (=10)$, $c \ll 1 (\sim 0.01)$

$$\mathcal{L} \sim \frac{1 + \frac{1}{2} + \frac{2}{3}kc}{k^2} = \frac{7.8}{5} \frac{1}{10} \frac{1}{10} \sim \frac{1}{k^2}$$

- high ss loop-gain, high quality LC-tank, BCS noise present:

e.g., $k \gg 1 (=10)$, $c \ll 1 (\sim 0.01)$

$$\mathcal{L} \sim \frac{k(\frac{1}{2} + kc)}{k^2} = \frac{\frac{1}{2} + kc}{k} = \frac{3}{5} \frac{1}{10} \sim \frac{1}{k}$$


- low ss loop-gain, low quality LC-tank, BCS noise present:

e.g., $k \sim 1 (=2)$, $c \sim 1 (\sim 0.5)$

$$\mathcal{L} \sim \frac{\frac{7}{6} + (1+k)\frac{3}{2}}{k^2} = \frac{5}{4} \sim 1$$

Single/Double-Switch CMOS LC-VCOs


$$i_N^2(G_{TK}) = 2KTG_{TK}$$

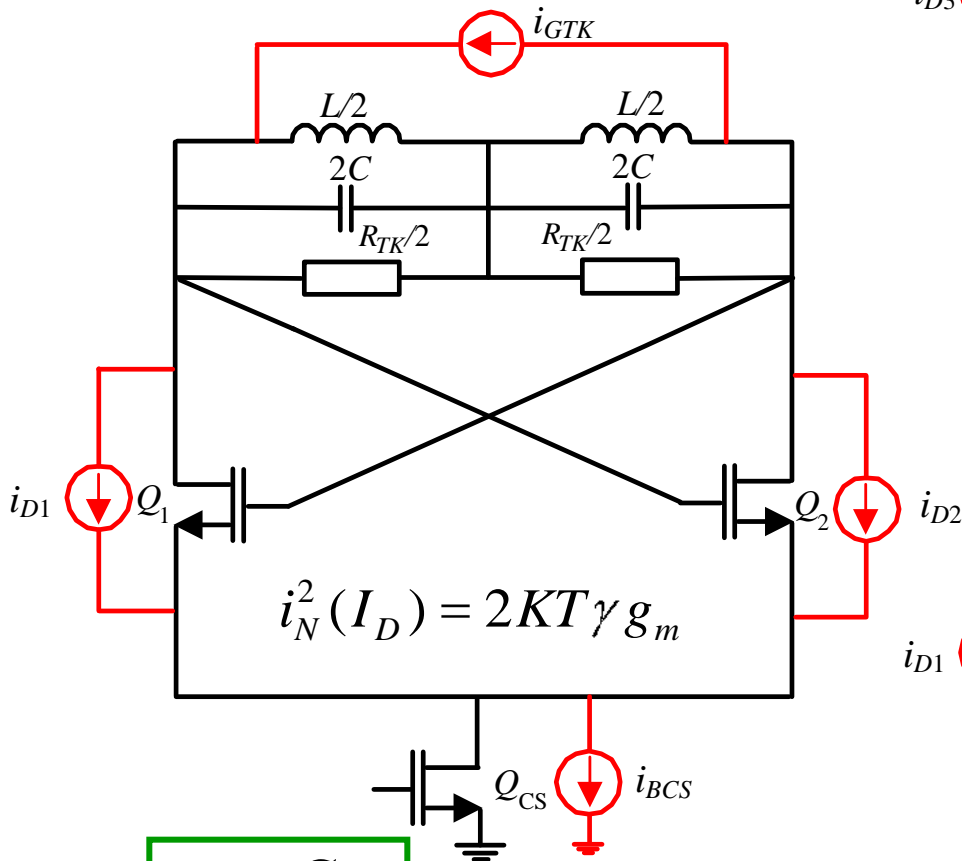

$$d_N = \frac{G_{TK}}{g_m}$$

$$i_N^2(I_{BCS}) = 2KT\gamma g_{m,CS}$$

A. Tasic © 2009

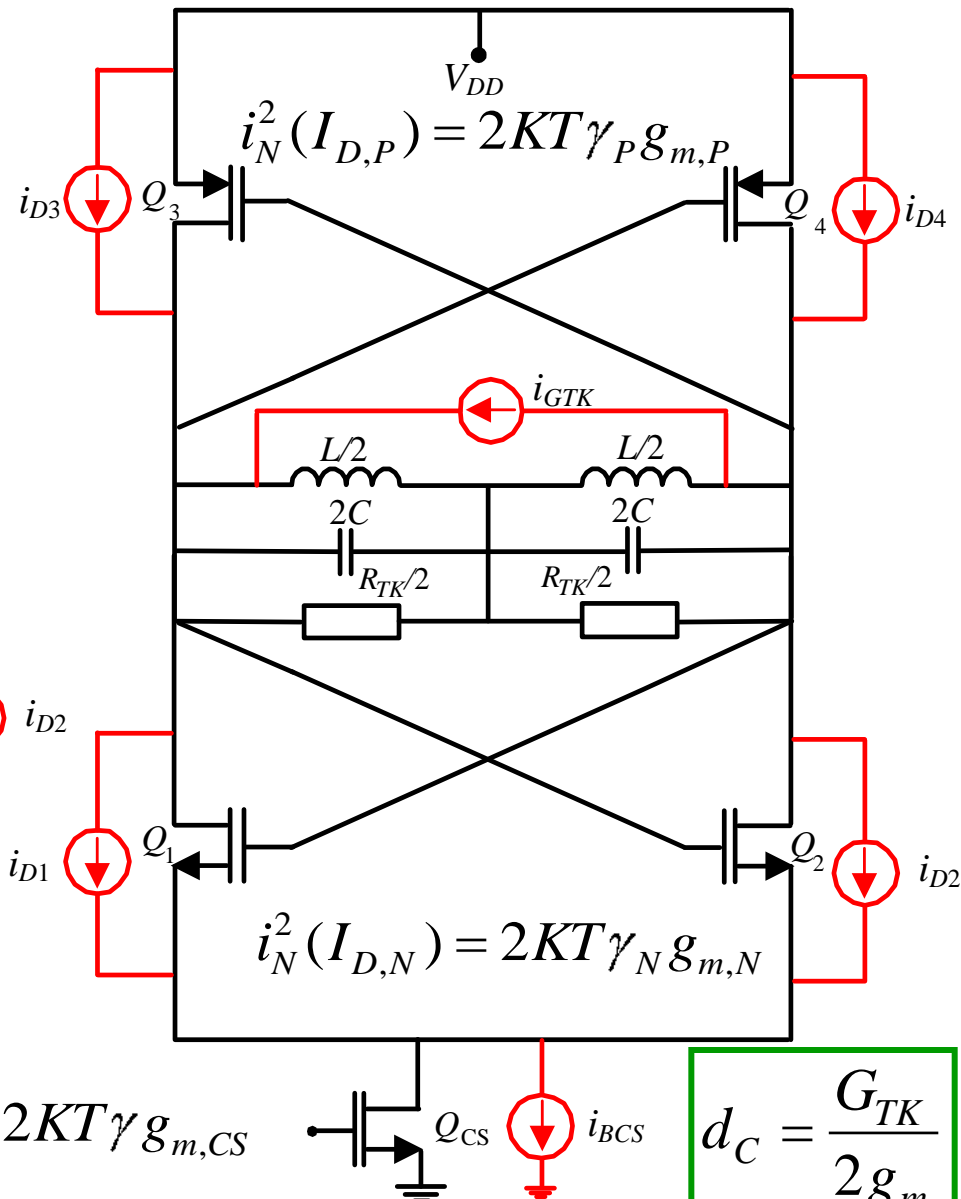

$$i_N^2(I_{D,N}) = 2KT\gamma_N g_{m,N}$$

$$d_C = \frac{G_{TK}}{2g_m}$$

Phase Noise Model of CMOS LC-Oscillators

- Noise factor ($\gamma_N = \gamma_P$, $g_{m,N} = g_{m,P}$):

$$F_{SS} = F(R_{TK}) + F(2I_D) + F(I_{BCS})$$

$$F_{DS} = F(R_{TK}) + F(4I_D) + F(I_{BCS})$$

$$F_{SS} = 1 + \gamma + \gamma g_{m,CS} / (4G_{TK})$$

$$F_{DS} = 1 + \gamma + \gamma g_{m,CS} / G_{TK}$$

- Phase noise:

$$\mathcal{L} = \frac{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_D) + \mathcal{L}(I_{BCS})}{(4\pi C_{TOT} \Delta)^2} = \frac{4KTG_{TK} F}{v_s^2 (4\pi C_{TOT} \Delta)^2}$$

$$\mathcal{L}_{SS} = \frac{4KTG_{TK}}{(4\pi C \Delta)^2} \frac{1 + \gamma + \gamma g_{m,CS} / (4G_{TK})}{\left(\frac{2}{\pi} I_{TAIL} R_{TK}\right)^2}$$

$$\mathcal{L}_{DS} = \frac{4KTG_{TK}}{(4\pi C \Delta)^2} \frac{1 + \gamma + \gamma g_{m,CS} / G_{TK}}{\left(\frac{4}{\pi} I_{TAIL} R_{TK}\right)^2}$$

Phase Noise Model of CMOS LC-Oscillators

$$F = 1 + \gamma + \gamma g_{m,CS} / G_{TK}$$

- **Constant phase-noise contributions**
 - LC-tank noise contribution ~ 1
 - g_m -cell drain-current thermal noise contribution $\sim \gamma$
- **Small-signal loop-gain related contributions (?)**
 - bias current source noise contribution $\sim \gamma g_{m,CS} / G_{TK} (k\gamma)$

CMOS vs. Bipolar LC-Oscillators

- noise factors (for removed BCS noise):

$$F_{BIP} = 1 + \frac{1}{2} + \frac{2}{3}kc$$

$$F_{CMOS} = 1 + \gamma$$

- bipolar VCO better for the same power consumption ($v_{s,BIP} = v_{s,CMOS}$)

$$\frac{3}{2} + \frac{2}{3}kc < \frac{5}{3} \quad \Rightarrow$$

$$kr_B < \frac{R_{TK}}{8}$$

- e.g., $k=10$, $R_{TK}=800\Omega$

$$r_B < \frac{800}{80} = 10 \Omega$$

- e.g., $k=10$, $R_{TK}=80\Omega$

$$r_B < \frac{80}{80} = 1 \Omega$$

CMOS vs. Bipolar LC-Oscillators

- power consumption figure of merit:

$$FOM = 10 \log \left(\mathcal{L}(\Delta) \left(\frac{\Delta}{\omega_0} \right)^2 V_{CC} I_{CC} \right)$$

- $V_{CC}=1.8V$, $v_{s,BIP}=0.4V$, $v_{s,SS-CMOS}=1.2V$, ($3I_{CC,BIP}=I_{CC,SS-CMOS}$)

$$FOM_{BIP} = FOM_{SS-CMOS} + 4.8dB$$

- $V_{CC}=1.8V$, $v_{s,BIP}=0.4V$, $v_{s,DS-CMOS}=1.2V$, ($1.5I_{CC,BIP}=I_{CC,DS-CMOS}$)

$$FOM_{BIP} = FOM_{DS-CMOS} + 7.8dB$$


Phase-Noise Model Conclusions

- Parametric Phase-Noise Model
 - electrical circuit parameters (ss loop gain)
 - worst-case phase noise (bandwidth unlimited)
- Bipolar vs. CMOS LC-Oscillators
 - bipolar ss loop-gain related contributions
 - $V_{S,BIP} \sim k (\ll V_{CC}), V_{S,CMOS} \sim V_{CC}$
 - bipolar capacitive tapping for larger $v_{S,BIP}$, but also larger k -related noise contributions and power consumption

Verification of the Phase-Noise Model

VCO Noise Contributions

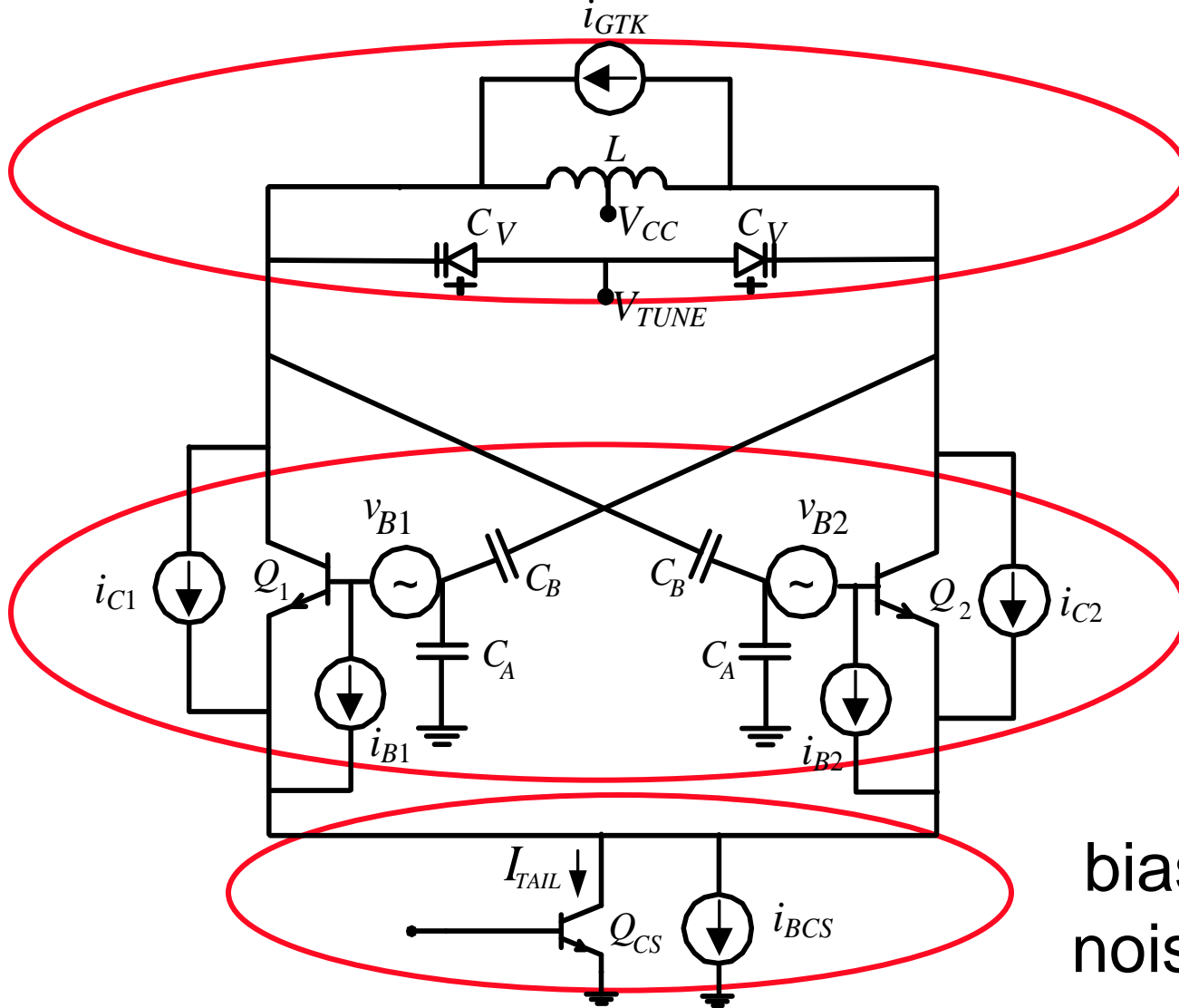- $f_0 \sim 5.74\text{GHz}$, $R_{TK} \sim 340\Omega$, $n \sim 1.65$, $c \sim 0.25$, $V_{CC} = 2.2\text{V}$




LC-tank
noise ~ 1

transconductor
noise \sim
 $n(0.5 + 0.66c \cdot k)$



bias current-source
noise $\sim n(0.5 + c \cdot k) \cdot k$

g_m -Cell Noise Contributions

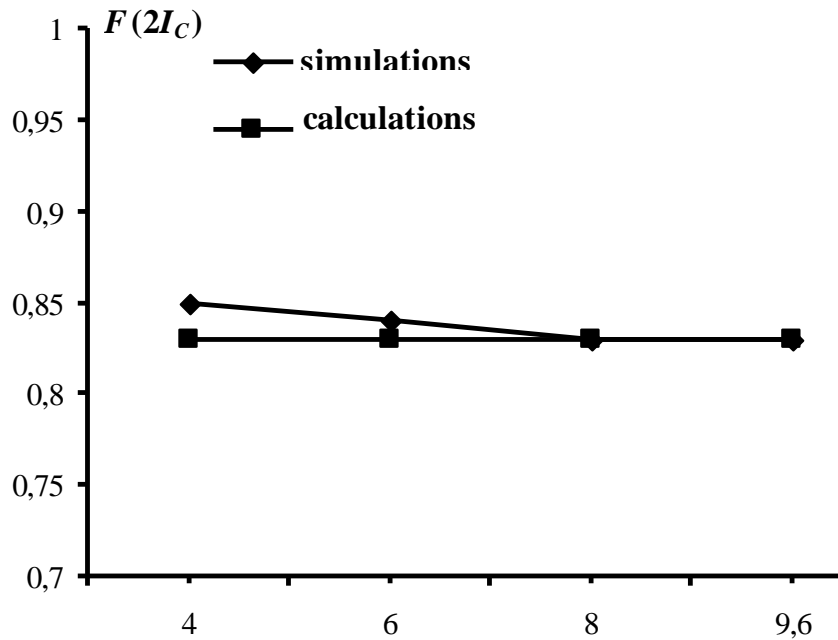- $k=0.5g_m R_{TK} < 0.5g_{m,actual} R_{TK} = 0.5g_m R_{TK} / (1+g_m r_E) = k_{actual}$



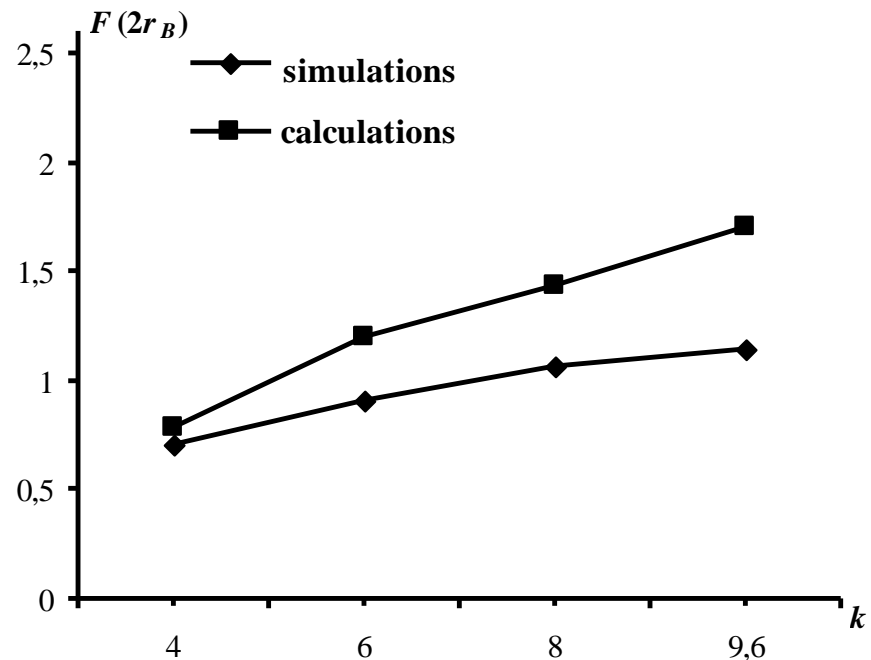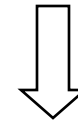
$$F(2r_B) = \frac{2}{3} nkc = \frac{2}{3} 1.65 \cdot 0.25 \cdot k \cong 0.27 \cdot k$$





$$F(I_C) = \frac{n}{2} \cong 0.87$$

Bias Noise Contributions

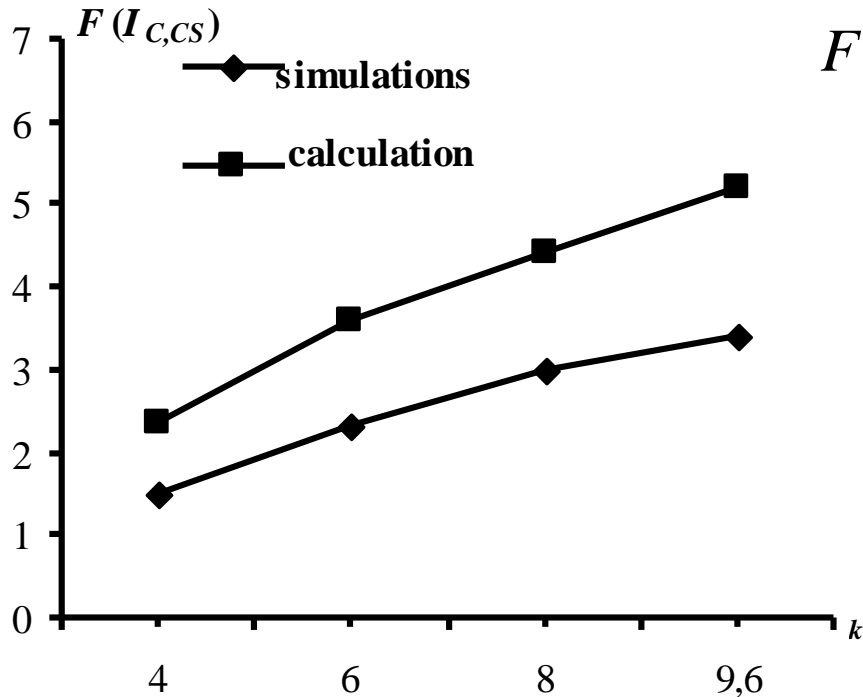
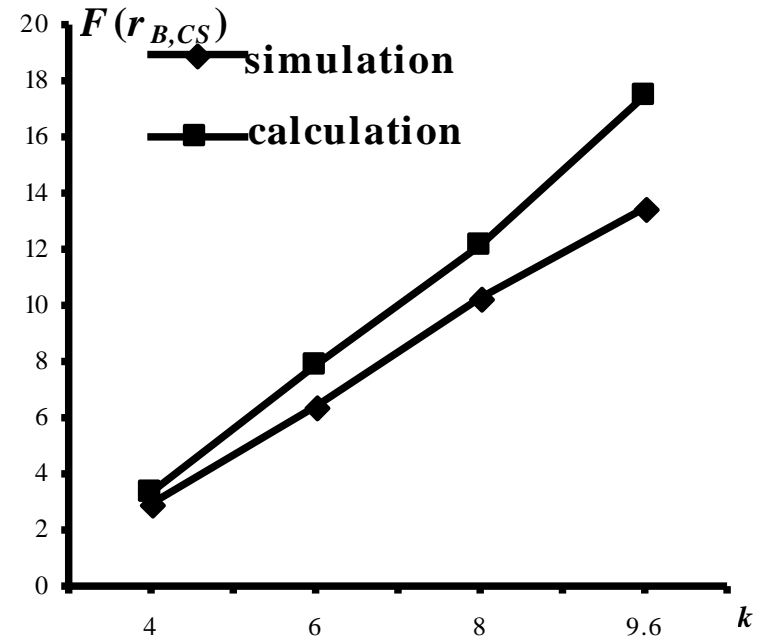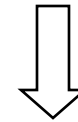
$$F(r_{B,CS}) = knkc = 1.65 \cdot 0.25 \cdot k^2 \cong 0.41 \cdot k^2$$




$$F(I_{C,CS}) = \frac{1}{2}nk = 0.82k$$

Suppression of Bias Current-Source Noise in LC-Oscillators

Outline

- Contribution of Bias Current-Source Noise to Phase Noise of LC-Oscillators
- Techniques for Reduction of Bias Current-Source Noise
- Noise Analysis of Degenerated Bias Current Source
- Bias Noise Suppression - Design Example

VCO Noise Contributions

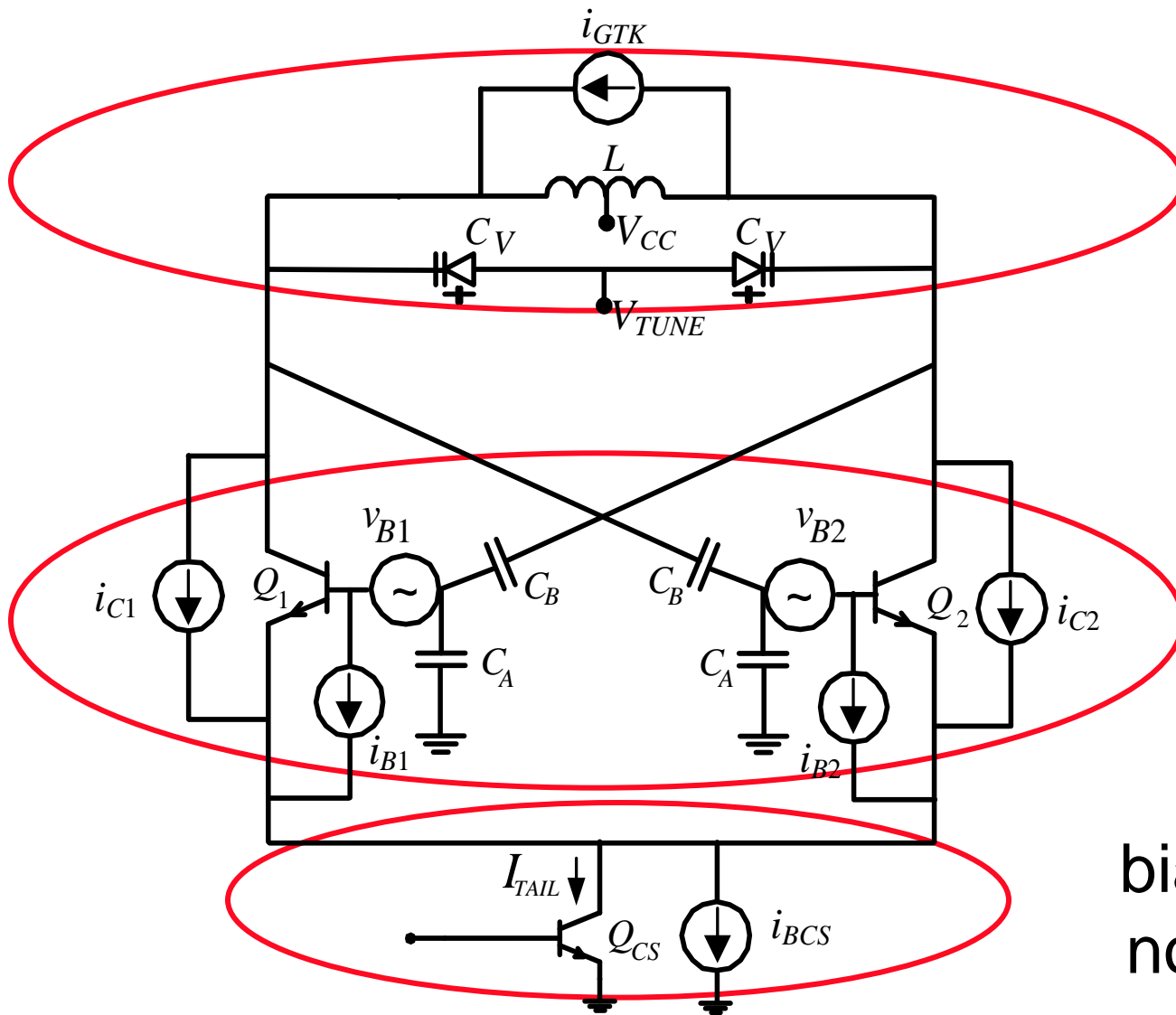


LC-tank
noise ~ 1

transconductor
noise $\sim 0.5+c \cdot k$

bias current-source
noise $\sim (0.5+c \cdot k) \cdot k$


VCO Noise Contributions

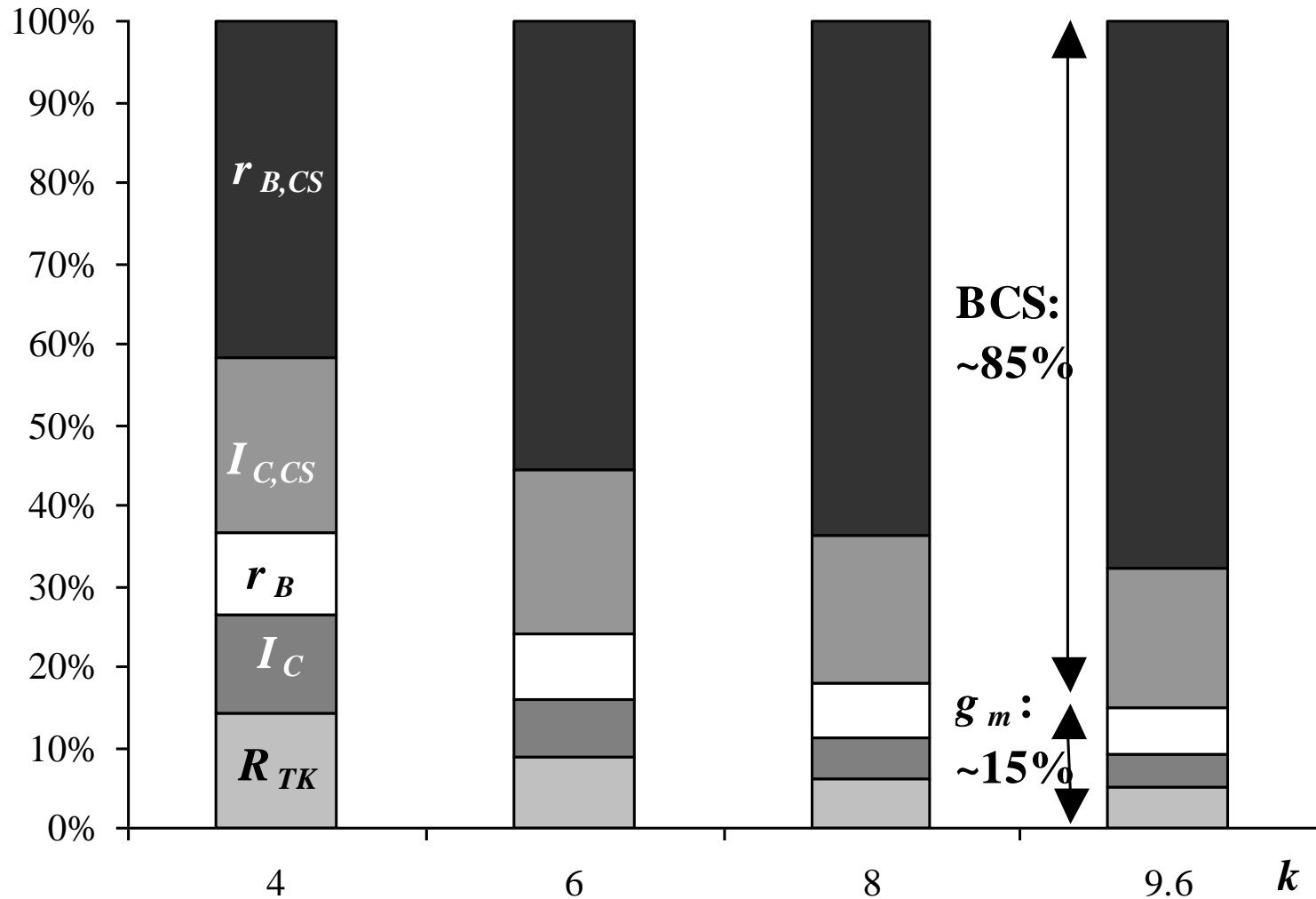- $f_0 \sim 5.74\text{GHz}$, $R_{TK} \sim 340\Omega$, $n \sim 1.65$, $c \sim 0.25$, $V_{CC} = 2.2\text{V}$




Phase-Noise Ratio
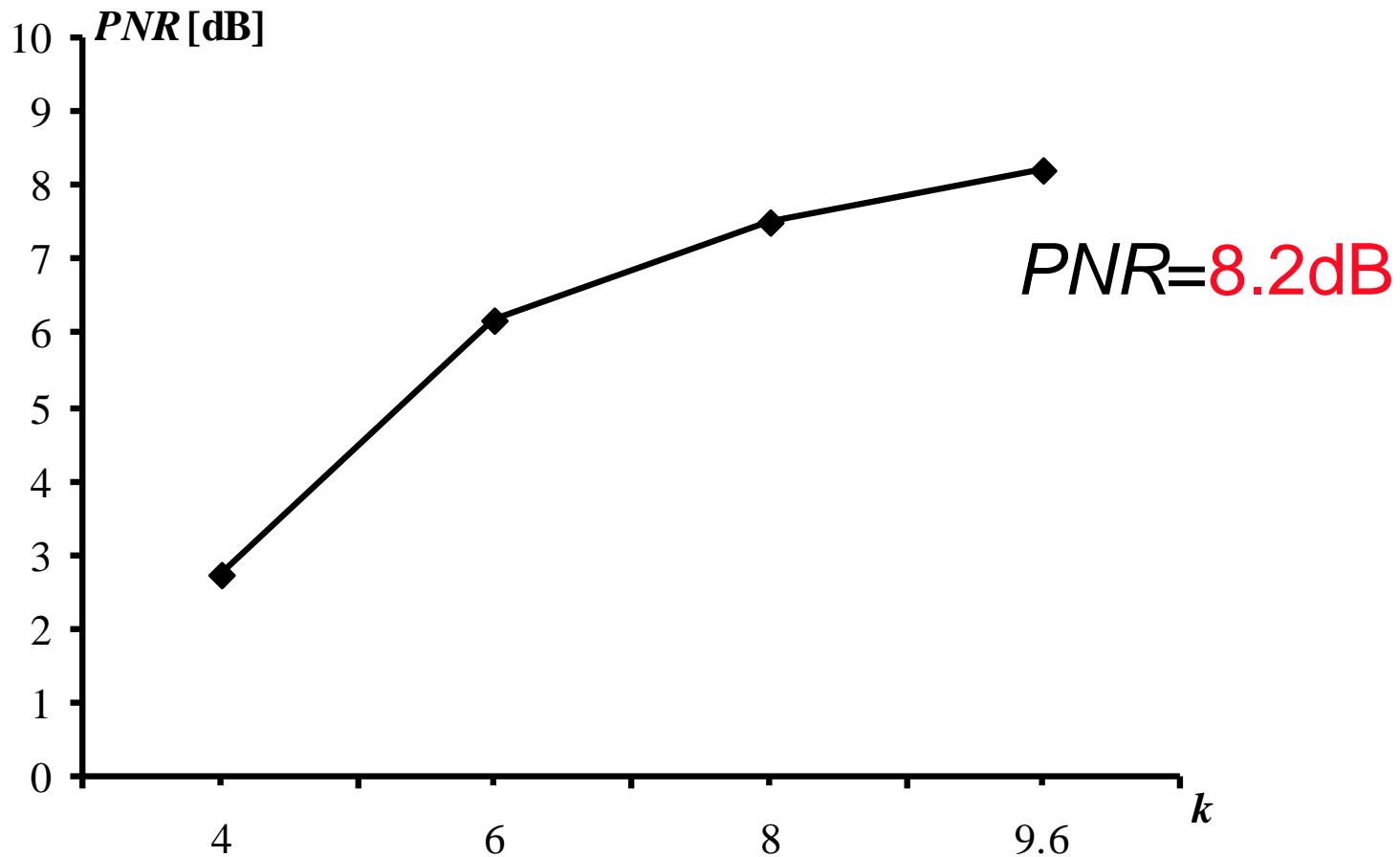
$$PNR = \frac{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_C) + \mathcal{L}(2r_B) + \mathcal{L}(I_{BCS})}{\mathcal{L}(R_{TK}) + \mathcal{L}(2I_C) + \mathcal{L}(2r_B)} = 1 + \frac{k(\frac{n}{2} + nkc)}{1 + \frac{n}{2} + \frac{2}{3}nkc}$$




Bias Noise Reduction Techniques

resistive
degeneration

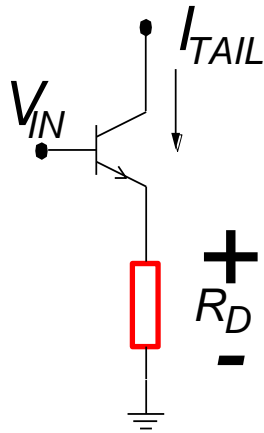


☹ high supply
required

inductive
degeneration

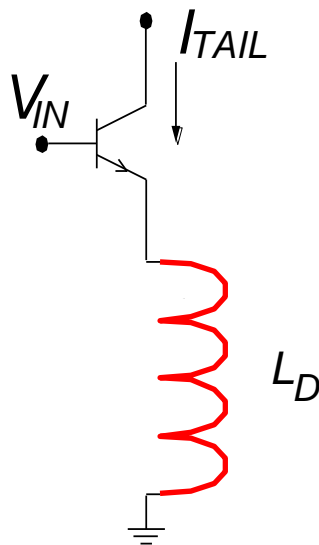



☹ large area if
integrated
☹ noise injection if
discrete

filtering?

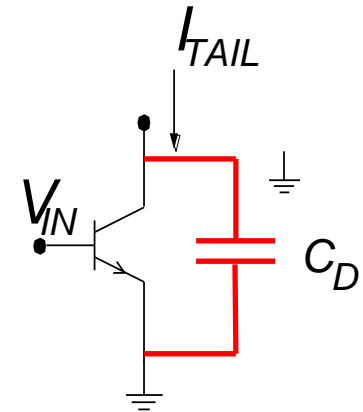



☹ transconductor
noise always ON
☹ reduced output
impedance

Capacitive Filtering

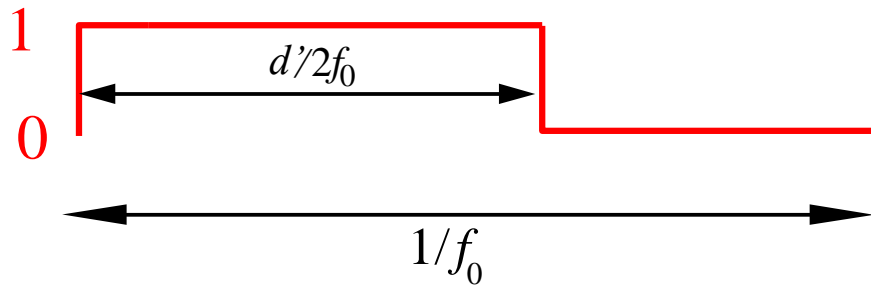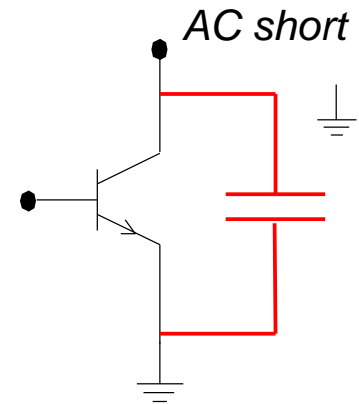

$$d' = \frac{1}{2}(1 + d)$$

$$F'(2I_C) \sim k \frac{n}{2}$$

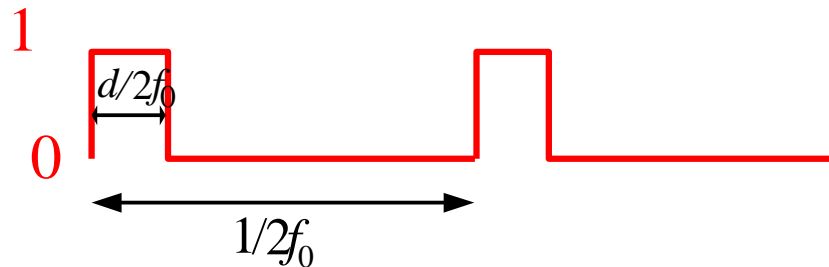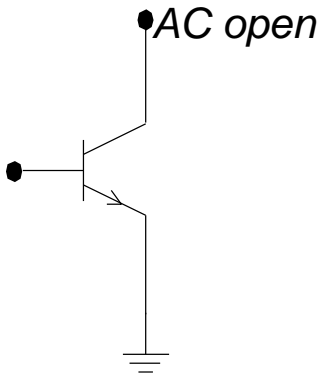


$$d = \frac{1}{2k}$$

$$F(2I_C) \sim \frac{n}{2}$$


- for $k=10$, $d=5\%$, $d'=52.5\%$, and $F' > F$

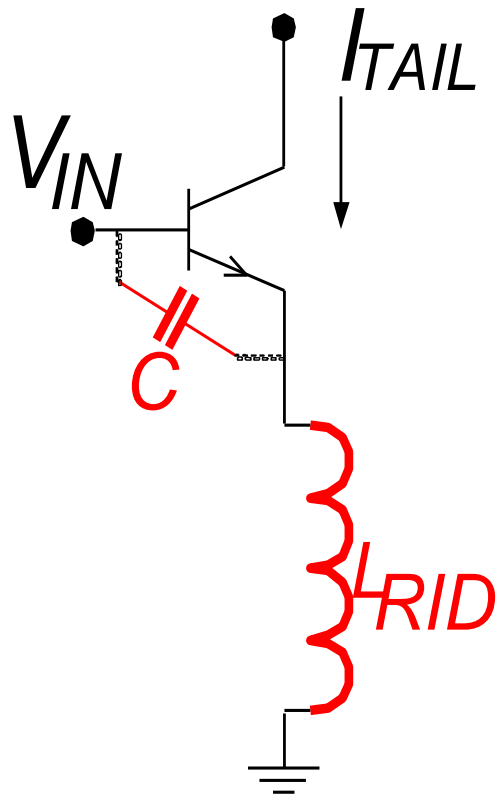Bias Current Source with Resonant-Inductive Degeneration



- L_{RID} matched to C_{Π} at $2f_0$
- $r_{B,CS}$ noise contribution reduced
 - transconductance gain small at resonance
 - series resonance
- $I_{B,CS}$ noise contribution small
 - common-base like configuration (gain of 1)
- $I_{C,CS}$ noise contribution removed
 - parallel resonance
 - emitter open at resonance ($I_{C,CS}$ floats)

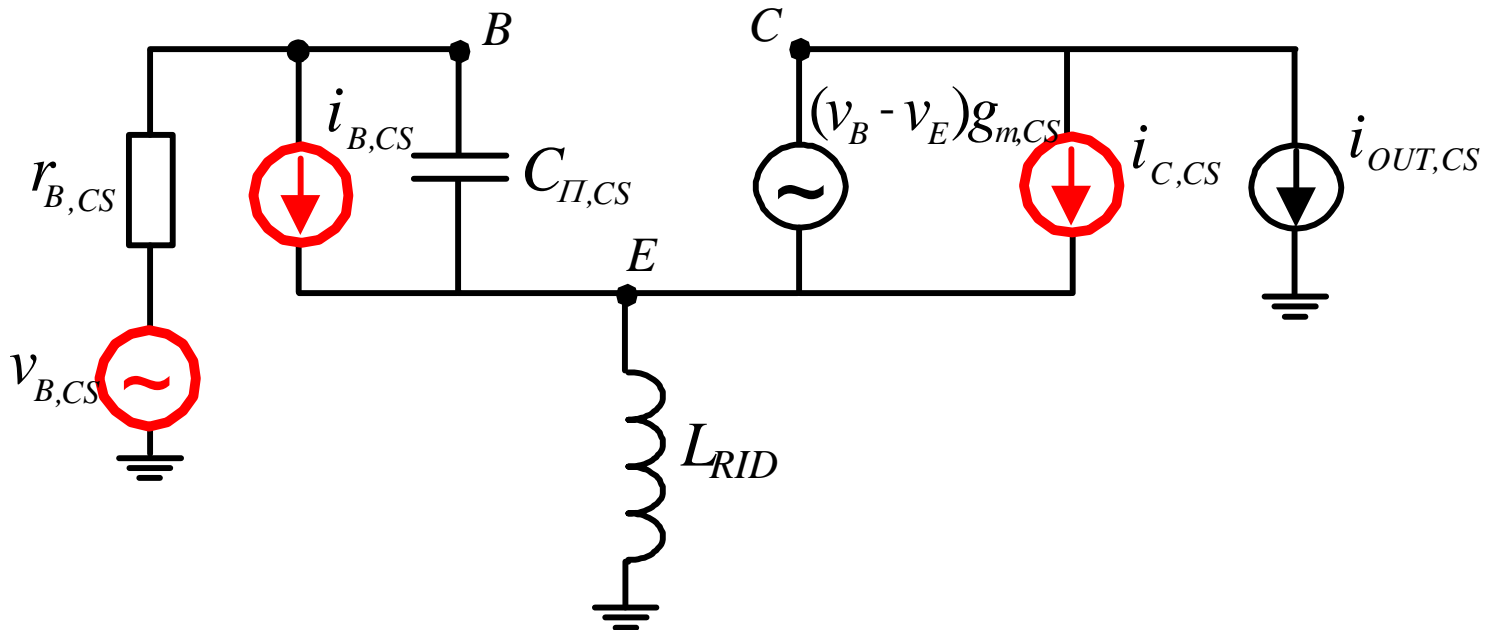Circuit Diagram for Noise Transfer Functions



- $i_{C,CS}$ to i_{OUT} : $v_{B,CS}$ short, $i_{B,CS}$ open
- $i_{B,CS}$ to i_{OUT} : $v_{B,CS}$ short, $i_{C,CS}$ open
- $v_{B,CS}$ to i_{OUT} : $i_{C,CS}$ open, $i_{B,CS}$ open

Bias Current-Source Noise Contributions

$$\frac{i_{OUT}}{v_N(r_{B,CS})}(f) = -\frac{1}{\omega_T L_{RID} + \underbrace{j\omega L_{RID} + \frac{1}{j\omega C_{\Pi}}}_{\text{series resonance}}} \frac{\omega_{T,CS}}{\omega} = -g_m \left(\frac{f}{f_{T,CS}} \right)$$

series resonance

$$\frac{i_{OUT}}{i_N(I_{B,CS})}(f) = \frac{g_{m,CS}}{g_{m,CS} + \frac{C_{\Pi} r_{B,CS}}{L_{RID}} + \underbrace{j\omega C_{\Pi} + \frac{1}{j\omega L_{RID}}}_{\text{parallel resonance}}} = \frac{1}{1 + r_B g_m \left(\frac{f}{f_T} \right)^2} \cong 1$$

parallel resonance

$$\frac{i_{OUT}}{i_N(I_{C,CS})}(f) = 1 - \frac{g_{m,CS}}{g_{m,CS} + \frac{C_{\Pi} r_{B,CS}}{L_{RID}} + \underbrace{j\omega C_{\Pi} + \frac{1}{j\omega L_{RID}}}_{\text{parallel resonance}}} = 1 - \frac{1}{1 + r_B g_m \left(\frac{f}{f_{T,CS}} \right)^2} \cong 0$$

parallel resonance

BCS w/ RID vs. BCS w/o RID

- BCS noise **with** degeneration

$$i_{CS,RID}^2 = 4kT \frac{g_{m,CS}}{2} \left[0 + \left(\frac{f_{T,CS}}{2f_0} \right)^2 \frac{1}{\beta} + 2r_{B,CS} g_{m,CS} \right] \left(\frac{2f_0}{f_{T,CS}} \right)^2$$

- BCS noise **without** degeneration

$$i_{CS}^2 = 4kT \frac{g_{m,CS}}{2} \left[1 + 0 \left[\left(\frac{f_{T,CS}}{2f_0} \right)^2 \frac{1}{\beta} + 2r_{B,CS} g_{m,CS} \right] \right]$$


- more than a factor $(f_{T,CS}/2f_0)^2$ noise reduction after RID

$$i_{CS,RID}^2 < i_{CS}^2 \left(\frac{2f_0}{f_{T,CS}} \right)^2$$


- for $(f_{T,CS}/2f_0)=5$, a factor of **25** reduction

VCO Noise Contributions after RID applied to BCS

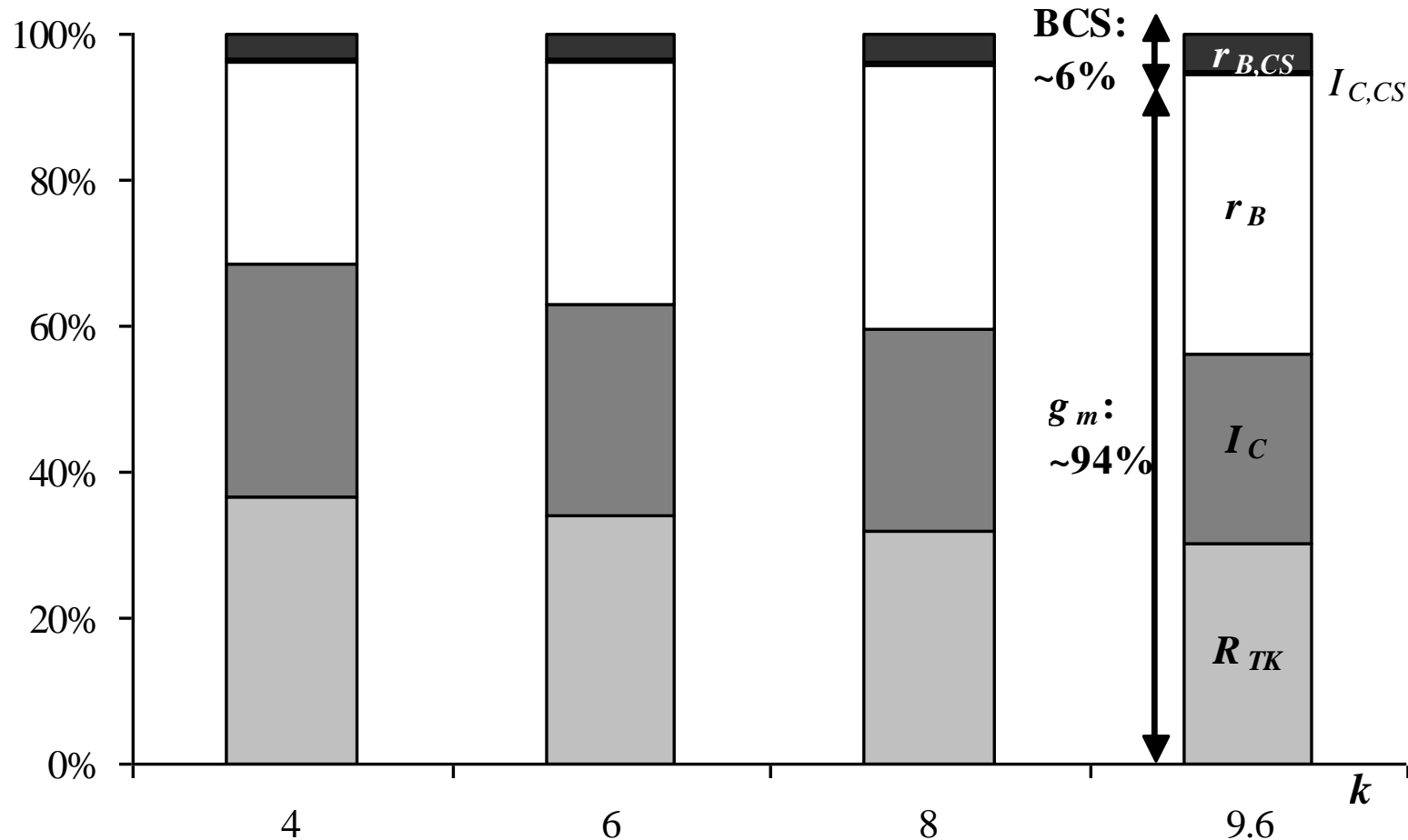- $f_0 \sim 5.74\text{GHz}$, $L_{RID} \sim 1.3\text{nH}$, $R_{TK} \sim 340\Omega$, $n \sim 1.65$, $c \sim 0.25$, $V_{CC} = 2.2\text{V}$





5.7GHz-band VCO

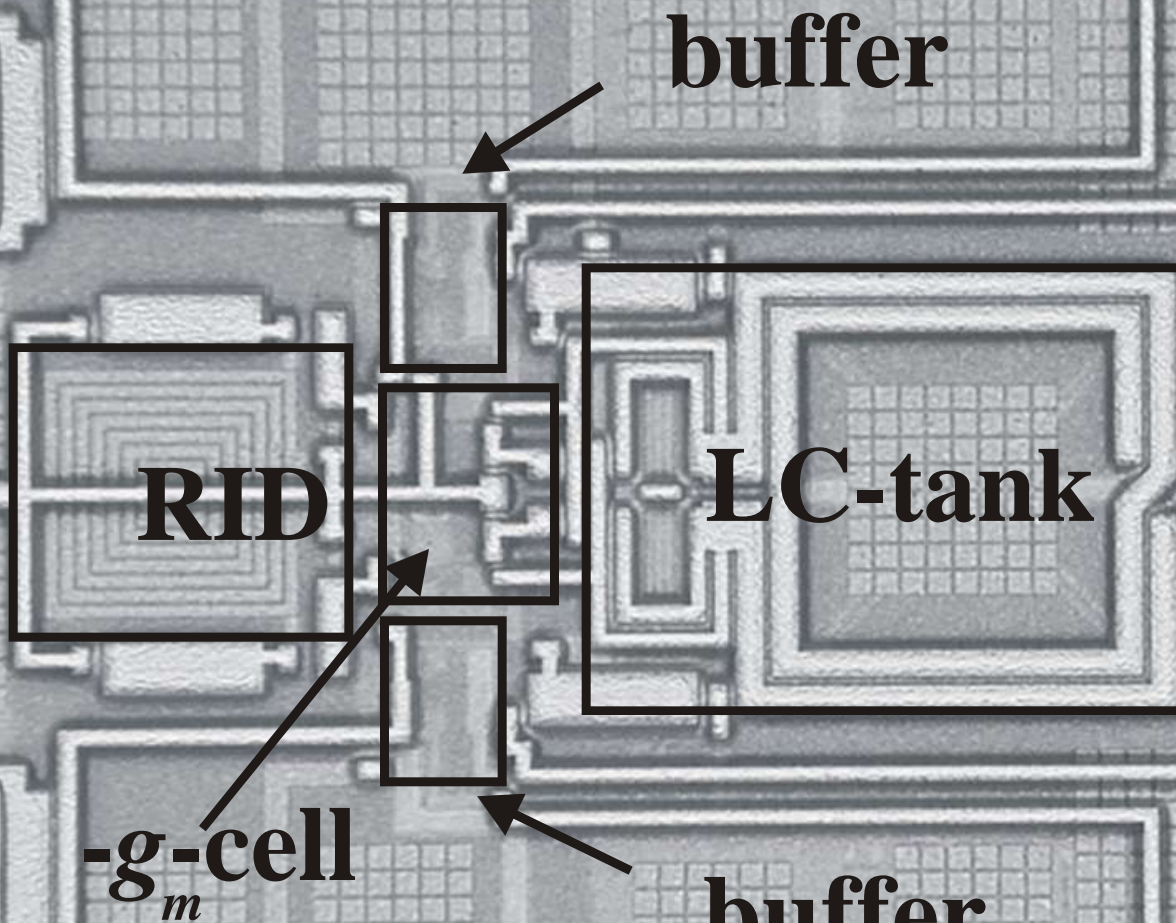


- 5 metals
- active area 0.1mm^2
- $L_{RID}=2.6\text{nH}$, 7-turns, 0.01mm^2

VCO w/ RID vs. VCO w/o RID

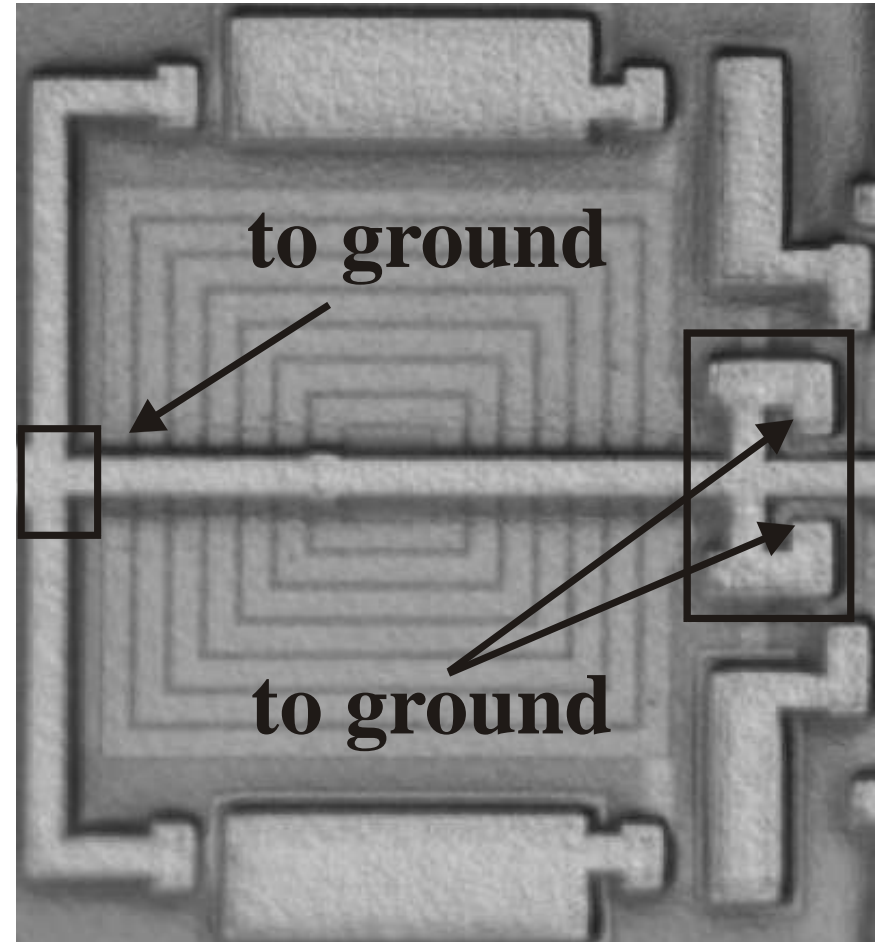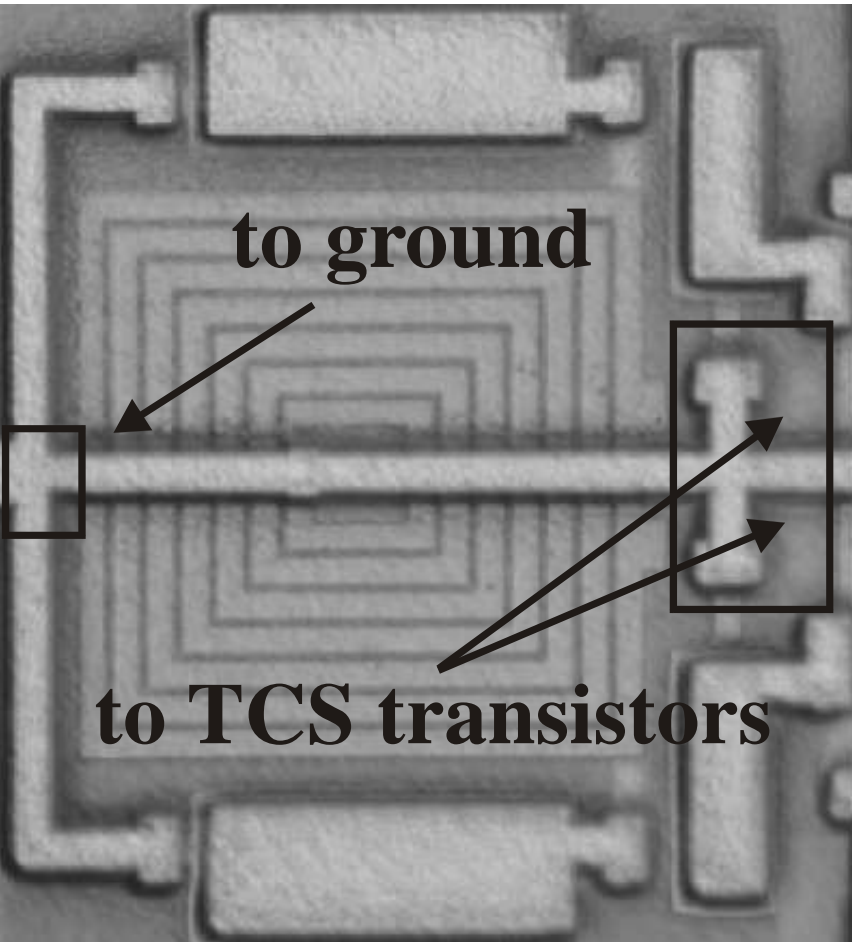

Phase Noise (w/ RID vs. w/o RID)

Ref -10 dBm

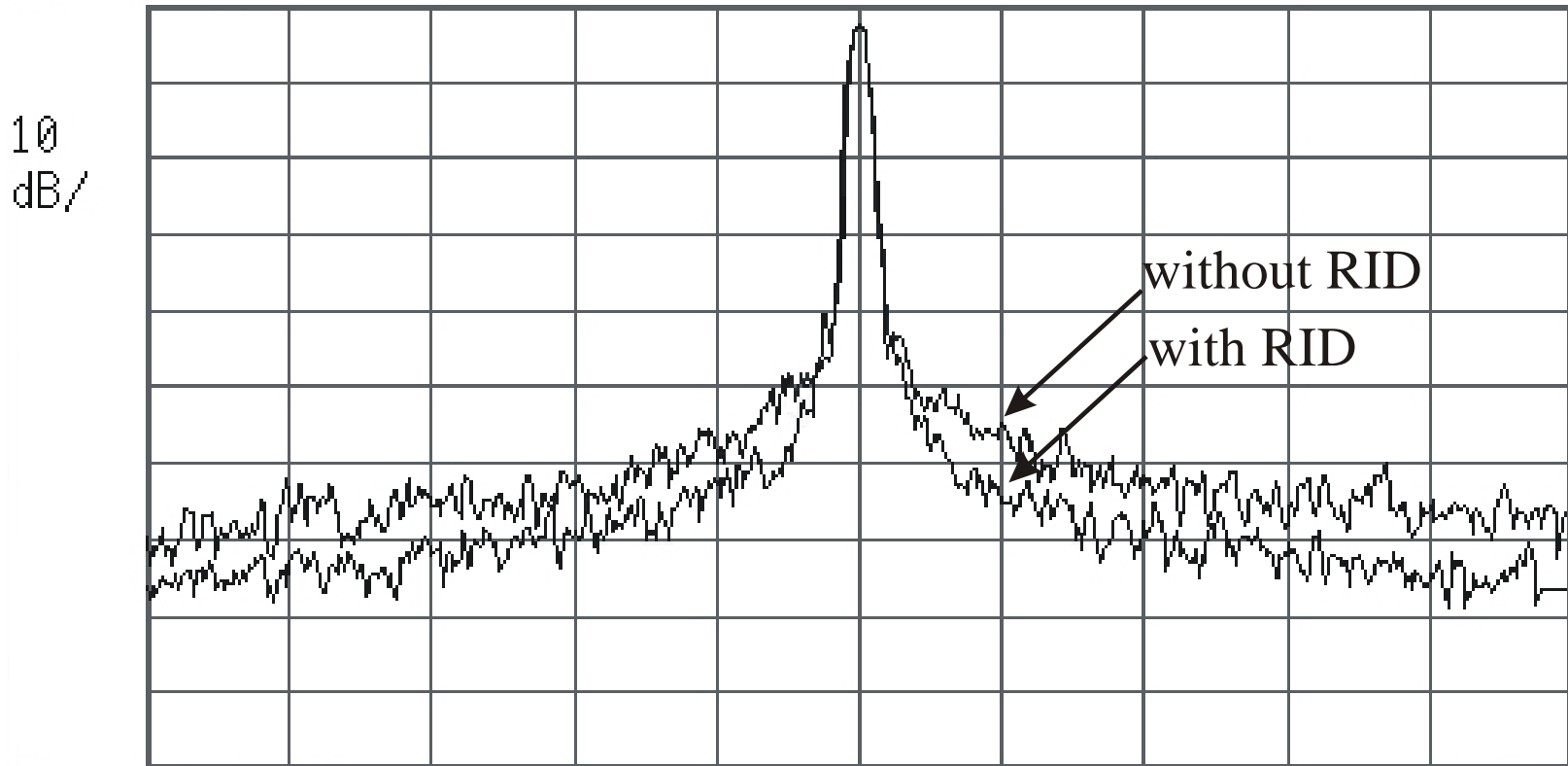

Center 5.73 GHz

Span 10 MHz

#Res BW 100 kHz

#VBW 10 kHz

Sweep 7.88 ms (601 pts)

- **6dB** phase-noise improvement with RID
- **-112dBc/Hz @ 1MHz from 5.7GHz @ 4.8mA&2.2V**

RID Conclusions

- BCS noise \gg g_m -cell and LC-tank noise
- Resonant inductive degeneration
 - ☺ good suppression of high frequency BCS noise
 - ☺ low voltage operation
 - ☺ small chip area (vs. discrete solutions)

 - ☹ BCS DC noise upconversion
 - ☹ large area (vs. resistive degeneration)
 - ☹ poorer noise suppression at high supplies (vs. resistive degeneration)

Oscillator Conclusions

- Spectral Analysis of Noise in LC-Oscillators
- Phase-Noise Model
 - LC-tank, g_m -cell, bias current source contributions
- Bipolar vs. CMOS LC-Oscillators
- Oscillator Noise Reduction Methods
 - Resonant-Inductive Degeneration

Future Worries

- Low-(Supply and Swing)-Voltage Operation
 - Linear and Quasi-Linear Phase-Noise Model
 - Low-Performance Oscillators
 - Noise-Reduction Methods

Conclusions

Conclusions

- **Spectral Analysis of Noise in LC-Oscillators**
 - LC-tank, g_m -cell, bias current source noise contributions
- **Bipolar and CMOS VCO Noise Factors**
- **LC-Oscillators Noise Reduction Methods**
- **Mixer Noise Factor from VCO Noise Factor**
- **Oscillator Phase Noise in Receiver's SNR**
- **Mixer Noise Factor in a Receiver**
- **LNA Noise Factor in a Receiver**
- **BBFilter Noise Transfer vs. LO/Mix Duty**