

**EECS 142**



Integrated Circuits for Communication


## *Lecture 7: Distortion Analysis*

Prof. Ali M. Niknejad

University of California, Berkeley

Copyright © 2005 by Ali M. Niknejad

# Introduction to Distortion

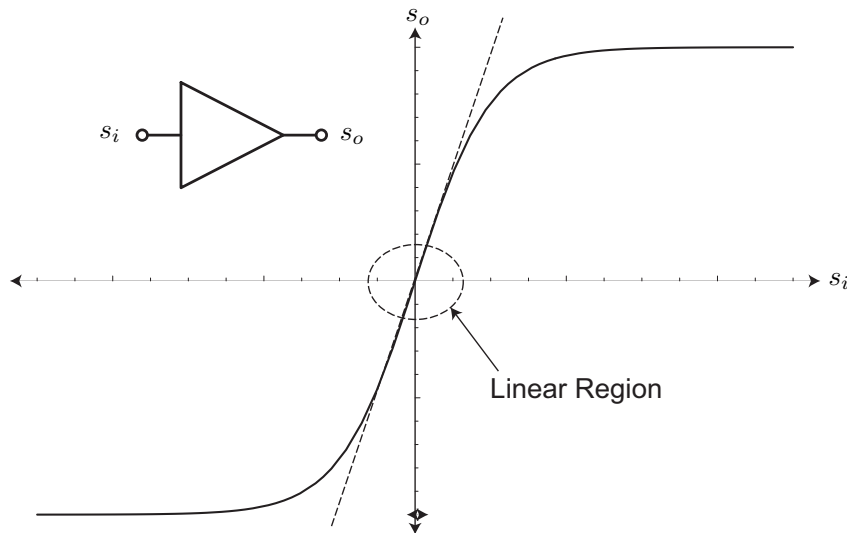

- Up to now we have treated amplifiers as small-signal linear circuits. Since transistors are non-linear, this assumption is only valid for extremely small signals.


- Consider a class of memoryless non-linear amplifiers. In other words, let's neglect energy storage elements.
- This is the same as saying the output is an instantaneous function of the input. Thus the amplifier has no memory.

# Distortion Analysis Assumptions


- We also assume the input/output description is sufficiently smooth and continuous as to be accurately described by a power series

$$s_o = a_1 s_i + a_2 s_i^2 + a_3 s_i^3 + \dots$$

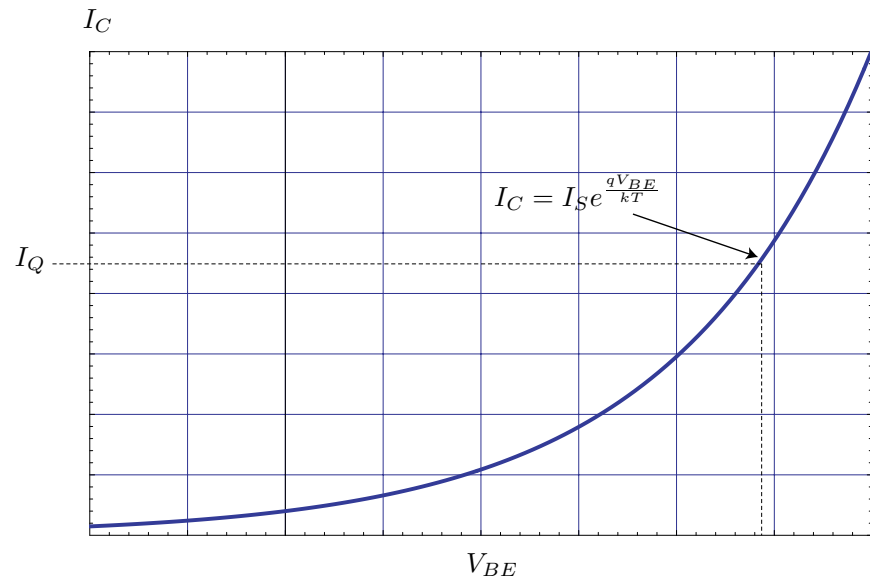For instance, for a BJT (Si, SiGe, GaAs) operated in forward-active region, the collector current is a smooth function of the voltage  $V_{BE}$




# BJT Distortion

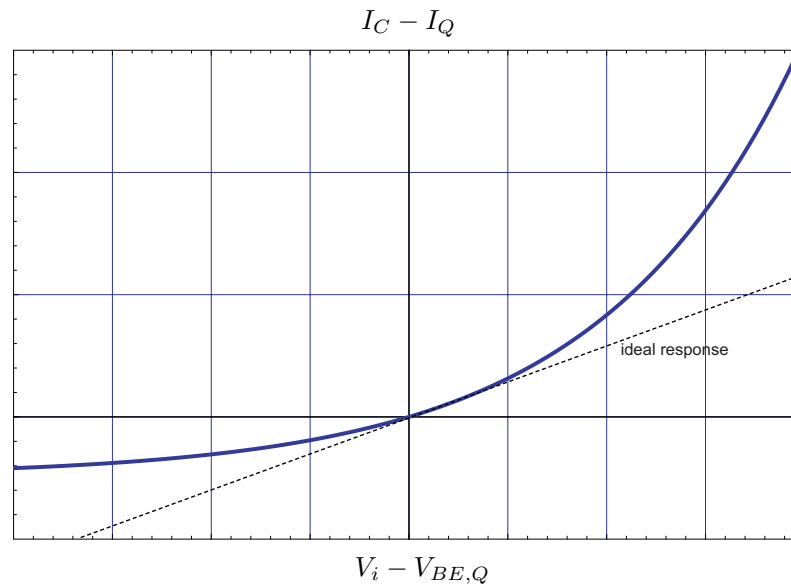

- We shift the origin by eliminating the DC signals,  $i_o = I_C - I_Q$ . The input signal is then applied around the DC level  $V_{BE,Q}$ .
- Note that an ideal amplifier has a perfectly linear line.


# JFET Distortion

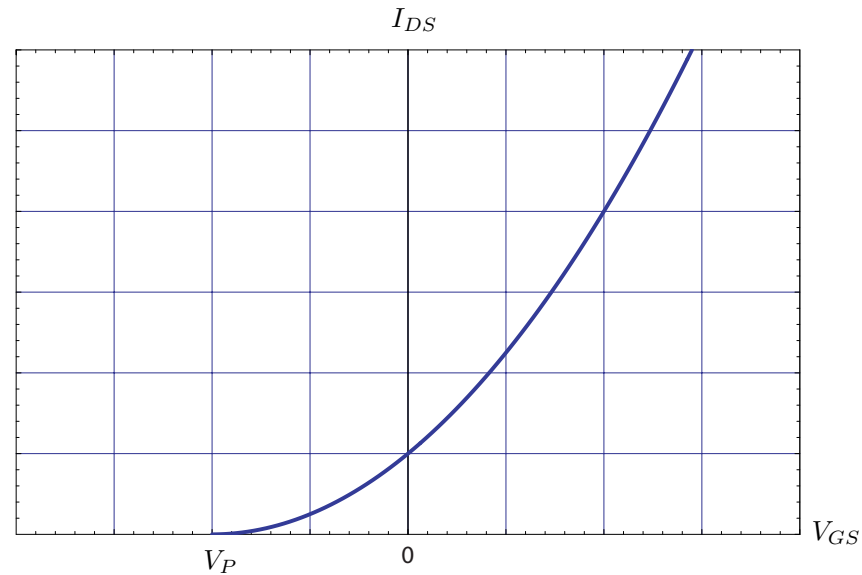

- JFETs are more common devices in RF circuits. The I-V relation is also approximately square law

$$I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

# MOSFET Distortion

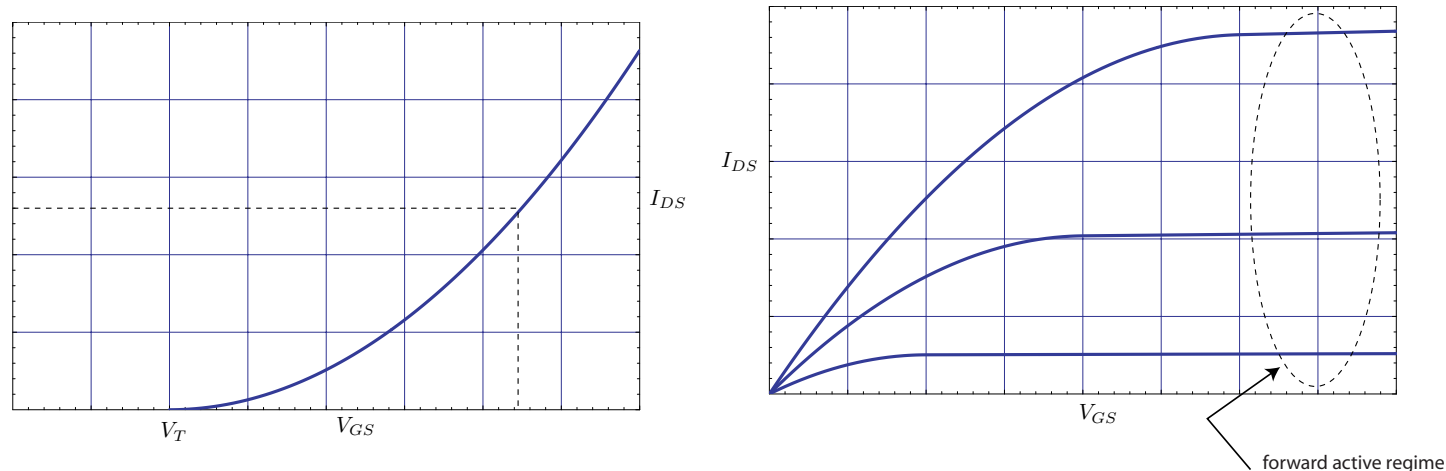

- The long-channel device also follows the square law relation (neglecting bulk charge effects)


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_t)^2 (1 + \lambda V_{DS})$$

- This is assuming the device does not leave the forward active (saturation) regime.

# MOSFET Model

- Note that the device operation near threshold is not captured by our simple square-law equation
- The I-V curve of a MOSFET in moderate and weak inversion is easy to describe in a “piece-meal” fashion, but difficult to capture with a single equation.
- Short-channel devices are even more difficult due to velocity saturation and drain induced barrier lowering.

# Differential Pair

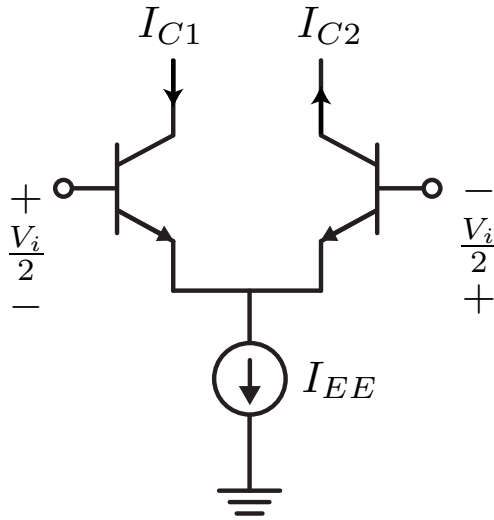

The differential pair is an important analog and RF building block.


- For a BJT diff pair, we have  $V_i = V_{BE1} - V_{BE2}$

$$I_{C1,2} = I_S e^{\frac{qV_{BE1,2}}{kT}}$$

- The sum of the collector currents are equal to the current source  $I_{C1} + I_{C2} = I_{EE}$



# BJT Diff Pair

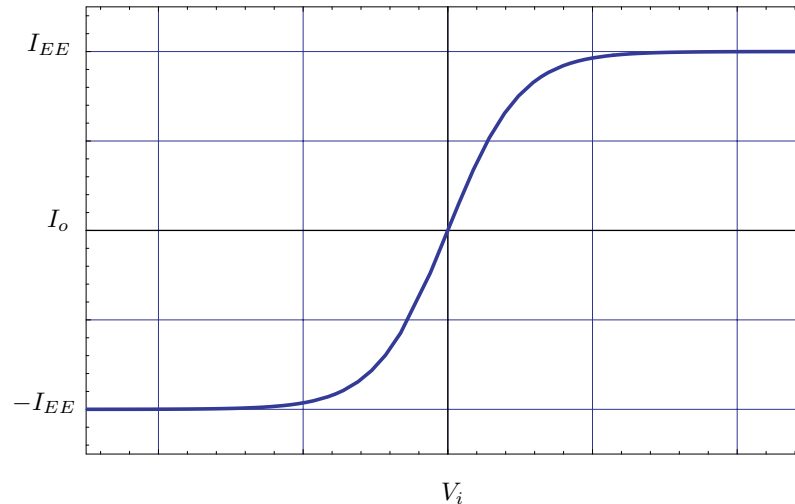

- The ideal BJT diff pair I-V relationship (neglecting base and emitter resistance) is given by

$$I_o = I_{C1} - I_{C2} = \alpha I_{EE} \tanh \frac{qV_i}{2kT}$$

- Notice that the output current saturates for large input voltages

# Power Series Relation

- For a general circuit, let's represent this behavior with a power series

$$s_o = a_1 s_i + a_2 s_i^2 + a_3 s_i^3 + \dots$$

- $a_1$  is the small signal gain
- The coefficients  $a_1, a_2, a_3, \dots$  are independent of the input signal  $s_i$  *but* they depend on bias, temperature, and other factors.

# Harmonic Distortion

- Assume we drive the amplifier with a time harmonic signal at frequency  $\omega_1$

$$s_i = S_1 \cos \omega_1 t$$

- A linear amplifier would output  $s_o = a_1 S_1 \cos \omega_1 t$  whereas our amplifier generates

$$s_o = a_1 S_1 \cos \omega_1 t + a_2 S_1^2 \cos^2 \omega_1 t + a_3 S_1^3 \cos^3 \omega_1 t + \dots$$


or

$$s_o = a_1 S_1 \cos \omega_1 t + \frac{a_2 S_1^2}{2} (1 + \cos 2\omega_1 t) + \frac{a_3 S_1^3}{4} (\cos 3\omega_1 t + 3 \cos \omega_1 t) + \dots$$

# Harmonic Distortion (cont)


- The term  $a_1 s_1 \cos \omega_1 t$  is the wanted signal.
- Higher harmonics are also generated. These are unwanted and thus called “distortion” terms. We already see that the second-harmonic  $\cos 2\omega_1 t$  and third harmonic  $\cos 3\omega_1 t$  are generated.
- Also the second order non-linearity produces a DC shift of  $\frac{1}{2} a_2 S_1^2$ .
- The third order generates both third order distortion and more fundamental. The sign of  $a_1$  and  $a_3$  determine whether the distortion product  $a_3 S_1^3 \frac{3}{4} \cos \omega_1 t$  adds or subtracts from the fundamental.
- If the signal adds, we say there is gain expansion. If it subtracts, we say there is gain compression.

# Second Harmonic Distortion Waveforms

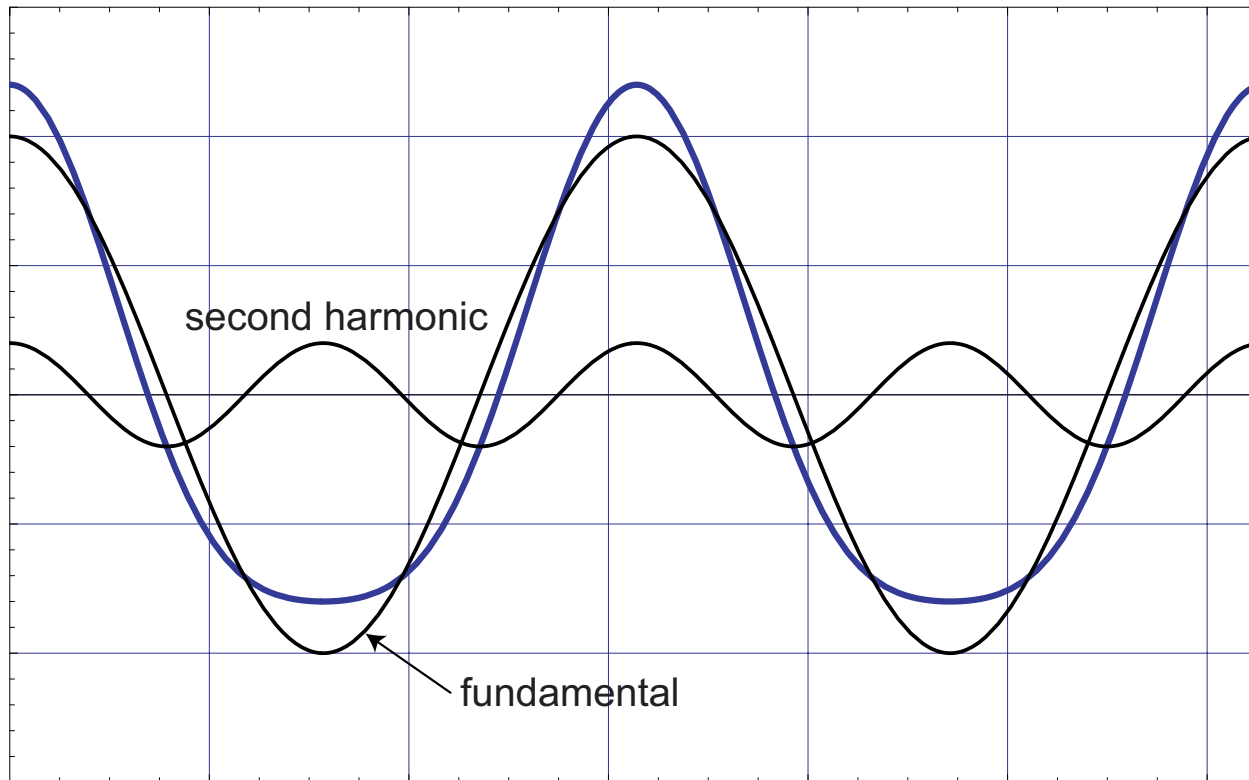


- The figure above demonstrates the waveform distortion due to second harmonic only.

# Third Harmonic Distortion Waveform

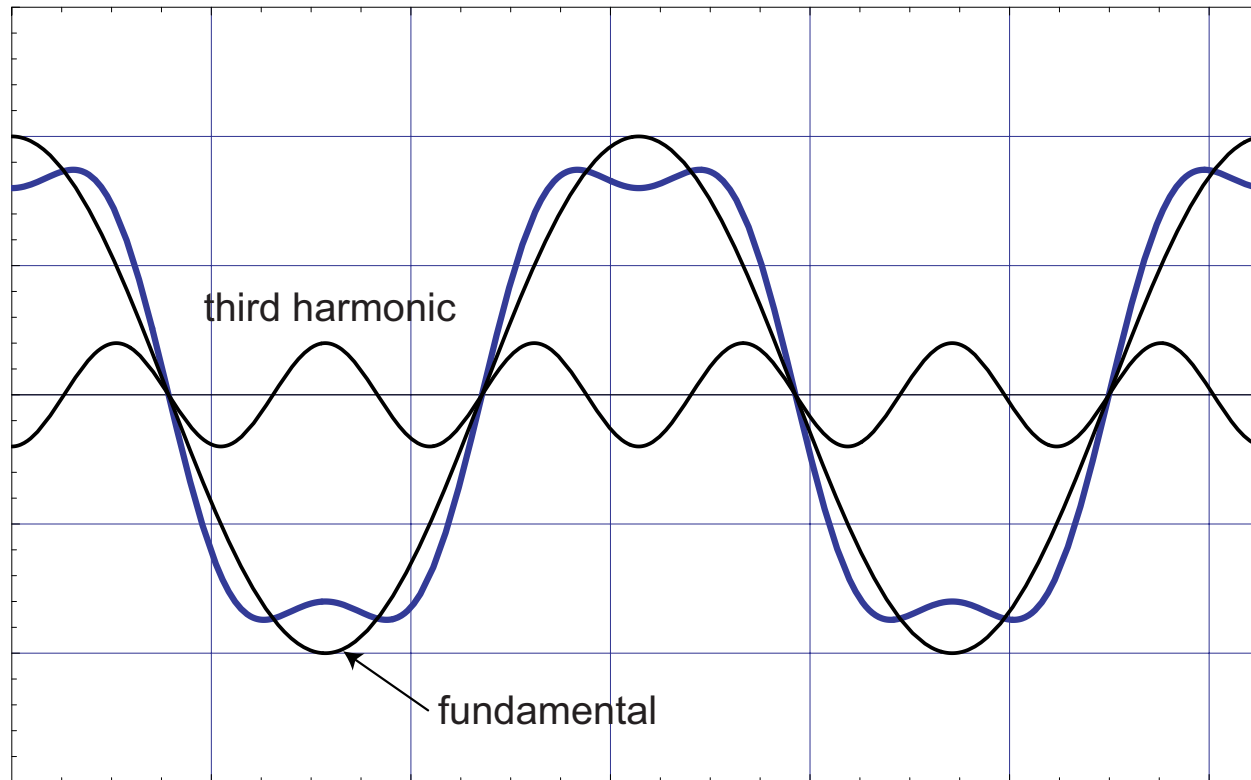

- The above figure shows the effects of the third harmonic, where we assume the third harmonic is in phase with the fundamental.

# Third Harmonic Waveform (cont)

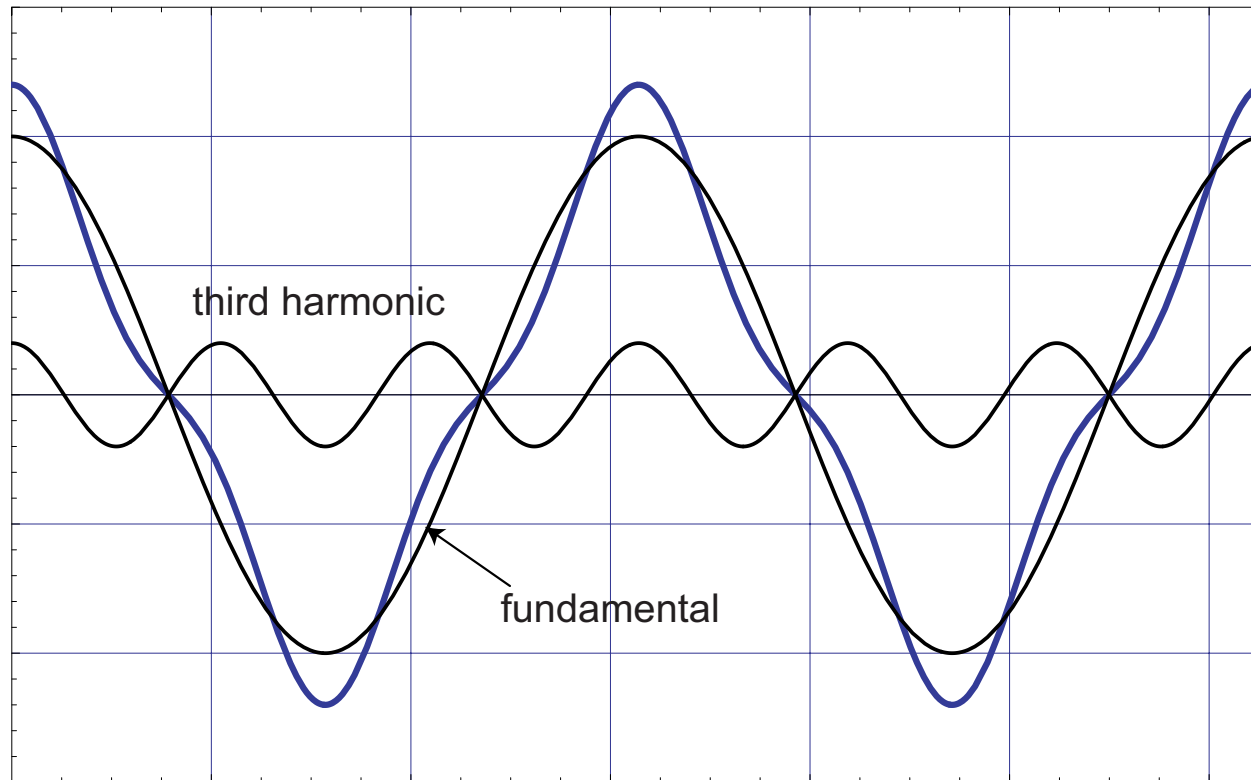

- The above figure shows the effects of the third harmonic, where we assume the third harmonic is out of phase with the fundamental.

# General Distortion Term

- Consider the term  $\cos^n \theta = \frac{1}{2^n} (e^{j\theta} + e^{-j\theta})^n$ . Using the Binomial formula, we can expand to

$$= \frac{1}{2^n} \sum_{k=0}^n \binom{n}{k} e^{jk\theta} e^{-j(n-k)\theta}$$

- For  $n = 3$

$$= \frac{1}{8} \left( \binom{3}{0} e^{-j3\theta} + \binom{3}{1} e^{j\theta} e^{-j2\theta} + \binom{3}{2} e^{j2\theta} e^{-j\theta} + \binom{3}{3} e^{j3\theta} \right)$$

$$= \frac{1}{8} \left( e^{-j3\theta} + e^{j3\theta} \right) + \frac{1}{8} 3 \left( e^{j\theta} + e^{-j\theta} \right) = \frac{1}{4} \cos 3\theta + \frac{3}{4} \cos \theta$$



# General Distortion Term (cont)

- We can already see that for an odd power, we will see a nice pairing up of positive and negative powers of exponentials
- For the even case, the middle term is the unpaired DC term

$$\binom{2k}{k} e^{jk\theta} e^{-jk\theta} = \binom{2k}{k}$$

- So only even powers in the transfer function can shift the DC operation point.
- The general term in the binomial expansion of  $(x + x^{-1})^n$  is given by

$$\binom{n}{k} x^{n-k} x^{-k} = \binom{n}{k} x^{n-2k}$$

# General Distortion Term (cont)

- The term  $\binom{n}{k} x^{n-2k}$  generates every other harmonic.
- If  $n$  is even, then only even harmonics are generated. If  $n$  is odd, likewise, only odd harmonics are generated.
- Recall that an “odd” function  $f(-x) = -f(x)$  (anti-symmetric) has an odd power series expansion

$$f(x) = a_1x + a_3x^3 + a_5x^5 + \dots$$

- Whereas an even function,  $g(-x) = g(x)$ , has an even power series expansion

$$g(x) = a_0 + a_2x^2 + a_4x^4 + \dots$$