


## Diode Circuits

Prof. Ali M. Niknejad and Prof. Rikky Muller

U.C. Berkeley  
Copyright © 2017 by Ali M. Niknejad


March 2, 2017

# Diode Introduction

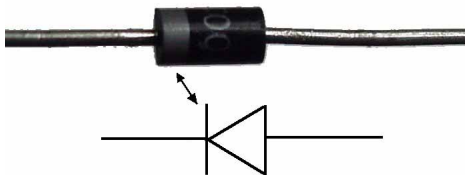


- A diode is a non-linear element. To a very good approximation, the current through the diode is exponentially related to the voltage across the diode.
- In most of today's lecture, we will excite the diode with "large" signals and therefore we cannot use the small-signal model.
- Diodes are manufactured primarily using a semiconducting process. The junction between two semiconducting materials creates a diode.

# Light Emitting Diode (LED)

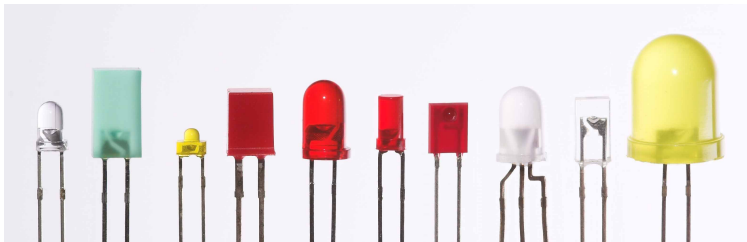


- A light emitting diode emits light (of a particular color) when current flows through the diode. The conversion efficiency is much better than light bulbs.

# Diode I-V Curve (Forward)

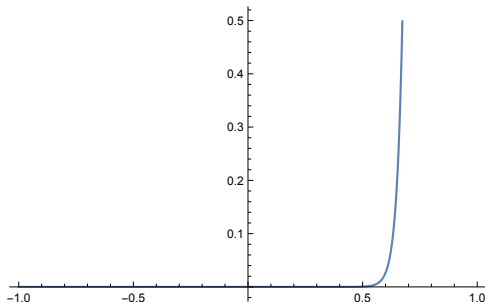

- When a “forward-bias” is applied across the diode, lowering the built-in potential, a rush of current flows across the junction. It can be shown that this current is an exponential function of the barrier height.
- When a “reverse-bias” is applied, the barrier height increases, and so no current flows.

# Diode Leakage and Reverse Breakdown

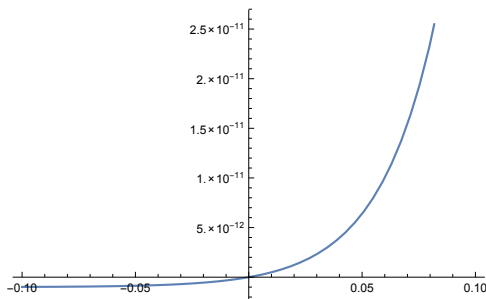

- Even without a forward bias voltage, some small leakage current flows through the diode. This is because there are always a very small number of electrons (holes) in the p-type (n-type) material that are moving around. If they reach the potential barrier, they “float up” (remember they are electrons) or “fall” off the barrier. There are so few electrons (holes) in the p-type (n-type) material that this is a rare occurrence.

# Diode Leakage and Reverse Breakdown

- Note that by this argument, the leakage current is independent of the reverse bias. Electrons will 'float' up the barrier no matter the height! Holes will 'fall' down the barrier no matter the height.
- If a sufficiently negative voltage is applied, the internal barrier height gets so large that breakdown occurs. Then a seemingly unlimited current can flow.

- When breakdown occurs, the diode behaves like a battery. No matter what current is drawn, the voltage is nearly constant. This is often used as a voltage reference.
- The breakdown mechanism can be due to quantum mechanical tunneling or due to avalanche breakdown.

- An ideal diode only allows current to flow in one direction. That's because the current is zero when a negative voltage is applied. When a positive voltage is applied, any current can flow and so the diode looks nearly like a short circuit.
- The “on” voltage is related to the required forward bias, which for Si is about 0.7V.



# Really Ideal Diode Model

- An ideal diode only allows current to flow in one direction. That's because the current is zero when a negative voltage is applied. When a positive voltage is applied, any current can flow and so the diode looks nearly like a short circuit.
- Can you give an argument for why this ideal diode cannot exist? *Hint:* Try a thermodynamic argument.

# Half-Wave Rectifier

- The simple circuit shown above will only conduct during the positive cycle of the sinusoidal voltage.
- This is called “rectification” because it fixes the AC voltage if you’re trying to get rid of it’s negative polarity. As we’ll see soon, this way we can easily convert AC to DC.

# Precision Half-Wave Rectifier

- Use an op-amp to make the circuit precise.

- This bridge circuit will conduct current during both cycles. Due to the polarity of the diodes, current is always flowing in the same direction through the load, even for a negative voltage.
- This means that the circuit performs an absolute value function.

# Filtered Rectified Voltage

- The capacitor is used to filter out the variations in the voltage.
- During the positive cycle, the capacitor is charged and it holds its output steady. The charging time is very fast because the diode “on” resistance is very small.
- During the negative cycle, the diode turns off and the output voltage is provided by the capacitor. If the load current is sufficiently small, then the discharge time constant is relatively long, and so the voltage droops only a bit.

# Full-Wave Filtered Output

- The same idea works for the full-wave rectifier, and now the output variation is even less.
- Bridge rectifiers are ubiquitous in equipment used to convert AC line voltages to DC voltages used by most electronic equipment. A transformer is needed to bring down the line voltage. Increasingly, transformers are replaced by switching power supplies, something we'll learn about later.

- The capacitor is charged to the peak voltage and the output is held at the peak. Any excursions below peak cannot forward bias the capacitor. If a voltage excursion exceeds the peak up to a given point, then the capacitor is quickly charged by the forward biased diode.
- If you flip the direction of the diode, you get a negative peak detector.

- Diodes are often used to limit the voltage excursion, especially to protect a circuit.
- When DC sources are used in series with the diodes, the clip point can be set to any desired value. Zener references are handy for this application.



- Diodes are used to protect for over-voltage (both positive and negative)
- ESD ring is drawn around periphery of chip. A “clamp” will short supply-to-ground if it exceeds a threshold voltage. For example a Zener could be placed as the clamp but in practice another kind of circuit is used.

- In this circuit the diode turns on initially and charges the capacitor to the AC voltage. Note that once the voltage starts to drop, the diode turns off.
- The output voltage is therefore level shifted by the DC voltage held on the capacitor.
- In this case the voltage excursions are now negative and never rise above zero! If a load is connected, then the capacitor should be large enough to minimize the droop.

# Another Level Restorer

- If we now flip the direction of the diode, the current will only flow during the negative half cycle, charging the capacitor now in the opposite direction.
- Then output is now lifted by the DC voltage stored on the capacitor. The voltage will now always remain positive and never go below zero!


- If we rectify the above voltages, we can generate positive or negative DC voltages of twice the magnitude. This is a voltage doubler!

- $RC$  time constant fast enough to follow signal transitions but low enough to reject high frequency components of signal.
- A simple diode can be used to detect an AM (Amplitude Modulated) signal.
- How do you demodulate an FM or PM signal? Hint: You can use the same circuit if you first convert the signal from phase/frequency modulation to amplitude modulation

# Detecting Digital Bits

- The top circuit detects the signal envelope
- The bottom circuit detects the peak of the signal
- Comparator looks for transitions away from peak

# Solar Cells

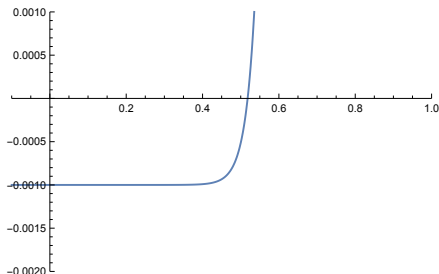

- Note that a solar cell is equivalent to a forward biased diode in parallel with a current source.
- Since the I-V curve falls in the fourth quadrant, it can supply power !
- We can easily measure the short-circuit current ( $I_{short}$ ) and the open-circuit voltage ( $V_{open}$ ). There's an optimal point to operate the solar cell to get the most power output (maximized product of  $i$  and  $v$ ). In absence of loss, it's the load resistance that is the ratio of  $V_{open}/I_{short}$