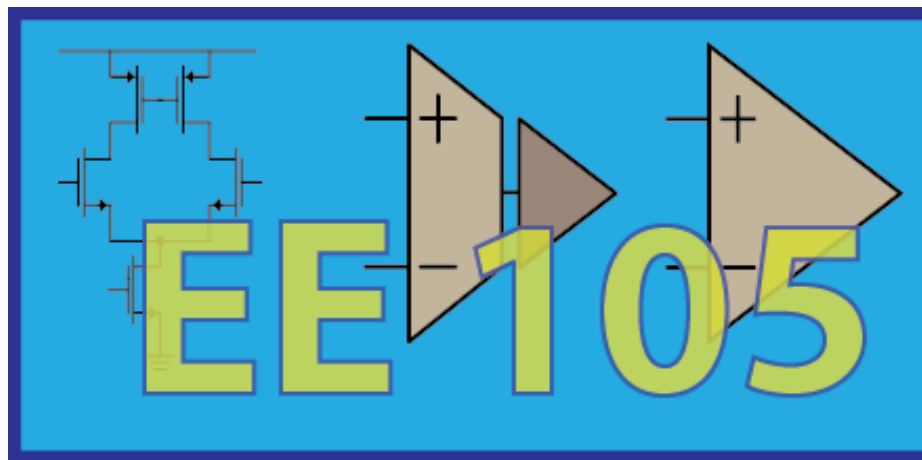




Single-Stage Amplifiers

Prof. Ali M. Niknejad
Prof. Rikky Muller






Announcements


- HW8 due on Friday

One-Port Models (EECS 16A)

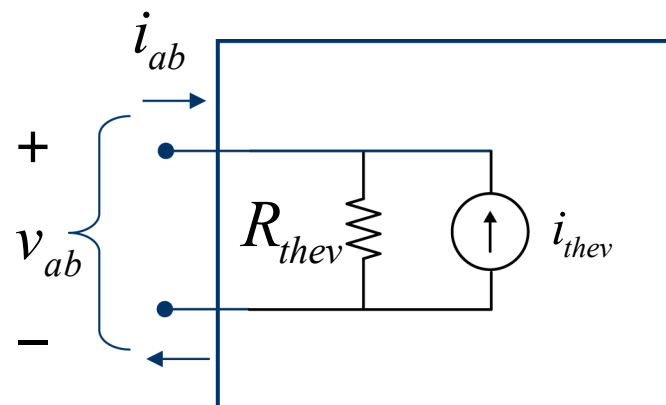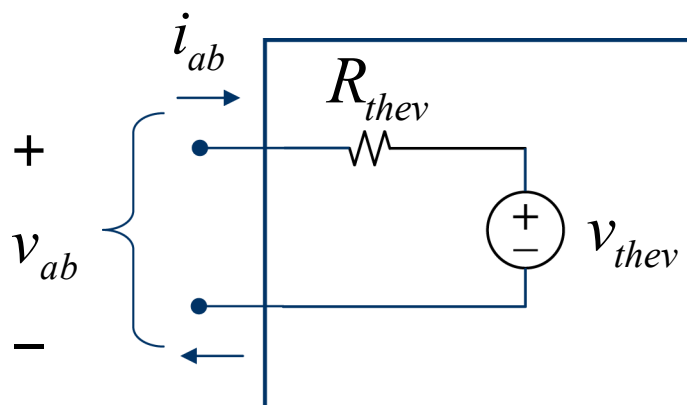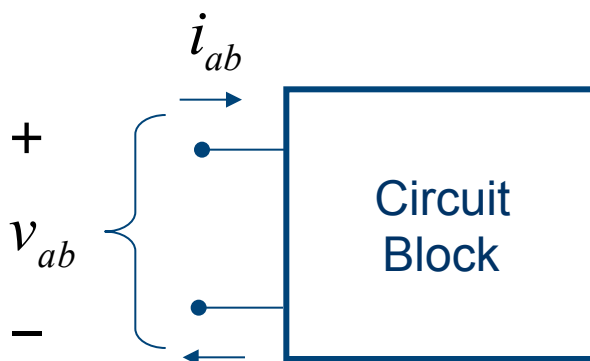- A terminal pair across which a voltage and associated current are defined




Small-Signal Two-Port Models

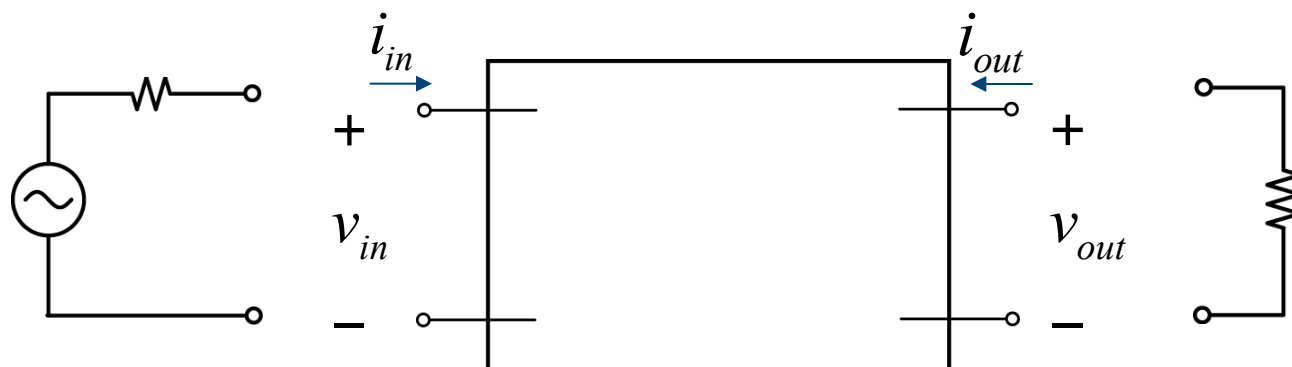


- We assume that input port is linear and that the amplifier is *unilateral*:
 - Output depends on input but input is independent of output.
- Output port : depends linearly on the current and voltage at the input and output ports
- Unilateral assumption is good as long as “overlap” capacitance is small (MOS)

Two-Port Small-Signal Amplifiers

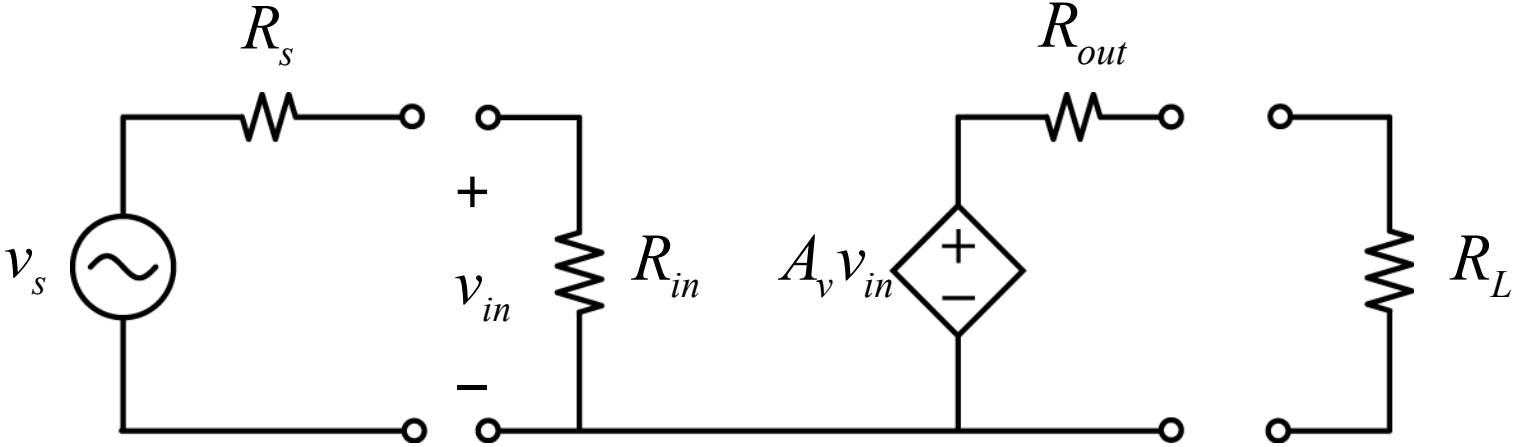


Voltage Amplifier

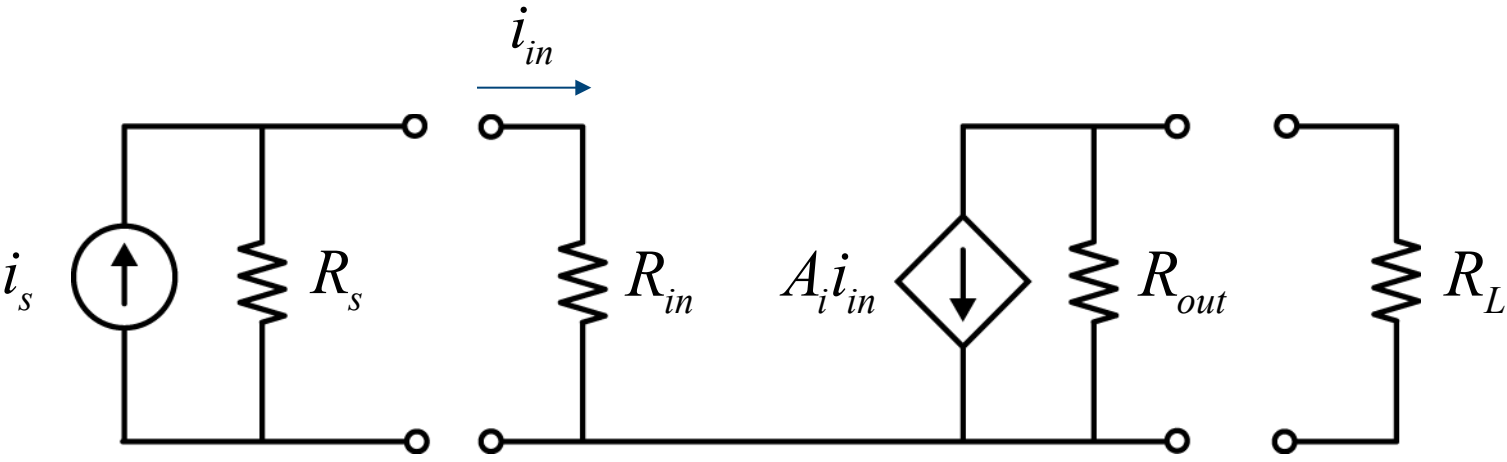


Current Amplifier

Two-Port Small-Signal Amplifiers

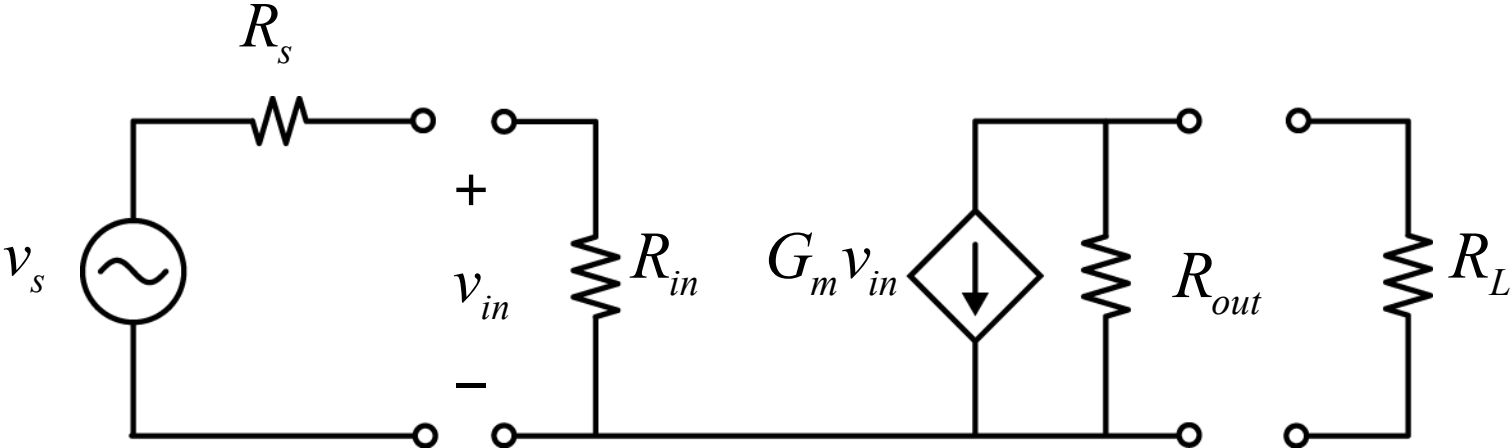


Transconductance Amplifier

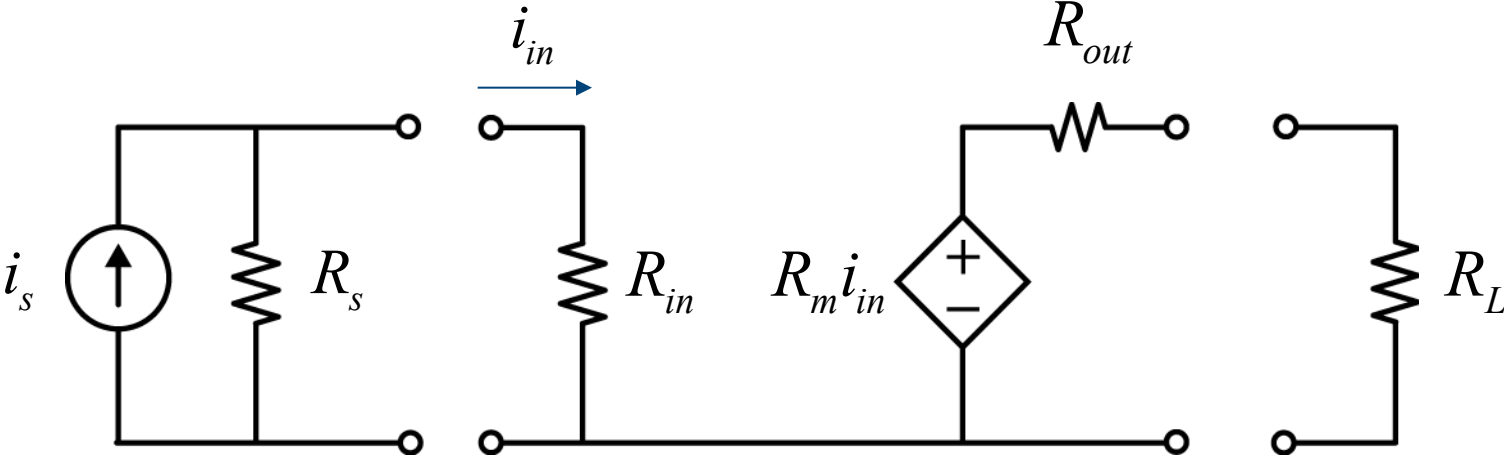


Transresistance Amplifier

Input Impedance Z_{in}

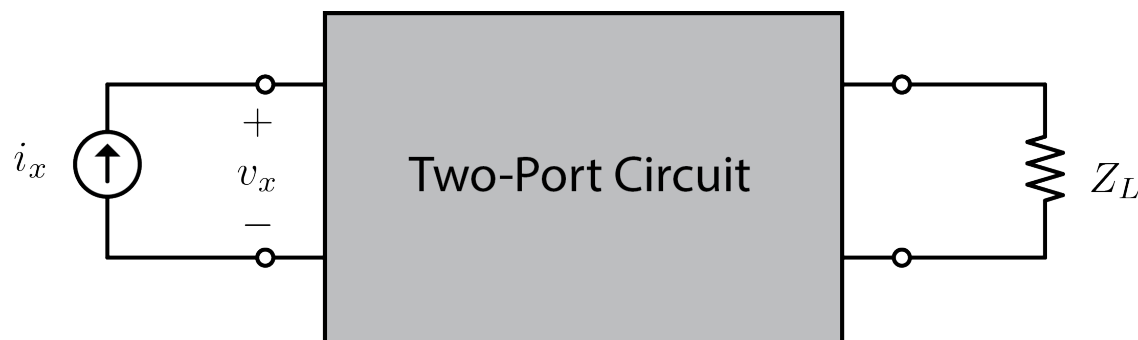Looks like a Thevenin resistance measurement, but note that the output port has the load resistance attached





$$Z_{in} = \left. \frac{v_x}{i_x} \right|_{Z_S \text{ removed}, Z_L \text{ attached}}$$

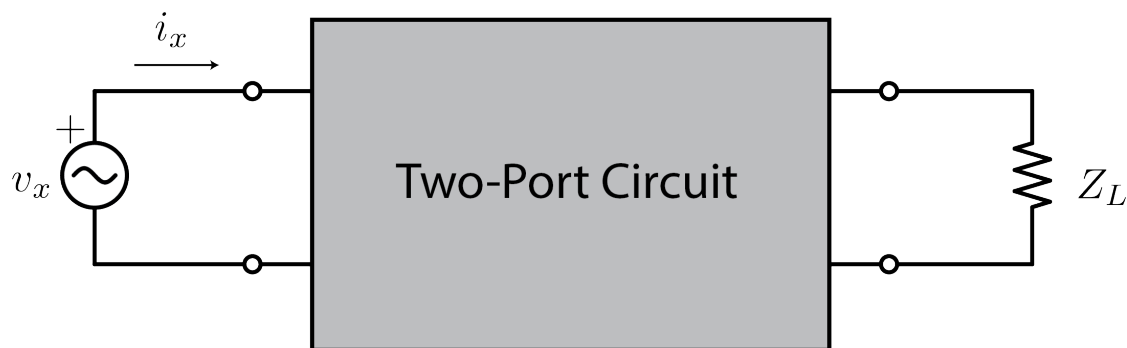


Output Impedance Z_{out}

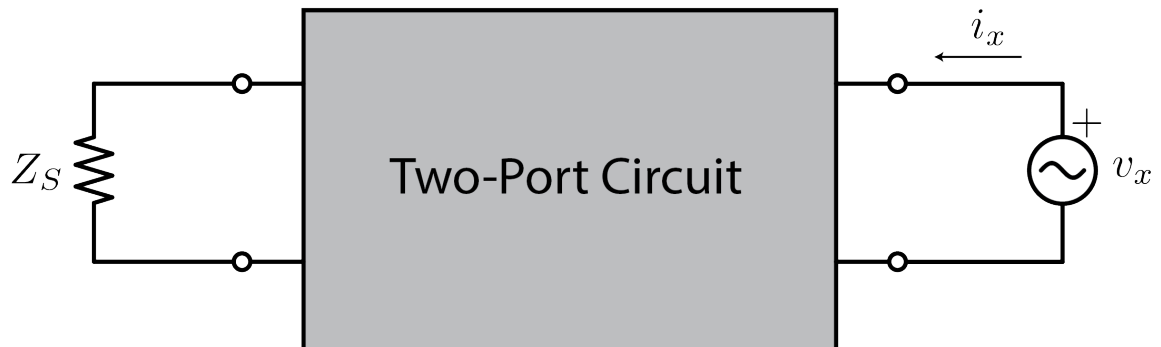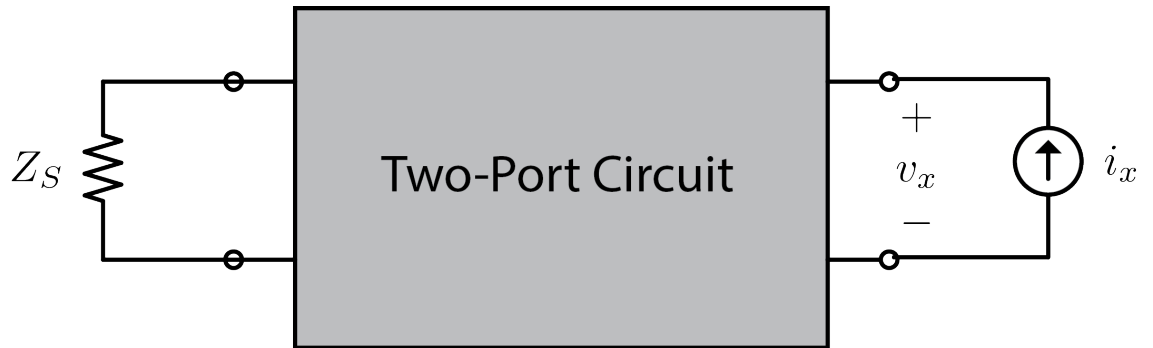Looks like a Thevenin resistance measurement, but note that the *input* port has the *source* resistance attached




$$Z_{out} = \left. \frac{v_x}{i_x} \right|_{Z_L \text{ removed}, Z_S \text{ attached}}$$


Single-Stage Amplifier Types

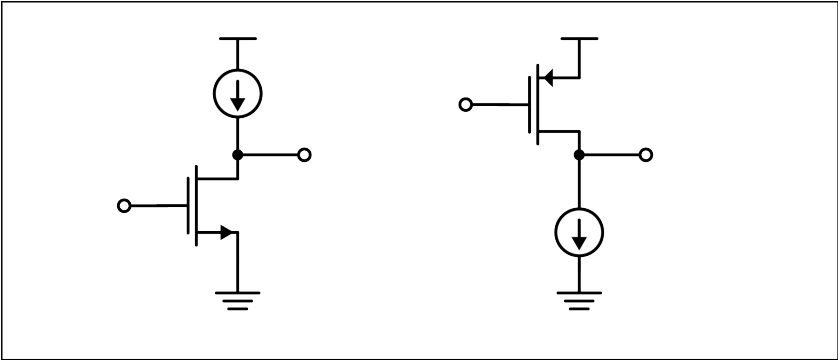

Common Source (CS)

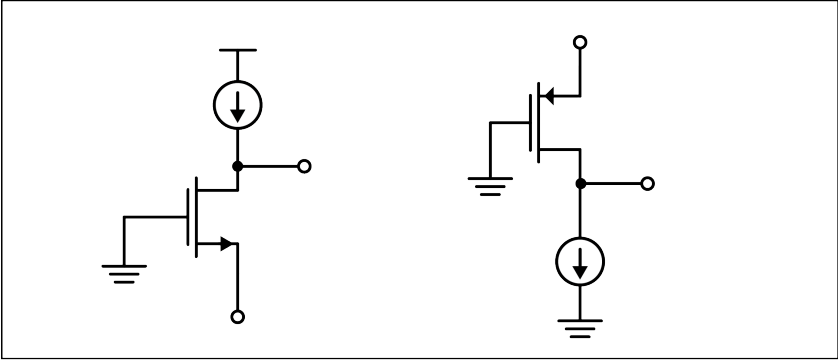

Common Gate (CG)

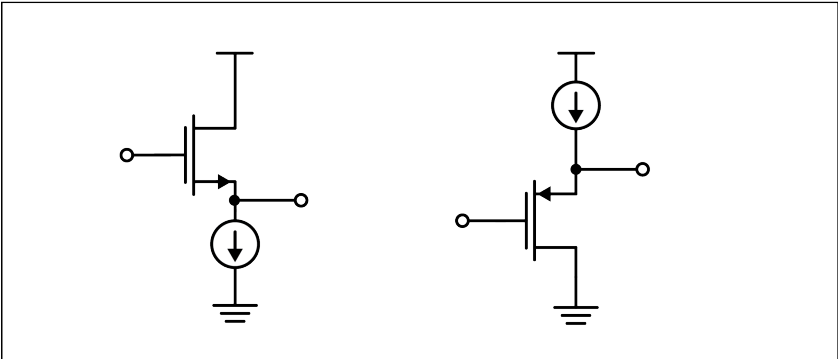


Common Drain (CD)


Common Gate (CG) Amplifier

DC bias:


$$I_{SUP} = I_Q = I_{DS}$$

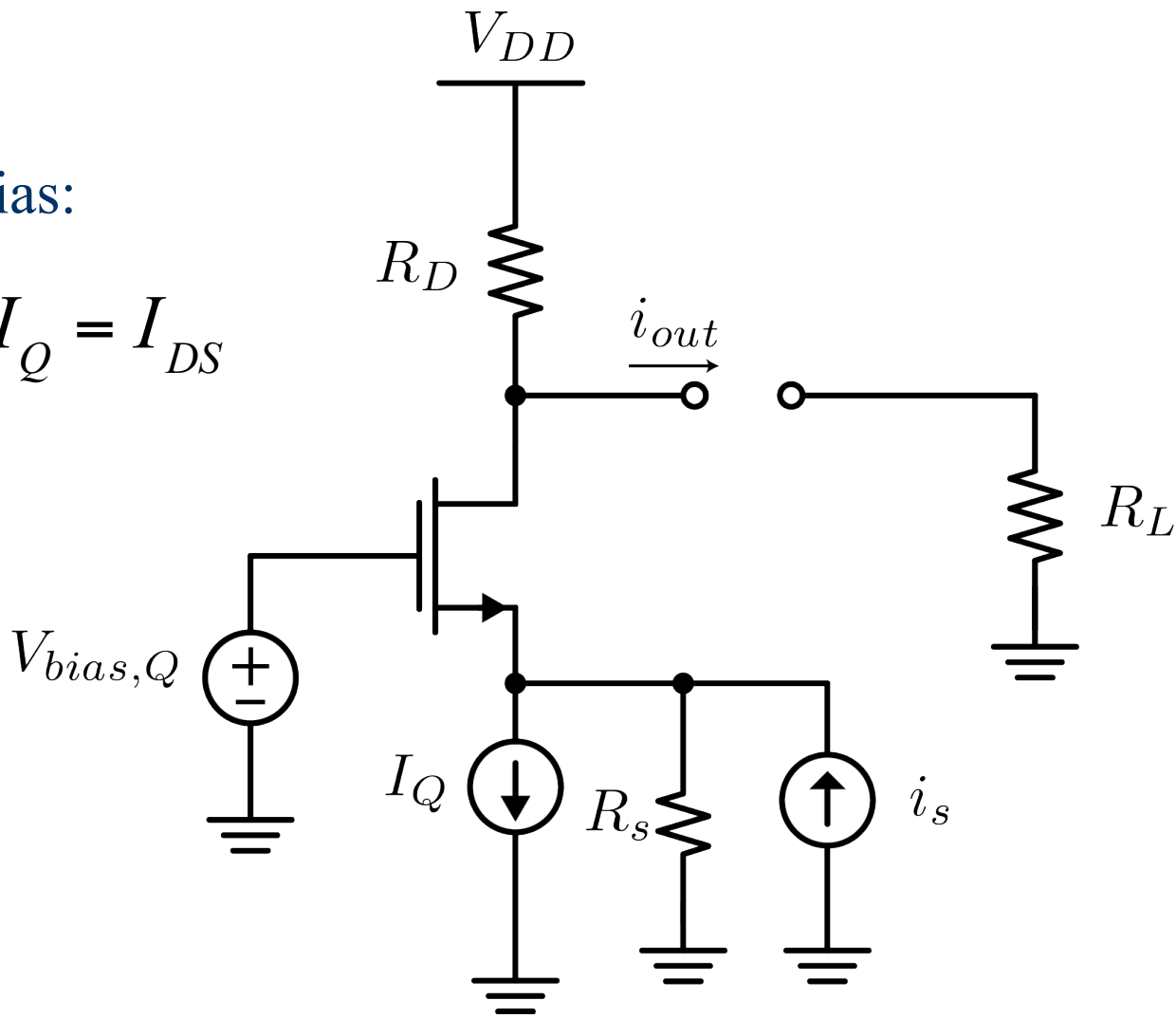


Common Gate AC Model

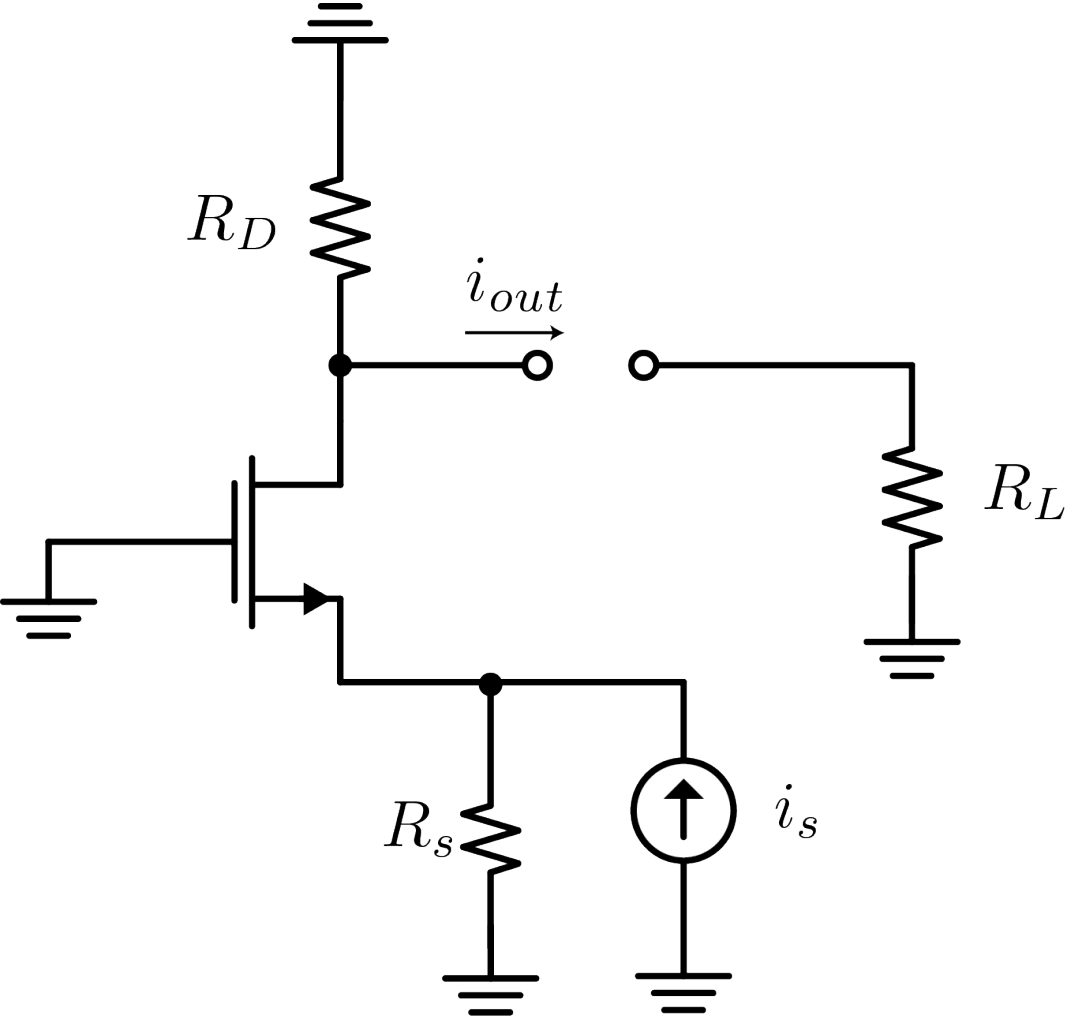

Common Gate Small Signal

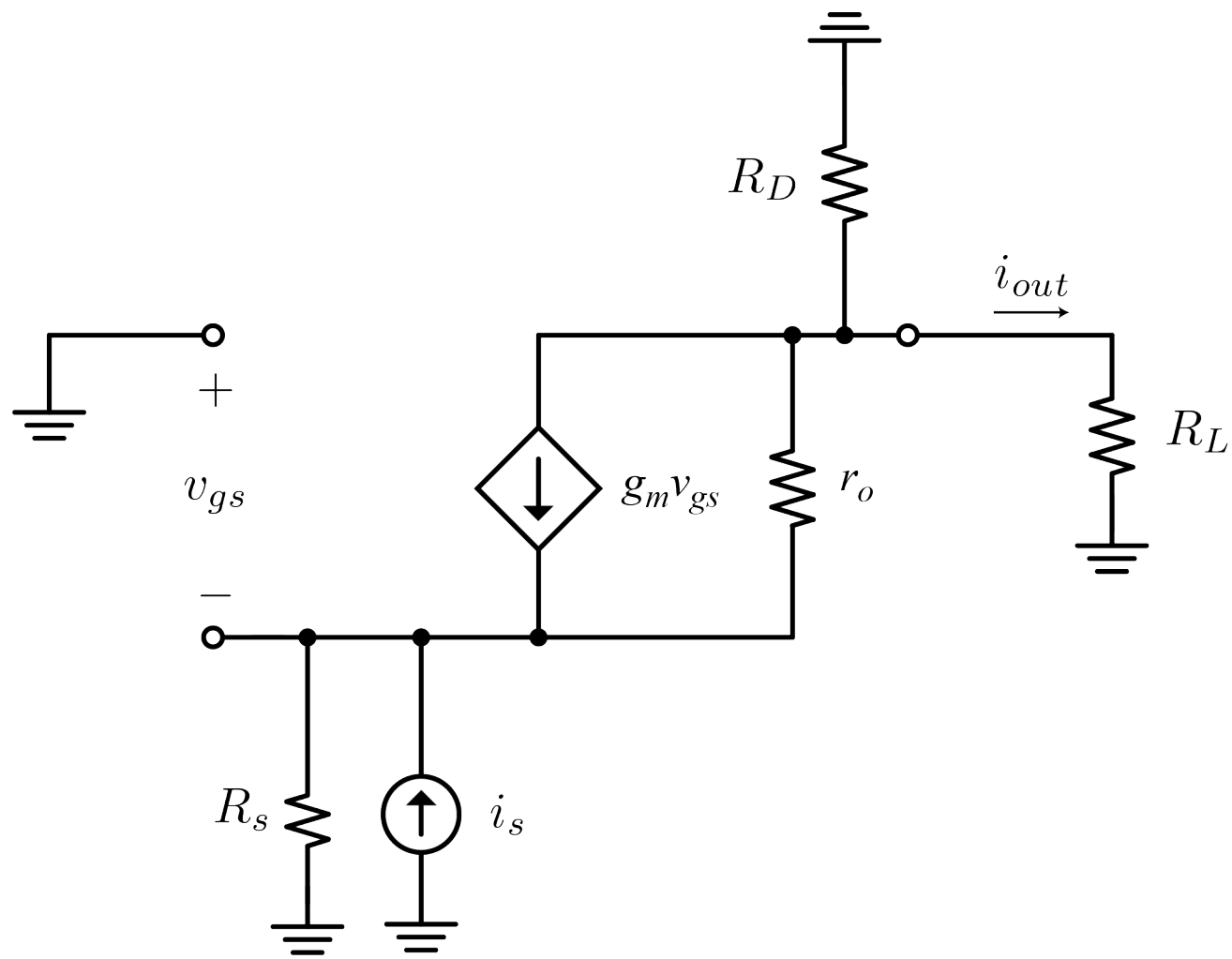


CG as a Current Amplifier: Find A_i

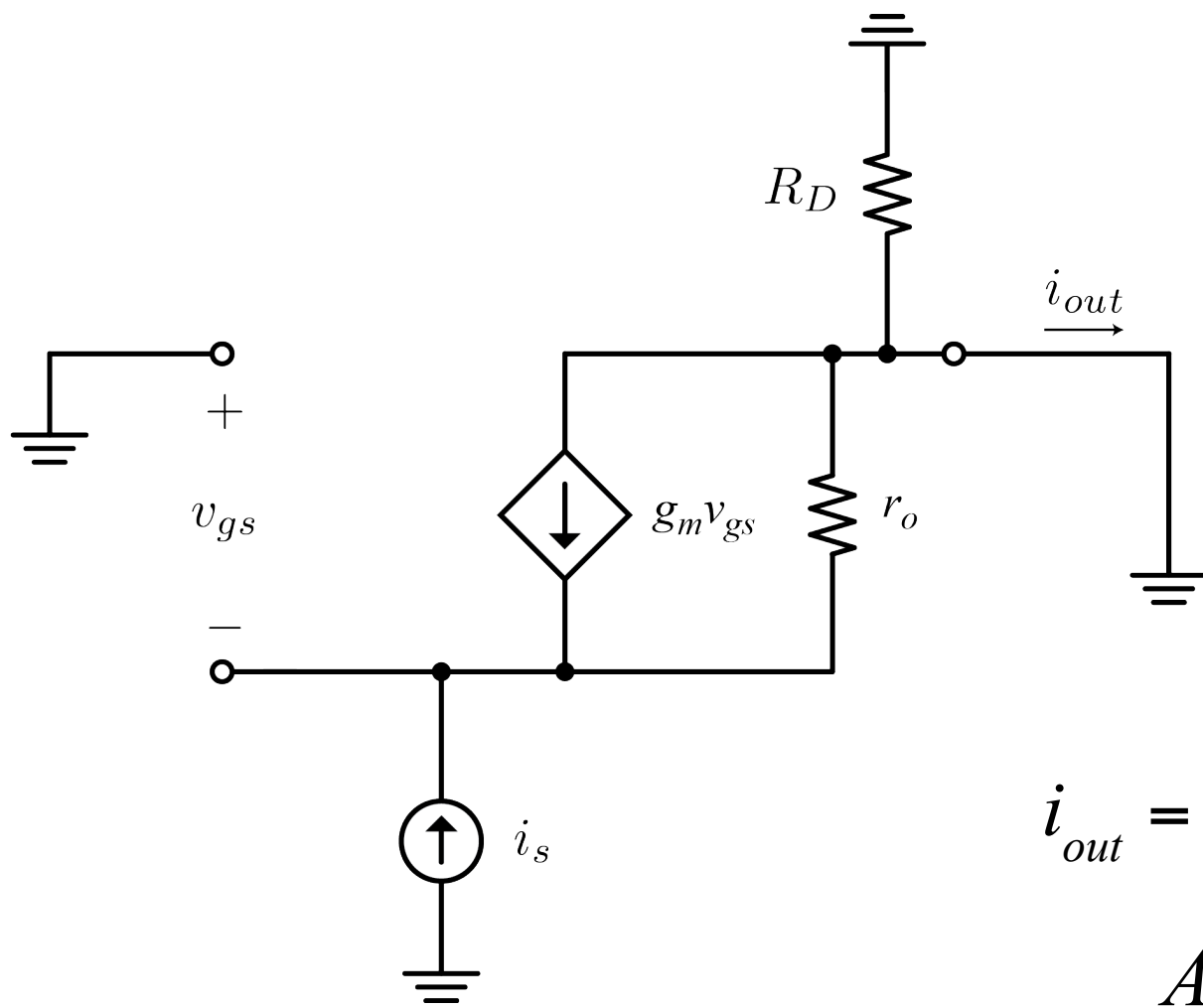

$$i_{out} = i_d = -i_s$$

$$A_i = -1$$

CG Input Resistance

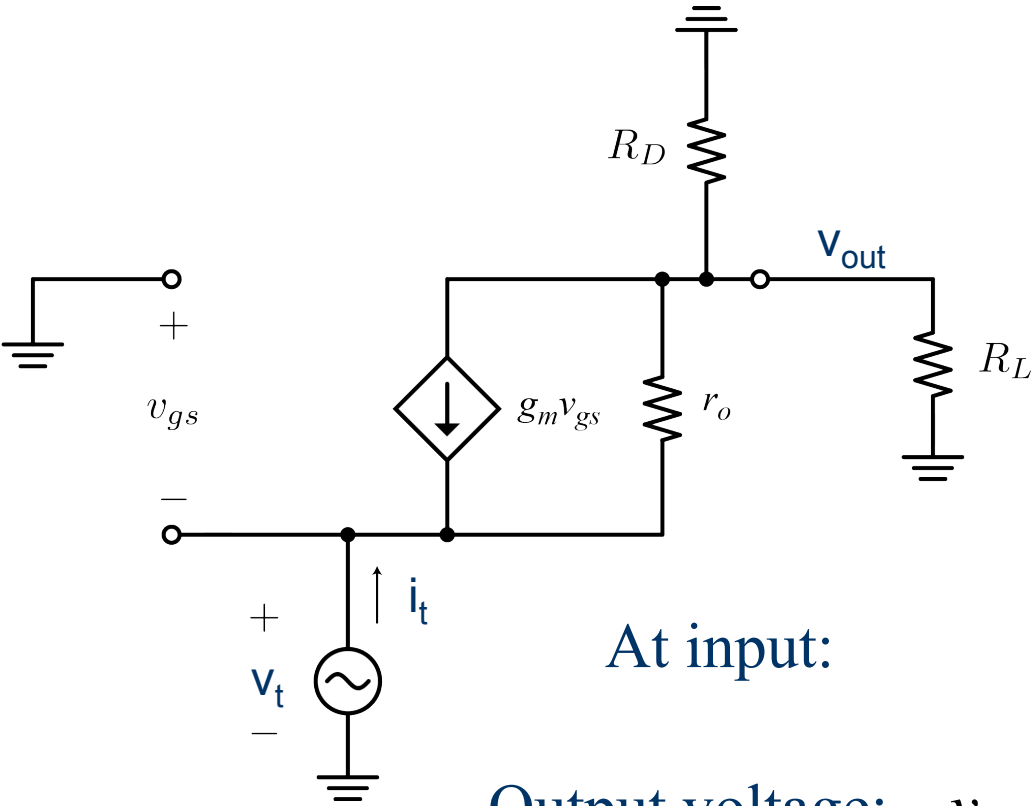

At input:

$$i_t = -g_m v_{gs} + \left(\frac{v_t - v_{out}}{r_o} \right)$$

Output voltage:

$$v_{out} = -i_d (R_D \parallel R_L) = i_t (R_D \parallel R_L)$$

$$i_t = g_m v_t + \left(\frac{v_t - (R_D \parallel R_L) i_t}{r_o} \right)$$

Approximations...

- We have this messy result


$$\frac{1}{R_{in}} = \frac{i_t}{v_t} = \frac{g_m + \frac{1}{r_o}}{1 + \frac{R_D \parallel R_L}{r_o}}$$

- But we don't need that much precision. Let's start approximating:

$$g_m \gg \frac{1}{r_o} \qquad R_D \parallel R_L \approx R_L \qquad \frac{R_L}{r_o} \approx 0$$

$$R_{in} = \frac{1}{g_m}$$

CG Output Resistance

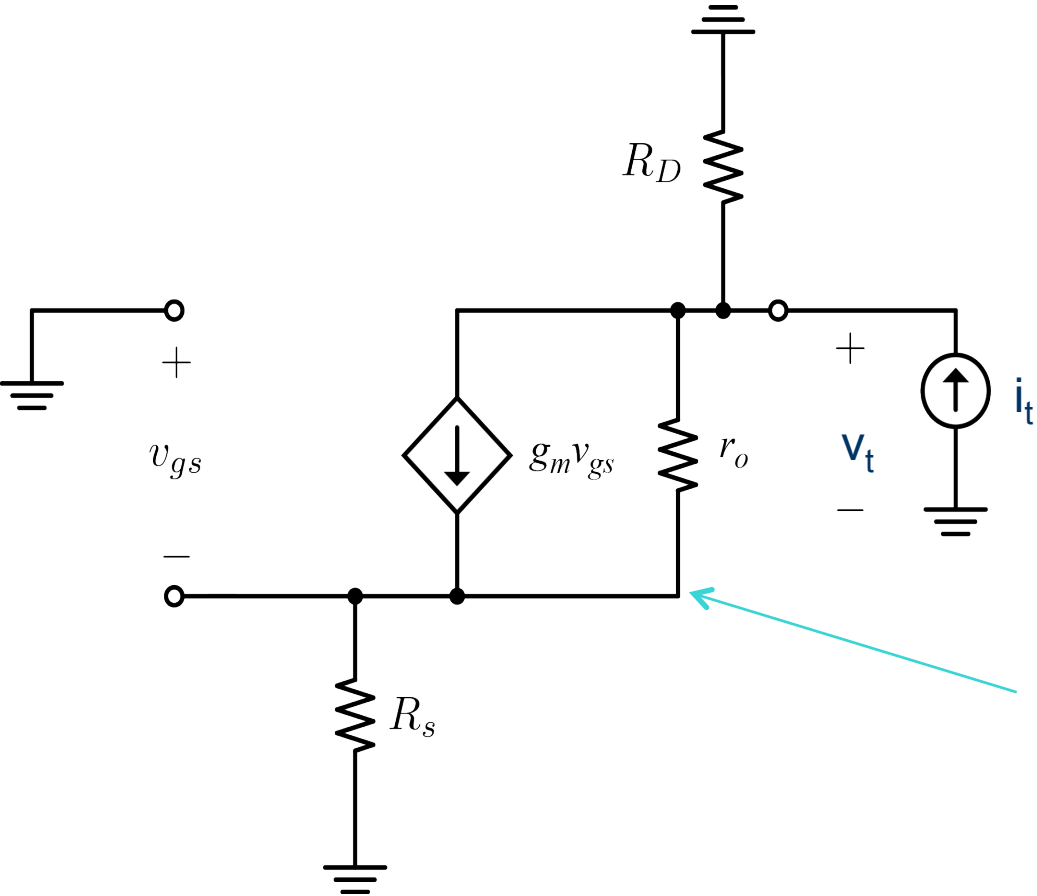

$$\frac{v_s}{R_s} - g_m v_{gs} + \frac{v_s - v_t}{r_o} = 0$$

$$v_s \left(\frac{1}{R_s} + g_m + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

CG Output Resistance

Substituting $v_s = i_t R_S$

$$i_t R_S \left(\frac{1}{R_S} + g_m + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

The output resistance is $(v_t / i_t) \parallel R_D$

$$R_{out} = R_D \parallel \left(R_S \left(\frac{r_o}{R_S} + g_m r_o + 1 \right) \right)$$

$$R_{out} = R_D \parallel (r_o + g_m r_o R_S + R_S)$$

Approximating the CG R_{out}

The exact result is complicated, so let's try to make it simpler:


$$g_m \approx 500\mu S \qquad r_o \approx 200k\Omega$$

$$R_{out} \cong R_D \parallel [r_o + g_m r_o R_S + R_S]$$

Assuming the source resistance is less than r_o ,

$$R_{out} \approx R_D \parallel [r_o + g_m r_o R_S] = R_D \parallel [r_o (1 + g_m R_S)]$$

CG Two-Port Model

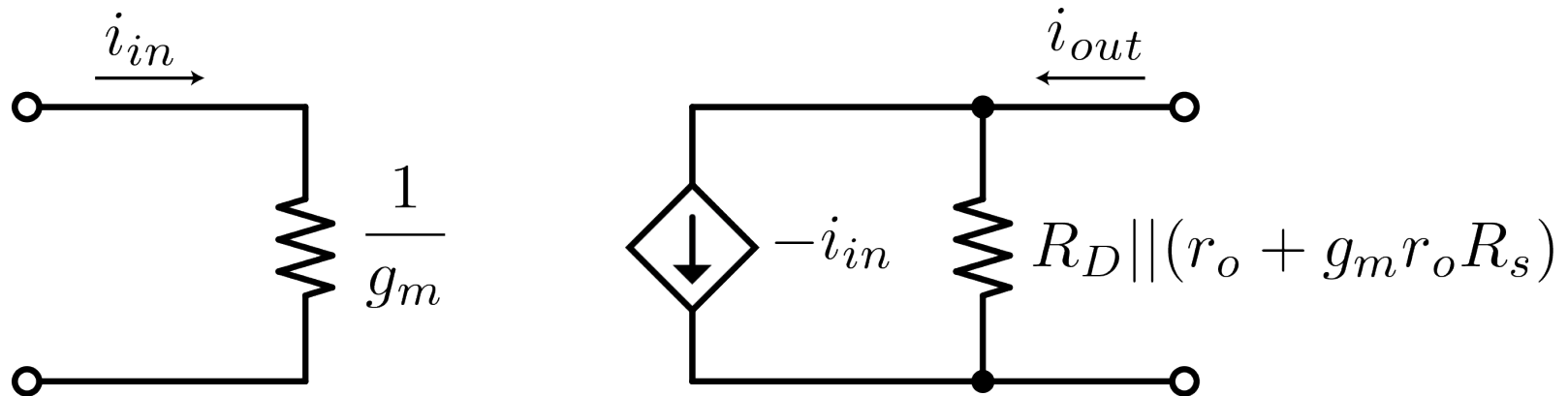


Function: a current buffer

- Low Input Impedance
- High Output Impedance

Common Gate as a “V Amplifier”

Common-Drain Amplifier

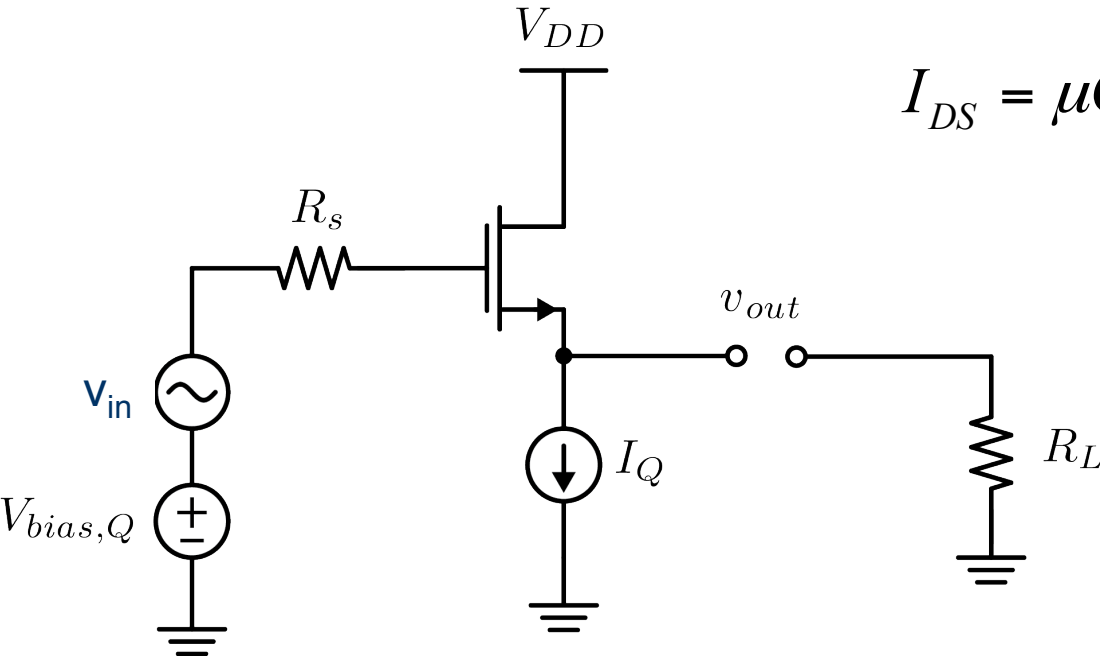


$$I_{DS} = \mu C_{ox} \frac{W}{L} \frac{1}{2} (V_{GS} - V_T)^2$$


$$V_{GS} = V_T + \sqrt{\frac{2I_{DS}}{\mu C_{ox} \frac{W}{L}}}$$

Weak I_{DS} dependence

Common Drain AC Schematic

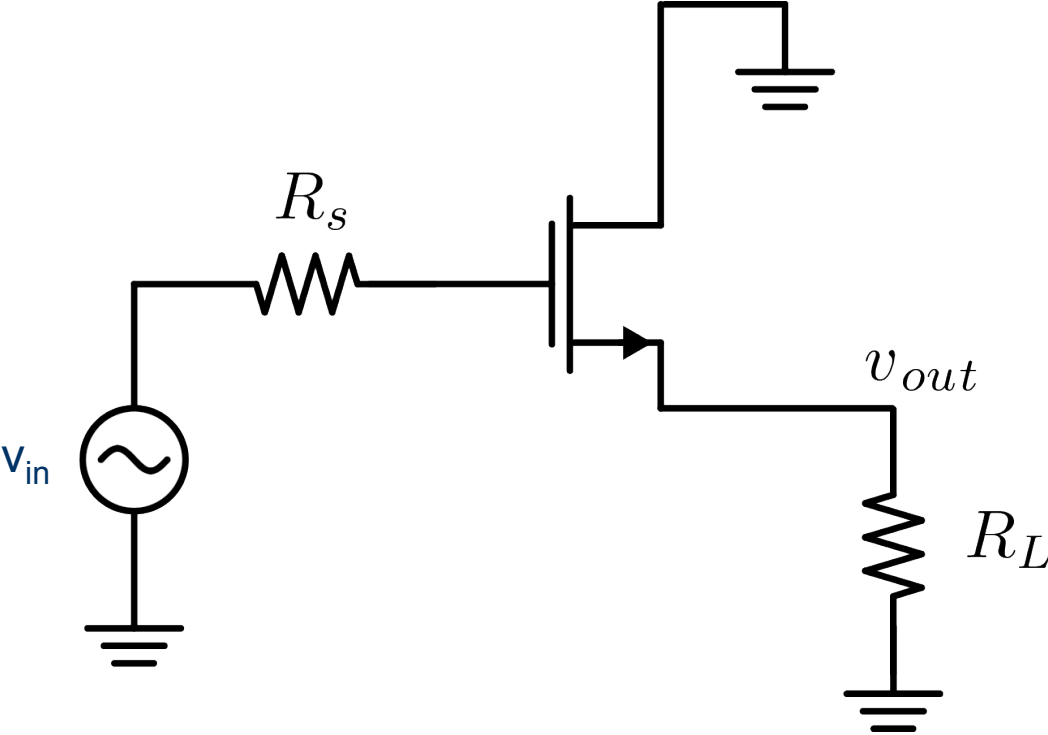

CD Voltage Gain

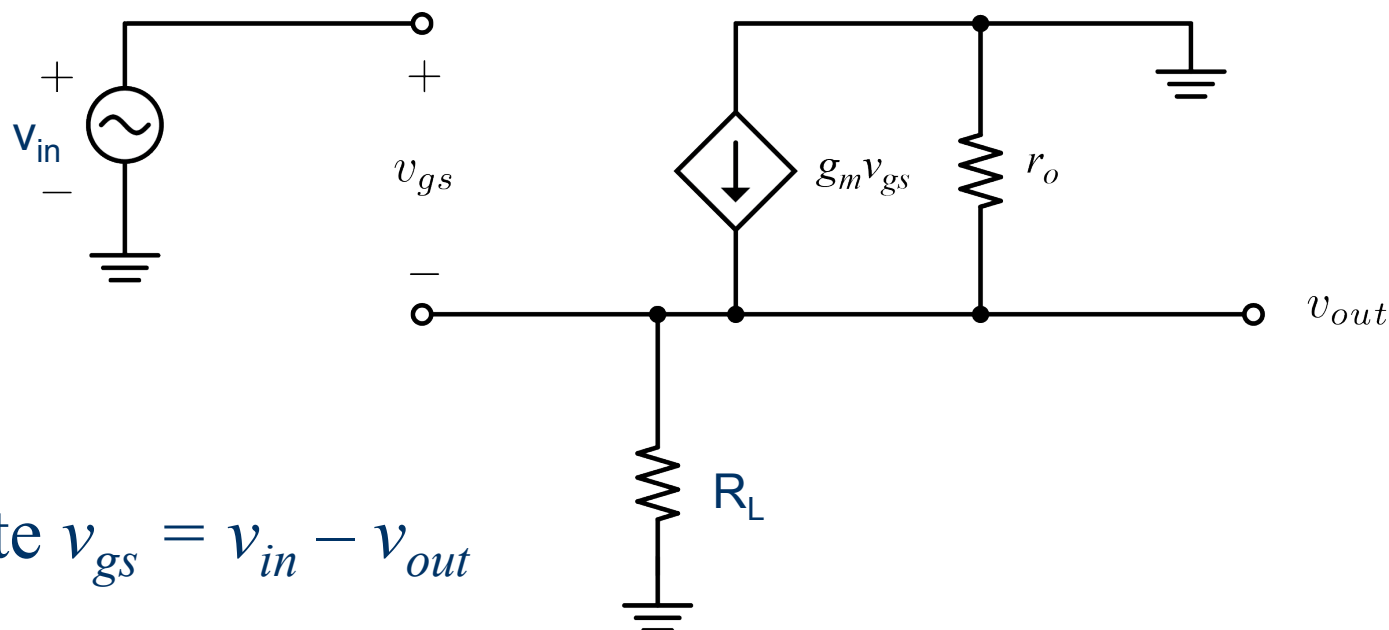

Note $v_{gs} = v_{in} - v_{out}$

$$\frac{v_{out}}{R_L \parallel r_o} = g_m v_{gs}$$

$$\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out})$$

CD Voltage Gain (Cont.)

KCL at source node: $\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out})$


$$\left(\frac{1}{R_L \parallel r_o} + g_m \right) v_{out} = g_m v_{in}$$

Voltage gain:

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{\frac{1}{R_L \parallel r_o} + g_m}$$

$$\frac{v_{out}}{v_{in}} \approx \frac{g_m}{1/R_L + g_m} \approx 1$$

CD Output Resistance

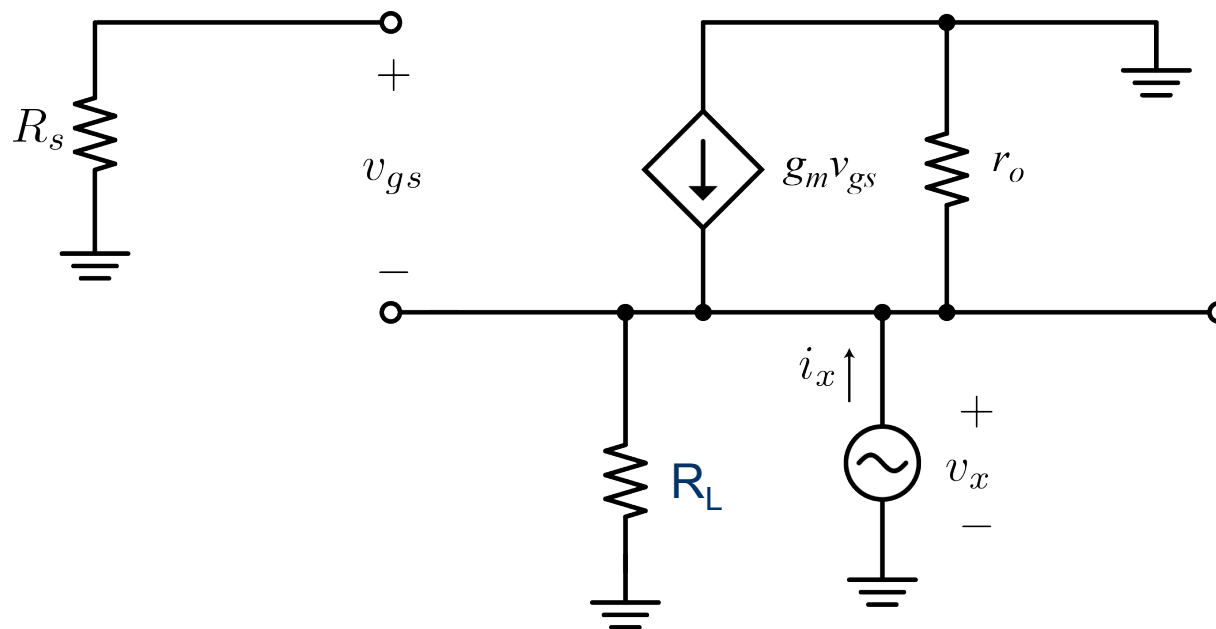


Sum currents at output (source) node:

$$i_x = g_m v_x \quad R_{out} = r_o \parallel R_L \parallel \frac{v_x}{i_x} \quad R_{out} \approx \frac{1}{g_m}$$

CD Output Resistance (Cont.)


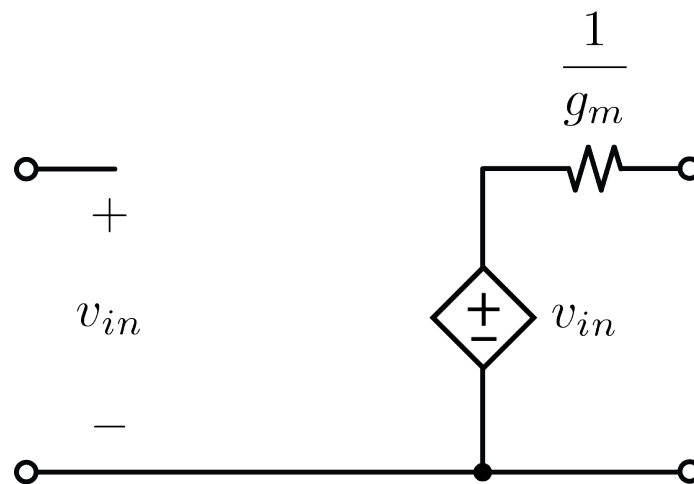
$r_o \parallel R_L$ is much larger than the inverses of the transconductances $\rightarrow$ ignore





Function: a voltage buffer

- High Input Impedance
- Low Output Impedance



Transistor Amplifiers → Gm/V/I

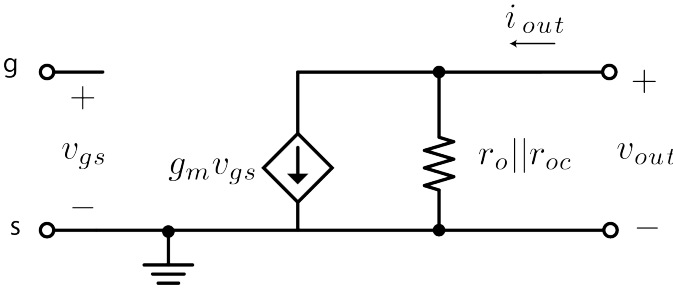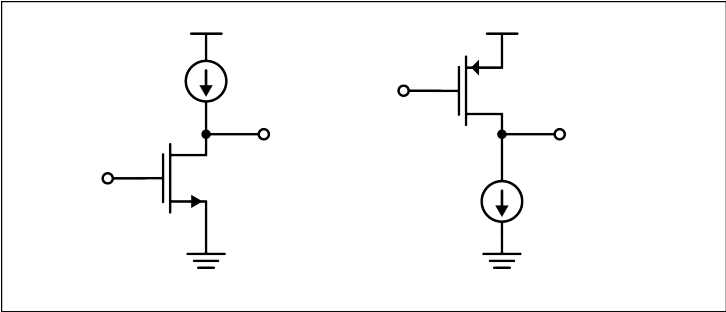

Gm
Amplifier
Common
Source

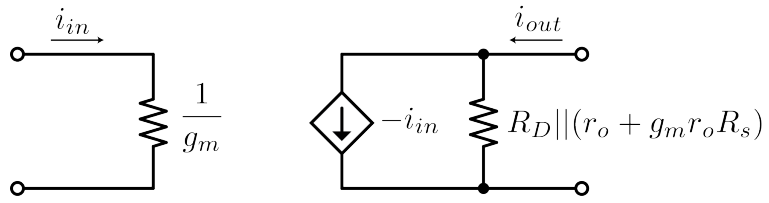
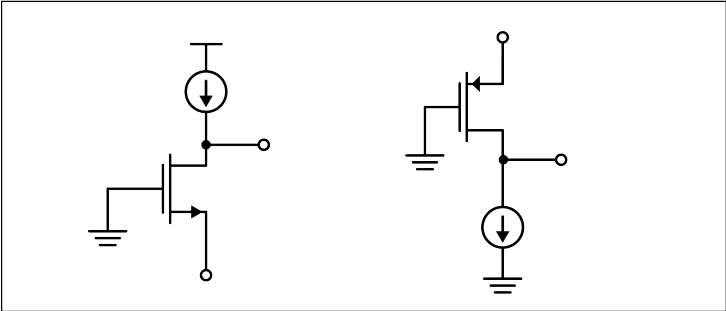


I-Buffer
Common
Gate

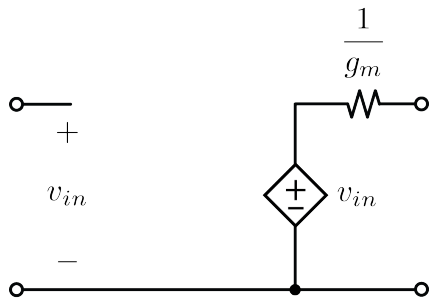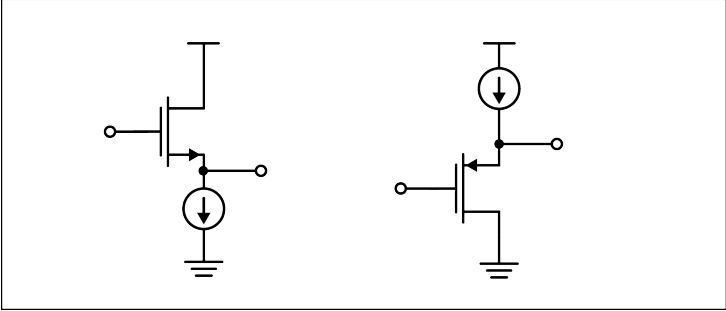

V-Buffer
Source
Follower

Body Effect

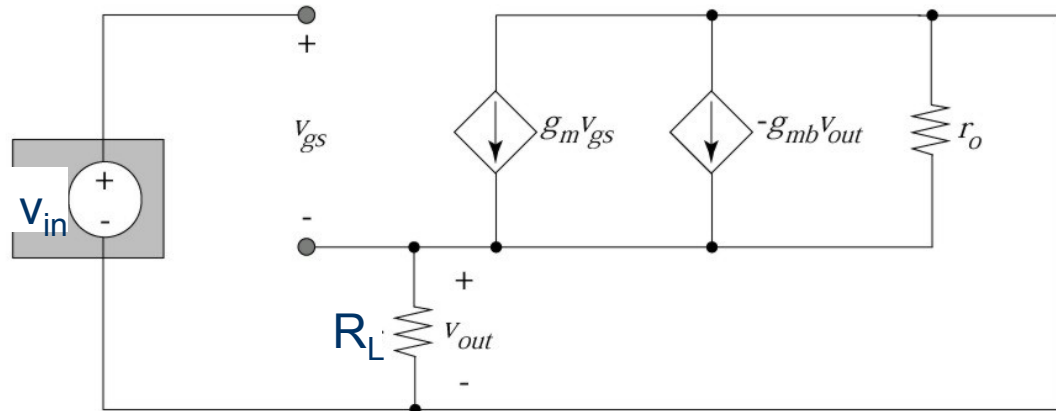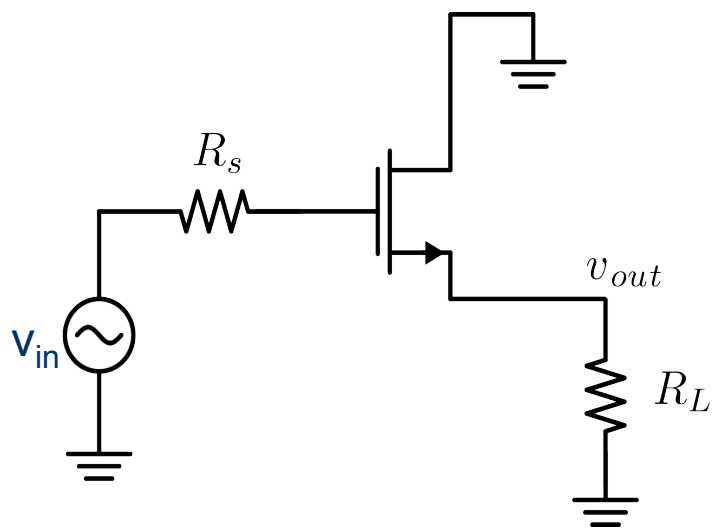

If the backgate is tied to ground you cannot ignore the body effect. How does this effect the gain?

$$\frac{v_{out}}{R_L \parallel r_o} = g_m v_{gs} - g_{mb} v_{out}$$

$$\frac{v_{out}}{v_{in}} = ?$$