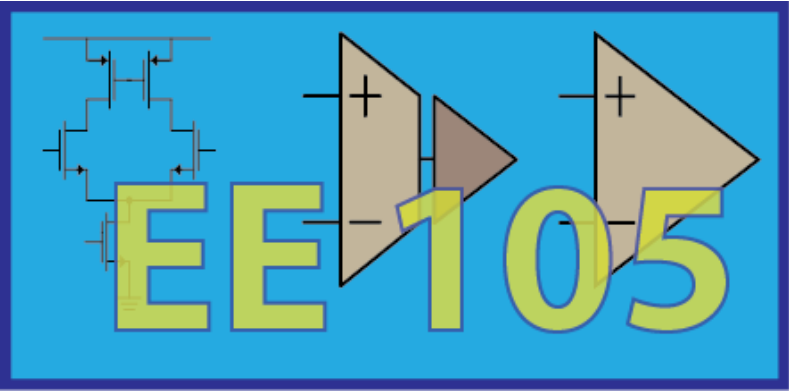




“1-T”

Single-Stage Amplifiers

Prof. Ali M. Niknejad
Prof. Rikky Muller




Announcements

- HW8 due on Friday


– PICK UP EXAM

One-Port Models (EECS 16A)

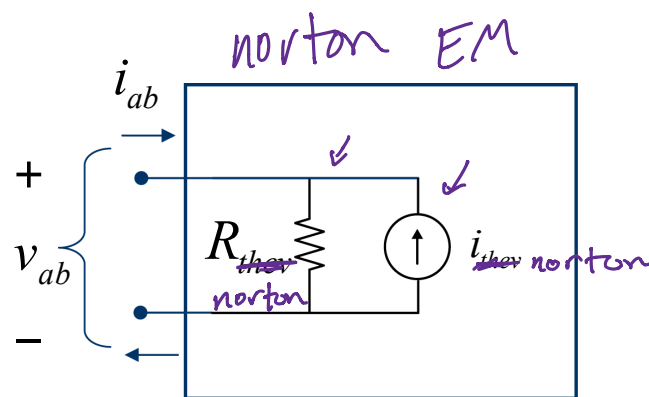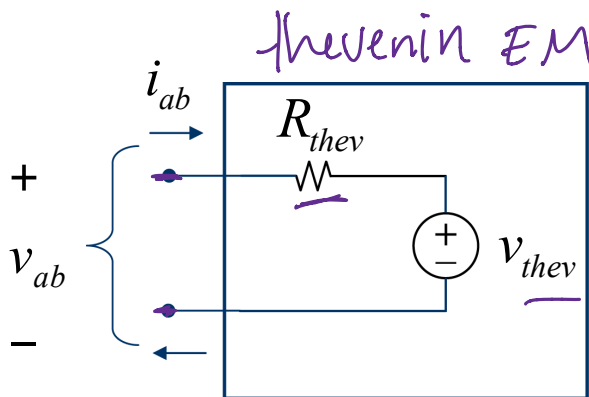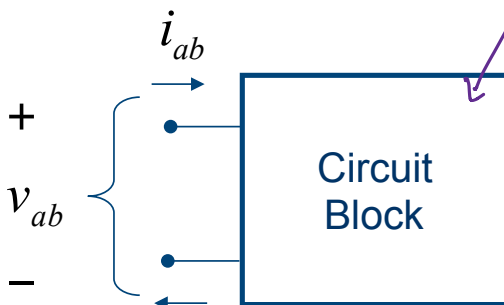- A terminal pair across which a voltage and associated current are defined




Small-Signal Two-Port Models

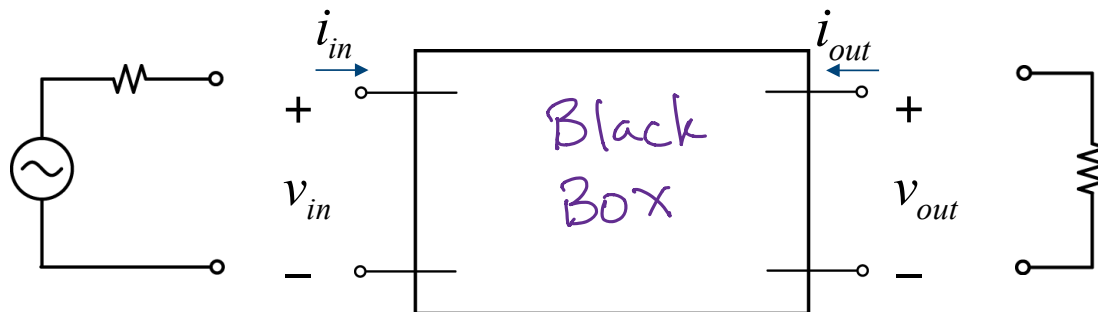


- We assume that input port is linear and that the amplifier is *unilateral*:
 - Output depends on input but input is independent of output.
- Output port : depends linearly on the current and voltage at the input and output ports
- Unilateral assumption is good as long as “overlap” capacitance is small (MOS)

Two-Port Small-Signal Amplifiers


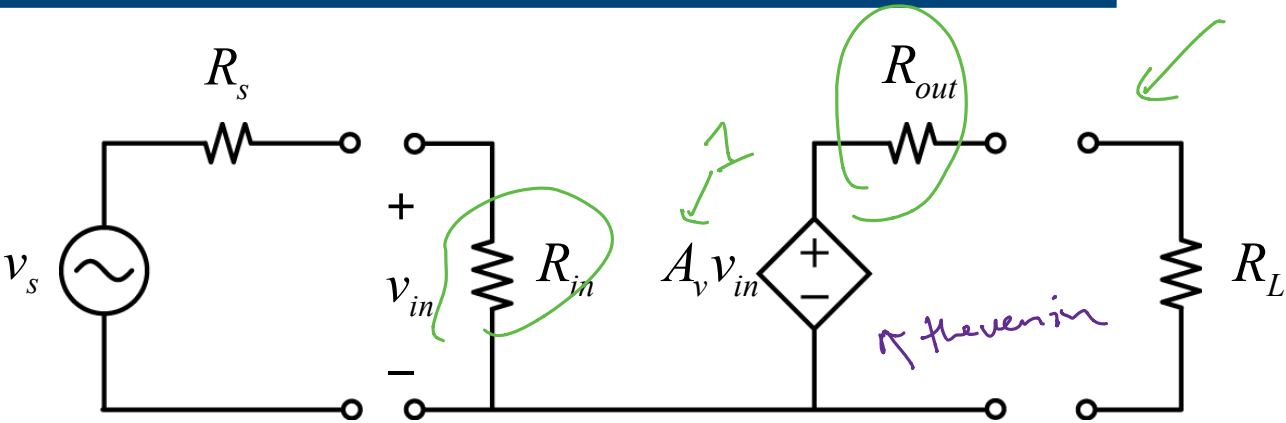


Voltage Amplifier

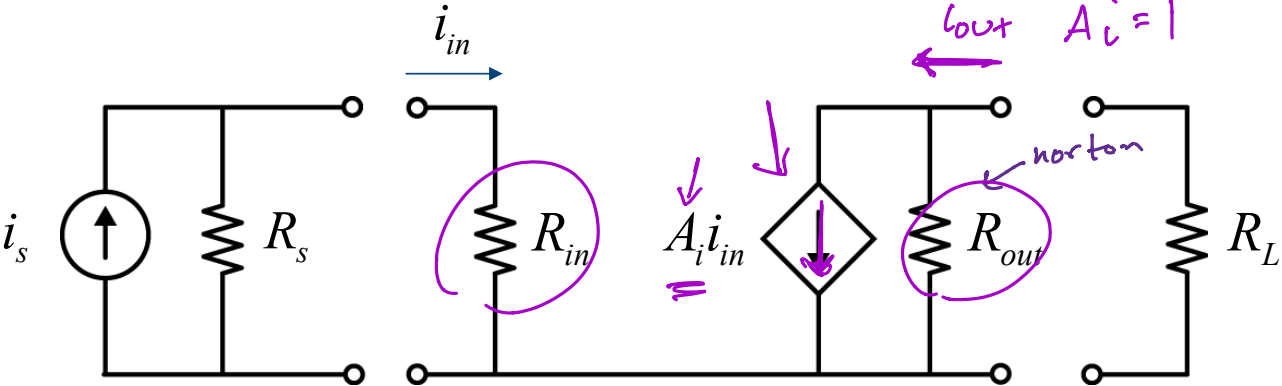



Current Amplifier

Two-Port Small-Signal Amplifiers

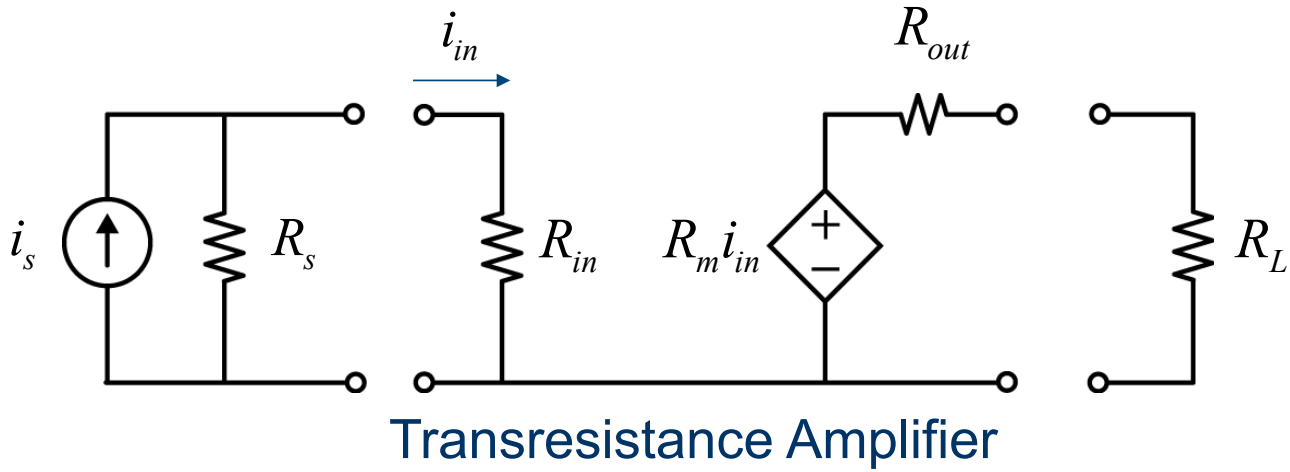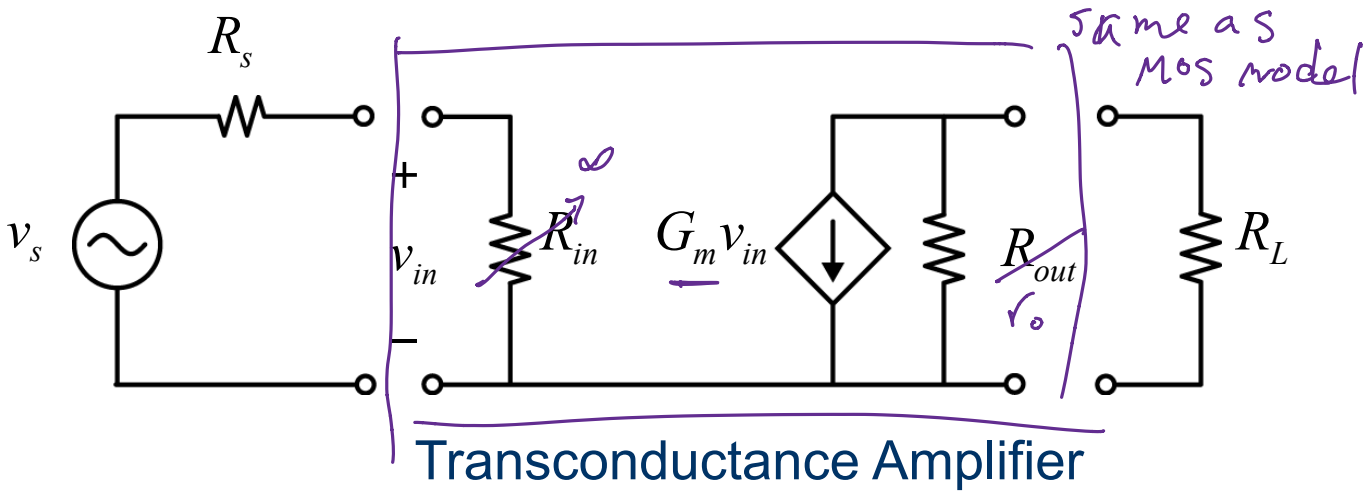

Input Impedance Z_{in}

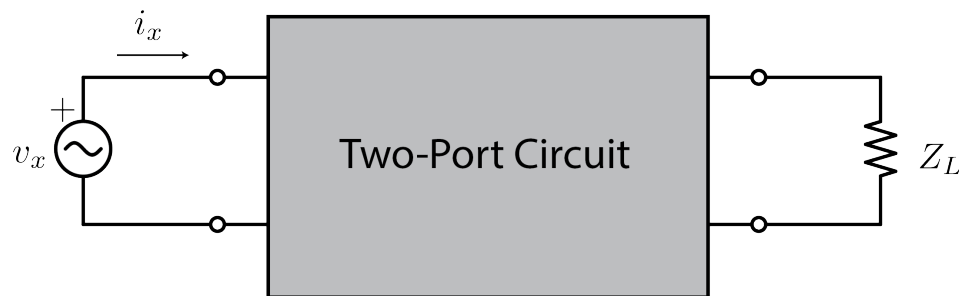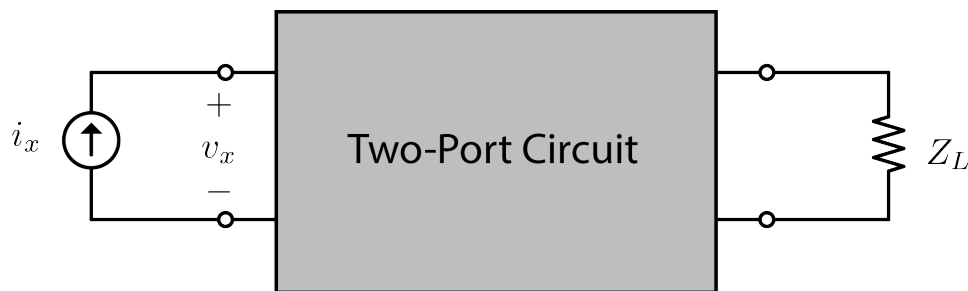Looks like a Thevenin resistance measurement, but note that the output port has the load resistance attached





$$Z_{in} = \left. \frac{v_x}{i_x} \right|_{Z_S \text{ removed}, Z_L \text{ attached}}$$


Output Impedance Z_{out}

Looks like a Thevenin resistance measurement, but note that the *input* port has the *source* resistance attached


$$Z_{out} = \frac{v_x}{i_x} \bigg|_{\substack{Z_L \text{ removed,} \\ Z_S \text{ attached}}}$$

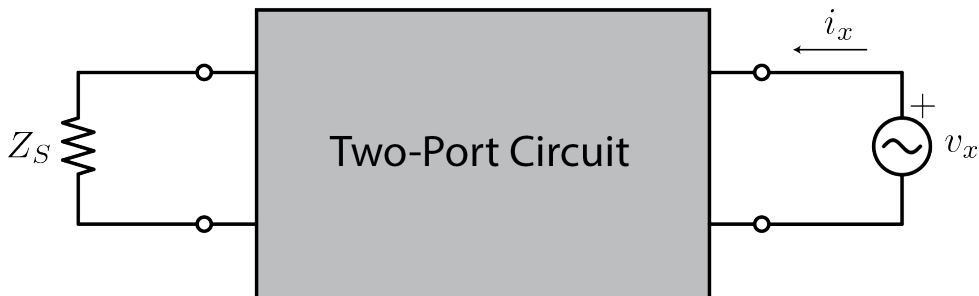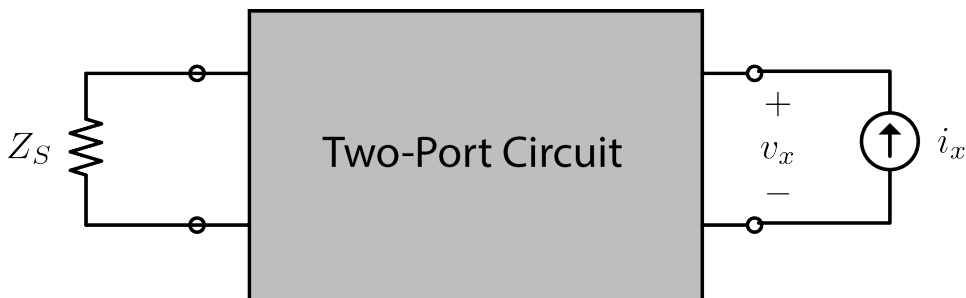


Single-Stage Amplifier Types

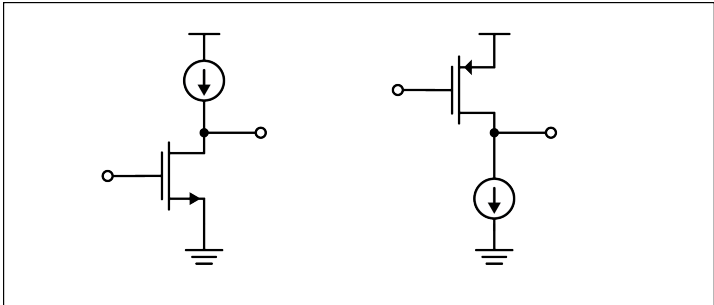

Common Source (CS)

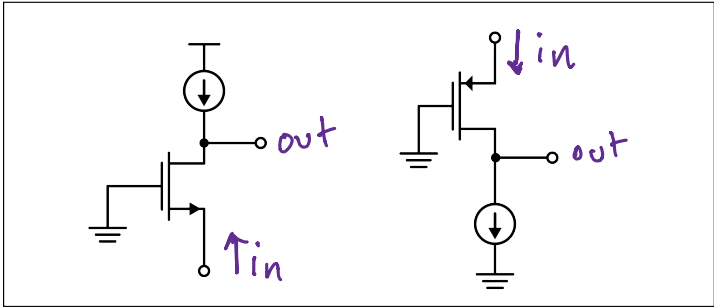

Common Gate (CG)

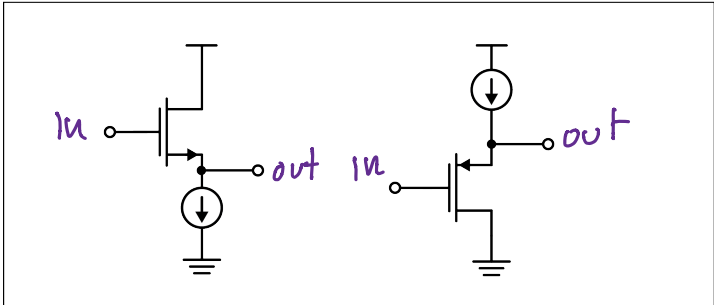


Common Drain (CD)




Common Gate (CG) Amplifier

DC bias:


$$I_{SUP} = I_Q = I_{DS}$$

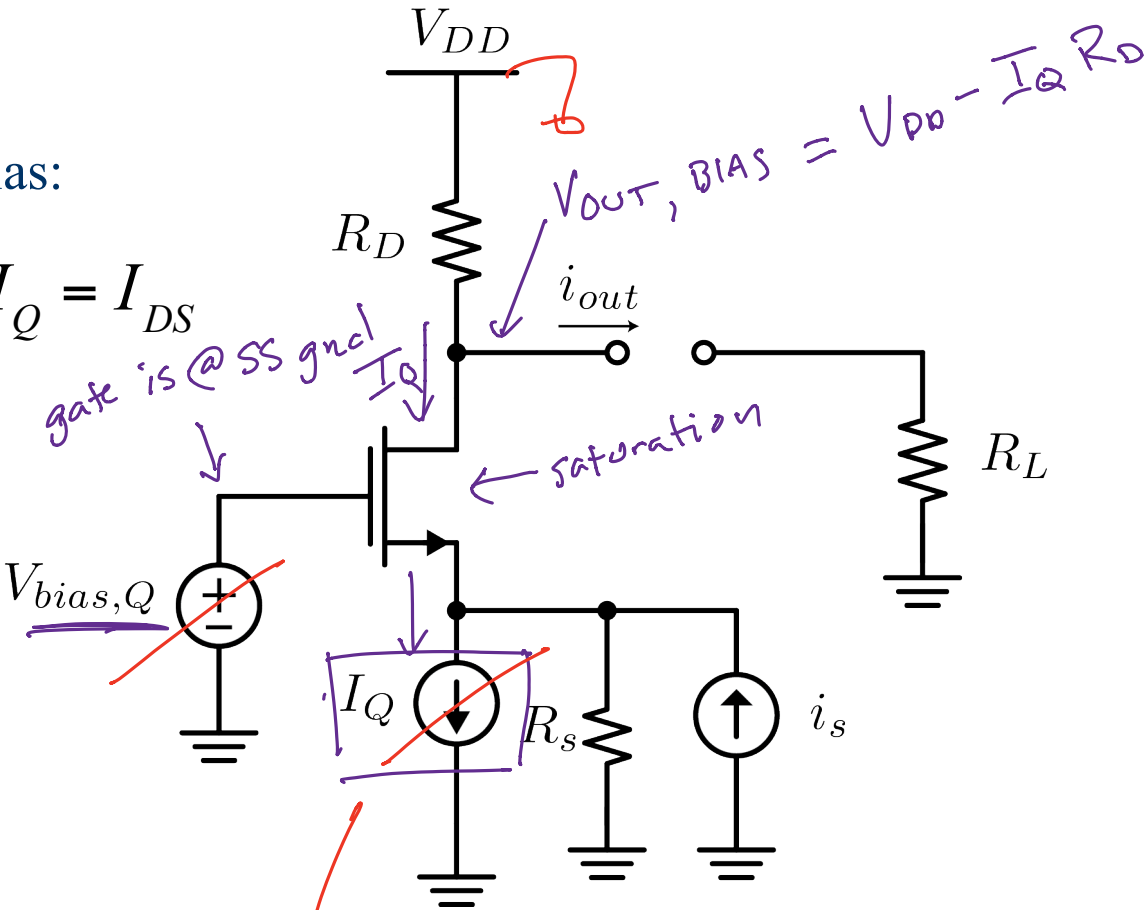


Common Gate AC Model

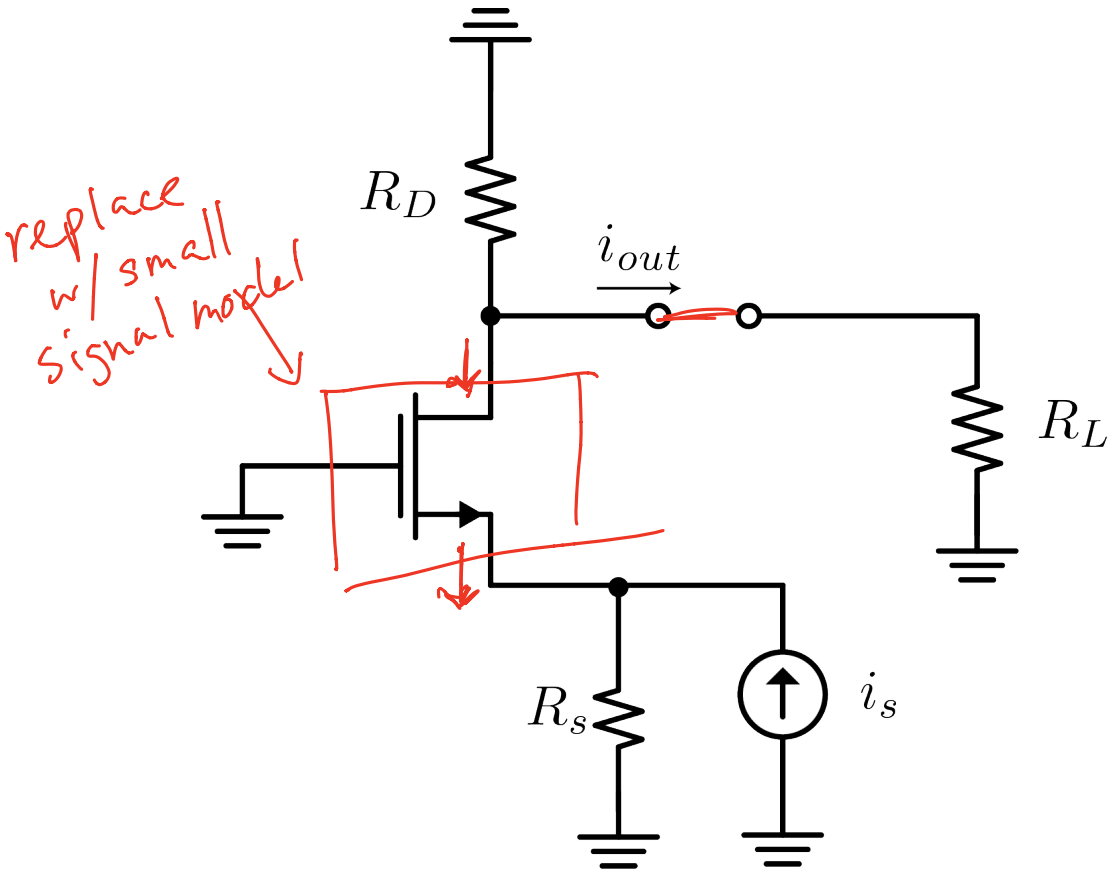


Common Gate Small Signal

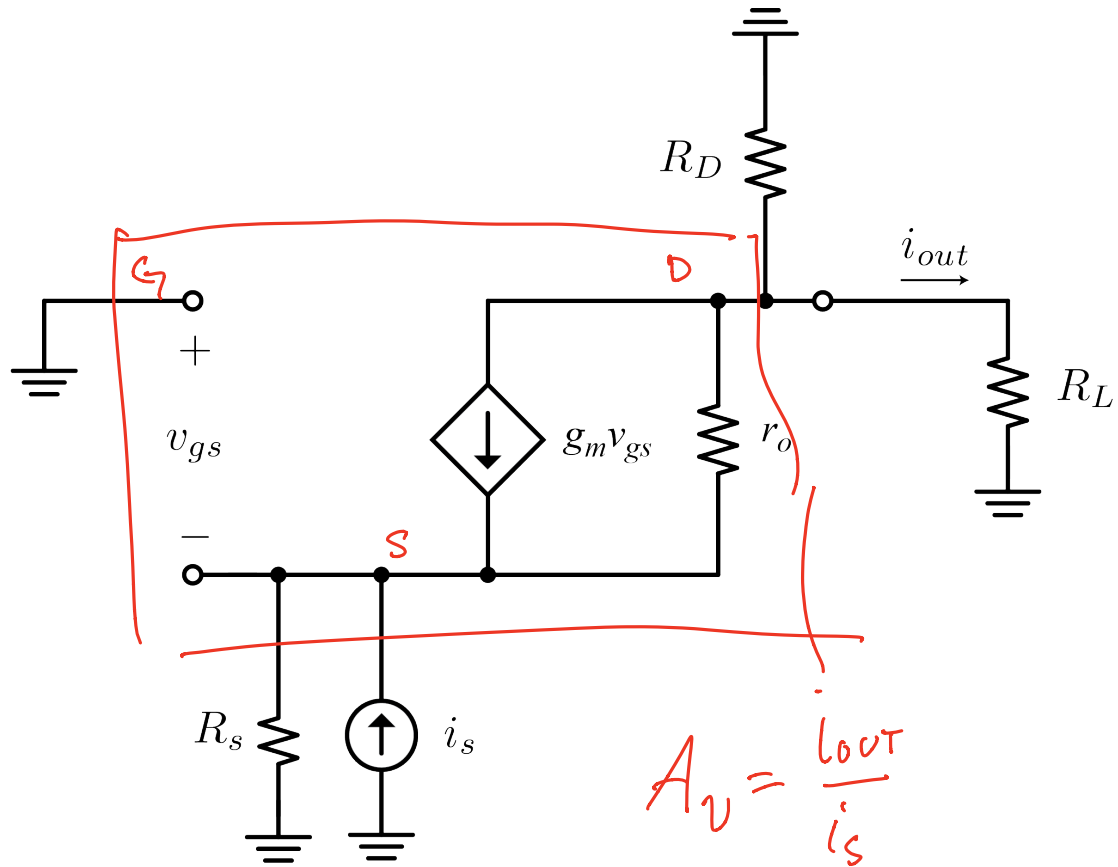

CG as a Current Amplifier: Find A_i

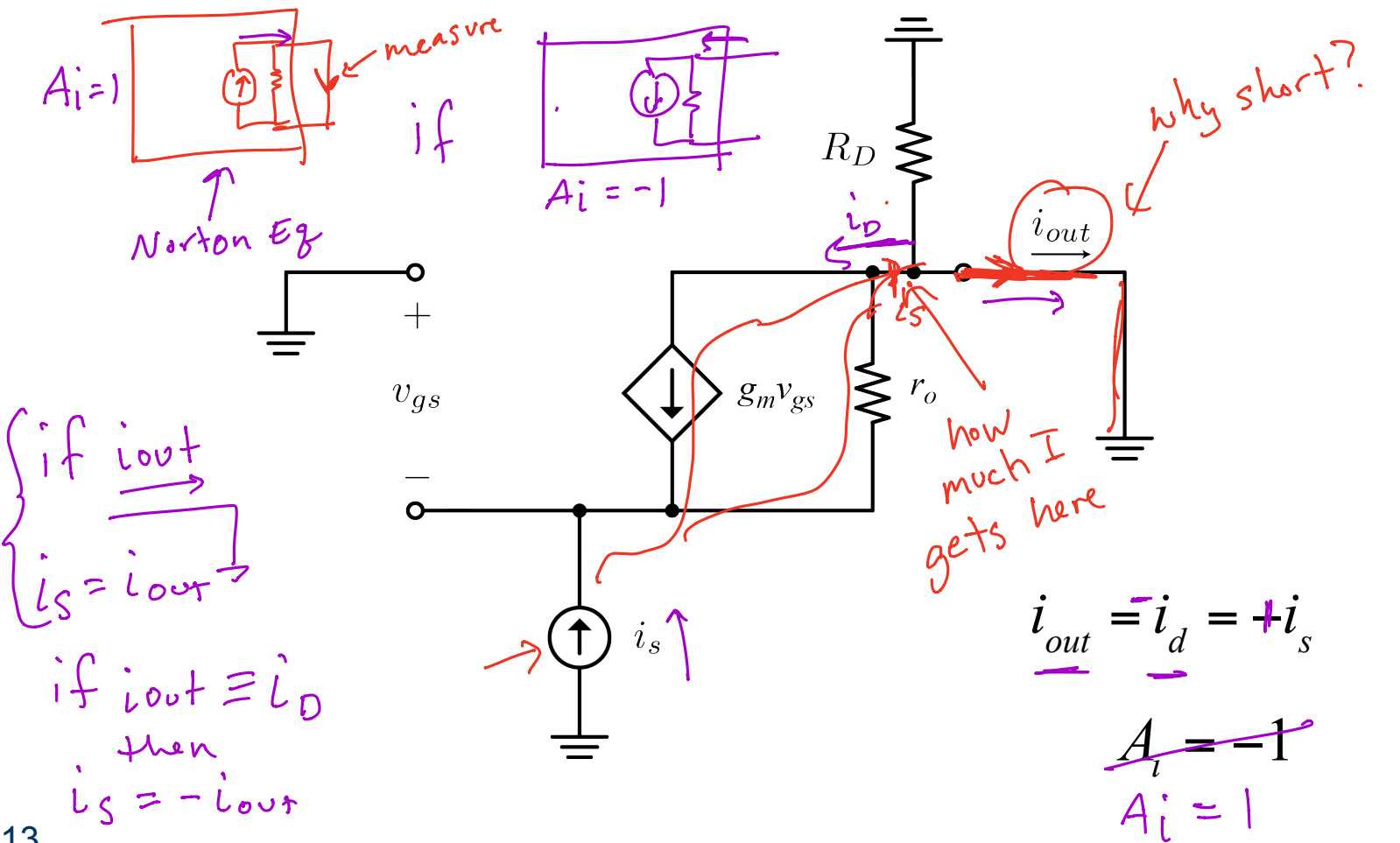

CG Input Resistance

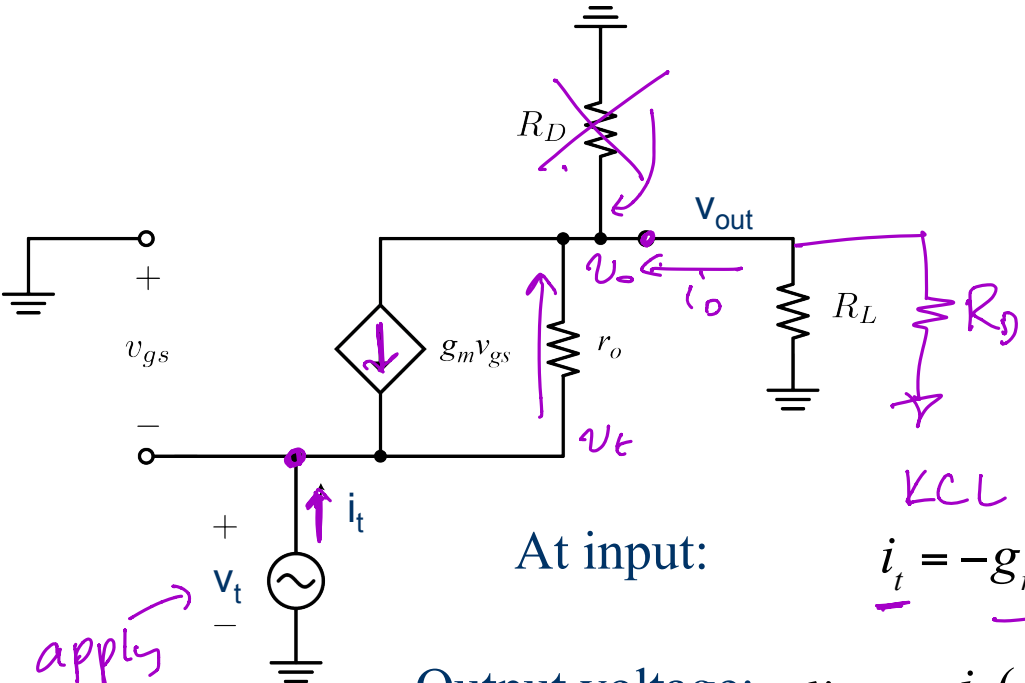

apply
test
voltage (v_t)
measure i_t

At input:

KCL

$$i_t = -g_m v_{gs} + \left(\frac{v_t - v_{out}}{r_o} \right)$$

Output voltage:

$$v_{out} = -i_d (R_D \parallel R_L) \approx i_t (R_D \parallel R_L)$$

$$i_t = g_m v_t + \left(\frac{v_t - (R_D \parallel R_L) i_t}{r_o} \right)$$

Approximations...

- We have this messy result

$$\boxed{\frac{1}{R_{in}}} = \boxed{\frac{i_t}{v_t}} = \frac{g_m + \frac{1}{r_o}}{1 + \frac{R_D \parallel R_L}{r_o}}$$

$\frac{1}{R_{in}} \approx g_m$


- But we don't need that much precision. Let's start approximating:

$g_m \gg \frac{1}{r_o}$ *give you this information*


$R_D \parallel R_L \approx R_L$ *smaller*

$\frac{R_L}{r_o} \approx 0$

r_o is large

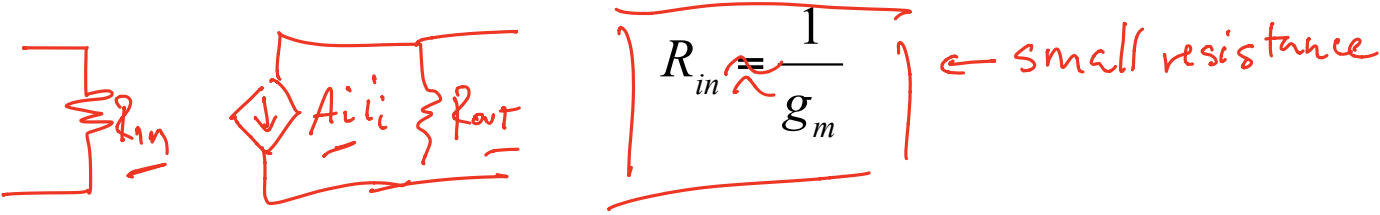

CG Output Resistance

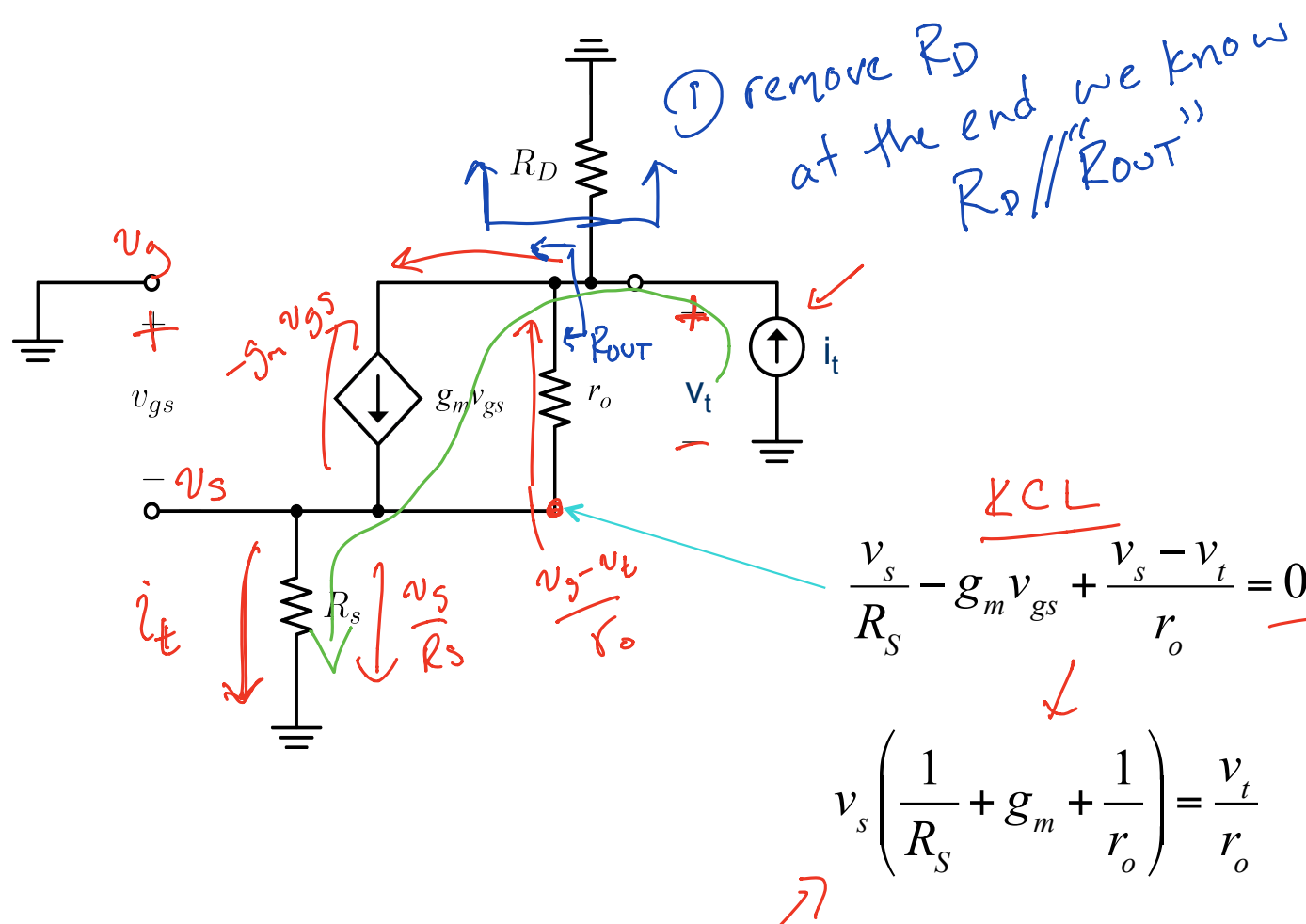

CG Output Resistance


Substituting $v_s = i_t R_S$

$$R_t = \frac{v_t}{i_t}$$

$$i_t R_S \left(\frac{1}{R_S} + g_m + \frac{1}{r_o} \right) = \frac{v_t}{r_o}$$

The output resistance is $(v_t / i_t) \parallel \underline{R_D}$


Bring R_D
back in

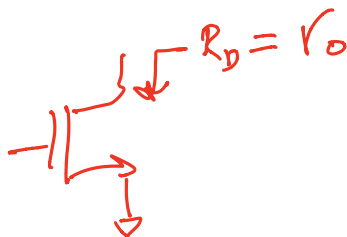

$$R_{out} = R_D \parallel \left(R_S \left(\frac{r_o}{R_S} + g_m r_o + 1 \right) \right)$$

$$R_{out} = R_D \parallel \left(\underline{r_o + g_m r_o R_S + R_S} \right)$$

resistance is
large

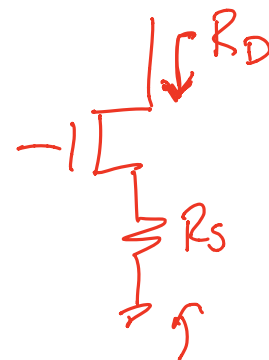

source
degeneration

Approximating the CG R_{out}

The exact result is complicated, so let's try to make it simpler:

$$g_m \approx \underline{500\mu S}$$


$$r_o \approx \underline{200k\Omega}$$

$$R_{out} \cong R_D \parallel [r_o + g_m r_o R_S + \cancel{R_S}] \quad R_S \ll r_o$$

Assuming the source resistance is less than r_o ,


$$R_{out} \approx R_D \parallel [\underline{r_o + g_m r_o R_S}] = \underline{R_D} \parallel [\underline{r_o(1 + g_m R_S)}] \quad \text{good approximation}$$

CG Two-Port Model

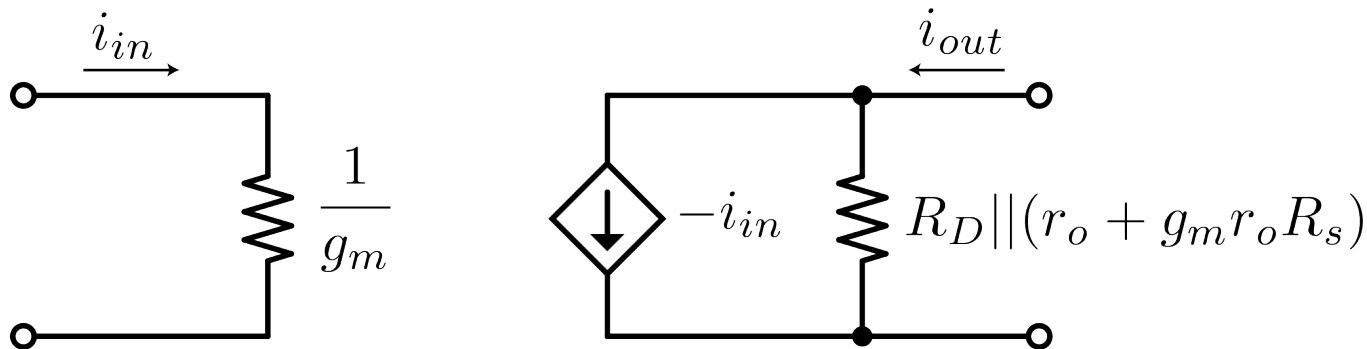


Function: a current buffer

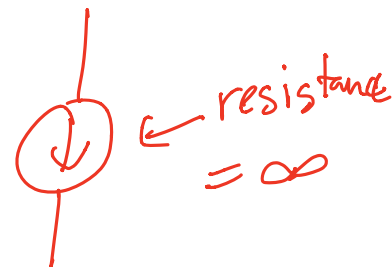
- Low Input Impedance
- High Output Impedance



Common Gate as a “V Amplifier”

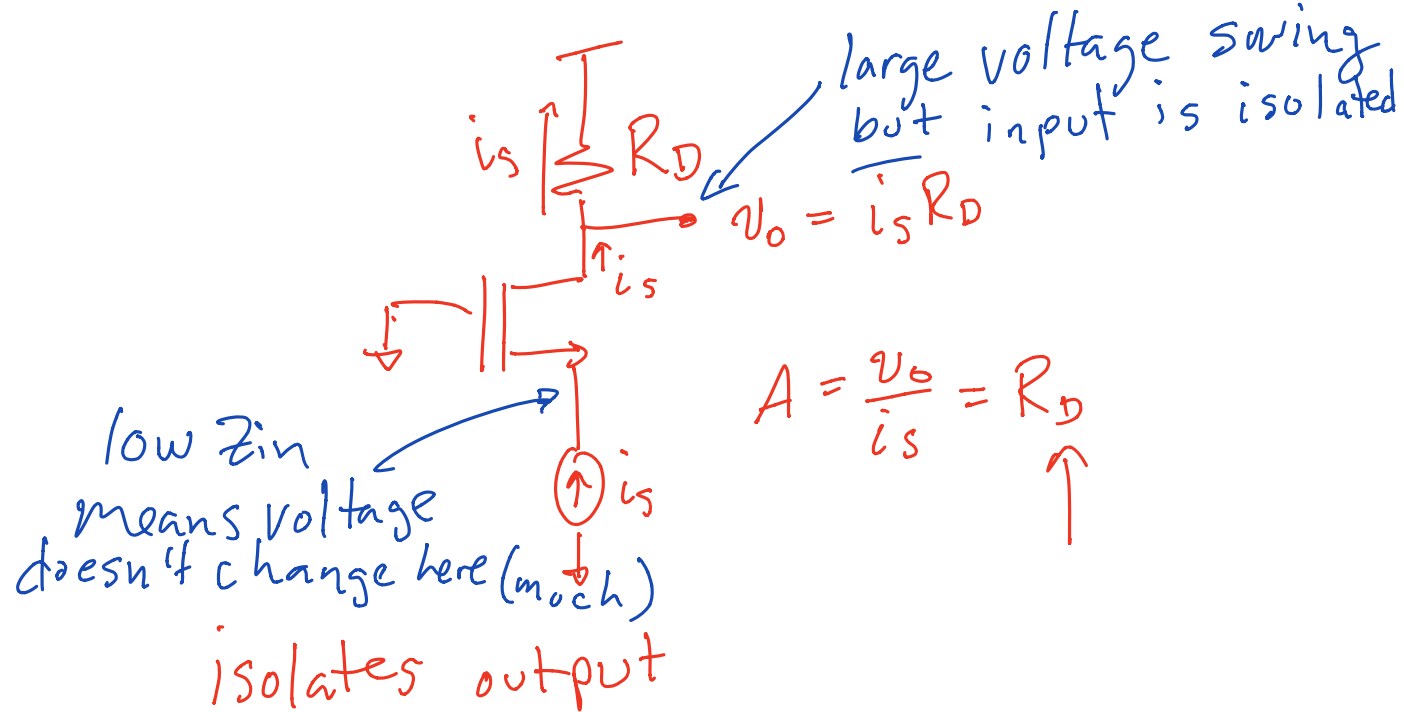



Common-Drain Amplifier

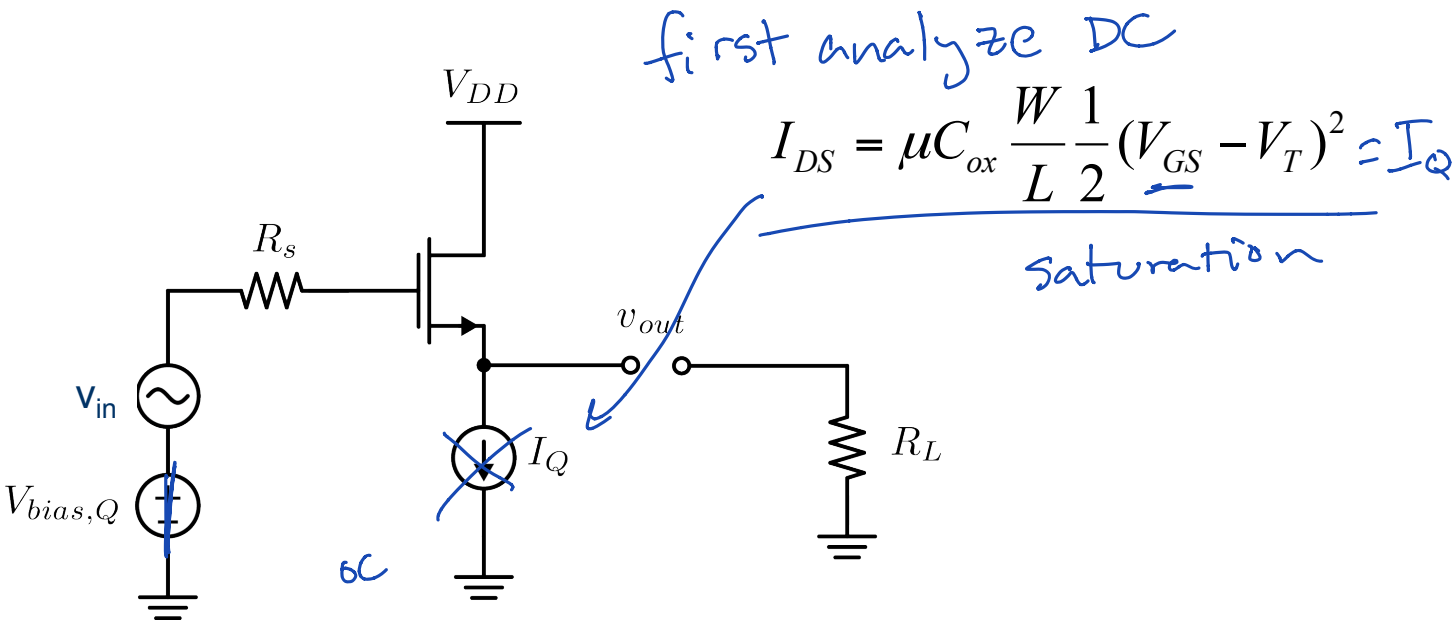


$$\underline{V_{GS}} = V_T + \sqrt{\frac{2I_{DS}}{\mu C_{ox} \frac{W}{L}}}$$

Weak I_{DS} dependence

Common Drain AC Schematic

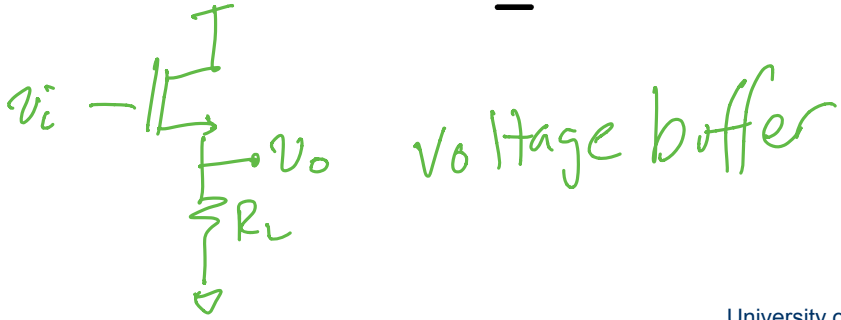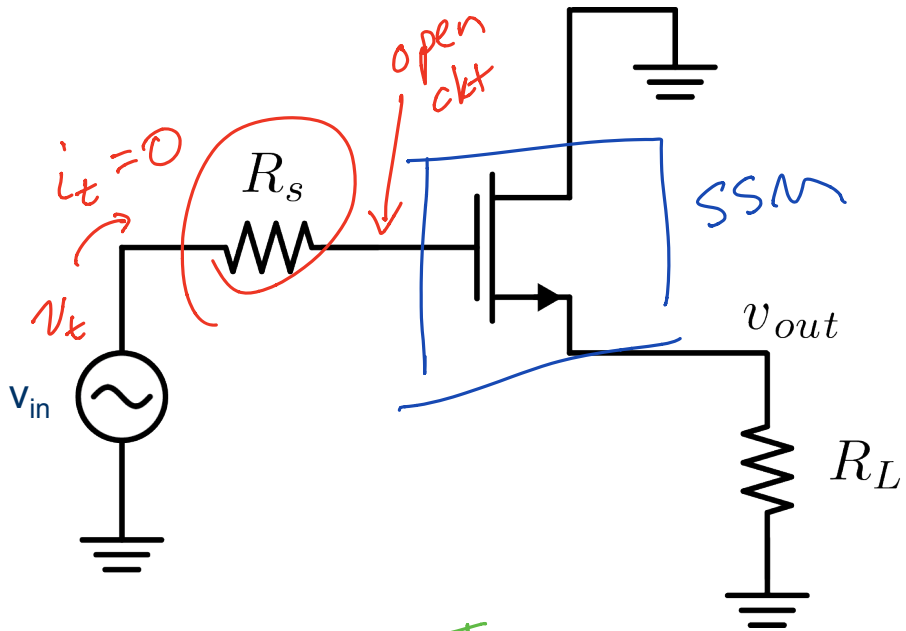

CD Voltage Gain

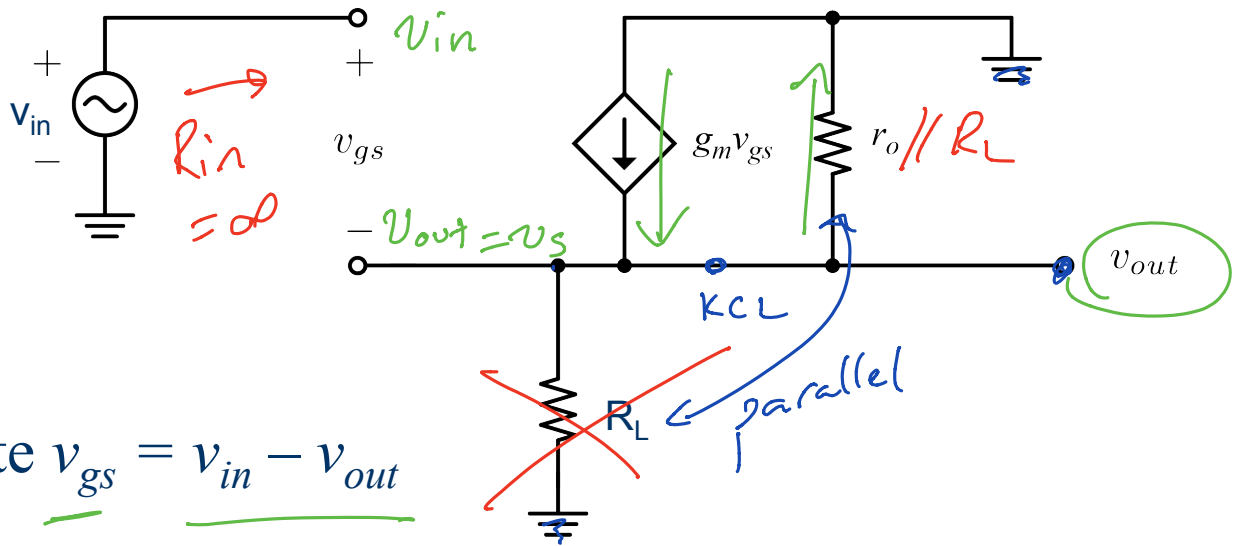

Note $v_{gs} = v_{in} - v_{out}$

$$\frac{v_{out}}{R_L \parallel r_o} = g_m v_{gs}$$

$$\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out})$$

CD Voltage Gain (Cont.)

KCL at source node: $\frac{v_{out}}{R_L \parallel r_o} = g_m (v_{in} - v_{out})$

$$\left(\frac{1}{R_L \parallel r_o} + g_m \right) \underline{v_{out}} = g_m \underline{v_{in}}$$

Voltage gain:

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{\frac{1}{R_L \parallel r_o} + g_m}$$

$r_o \rightarrow \text{large}$
 $R_L \parallel r_o \approx R_L$


want R_L large

$$\frac{v_{out}}{v_{in}} \approx \frac{g_m}{\underbrace{1/R_L + g_m}} \approx 1$$

$g_m > \frac{1}{R_L} \leftarrow \text{if } R_L \text{ large}$

$\sim 0.97 \rightarrow \text{always } < 1$

CD Output Resistance

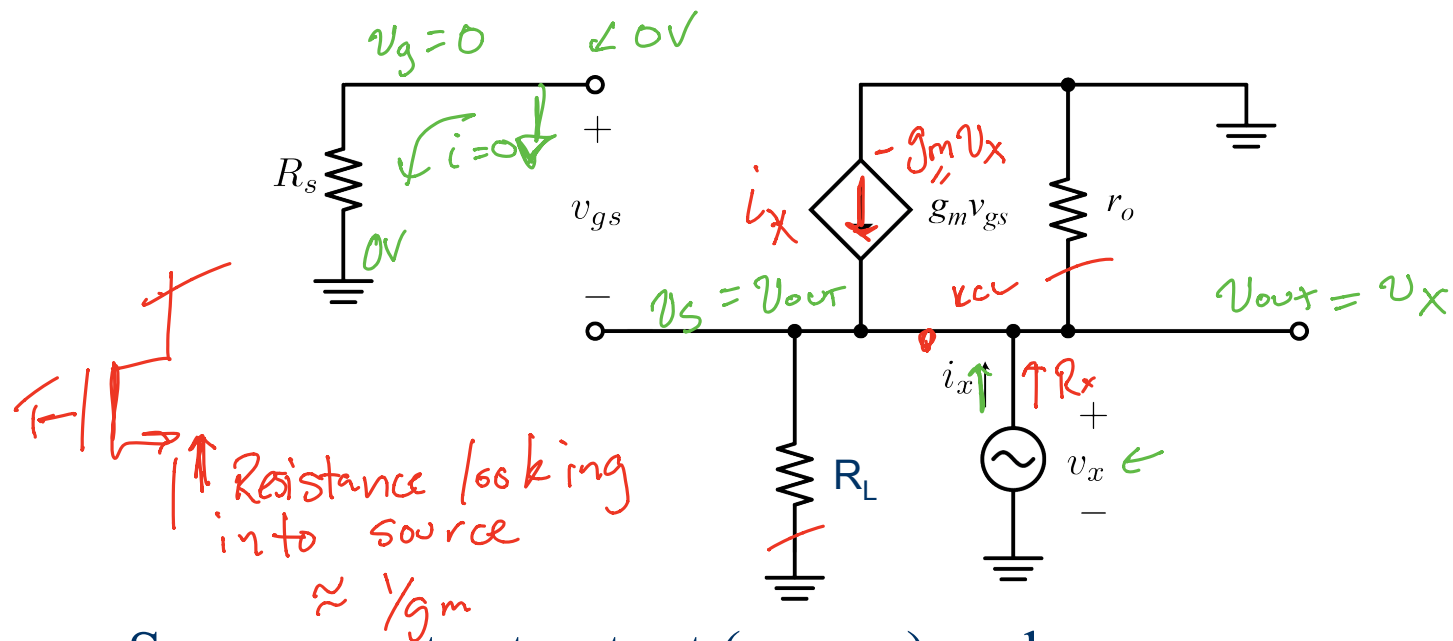

Sum currents at output (source) node:

$$i_x = g_m v_x$$

$$R_{out} = r_o \parallel R_L \parallel \left(\frac{v_x}{i_x} \right) = \frac{1}{g_m}$$


$$R_{out} \approx \frac{1}{g_m}$$

Handwritten notes:

- $\frac{v_x}{i_x} = \frac{1}{g_m}$ (red)

CD Output Resistance (Cont.)


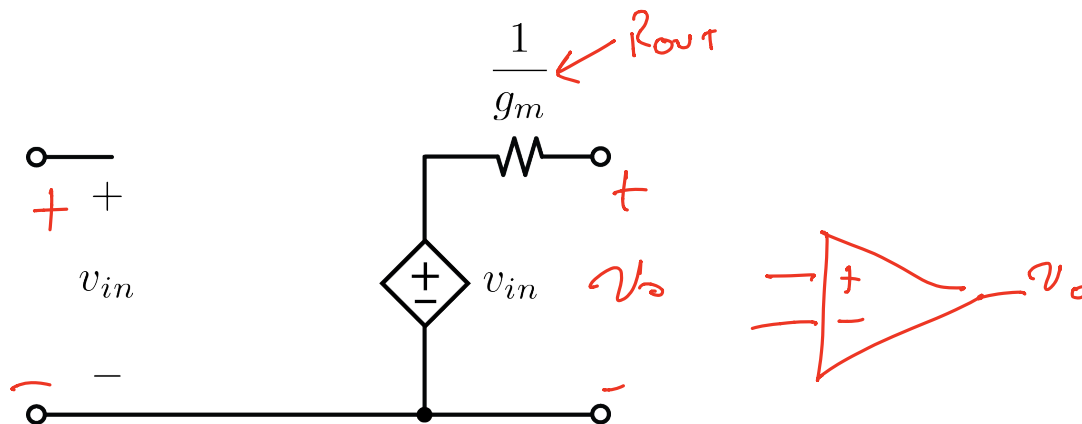
$r_o \parallel R_L$ is much larger than the inverses of the transconductances $\rightarrow$ ignore





Function: a voltage buffer

- High Input Impedance
- Low Output Impedance



Transistor Amplifiers → Gm/V/I

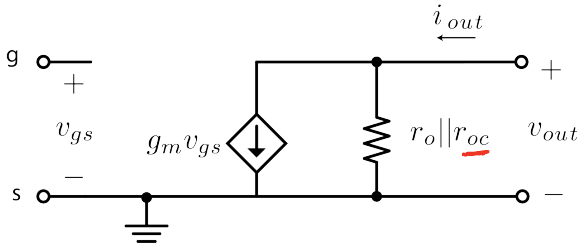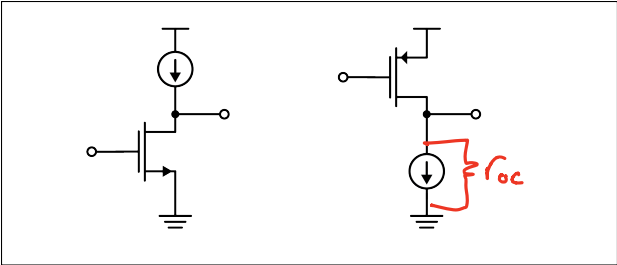

Gm
Amplifier
Common
Source

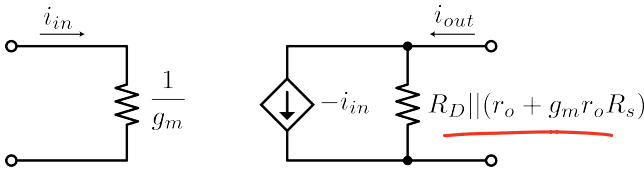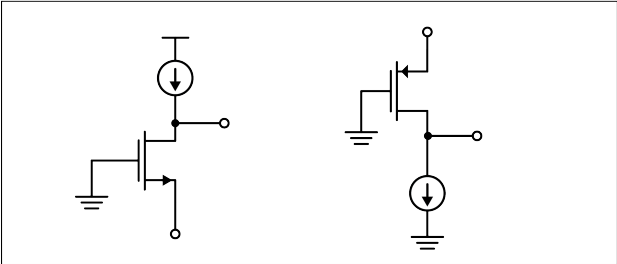

I-Buffer
Common
Gate

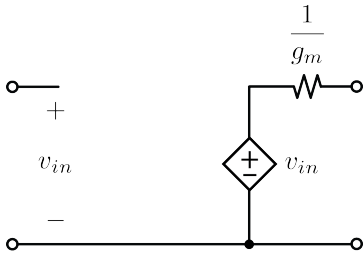
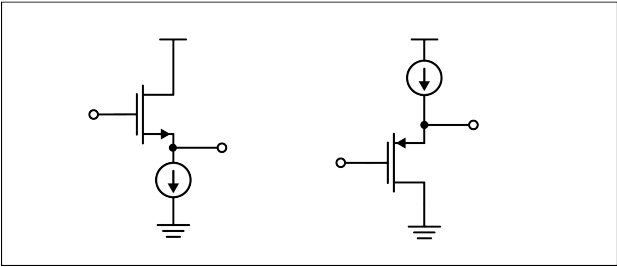


V-Buffer
Source
Follower

$R_s \approx \frac{1}{g_m}$

$r_o + R_s + g_m r_o R_s \approx r_o (1 + g_m R_s)$


Body Effect

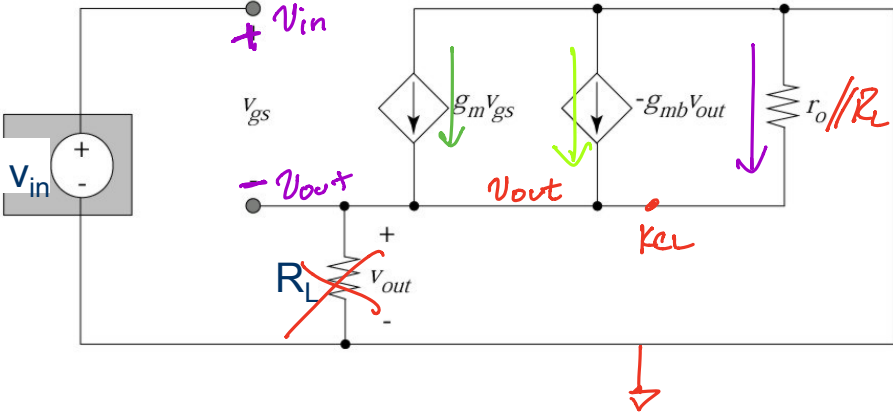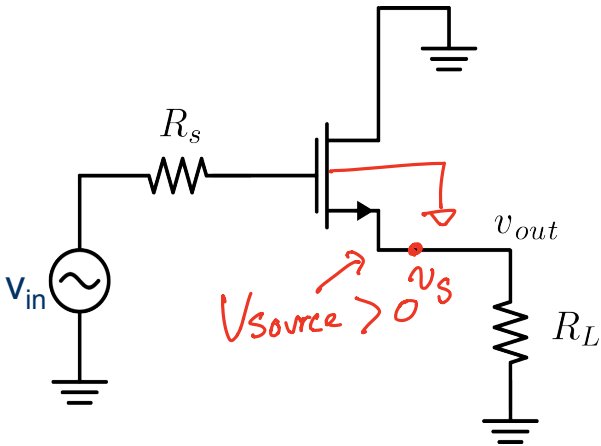

If the backgate is tied to ground you cannot ignore the body effect. How does this effect the gain?

SSM
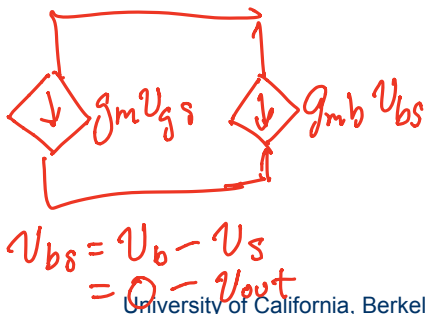
$$\frac{v_{out}}{R_L \parallel r_o} = \underbrace{g_m v_{gs}} - \underbrace{g_{mb} v_{out}} - \frac{v_{out}}{R_L \parallel r_o} = 0$$
$$\frac{v_{out}}{v_{in}} = ?$$
$$\frac{v_{out}}{R_L \parallel r_o} + g_{mb} v_{out} = g_m v_{gs}$$



$$v_{gs} = v_{in} - v_{out} \quad \checkmark$$


$$\frac{v_{out}}{R_L // r_o} + g_{mb} v_{out} + \underline{g_m v_{out}} = g_m v_{in}$$

$$v_{out} \left(\frac{1}{R_L // r_o} + g_{mb} + g_m \right) = g_m v_{in}$$

$$\frac{v_{out}}{v_{in}} = \frac{g_m}{\underbrace{\frac{1}{R_L // r_o} + g_{mb}}_{\text{small}} + g_m}$$

approximations
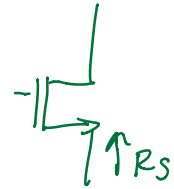
$$\frac{v_{out}}{v_{in}} \approx \frac{g_m}{g_{mb} + g_m}$$



$$\frac{1}{g_m} \\ \sim \frac{1}{g_m + g_{mb}}$$