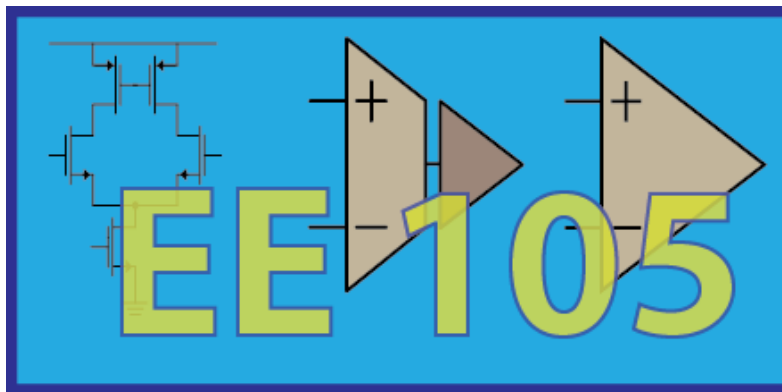




Differential Amplifiers


Prof. Ali M. Niknejad
Prof. Rikky Muller



Announcements

- HW11 due on Friday, last homework!
- Lab 6 due this week, last lab!
- Check web site for updates on RRR & finals week office hours and review sessions:
- <http://rfic.eecs.berkeley.edu/105/lectures.html>

Multistage Analysis Example

 


Cutting Through the Complexity


- 1. Identify the “signal path” between the input and output
- 2. Eliminate “background” transistors to reduce clutter
↳ biasing
- 3. For “background” transistors, understand their role (e.g. DC biasing)
- 4. For frequency response, identify “hi-Z” nodes.

$\tau = RC$ look for high R
 contributes to dom. pole / BW


Eliminate Clutter

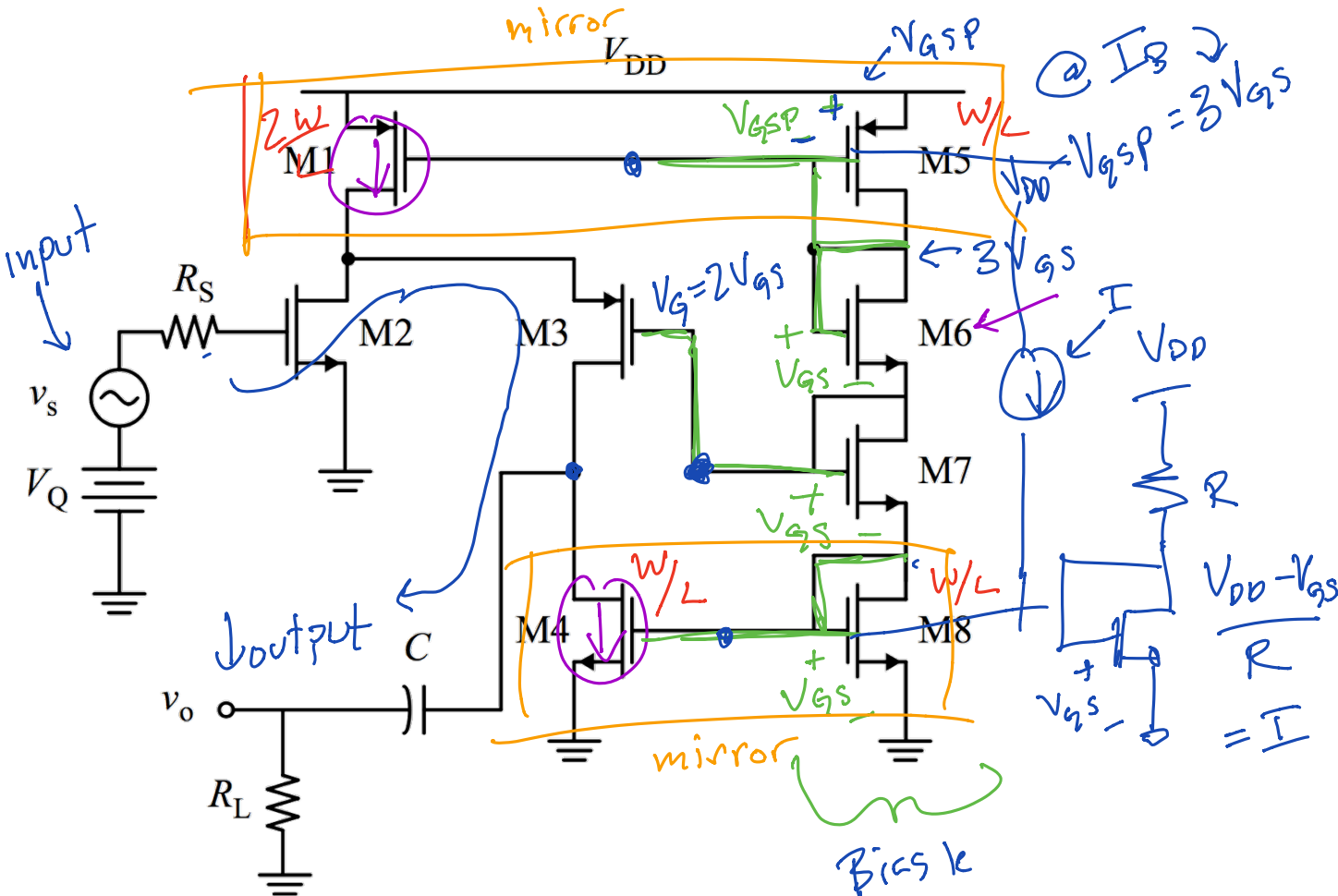

Identify Signal Path & Amplifier Stages

 

DC Biasing

 


Small-Signal Models


"folded"
Cascode

Cascode disadv.
= output swing

folded cascode.
= improved
output swing

 


Two-Port Model

 


Basic Amplifier Types


Common Source

 


Common Gate

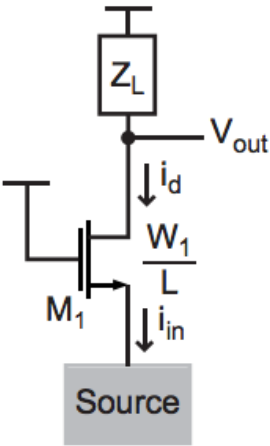


Source Follower

 


Common Source with Source Degeneration

 


Current Mirror

 

Differential Amplifier

 

Differential & Common Mode Signals

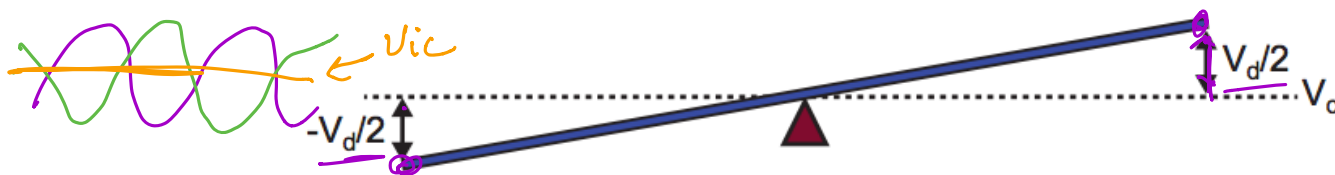

- Consider positive and negative input terminal signals V_i^+ and V_i^-
- Define differential signal as: $V_{id} = V_{in}^+ - V_{in}^-$ ←
- Define common mode signal as: $V_{ic} = (V_{in}^+ + V_{in}^-)/2$
- We can create arbitrary V_i^+ and V_i^- signals from differential and common mode components: ↑ average value

$$V_{in}^+ = \underline{V_{ic}} + \underline{\frac{1}{2}V_{id}}$$

$$V_{in}^- = \underline{V_{ic}} - \underline{\frac{1}{2}V_{id}}$$


- This also applies to differential output signals:

$$V_o^+ = V_{oc} + \frac{1}{2}V_{od}$$


$$V_o^- = V_{oc} - \frac{1}{2}V_{od}$$

Why Differential?

- Differential circuits are much less sensitive to noises and interferences
- Differential configuration enables us to bias amplifiers and connect multiple stages without using coupling or bypass capacitors
- Differential amplifiers are widely used in IC's
 - Excellent matching of transistors, which is critical for differential circuits
 - Differential circuits require more transistors → not an issue for IC



 


Brain-Machine Interfaces


 


Source: Hochberg et al., *Nature* '12

Neural Recording

   


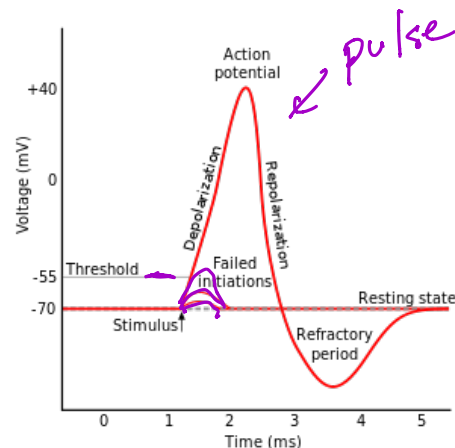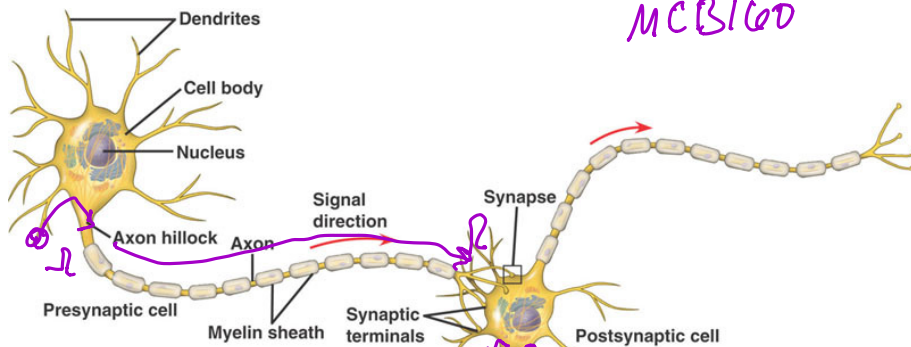- An array of electrodes is implanted in the motor cortex and senses extracellular signals that include firing from nearby neurons




- The propagation of signals from neuron to neuron is called an Action Potential, which is analogous to a digital “pulse”

Extracellular Neuronal Signals

 


- The goal of a neural recording device is to record the small-amplitude neural signals and pick out the meaningful signals from the “noise”.
- These signals are then decoded to create trajectories, movements, and speeds for controlling prostheses, computers, etc.

60Hz and Other Interferers

 


- In reality, the tiny signals recorded from the brain can get corrupted by numerous interferers.
- Ambient 60Hz noise couples into electrical signals in and on the body
- Motion can cause voltage artifacts from the movement of the electrodes relative to the neurons

Key Idea: Differential Recording

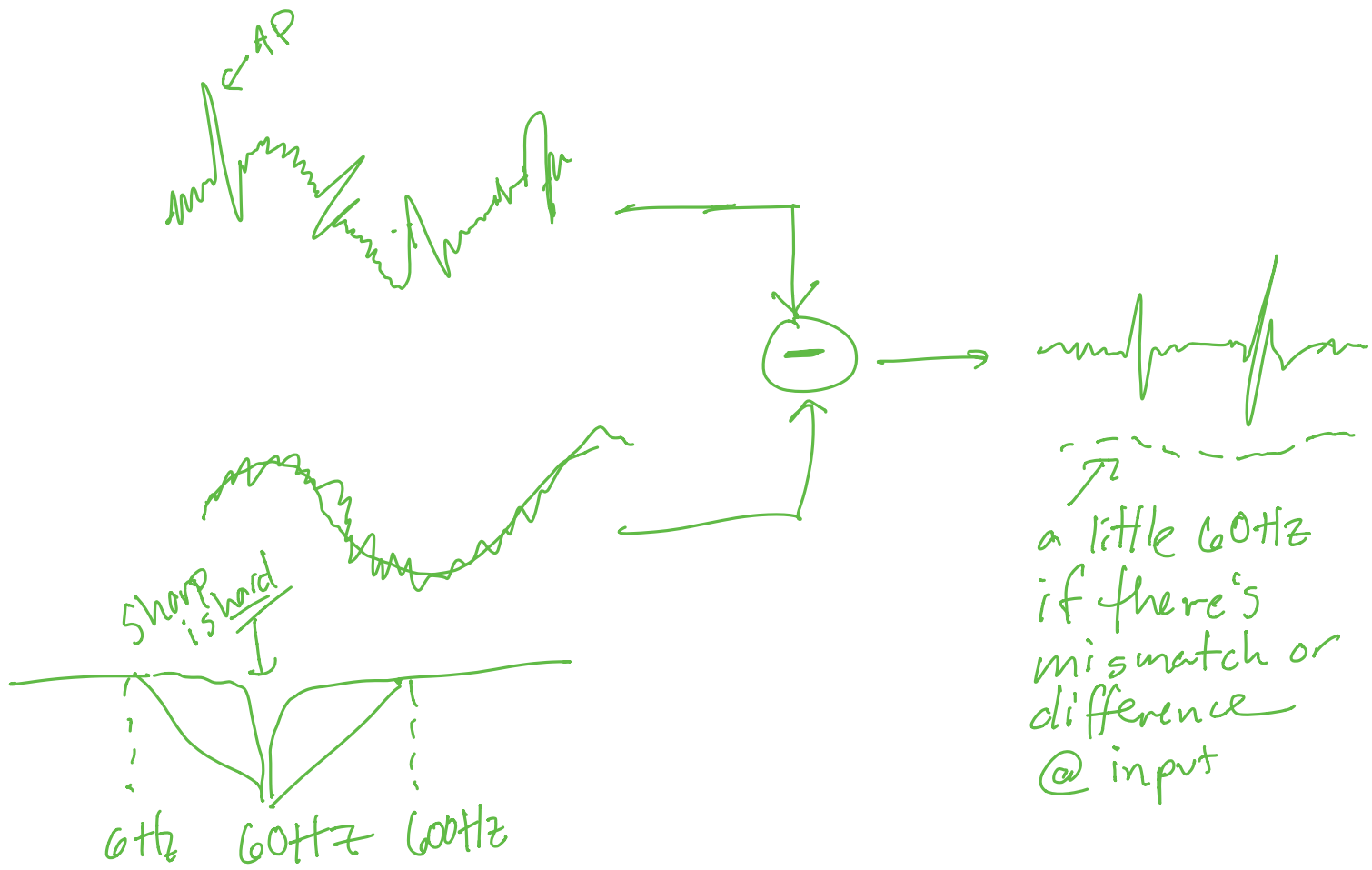

MOS Differential-Pair

Basic Configuration

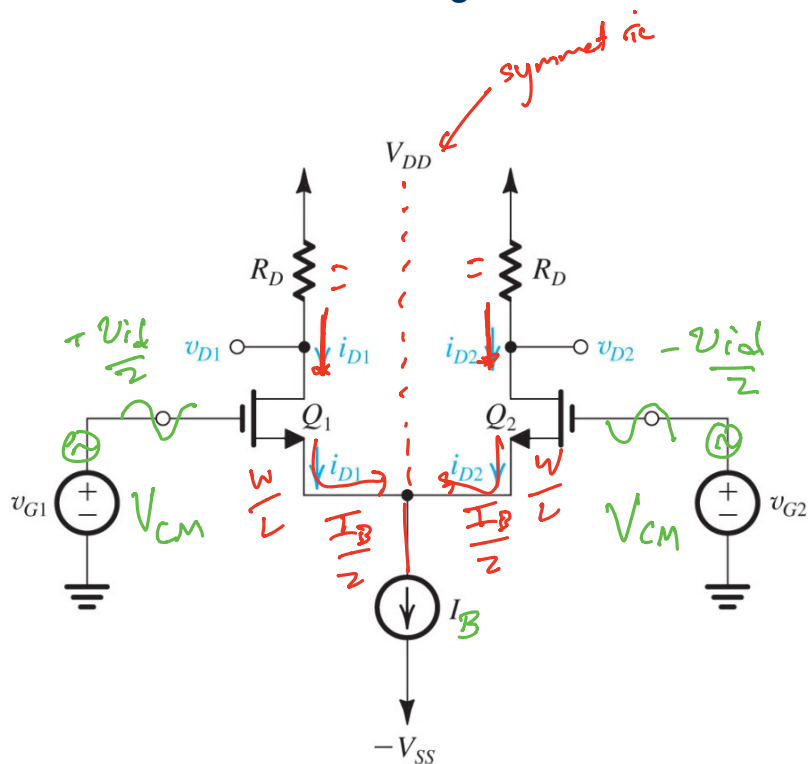

Two matched MOS transistors

Common current bias

"Differential signals" applied to v_{G1} and v_{G2}
(equal amplitude but opposite sign)

"Differential outputs" are produced
at v_{D1} and v_{D2}


Note in differential configuration,
 V_{GS} is fixed for both Q_1 and Q_2

$$I_{D1} = I_{D2} = \frac{I}{2} \leftarrow = \frac{I_B}{2}$$

$$\frac{I}{2} = \frac{k_n}{2} (V_{GS} - V_{Tn})^2 = \mu C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$V_{GS} = V_{Tn} + \sqrt{\frac{I}{k_n}}$$

 Large Signal Behavior of Diff Mode Operation



$$v_{id} = v_{in+} - v_{in-} = \left(V_{Tn} + \sqrt{\frac{I_1}{k_n}} \right) - \left(V_{Tn} + \sqrt{\frac{I_2}{k_n}} \right)$$


$$v_{id} = \sqrt{\frac{I_1}{k_n}} - \sqrt{\frac{I_2}{k_n}} = \sqrt{\frac{I/2 + \Delta i/2}{k_n}} - \sqrt{\frac{I/2 - \Delta i/2}{k_n}}$$

$\Delta i = i_{D1} - i_{D2}$
solve

$$\Delta i = k_n v_{id} \sqrt{\frac{2I}{k_n} - v_{id}^2}$$


$$v_{id} \leq \sqrt{\frac{I}{k_n}}$$

 $I_1 = \frac{I}{2} + \frac{\Delta i}{2}$
 $I_2 = \frac{I}{2} - \frac{\Delta i}{2}$



v_{id} small enough
that Δi
is linear


Small Signal Modeling: Step 1

 

■ Small signal analysis assumes linearity

- Impact of M_4 on amplifier is to simply present its drain impedance to the diff pair transistors (M_1 and M_2)
- Impact of V_{in+} and V_{in-} can be evaluated separately and then added (i.e., superposition)
 - By symmetry, we need only determine impact of V_{in+}
 - Calculation of V_{in-} impact directly follows


Method 1: Use Small Signal Model

 

- Analysis follows easily, but there is a simpler way!


Method 2: Differential Amplifier Analysis

"diff amp"

 

- Partition input signals into common-mode and differential components
- By superposition, we can add the results to determine the overall impact of the input signals


Differential Analysis

 

Key observations

- Inputs are equal in magnitude but opposite in sign to each other
- By linearity and symmetry, i_{s1} must equal $-i_{s2}$
 - This implies i_R is zero, so that voltage drop across r_{o4} is zero
 - The sources of M_1 and M_2 are therefore at incremental ground and decoupled from each other!
- Analysis can now be done on identical "half-circuits"

Find Differential Gain

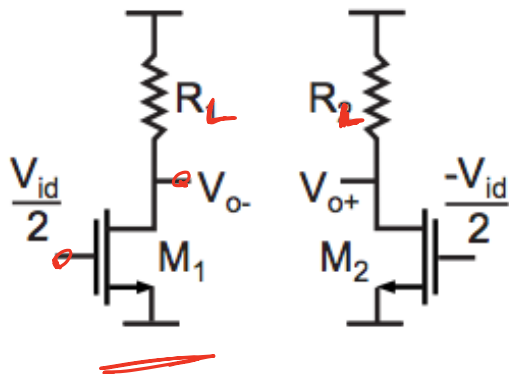

$$g_{m1} = g_{m2}$$

$$r_{o1} = r_{o2}$$

$$\frac{V_{o-}}{\frac{V_{id}}{2}} = -g_{m1}(r_{o1} \parallel R_L)$$

$$\frac{V_{o-}}{\frac{V_{id}}{2}} = -g_m(r_o \parallel R_L)$$

$$\frac{V_{o+}}{-\frac{V_{id}}{2}} = -g_{m2}(r_{o2} \parallel R_L)$$


$$\frac{V_{o+}}{-\frac{V_{id}}{2}} = -g_m(r_o \parallel R_L)$$

$$\frac{V_{od}}{V_{id}} = \frac{V_{o+}}{V_{id}} - \frac{V_{o-}}{V_{id}}$$

$$= -\frac{1}{2} g_m(r_o \parallel R_L) - \left(-\frac{1}{2} g_m(r_o \parallel R_L) \right)$$

$$= -g_m(r_o \parallel R_L)$$


Common Mode Analysis

 

■ Key observations

- Inputs are equal to each other
- By linearity and symmetry, i_{s1} must equal i_{s2}
 - This implies $i_R = 2i_{s1} = 2i_{s2}$
- We can view r_{o4} as two parallel resistors that have equal current running through them
- Analysis can also be done on two identical half-circuits

Common Mode Analysis

 

Common-Source
with degeneration


$$\frac{v_{o-}}{v_{ic}} = \frac{v_{o+}}{v_{ic}} = \frac{-R_L}{1/g_m + 2r_{o4}} = \frac{-g_m R_L}{1 + 2g_m r_{o4}}$$

Since $2r_{o4} \gg 1/g_m$,

$$\frac{v_{o-}}{v_{ic}} = \frac{v_{o+}}{v_{ic}} \approx \frac{-R_L}{2r_{o4}}$$

$$v_{od} = v_{o+} - v_{o-} = 0$$

Useful Metric for Diff Amps: CMRR

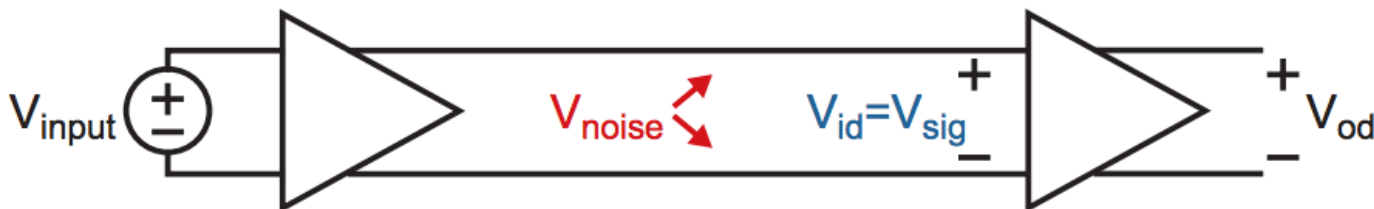

■ Common Mode Rejection Ratio (CMRR)

- Define: a_{vd} : differential gain, a_{vc} : common mode gain


$$\text{CMRR} = \left(\frac{a_{vd}}{a_{vc}} \right)$$

- CMRR corresponds to ratio of differential to common mode gain and is related to received signal-to-noise ratio

$$V_{od} = a_{vd} V_{sig} + a_{vc} V_{noise}$$

$$\Rightarrow \frac{\text{Signal}}{\text{Noise}} = \left(\frac{a_{vd}}{a_{vc}} \right) \left(\frac{V_{sig}}{V_{noise}} \right) = \text{CMRR} \left(\frac{V_{sig}}{V_{noise}} \right)$$

Current-Source Loads


 


Q_3 and Q_4 are
PMOS current sources

From half-circuit:

$$A_d = \frac{v_{od}}{v_{id}} = -g_{m1} (r_{o1} \parallel r_{o3})$$

Cascode Differential Amplifier

  

Cascode configurations for both amplifying transistors and current source loads.

From half-circuit

$$A_d = \frac{v_{od}}{v_{id}} = g_{m1} (R_{on} \parallel R_{op})$$

$$R_{on} = (g_{m3} r_{o3}) r_{o1}$$


$$R_{op} = (g_{m5} r_{o5}) r_{o7}$$

If all transistors are identical,

$$R_{on} = R_{op} = g_m r_o^2$$

$$A_d = \frac{1}{2} g_m^2 r_o^2$$

Common Mode Voltage Range

 

- **While keeping all devices in saturation:**
 - **What is the maximum common mode output range?**
 - Assume $V_{id} = 0$
 - **What is the maximum common mode input range?**
 - Assume $V_{od} = 0$