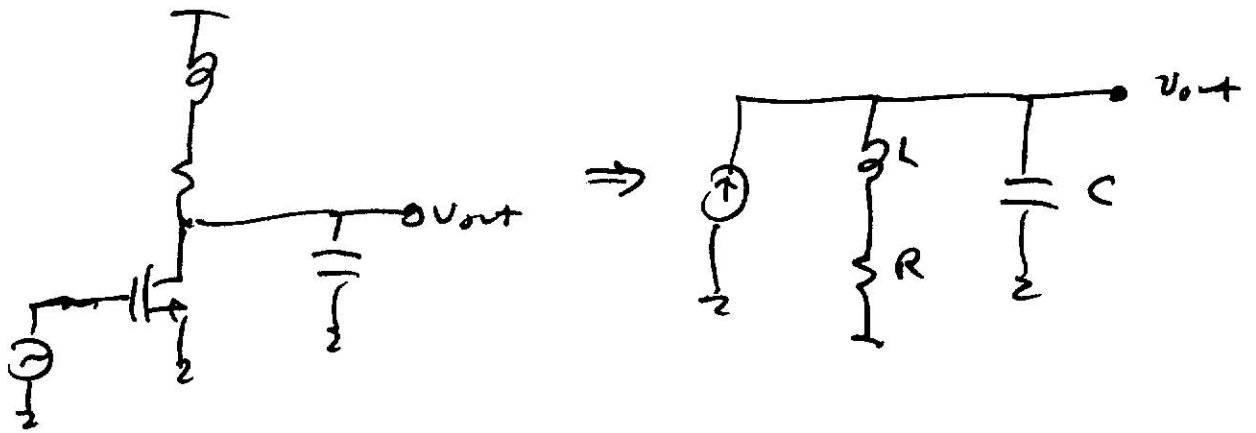


LECTURE 24

SHUNT-PEAKED AMPLIFIER



$$Z(s) = (sL + R) \parallel \frac{1}{sC} = \frac{R(sL/R + 1)}{s^2 LC + sRC + 1}$$

$$Z(j\omega) = R \sqrt{\frac{(\omega L/R)^2 + 1}{(1 - \omega^2 LC)^2 + (\omega RC)^2}}$$

$$m \equiv \frac{RC}{L/R}$$

$$Z(s) = \frac{R(Ts + 1)}{s^2 T^2 m + sTm + 1}$$

$$\left| \frac{Z(j\omega)}{R} \right| = \sqrt{\frac{(\omega T)^2 + 1}{(1 - \omega^2 T^2 m)^2 + (\omega Tm)^2}}$$

(SOLVE QUADRATIC = $\frac{1}{\sqrt{2}}$

$$\frac{\omega}{\omega_1} = \sqrt{\left(-\frac{m^2}{2} + m + 1\right) + \sqrt{\left(-\frac{m^2}{2} + m + 1\right)^2 + m^2}}$$

~~$\omega = \omega_1$~~

$$\omega\tau = 1$$

$$Z'(\omega_1) = \frac{2}{\sqrt{(1-m)^2 + m^2}}$$

$$Z(\omega_0) = \frac{1}{\sqrt{2}} Z(0) = \frac{R}{\sqrt{2}}$$

~~$\frac{1}{\sqrt{2}}$~~

$$\frac{1}{2} = \frac{(\omega\tau)^2 + 1}{(1 - \omega^2\tau^2 m)^2 + (\omega\tau m)^2}$$

$$(1 - \omega^2\tau^2 m)^2 + (\omega\tau m)^2 = 2(\omega\tau)^2 + 2$$

~~$2\omega^4\tau^4 m^2 + \omega^2$~~

$$0 = 1 - 2\omega^2\tau^2 m + \omega^4\tau^4 m^2 + (\omega\tau m)^2 - 2(\omega\tau)^2 - 2$$

$$x = \omega\tau$$

$$1 - 2x^2 m + x^4 m^2 + x^2 m^2 - 2x^2 - 2 = 0$$

$$x^4 m^2 + x^2 (m^2 - 2m - 2) - 1 = 0$$

$$x^2 = \frac{(-m^2 - 2m - 2) \pm \sqrt{(m^2 - 2m - 2)^2 + 4m^2}}{2}$$

$$\text{MAX BW} \quad m = \sqrt{2} = 1.41$$

1.85 x BW ENHANCEMENT!

↘ 20% PEAKING

$$\text{COMPROMISE} \quad \frac{\omega_2}{\omega_1} = \sqrt{1 + \sqrt{5}} = 1.8$$

$m = 2$

3% PEAKING

$$\text{NO PEAKING} \quad m = 1 + \sqrt{2} \approx 2.41$$

LINEAR PHASE DELAY (EQUAL TIME DELAY)

$$T_D = -\frac{d\phi}{d\omega}$$


$$m = 1 + \left(\frac{3+\sqrt{5}}{2}\right)^{1/3} + \left(\frac{3-\sqrt{5}}{2}\right)^{1/3} \approx 3.10$$

ACTIVE FILTER CMOS LNA

CONSIDER THE INPUT IMPEDANCE OF THE INDUCTIVELY DEGENERATED LNA:

IGNORE C_{gd} :
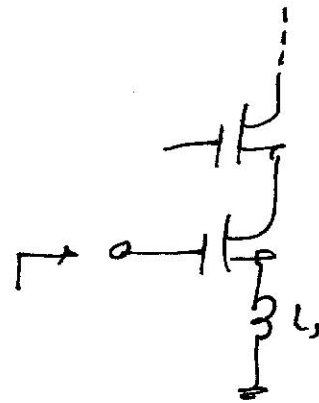
$$Z_1 = \begin{pmatrix} R_G + \frac{1}{j\omega C_{gs}} & 0 \\ \frac{-g_m r_{oll} \frac{1}{j\omega C_{gs}}}{j\omega C_{gs}} & r_{oll} \frac{1}{j\omega C_{gs}} \end{pmatrix}$$



$$Z_2 = j\omega L_s \begin{pmatrix} 1 & 1 \\ 1 & 1 \end{pmatrix}$$

$$Z'_{in} = Z_1 + Z_2$$

$$Z'_{in} = j\omega L_s + \frac{1}{j\omega C_{gs}} + R_G$$


$$Z_{in} = j\omega L_s + \frac{1}{j\omega C_{gs}} + R_G - \frac{(j\omega L_s) \left(\frac{-g_m r_{oll} \frac{1}{j\omega C_{gs}}}{j\omega C_{gs}} \right)}{r_{oll} \frac{1}{j\omega C_{gs}} + R_L}$$

$$\approx j\omega L_s + \frac{1}{j\omega C_{gs}} + R_G + \omega L_s \left(\frac{g_m}{C_{gs}} \right) \underbrace{\frac{r_{oll} \frac{1}{j\omega C_{gs}}}{r_{oll} \frac{1}{j\omega C_{gs}} + R_L}}_{\approx 1}$$

$$\text{Re}(Z_{in}) = R_G + \omega_T L_s = R'$$


$$\text{Im}(Z_{in}) = j\omega L_s + \frac{1}{j\omega C_{gs}}$$

EQ CIRCUIT IS A SERIES RLC CIRCUIT

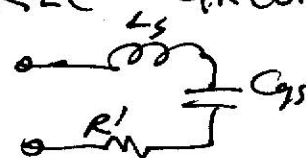


BUT INPUT RESONANCE IS NOT AT FREQ ω_0 .
 THE Q IS ALSO NOT UNDER OUR CONTROL ...

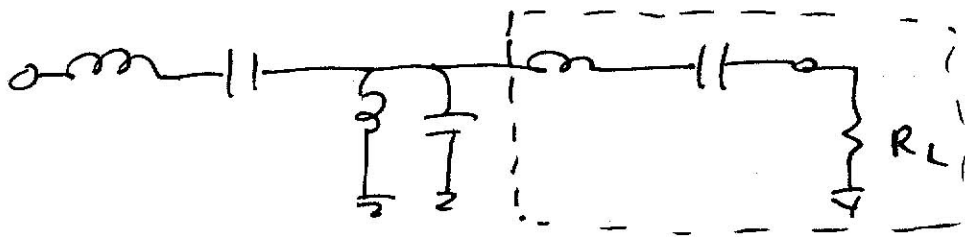OBSERVATION: A FILTER (BANDPASS) LOOKS LIKE



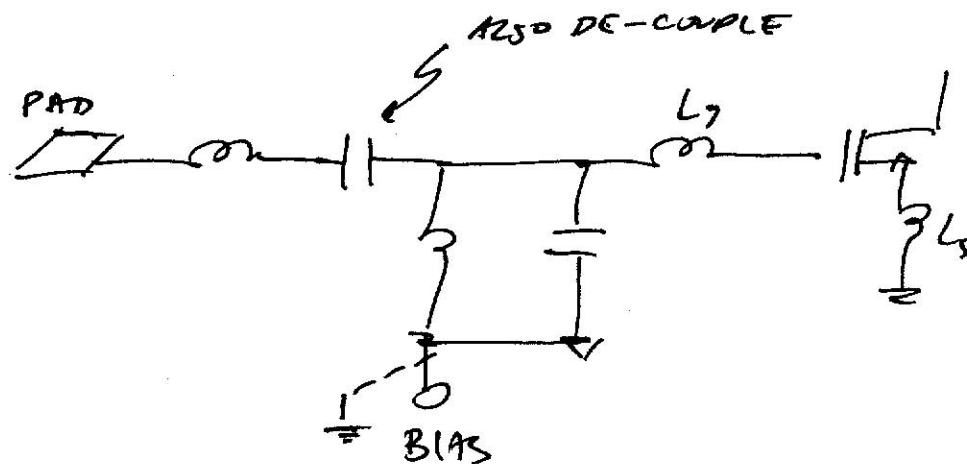WE CAN ABSORB THE AMPLIFIER INPUT INTO THE FILTER



CHEBYCHEV FILTER: RIPPLE GIVEN BY S_p

$$|\Gamma|^2 = 1 - \frac{1}{S_p}$$

CHOOSE RIPPLE SMALL ENOUGH TO MEET INPUT SPECS

$$|\Gamma| < -10 \text{ dB} \Rightarrow S_p < 0.46 \text{ dB}$$

GAIN

$$\frac{v_o}{v_{in}} = - \frac{g_m W(s)}{s C_{gs} R_s} \times Z_L(s)$$

$$Z_{in} = \frac{R_s}{W(s)}$$

W(S) CHEBYCHEV FILTER
TRANSFER FUNC

$$|W(s)| \approx 1 \quad \text{IN BAND}$$


$$|W(s)| \approx 0 \quad \text{OUT OF BAND}$$

$$i_{in} = \frac{v_{in} W(s)}{R_s}$$

$$\beta = \frac{g_m}{s C_{gs}} \quad \text{(CURRENT GAIN)}$$

USE A SHUNT-PEAKED LOAD TO EXTEND BW
& COMPENSATE FOR CURRENT GAIN ROLL-OFF
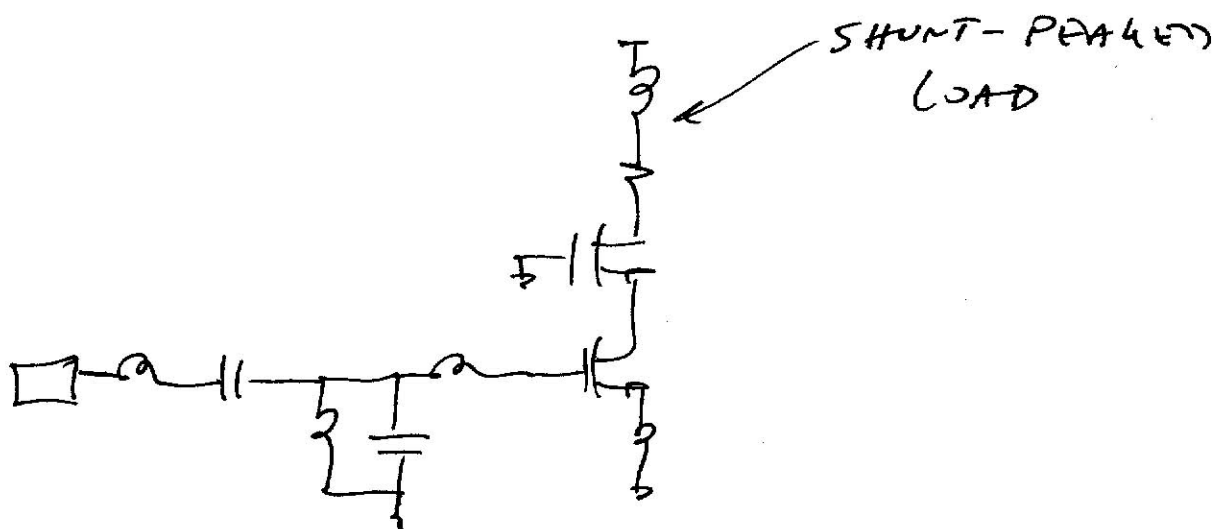
$$Z_L(s) = \frac{R_L (1 + s L_L / R_L)}{1 + s R_L C_{out} + s^2 L_L C_{out}}$$



NOISE ANALYSIS

EQUIV INPUT GENERATORS: $i_n = i_{ng} + \frac{j\omega C_{gs}}{g_m} i_{nd}$

$$e_n = j\omega L_s i_{ng} + (1 - \omega^2 C_{gs} L_s) \frac{i_{nd}}{g_m}$$

$$\approx \frac{i_{nd}}{g_m} + j\omega L_s i_{ng}$$

$$\overline{i_{ng}^2} = 4kT\delta \frac{\omega^2 C_{gs}^2}{5g_{d0}}$$

$$\overline{i_{nd}^2} = 4kT\delta g_{d0}$$

⇒ STANDARD ANALYSIS ...

$$R_{opt} = \sqrt{\frac{R_u}{G_n} + R_c^2} = \sqrt{\frac{R_u}{G_n}}$$

$$= \frac{p\alpha\chi\sqrt{1-|c|^2}}{\omega C_{gs}(1+2|c|p\alpha\chi+p^2\alpha^2\chi^2)}$$

$$X_{opt} = -X_c$$

$$Z_c = jX_c = \frac{1 - \omega^2 L_s C_{gs}}{j\omega C_{gs}} \frac{1 + 2|c|p\alpha\chi + p^2\alpha^2\chi^2}{1 + |c|p\alpha\chi} \frac{1 + 2|c|p\alpha\chi + p^2\alpha^2\chi^2}{1 + |c|p\alpha\chi}$$

$$p = \frac{C_{gs}}{C_t}$$



$p=1$ IN THIS CASE

$$\chi = \sqrt{\delta/5\delta}$$


$$c = \frac{\langle i_{ng} i_{nd} \rangle}{\sqrt{\overline{i_{ng}^2} \overline{i_{nd}^2}}} \approx 0.4j$$

$$\alpha = \frac{g_m}{g_{d0}}$$

DESIGN EXAMPLE 3-10 GHz LNA

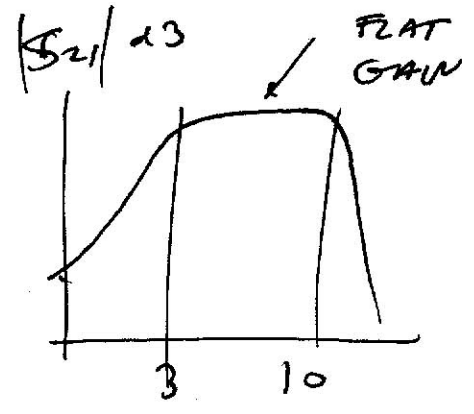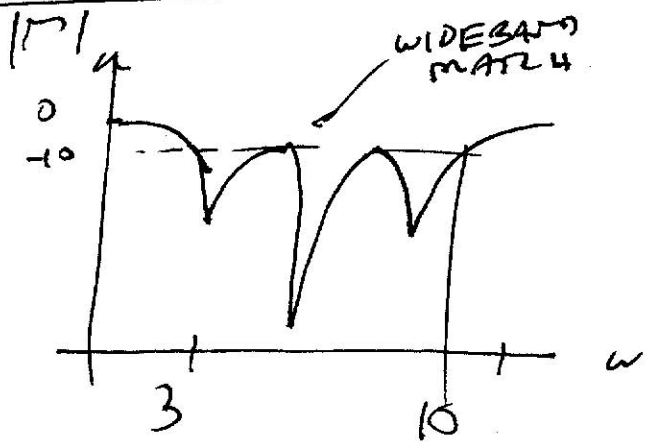


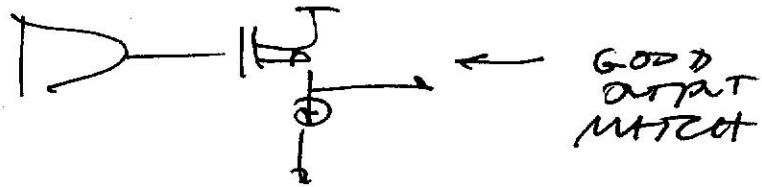COMPLETE AMP CAN DRIVE MIXER INPUT DIRECTLY OR A REAL LOAD THRU A BUFFER



CAN SHOW THAT NEARLY OPTIMUM NOISE PERF CAN BE ACHIEVED WITH A POWER MATCH.

NOISE IN SHUNT FB AMP

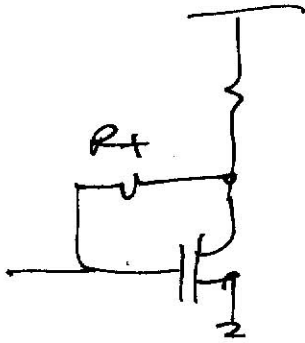

$$Y_{FET} \approx \begin{pmatrix} j\omega C_{gs} & 0 \\ g_m & j\omega C_{cs} \end{pmatrix}$$

$$Y_f = \begin{pmatrix} G_f & -G_f \\ -G_f & G_f \end{pmatrix}$$

$$Y_{in} = Y_{11} - \frac{Y_{12}Y_{21}}{Y_{22} + Y_L}$$

$$= G_f + j\omega C_{gs} - \frac{-G_f \cdot (g_m - G_f)}{j\omega C_{cs} + G_f + G_L}$$

$$= G_f + j\omega C_{gs} + \frac{G_f (g_m - G_f)}{j\omega C_{cs} + G_f + G_L}$$

$$\text{Re}\{Y_{in}(\text{LOW FREQ})\} = G_f + \frac{G_f (g_m - G_f)}{G_f + G_L}$$

$$\approx \cancel{G_f} + \frac{\cancel{G_f} g_m}{\cancel{G_f}} - \frac{\cancel{G_f}^2}{\cancel{G_f}} \approx g_m$$

→ LOW FREQ

→ HIGH LOAD IMPEDANCE (BUFFER)

WANT $|G_f + G_L| \gg |\jmath \omega C_{ds}| = \omega(C_{ds} + C_L)$


$$\omega < \frac{G_f + G_L}{C_{ds} + C_L} \approx \frac{1}{R_f(C_{ds} + C_L)}$$

SAY $\omega_0 = 10 \text{ GHz} \cdot 2\pi \Rightarrow R_f \approx \frac{1}{\omega_0 G_f}$
 $C_{ds} + C_L \approx 50 \text{ f}$

$$R_f < \frac{1}{2\pi \times 10 \times 10^9 \times 50 \times 10^{-15}}$$

$$= \frac{1}{\cancel{2\pi} \cdot 10^{12} \cdot 10^{-15} \cdot \cancel{5}} \approx \frac{10^3}{\pi} \approx 300 \Omega$$

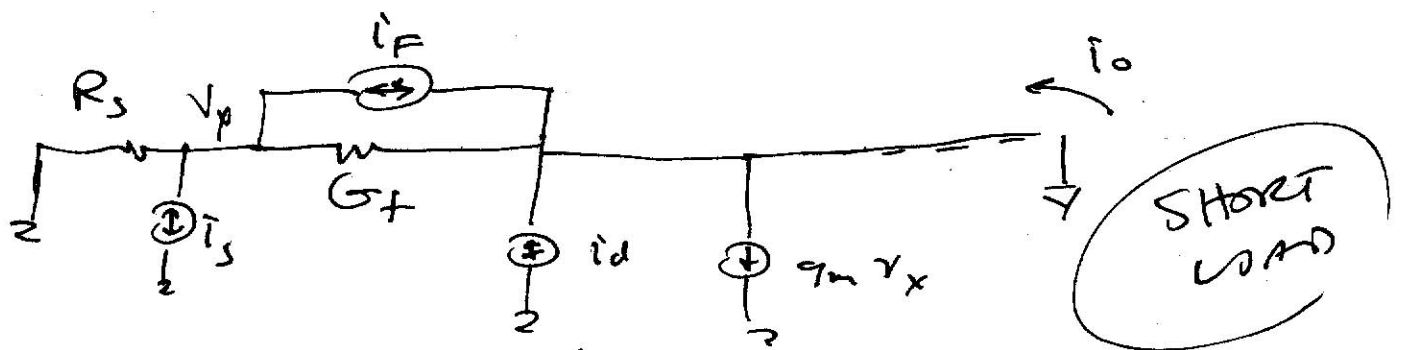
WHAT ABOUT NOISE? CONSIDER ONLY DRAIN NOISE



$$i_o = g_m v_x + i_d + i_F + i_s \frac{G_f}{G_f + G_s}$$

~~$$v_x = i_s \frac{G_s}{G_s + G_f} R_s$$~~
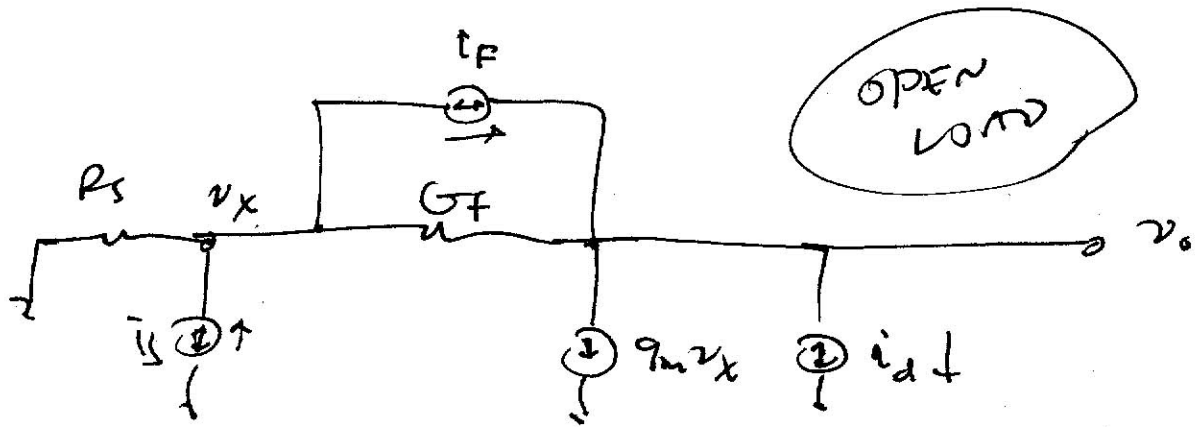
$$\frac{v_x}{R_s} + i_s + i_F + \frac{v_x}{R_f} = 0$$



$$(v_o - v_x) G_f + g_m v_x + i_d - i_F = 0$$

$$v_x G_s + i_F + (v_x - v_o) G_f - i_s = 0$$

$$v_x (G_s + G_f) = v_o G_f + i_s - i_F$$

$$v_o G_f + (g_m - G_f) v_x = i_F - i_d$$

$$v_o G_f + \frac{(g_m - G_f)}{G_s + G_f} (v_o G_f + i_s - i_F) = i_F - i_d$$

$$v_o G_f \left(1 + \frac{g_m - G_f}{G_s + G_f} \right) = i_F \left(1 + \frac{g_m - G_f}{G_s + G_f} \right) - i_d$$

$$- i_s \frac{(g_m - G_f)}{G_s + G_f}$$

$$v_o G_f (G_s + g_m) = i_F (g_m + G_s) - i_s (g_m - G_f) - i_d (G_s + G_f)$$

$$v_o = i_P R_F - i_S R_F \frac{g_m - G_f}{g_m + G_S} - i_d R_F \frac{(G_S + G_f)}{G_S + g_m}$$

$$\overline{v_o^2} = R_F^2 \overline{i_P^2} + R_F^2 \frac{(g_m - G_f)^2}{(g_m + G_S)^2} \overline{i_S^2} + R_F^2 \frac{(G_S + G_f)^2}{(G_S + g_m)^2} \overline{i_d^2}$$

$$F = 1 + \frac{G_f}{G_S} \left(\frac{g_m + G_S}{g_m - G_f} \right)^2 + \frac{\delta g_{d0}}{G_S} \left(\frac{G_S + G_f}{g_m - G_f} \right)^2$$

$$\approx 1 + \frac{R_S}{R_F} \frac{4g_m^2}{g_m^2} + \frac{\delta}{\alpha} (g_m R_S) \frac{g_m^2}{g_m^2}$$

$$g_m R_S = 1$$

$$G_S \gg G_f$$

$$F = 1 + \frac{\delta}{\alpha} + \frac{R_S}{R_F} \times 4$$

$$= 1 + \frac{\delta}{\alpha} + \frac{1}{g_m R_F} \times 4$$

$$g_m R_F = 4$$

$$F = 2 + \delta/\alpha$$

HIGH

3AD

$g_m R_F \gg 1$
OK

BIPOLAR AMP =
 $I_C = 10 \text{ mA}$

$$g_m = \frac{I_C}{V_T}$$

$$\frac{1}{g_m} = 2.5 \Omega$$


$$R_F = 250 \Omega$$

$$\frac{1}{g_m} = 25 \Omega / (\text{mA})$$

SHUNT

NOISE IN BROADBAND^Y FEEDBACK AMP

CONSIDER DRAIN NOISE:

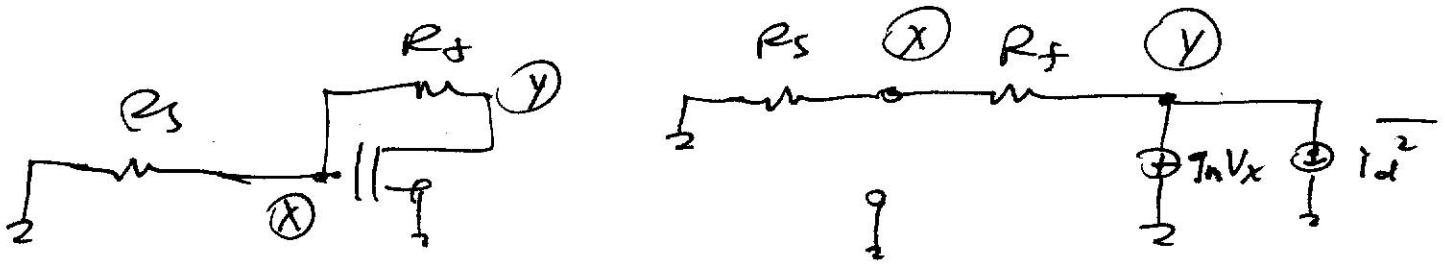

IGNORE ALL CAPS

$$V_x = V_y \frac{R_s}{R_s + R_d}$$


KCL AT (Y): $i_d + g_m V_x + \frac{V_y}{R_s + R_d} = 0$

OR $i_d = g_m V_x + \frac{1}{R_s} V_x$

$$V_x = \frac{R_s}{1 + g_m R_s} i_d$$

$$V_y = \frac{R_s + R_d}{1 + g_m R_s} i_d$$

THE NOISE ON NODE X & Y IS CORRELATED!

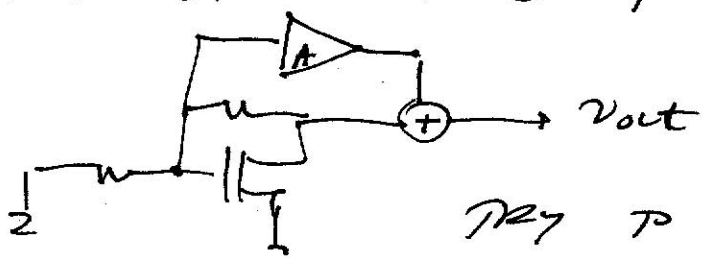

TRY TO CANCEL NOISE OUT!

$$-A v_x = v_y \Rightarrow -R_s A = R_s + R_f$$


$$A = - \left(1 + \frac{R_f}{R_s} \right)$$

WHAT ABOUT SIGNAL? DRAIN VOLTAGE IS 180° OUT OF PHASE SO SIGNALS ADD

$$v_y^{sig} = v_x (A_1 + A)$$

(OR) AMP

OR AMP :

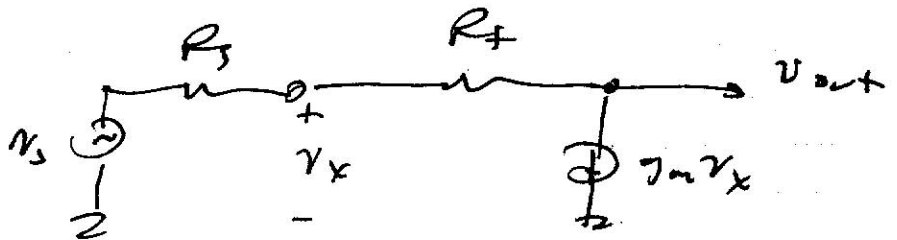

$$g_m v_x + \frac{v_{out} - v_s}{R_s + R_f} = 0$$

MATCH $v_x = \frac{1}{2} v_s$

$$\frac{g_m}{2} v_s + \frac{v_{out} - v_s}{R_s + R_f} = 0$$

$$v_{out} - v_s + \frac{g_m}{2} (R_s + R_f) v_s = 0$$

$$\frac{v_{out}}{v_s} = 1 + \frac{g_m}{2} (R_s + R_f)$$

GENERAL CASE:

$$\frac{V_x - V_S}{R_S} + \frac{V_x - V_{out}}{R_f} = 0$$

$$(V_x - V_S) R_f + (V_x - V_{out}) R_S = 0$$

$$V_x (R_f + R_S) = V_S R_f + V_{out} R_S$$

$$V_x = V_S \frac{R_f}{R_f + R_S} + V_{out} \frac{R_S}{R_f + R_S}$$

$$g_m V_S \frac{R_f}{R_f + R_S} + g_m V_{out} \frac{R_S}{R_f + R_S} + \frac{V_{out} - V_S}{R_f + R_S} = 0$$


$$(g_m R_f - 1) V_S = -(1 + g_m R_S) V_{out}$$

$$\frac{V_{out}}{V_S} = - \frac{g_m R_f - 1}{1 + g_m R_S} = \frac{1 - g_m R_f}{1 + g_m R_S}$$

$$g_m R_S = 1$$

$$\frac{V_{out}}{V_S} = \frac{1 - g_m R_f}{2}$$

COMPLETE AMP

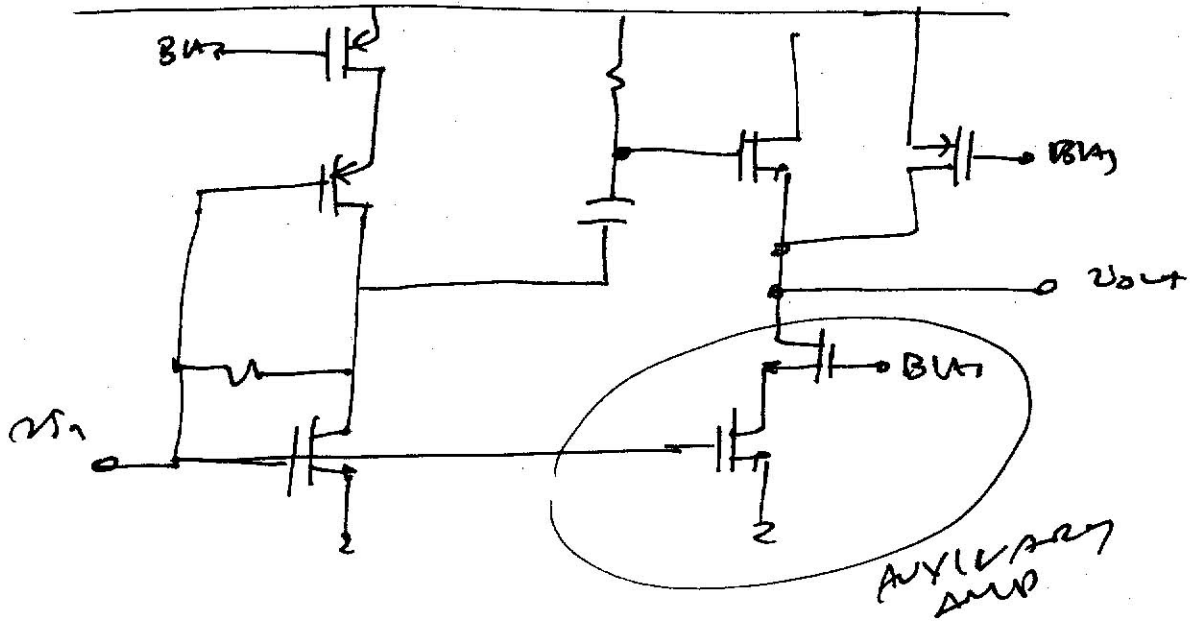

DESIGN AUX AMP FOR LOW NOISE
DESIGN MAIN AMP FOR MATCH