

# EECS 217

## *Lecture 4: Distributed Resonant Circuits*

Prof. Niknejad

University of California, Berkeley

# Open Line I/V

- The open transmission line has infinite VSWR and  $\rho_L = 1$ . At any given point along the transmission line

$$v(z) = V^+(e^{-j\beta z} + e^{j\beta z}) = 2V^+ \cos(\beta z)$$

whereas the current is given by

$$i(z) = \frac{V^+}{Z_0}(e^{-j\beta z} - e^{j\beta z})$$

or

$$i(z) = \frac{-2jV^+}{Z_0} \sin(\beta z)$$

# Open Line Impedance (I)


- The impedance at any point along the line takes on a simple form

$$Z_{in}(-\ell) = \frac{v(-\ell)}{i(-\ell)} = -jZ_0 \cot(\beta\ell)$$

- This is a special case of the more general transmission line equation with  $Z_L = \infty$ .
- Note that the impedance is purely imaginary since an open lossless transmission line cannot dissipate any power.
- We have learned, though, that the line stores reactive energy in a distributed fashion.
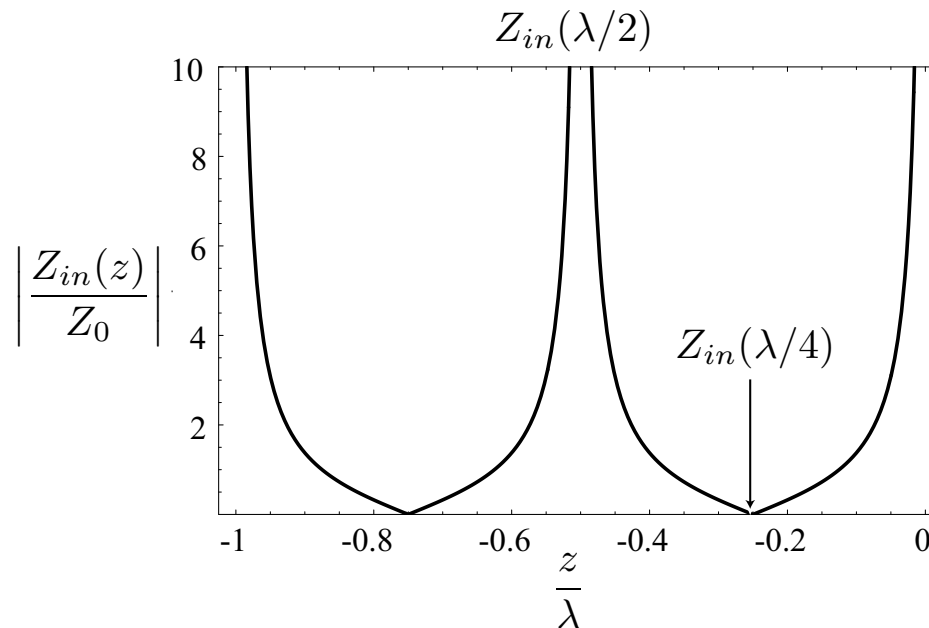
# Open Line Impedance (II)


- A plot of the input impedance as a function of  $z$  is shown below



- The cotangent function takes on zero values when  $\beta\ell$  approaches  $\pi/2$  modulo  $2\pi$

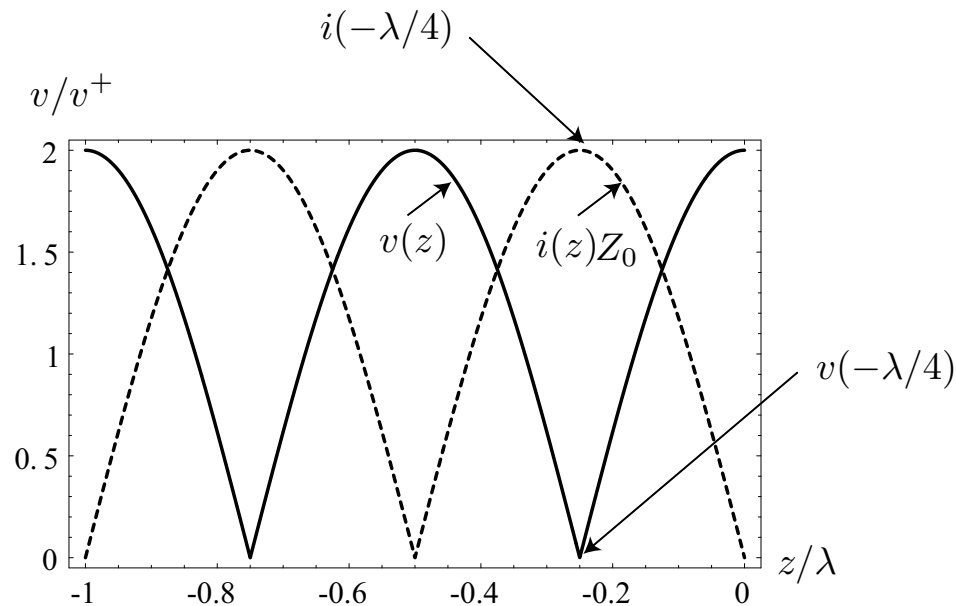
# Open Line Impedance (III)

- Open transmission line can have zero input impedance!
- This is particularly surprising since the short load is in effect transformed from an open.
- A plot of the voltage/current as a function of  $z$  is shown below.


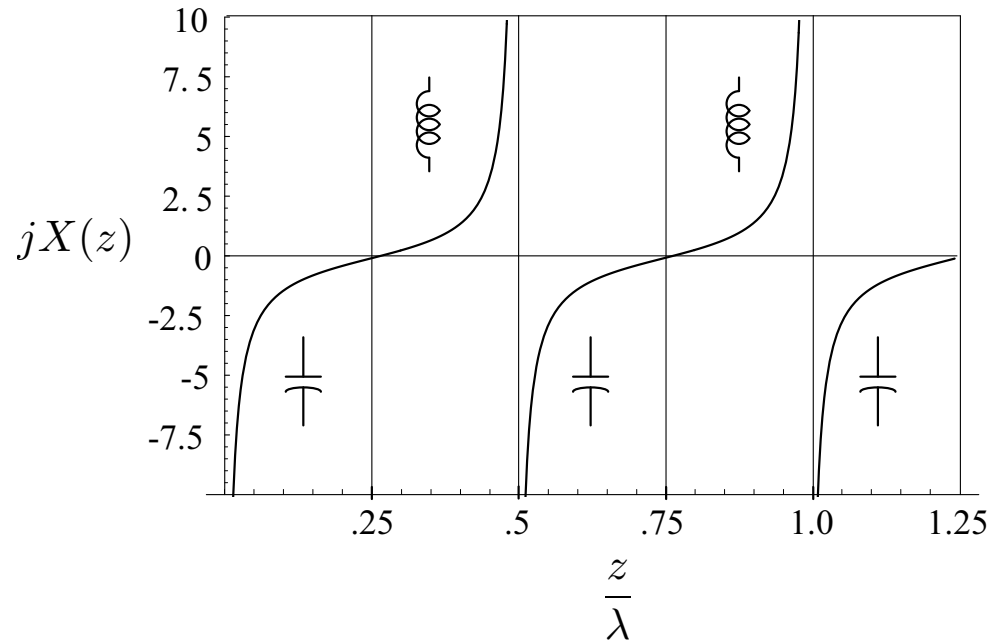
# Open Line Reactance

- $l \ll \lambda/4 \rightarrow$  capacitor
- $l < \lambda/4 \rightarrow$  capacitive reactance
- $l = \lambda/4 \rightarrow$  short (acts like resonant series LC circuit)
- $l > \lambda/4$  but  $l < \lambda/2 \rightarrow$  inductive reactance
- And the process repeats ...



# $\lambda/2$ Transmission Line

- Plug into the general T-line equation for any multiple of  $\lambda/2$

$$Z_{in}(-m\lambda/2) = Z_0 \frac{Z_L + jZ_0 \tan(-\beta\lambda/2)}{Z_0 + jZ_L \tan(-\beta\lambda/2)}$$

- $\beta\lambda m/2 = \frac{2\pi}{\lambda} \frac{\lambda m}{2} = \pi m$

- $\tan m\pi = 0$  if  $m \in \mathcal{Z}$

- $Z_{in}(-\lambda m/2) = Z_0 \frac{Z_L}{Z_0} = Z_L$


- Impedance does not change ... it's periodic about  $\lambda/2$  (not  $\lambda$ )

# $\lambda/4$ Transmission Line

- Plug into the general T-line equation for any multiple of  $\lambda/4$
- $\beta\lambda m/4 = \frac{2\pi}{\lambda} \frac{\lambda m}{4} = \frac{\pi}{2}m$
- $\tan m\frac{\pi}{2} = \infty$  if  $m$  is an odd integer
- $Z_{in}(-\lambda m/4) = \frac{Z_0^2}{Z_L}$
- $\lambda/4$  line transforms or “inverts” the impedance of the load



# $\lambda/4$ Impedance Match

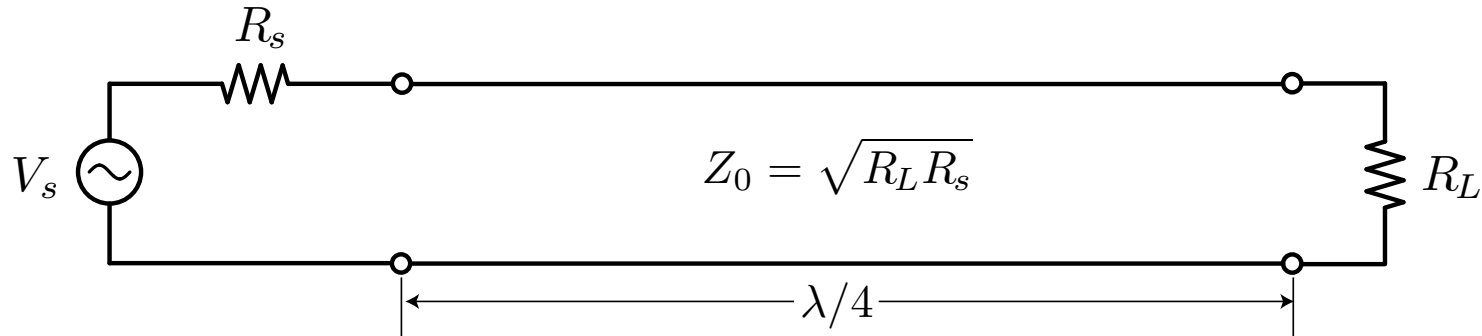

- If the source and load are real resistors, then a quarter-wave line can be used to match the source and load impedances
- Recall that the impedance looking into the quarter-wave line is the “inverse” of the load impedance

$$Z_{in}(z = -\lambda/4) = \frac{Z_0^2}{Z_L}$$

# SWR on $\lambda/4$ Line

- In this case, therefore, we equate this to the desired source impedance  $Z_{in} = \frac{Z_0^2}{R_L} = R_s$
- The quarter-wave line should therefore have a characteristic impedance that is the geometric mean  $Z_0 = \sqrt{R_s R_L}$

- Since  $Z_0 \neq R_L$ , the line has a non-zero reflection coefficient

$$SWR = \frac{R_L - \sqrt{R_L R_s}}{R_L + \sqrt{R_L R_s}}$$

- It also therefore has standing waves on the T-line
- The non-unity SWR is given by  $\frac{1+|\rho_L|}{1-|\rho_L|}$

# Interpretation of SWR on $\lambda/4$ Line

- Consider a generic lossless transformer ( $R_L > R_s$ )
- Thus to make the load look smaller to match to the source, the voltage of the source should be increased in magnitude
- But since the transformer is lossless, the current will likewise decrease in magnitude by the same factor
- With the  $\lambda/4$  transformer, the location of the voltage minimum to maximum is  $\lambda/4$  from load (since the load is real)
- Voltage/current is thus increased/decreased by a factor of  $1 + |\rho_L|$  at the load
- Hence the impedance decreased by a factor of  $(1 + |\rho_L|)^2$

# Lossy Transmission Line Attenuation

- The power delivered into the line at a point  $z$  is now non-constant and decaying exponentially

$$P_{av}(z) = \frac{1}{2} \Re (v(z)i(z)^*) = \frac{|v^+|^2}{2|Z_0|^2} e^{-2\alpha z} \Re (Z_0)$$

- For instance, if  $\alpha = .01\text{m}^{-1}$ , then a transmission line of length  $\ell = 10\text{m}$  will attenuate the signal by  $10 \log(e^{2\alpha\ell})$  or 2 dB. At  $\ell = 100\text{m}$  will attenuate the signal by  $10 \log(e^{2\alpha\ell})$  or 20 dB.

# Lossy Transmission Line Impedance

- Using the same methods to calculate the impedance for the low-loss line, we arrive at the following line voltage/current

$$v(z) = v^+ e^{-\gamma z} (1 + \rho_L e^{2\gamma z}) = v^+ e^{-\gamma z} (1 + \rho_L(z))$$

$$i(z) = \frac{v^+}{Z_0} e^{-\gamma z} (1 - \rho_L(z))$$

- Where  $\rho_L(z)$  is the complex reflection coefficient at position  $z$  and the load reflection coefficient is unaltered from before
- The input impedance is therefore

$$Z_{in}(z) = Z_0 \frac{e^{-\gamma z} + \rho_L e^{\gamma z}}{e^{-\gamma z} - \rho_L e^{\gamma z}}$$

# Lossy T-Line Impedance (cont)

- Substituting the value of  $\rho_L$  we arrive at a similar equation (now a hyperbolic tangent)

$$Z_{in}(-\ell) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma\ell)}{Z_0 + Z_L \tanh(\gamma\ell)}$$

- For a short line, if  $\gamma\delta\ell \ll 1$ , we may safely assume that

$$Z_{in}(-\delta\ell) = Z_0 \tanh(\gamma\delta\ell) \approx Z_0 \gamma \delta\ell$$

- Recall that  $Z_0 \gamma = \sqrt{Z'/Y'} \sqrt{Z'Y'}$
- As expected, input impedance is therefore the series impedance of the line (where  $R = R'\delta\ell$  and  $L = L'\delta\ell$ )

$$Z_{in}(-\delta\ell) = Z'\delta\ell = R + j\omega L$$

# Low Loss Line

- For a low loss line,  $\omega L' \gg R'$  and  $\omega C' \gg G'$ , so the prop. constant can be simplified

$$\gamma = \sqrt{(j\omega L' + R')(j\omega C' + G')}$$

$$\gamma = \sqrt{(j\omega)^2 L' C' \left( 1 - j \left( \frac{R'}{\omega L'} + \frac{G'}{\omega C'} \right) + \frac{R' G'}{(j\omega)^2 L' C'} \right)}$$

- Dropping the last term and using  $\sqrt{1+x} \approx 1 + \frac{1}{2}x$  for small  $x$

$$\gamma = \sqrt{(j\omega)^2 L' C' \left( 1 - j \frac{1}{2} \left( \frac{R'}{\omega L'} + \frac{G'}{\omega C'} \right) \right)}$$

# Low Loss Line (cont)

- Using the fact that  $Z_0 \approx \sqrt{L'/C'}$

$$\gamma = \alpha + j\beta = \frac{1}{2} \left( \frac{R'}{Z_0} + G'Z_0 \right) + j\omega\sqrt{L'C'}$$

- The low loss line is therefore dispersionless since  $\alpha$  is independent of frequency and  $\beta \propto \omega$ .
- The imaginary part of  $\gamma$  is identical to a lossless line, and thus the phase relationship is the same as the lossless case (quarter wavelength on a lossy line is the same length as on a lossless line)
- For all practical purposes, then, the low loss line behaves like a lossless line except the wave attenuates by  $e^{-\alpha z}$



# Dispersionless Line

- To find the conditions for the transmission line to be dispersionless in terms of the  $R$ ,  $L$ ,  $C$ ,  $G$ , expand

$$\begin{aligned}\gamma &= \sqrt{(j\omega L' + R')(j\omega C' + G')} \\ &= \sqrt{(j\omega)^2 LC \left(1 + \frac{R}{j\omega L} + \frac{G}{j\omega C} + \frac{RG}{(j\omega)^2 LC}\right)} \\ &= \sqrt{(j\omega)^2 LC} \sqrt{\square}\end{aligned}$$

- Suppose that  $R/L = G/C$  and simplify the  $\square$  term

$$\square = 1 + \frac{2R}{j\omega L} + \frac{R^2}{(j\omega)^2 L^2}$$

# Dispersionless Line (II)

- For  $R/L = G/C$  the propagation constant simplifies


$$\square = \left(1 + \frac{R}{j\omega L}\right)^2 \quad \gamma = -j\omega\sqrt{LC} \left(1 + \frac{R}{j\omega L}\right)$$

- Breaking  $\gamma$  into real and imaginary components

$$\gamma = R\sqrt{\frac{C}{L}} - j\omega\sqrt{LC} = \alpha + j\beta$$

- The attenuation constant  $\alpha$  is independent of frequency.  
For low loss lines,  $\alpha \approx -\frac{R}{Z_0}$  ✓
- The propagation constant  $\beta$  is a linear function of frequency ✓

# Example: IC Resistor

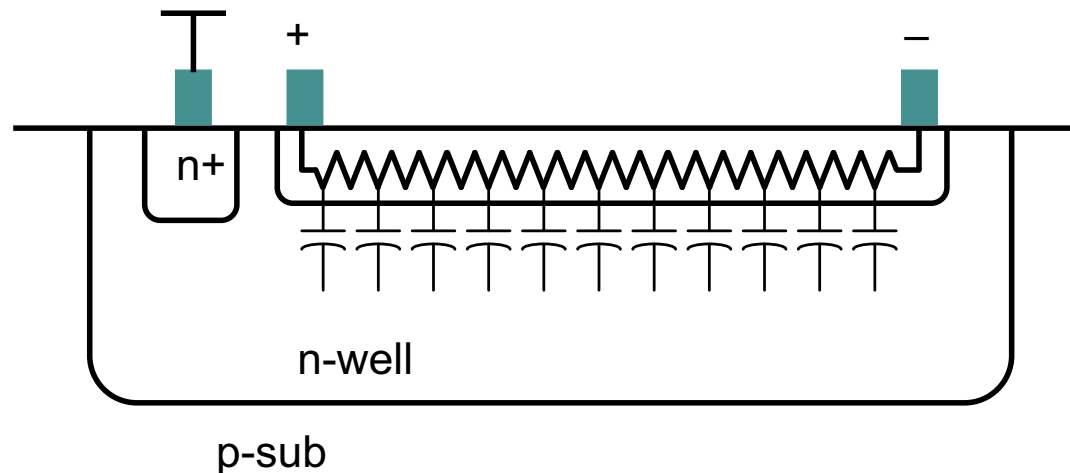

- The IC resistor shown above is common. A reverse biased diffusion resistor has capacitance to substrate arising from the reverse biased junction.
- A thin film resistor has capacitance to substrate due to its close proximity.
- For simplicity, assume the substrate is a perfect ground.

# Telegrapher's Equations

- The series impedance per unit length is predominantly resistive. For all frequencies of interest,  $\omega L' \ll R'$

$$Z' = j\omega L' + R' \approx R'$$

- Assuming the conductance per unit is capacitive,  $Y' = j\omega C'$ , the propagation constant is given by

$$\gamma = \sqrt{j\omega C' R'}$$

- which has a phase of  $45^\circ$ . Likewise, the characteristic impedance is given by

$$Z_0 = \sqrt{\frac{Z'}{Y'}} = \sqrt{j\omega C' R'}$$

# Resistor Sizing

- The optimal size of the resistor can be analyzed by noting that  $R' = R_{\square}/W$  and  $C' = W\epsilon/t_{dep}$  ( $t_{dep}$  = depletion region depth). Let  $C_x = \epsilon_{si}/t_{dep}$ . Then

$$\gamma = \sqrt{jR_{\square}\omega C_x}$$

- which is independent of the width  $W$ . The impedance, though, drops with  $W$

$$Z_0 = \frac{1}{W} \sqrt{\frac{R_{\square}}{j\omega C_x}}$$

# Resistance versus W


- For a shorted resistor, the input impedance is given by

$$Z_{in} = Z_0 \tanh \gamma \ell = \frac{1}{W} \sqrt{\frac{R_{\square}}{j\omega C_x}} \tanh \left( \sqrt{j R_{\square} \omega C_x} \ell \right)$$

- For a given desired resistance  $\frac{\ell}{W} R_{\square} = R_0$ , we can substitute for  $\ell$

$$Z_{in} = Z_0 \tanh \gamma \ell = \frac{1}{W} \sqrt{\frac{R_{\square}}{j\omega C_x}} \tanh \left( \sqrt{j R_{\square} \omega C_x} \frac{R_0}{R_{\square}} W \right)$$

# Plot of Input Impedance

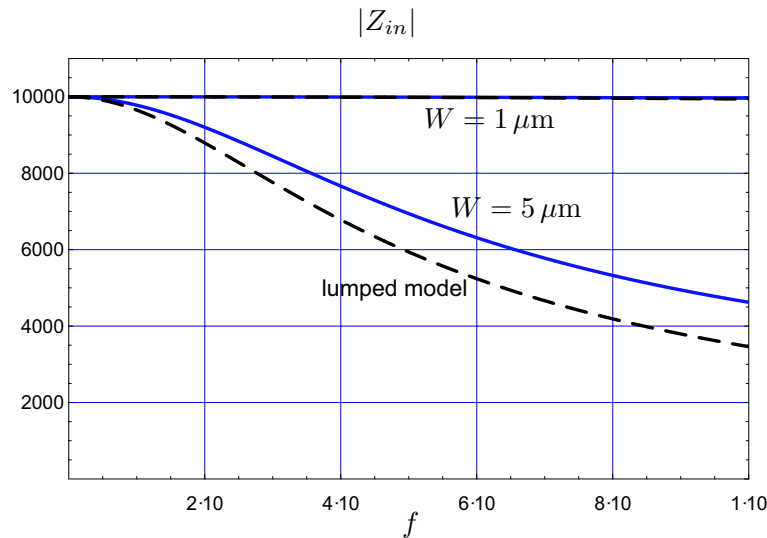


- The plot of  $|Z_{in}|$  for a nominally  $10\text{ k}\Omega$  resistor versus frequency is shown above.
- Say that for a thin film resistor has  $R_{\square} = 100\ \Omega/\square$  and

$$C_x = \epsilon_{\text{SiO}_2}/t_0 = 3.45 \times 10^{-5}\ \text{F}/\text{m}^2$$

- The  $W = 1\ \mu\text{m}$  resistor has a relatively flat frequency response up to 1 GHz, whereas the  $W = 5\ \mu\text{m}$  resistor rolls off quickly and is about half of its nominal size at 1 GHz.

# Impedance versus $W$

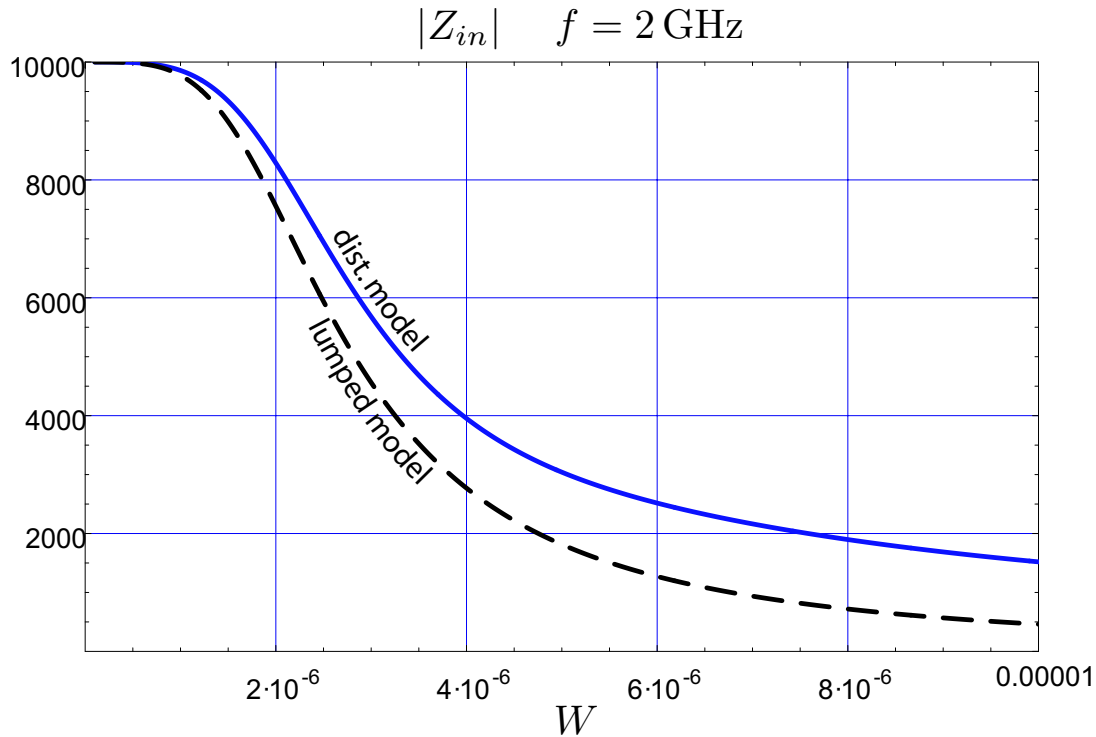

- The variation of the impedance magnitude versus  $W$  is shown above. Larger  $W$  resistors have better precision and matching, but clearly the extra capacitance hurts at high frequency.



# Review of Resonance (I)

- We'd like to find the impedance of a series resonator

near resonance  $Z(\omega) = j\omega L + \frac{1}{j\omega C} + R$

- Recall the definition of the circuit  $Q$

$$Q = \omega_0 \frac{\text{time average energy stored}}{\text{energy lost per cycle}}$$

- For a series resonator,  $Q = \omega_0 L / R$ . For a small frequency shift from resonance  $\delta\omega \ll \omega_0$

$$Z(\omega_0 + \delta\omega) = j\omega_0 L + j\delta\omega L + \frac{1}{j\omega_0 C} \left( \frac{1}{1 + \frac{\delta\omega}{\omega_0}} \right) + R$$

# Review of Resonance (II)

- Which can be simplified using the fact that  $\omega_0 L = \frac{1}{\omega_0 C}$

$$Z(\omega_0 + \delta\omega) = j2\delta\omega L + R$$

- Using the definition of  $Q$

$$Z(\omega_0 + \delta\omega) = R \left( 1 + j2Q \frac{\delta\omega}{\omega_0} \right)$$

- For a parallel line, the same formula applies to the admittance

$$Y(\omega_0 + \delta\omega) = G \left( 1 + j2Q \frac{\delta\omega}{\omega_0} \right)$$

- Where  $Q = \omega_0 C / G$

# $\lambda/2$ T-Line Resonators (Series)

- A shorted transmission line of length  $\ell$  has input impedance of  $Z_{in} = Z_0 \tanh(\gamma\ell)$
- For a low-loss line,  $Z_0$  is almost real
- Expanding the  $\tanh$  term into real and imaginary parts

$$\tanh(\alpha\ell + j\beta\ell) = \frac{\sinh(2\alpha\ell)}{\cos(2\beta\ell) + \cosh(2\alpha\ell)} + \frac{j \sin(2\beta\ell)}{\cos(2\beta\ell) + \cosh(2\alpha\ell)}$$

- Since  $\lambda_0 f_0 = c$  and  $\ell = \lambda_0/2$  (near the resonant frequency), we have  
$$\beta\ell = 2\pi\ell/\lambda = 2\pi\ell f/c = \pi + 2\pi\delta f\ell/c = \pi + \pi\delta\omega/\omega_0$$
- If the lines are low loss, then  $\alpha\ell \ll 1$

# $\lambda/2$ Series Resonance

- Simplifying the above relation we come to

$$Z_{in} = Z_0 \left( \alpha \ell + j \frac{\pi \delta \omega}{\omega_0} \right)$$

- The above form for the input impedance of the series resonant T-line has the same form as that of the series *LRC* circuit
- We can define equivalent elements

$$R_{eq} = Z_0 \alpha \ell = Z_0 \alpha \lambda / 2$$

$$L_{eq} = \frac{\pi Z_0}{2\omega_0}$$

$$C_{eq} = \frac{2}{Z_0 \pi \omega_0}$$

# $\lambda/2$ Series Resonance $Q$

- The equivalent  $Q$  factor is given by

$$Q = \frac{1}{\omega_0 R_{eq} C_{eq}} = \frac{\pi}{\alpha \lambda_0} = \frac{\beta_0}{2\alpha}$$

- For a low-loss line, this  $Q$  factor can be made very large. A good T-line might have a  $Q$  of 1000 or 10,000 or more
- It's difficult to build a lumped circuit resonator with such a high  $Q$  factor

# $\lambda/4$ T-Line Resonators (Parallel)

- For a short-circuited  $\lambda/4$  line

$$Z_{in} = Z_0 \tanh(\alpha + j\beta)l = Z_0 \frac{\tanh \alpha l + j \tan \beta l}{1 + j \tan \beta l \tanh \alpha l}$$

- Multiply numerator and denominator by  $-j \cot \beta l$

$$Z_{in} = Z_0 \frac{1 - j \tanh \alpha l \cot \beta l}{\tanh \alpha l - j \cot \beta l}$$

- For  $l = \lambda/4$  at  $\omega = \omega_0$  and  $\omega = \omega_0 + \delta\omega$

$$\beta l = \frac{\omega_0 l}{v} + \frac{\delta\omega l}{v} = \frac{\pi}{2} + \frac{\pi\delta\omega}{2\omega_0}$$

# $\lambda/4$ T-Line Resonators (Parallel)

- So  $\cot \beta l = -\tan \frac{\pi \delta \omega}{2\omega_0} \approx \frac{-\pi \delta \omega}{2\omega_0}$  and  $\tanh \alpha l \approx \alpha l$

$$Z_{in} = Z_0 \frac{1 + j\alpha l \pi \delta \omega / 2\omega_0}{\alpha l + j\pi \delta \omega / 2\omega_0} \approx \frac{Z_0}{\alpha l + j\pi \delta \omega / 2\omega_0}$$

- This has the same form for a parallel resonant  $RLC$  circuit

$$Z_{in} = \frac{1}{1/R + 2j\delta\omega C}$$

- The equivalent circuit elements are

$$R_{eq} = \frac{Z_0}{\alpha l} \quad C_{eq} = \frac{\pi}{4\omega_0 Z_0} \quad L_{eq} = \frac{1}{\omega_0^2 C_{eq}}$$


# $\lambda/4$ T-Line Resonators Q Factor

- The quality factor is thus

$$Q = \omega_0 RC = \frac{\pi}{4\alpha l} = \frac{\beta}{2\alpha}$$



# T-Line-C Resonator Q Factor

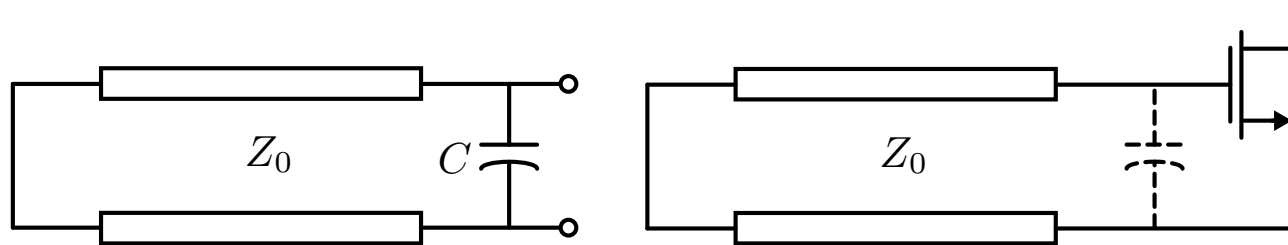

- Often transmission lines are used as resonant elements along with lumped elements.
- A good example, shown above, is a short section of transmission line resonating with the input capacitance of a transistor. For simplicity assume that the lumped input capacitance is lossless. What's the the  $Q$  factor of the resulting resonant circuit?

# Magnetic Energy Storage

- It's important to note that  $Q \neq \frac{1}{2}\beta/\alpha$  since this only applies to the transmission line in resonance, when the magnetic and electric energy are equal on the transmission line.
- In our case, we would like to use the transmission line as an inductor, so we will be concerned with the net magnetic energy on the line. The  $Q$  factor is therefore given by

$$Q = 2\omega_0 \frac{\text{net energy stored}}{\text{avg. power loss}} = \frac{2\omega_0(W_m - W_e)}{P_R + P_G}$$

- where  $W_m$  and  $W_e$  are the average magnetic and electric energy stored, and  $P_R$  represent the “series” resistive losses and  $P_G$  the “shunt” conductive losses.

# Inductive/Capacitive Q

- Defining the series inductive and shunt capacitive  $Q$  we have

$$Q_L = 2\omega_0 \frac{W_m}{P_R} \qquad Q_C = 2\omega_0 \frac{W_e}{P_G} \qquad \text{we}$$

can express the overall  $Q$  as

$$\frac{1}{Q} = \frac{1}{\eta_L Q_L} + \frac{1}{\eta_C Q_C}$$

$$\eta_L = 1 - \frac{W_e}{W_m} \qquad \eta_C = \frac{W_m}{W_e} - 1$$

# Magnetic/Electric Energy

- For a shorted transmission line, under the assumption of low loss, one can show that

$$W_m \approx \frac{1}{2} \frac{LV^{+2} \ell}{Z_0^2} \left( 1 + \operatorname{sinc} \left( \frac{4\pi \ell}{\lambda} \right) \right)$$



$$W_e \approx \frac{1}{2} CV^{+2} \ell \left( 1 - \operatorname{sinc} \left( \frac{4\pi \ell}{\lambda} \right) \right)$$

Thus we have

$$\frac{1}{\eta_L} = \frac{1}{2 \operatorname{sinc} \left( \frac{4\pi \ell}{\lambda} \right)} + \frac{1}{2}$$



$$\frac{1}{\eta_C} = \frac{1}{2 \operatorname{sinc} \left( \frac{4\pi \ell}{\lambda} \right)} - \frac{1}{2}$$

# “Shorted” T-Line

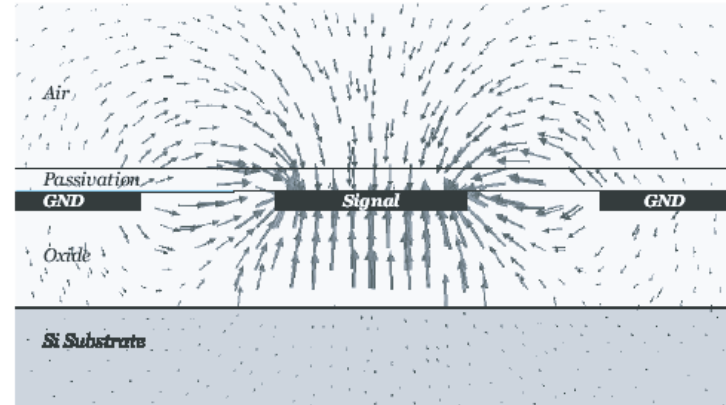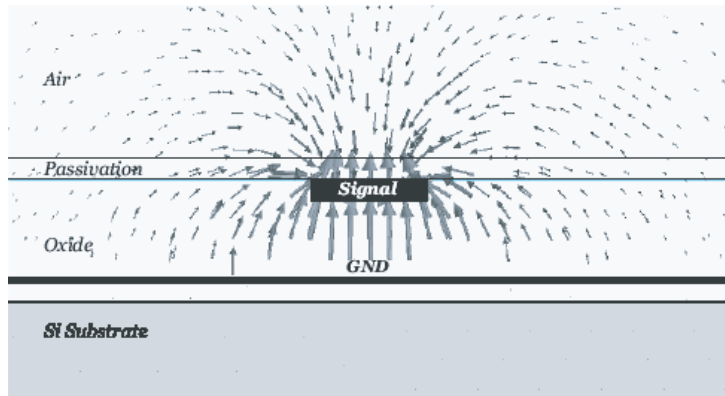

- For a shorted line, say  $\ell \ll \lambda$ , then  $\eta_C \gg \eta_L$ . For instance, if  $\ell < 0.1\lambda$ , then  $\eta_C > 7\eta_L$ . The net  $Q$  of such a resonant circuit is therefore  $Q \approx \eta_L Q_L$ .
- This explains why a Si coplanar line is preferred over a microstrip line in such an application.
- Due to the Si substrate losses, the resonant  $Q$  of the microstrip is higher. But the inductive  $Q_L$  of the coplanar line is higher since more magnetic energy can be stored per unit length.

# Co-Planar/Microstrip Tradeoff

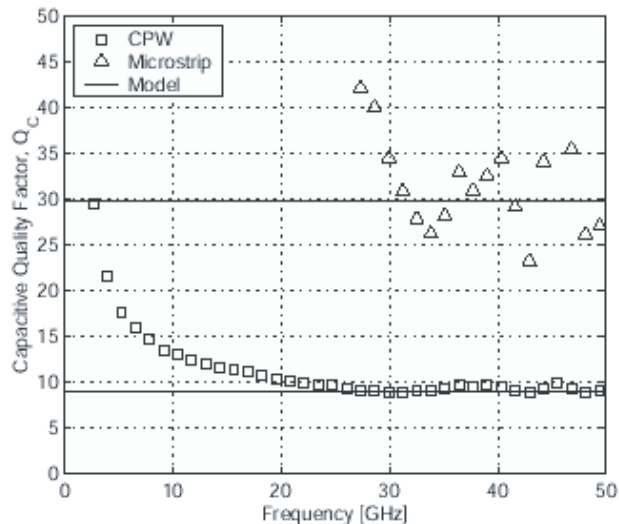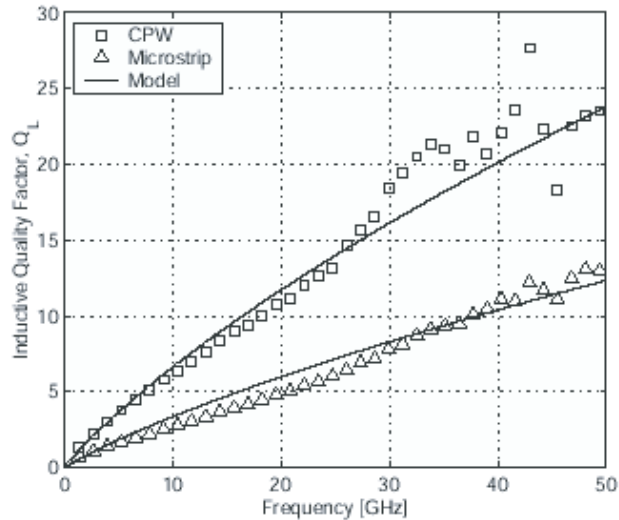

- Notice that the capacitive  $Q_C$  factor is larger for the microstrip, since most of the fields terminate on the M1 shield ground plane.
- The coplanar line, though, has electric fields that penetrate the substrate and cause loss due to the finite conductivity. This can be modeled as an effective frequency dependent dielectric loss.

# Co-planar/Microstrip Tradeoff (cont)

- The inductive  $Q_L$  is larger, though, since the width of the coplanar line can be made wider. The spacing predominately controls the impedance of the line.
- On the other hand, for a microstrip line, the spacing between the signal and ground is fixed, and thus the impedance can only be increased by reducing the conductor width.

For more details:

“Millimeter-Wave CMOS Design”

Doan, C.H.; Emami, S.; Niknejad, A.M.; Brodersen, R.W.,

*IEEE Journal of Solid-State Circuits*, Volume: 40 , Issue: 1 , Jan. 2005, Pages:144 - 155