

# **EECS 240**


# **Analog Integrated Circuits**

## **Topic 12: Settling Time**

**Ali M. Niknejad and Bernhard E. Boser**



**© 2006**

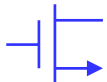**Department of Electrical Engineering and Computer Sciences**





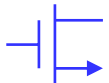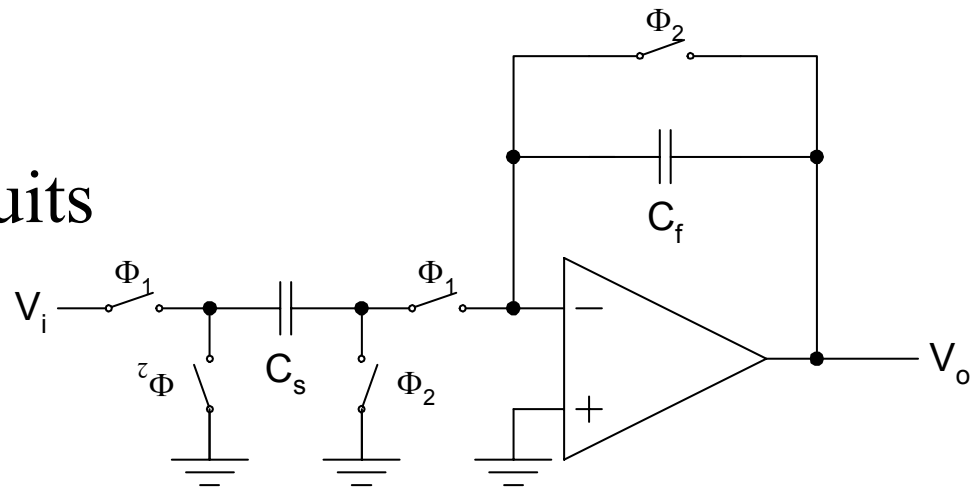
# Settling


- Speed/accuracy metrics
- Continuous time circuits
  - Bandwidth
  - Loop-gain, slew rate
    - distortion
- Switched capacitor circuits
  - Step response
  - Loop-gain
    - settling accuracy
  - Loop-bandwidth
    - settling time




# Step Response

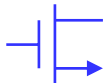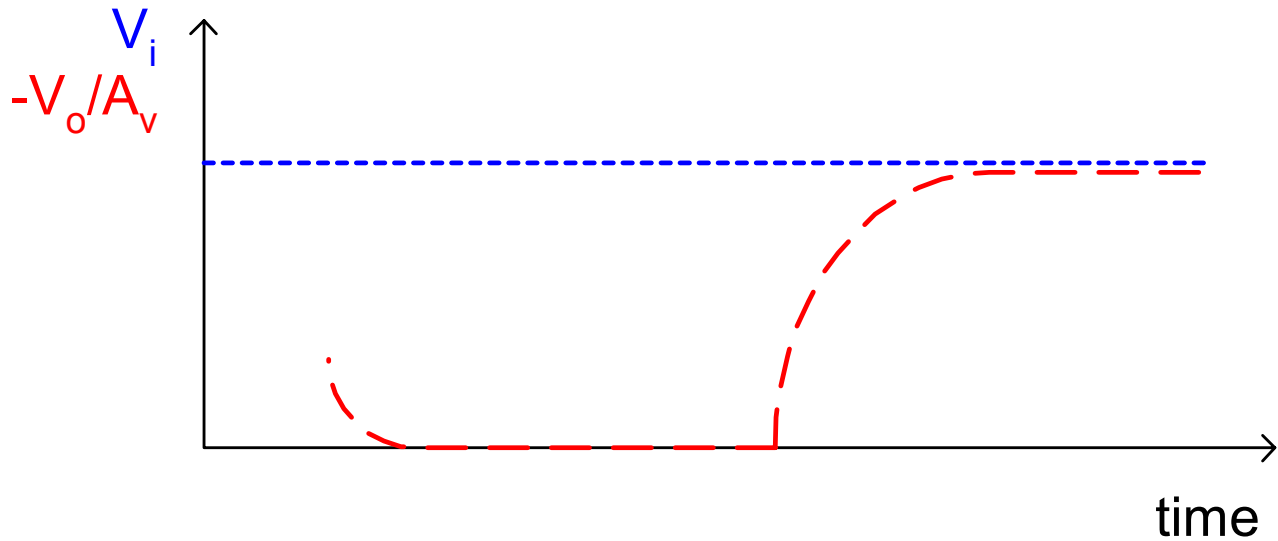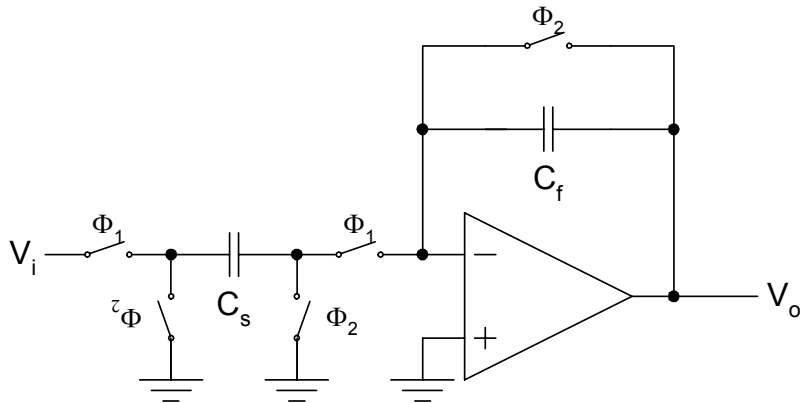


# Step Response Analysis

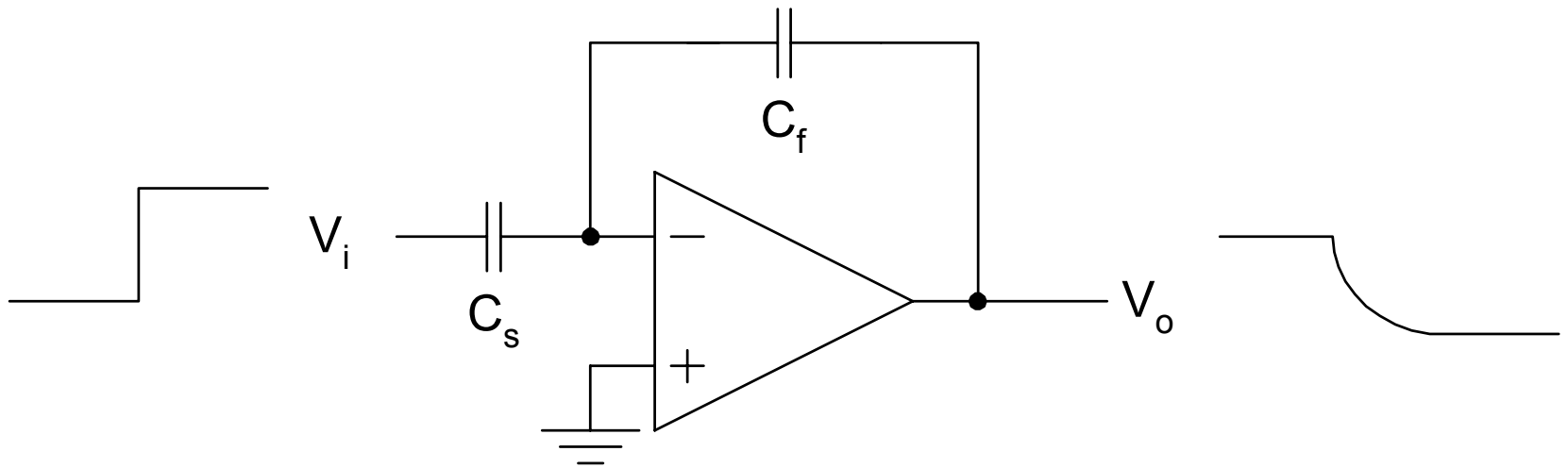

- Static error
- Dynamic error

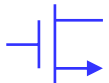

# Static Error

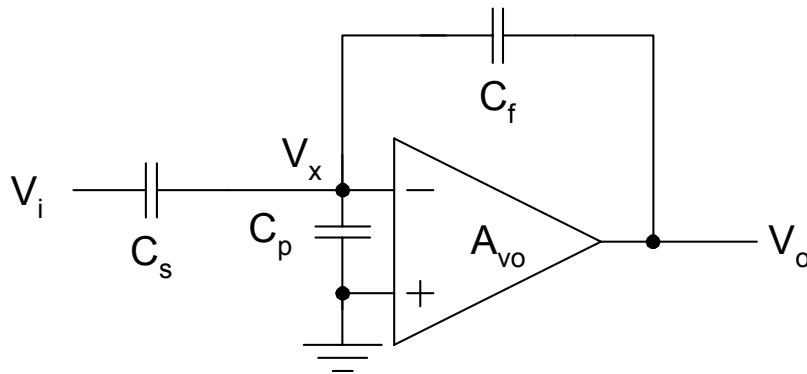

KCL  $\rightarrow$



$$\frac{V_o}{V_i} = - \frac{c}{1 + \underbrace{FA_{vo}}_{T_o}}$$

with

$$F = \frac{C_f}{C_f + C_s + C_p}$$

$$\frac{V_o}{V_x} = -A_{vo}$$

$$c = \frac{C_s}{C_f}$$

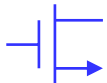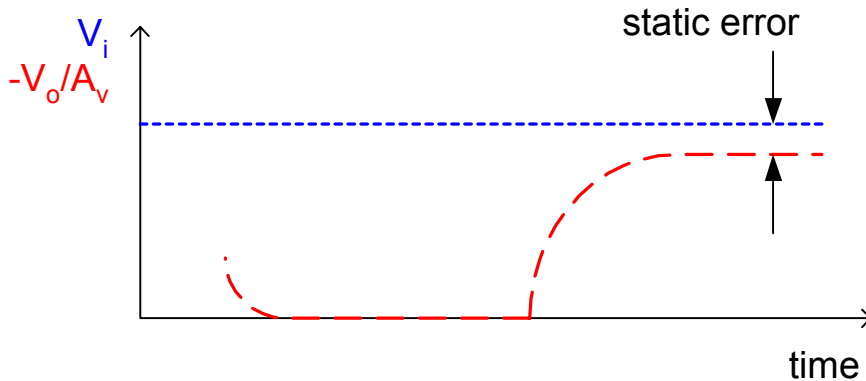

# Static Error (cont.)

## Example:

$$\frac{V_o}{V_i} = -\frac{c}{1 + \frac{1}{FA_{vo}}}$$
$$\cong -c \left( 1 - \frac{1}{\underbrace{FA_{vo}}_{\text{relative error}}} \right)$$

Closed loop gain:  $c = -4$


$C_f = 1\text{pF}$ ,  $C_s = 4\text{pF}$ ,  $C_p = 1\text{pF}$   
 $\rightarrow F = 1/6$  Note:  $C_p$  hurts!

Error specification:  $<0.1\%$

$\rightarrow FA_{vo} > 1000$


$\rightarrow \underline{A_{vo} \geq 6000}$  over output range

Beware: other (dynamic errors) add!

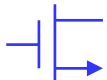

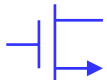
# Dynamic Errors

- Error sources
  - Finite bandwidth
  - Feedforward zero
  - Non-dominant poles
  - Doublets
  - Nonlinear effects: slewing
- Analysis approach
  - One error at a time!
  - In particular: treat static and dynamic errors separately
  - Final result: superposition of all individual errors



# Linear Settling

## Single Time Constant

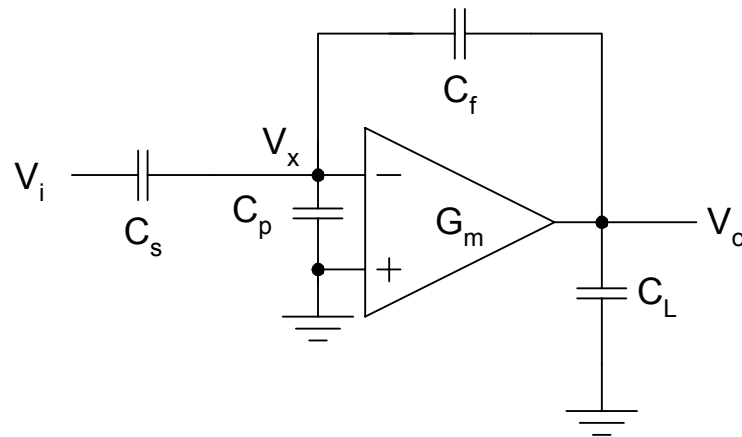


- Note:  $R_o$  irrelevant at frequencies of interest (and for  $T_o \gg 1$ )
- Solve KCL

$$v_x s C_T - v_o s C_f - v_i s C_s = 0$$

$$v_o s (C_f + C_L) - v_x s C_f + G_m v_x = 0$$
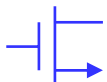
$$\frac{V_o}{V_i} = -c \frac{1 - s \frac{C_f}{G_m}}{1 + s \frac{C_L + (1 - F) C_f}{F G_m}}$$





# Linear Settling (cont.)

$$\frac{V_o}{V_i} = -c \frac{1 - s \frac{C_f}{G_m}}{1 + s \frac{C_L + (1 - F)C_f}{FG_m}}$$

$$= -c \frac{1 + \frac{s}{z}}{1 + \frac{s}{p}}$$

with

$$z = + \frac{G_m}{C_f}$$

$$p = - \frac{FG_m}{C_L + (1 - F)C_f}$$

- Loop bandwidth sets pole
- Feedforward through  $C_f$  contributes zero  
→ sets initial response



# Step Response

Frequency domain:

input step :

$$V_{i,step} = \frac{V_{step}}{s}$$

output step :

$$V_{o,step} = -c \frac{1 + \frac{s}{z}}{1 + \frac{s}{p}} V_{i,step}$$


$$= -c \frac{1 + \frac{s}{z}}{1 + \frac{s}{p}} \frac{V_{step}}{s}$$

Time domain:

(inverse Laplace transform)

$$v_{o,step}(t) = \underbrace{-V_{step}c}_{\text{ideal response}} \left[ 1 - \underbrace{\left( 1 - \frac{p}{z} \right)}_{\substack{\text{initial error} \\ \text{(feedforward)}}} e^{pt} \right]_{\text{exponentially decaying error}}$$

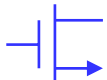Note: For  $p=z$  the error is zero and the circuit has infinite bandwidth.  
Applications?



# Step Response (cont.)


$$v_{o,step}(t) = \underbrace{-V_{step}c}_{\text{ideal response}} \left[ 1 - \left( 1 - \frac{p}{z} \right) e^{-t/\tau} \right]$$

with :

$$\tau = \frac{C_{Leff}}{FG_m}$$

$$\frac{p}{z} = -F \frac{C_f}{C_{Leff}}$$

$$C_{Leff} = C_L + (1 - F)C_f$$

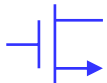

# Case 1: $-p/z \ll 1$

$$v_{o,step}(t) \cong \underbrace{-V_{step}c}_{\text{ideal response}} \left[ 1 - e^{-t/\tau} \right]$$

Relative settling error:

$$\varepsilon = \frac{v_o(t \rightarrow \infty) - v_o(t = t_s)}{v_o(t \rightarrow \infty)} = e^{-t_s/\tau}$$

$$\frac{t_s}{\tau} = -\ln \varepsilon$$

$\varepsilon$	$t_s/\tau$
0.01	4.6
0.001	6.9
$10^{-4}$	9.2
$10^{-5}$	11.5
$10^{-6}$	13.8

Example:

Specification :

$$c = 4$$

$$C_f = C_p = 1\text{pF}, \quad C_s = cC_f = 4\text{pF}, \quad C_L = 5\text{pF}$$

$$t_s = 10\text{ns} \quad \varepsilon = 10^{-3}$$

Solution :


$$F = 0.17$$

$$C_{Leff} = 5.83\text{pF}$$

$$\left| \frac{p}{z} \right| = F \frac{C_f}{C_{Leff}} = 0.03 \ll 1$$

$$\tau = \frac{10\text{ns}}{6.9} = 1.45\text{ns}$$
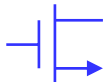
$$G_m = \frac{C_{Leff}}{F\tau} = \frac{5.83\text{pF}}{0.17 \times 1.45\text{ns}} = \underline{\underline{24\text{mS}}}$$



# Case 2: $-p/z$ not negligible

$$v_{o,step}(t) \cong \underbrace{-V_{step}c}_{\text{ideal response}} \left[ 1 - \left( 1 - \frac{p}{z} \right) e^{-t/\tau} \right]$$

Example:

Specification :

$$c = 0.25$$

$$C_f = 1\text{pF}, \quad C_s = cC_f = 250\text{fF}, \quad C_p = 250\text{fF}, \quad C_L = 1\text{pF}$$

$$t_s = 10\text{ns} \quad \varepsilon = 10^{-3}$$

Relative settling error:

$$\varepsilon = \frac{v_o(t \rightarrow \infty) - v_o(t = t_s)}{v_o(t \rightarrow \infty)} = \left( 1 - \frac{p}{z} \right) e^{-t_s/\tau}$$

$$\frac{t_s}{\tau} = -\ln \left( \frac{\varepsilon}{1 + F \frac{C_f}{C_{Leff}}} \right)$$


Solution :

$$F = 0.67$$

$$C_{Leff} = 1.3\text{pF}$$

$$\frac{t_s}{\tau} = -\ln \left( \frac{10^{-3}}{1 + 0.67 \times 0.77} \right) = 7.3$$
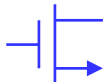
$$\begin{aligned} \frac{v_o(t = 0^+)}{V_{step}c} &= -\frac{p}{z} \\ &= F \frac{C_f}{C_{Leff}} = 0.52 \end{aligned}$$



# Non-Dominant Pole

- Ignore feed-forward zero for simplicity (homework?)

$$H(s) = \frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m}}$$

- Model for non-dominant pole

$$G_m(s) = \frac{G_{mo}}{1 - \frac{s}{p_2}}$$


$$p_2 = -K\omega_u$$

$\omega_u$  is unity gain bandwidth of  $T(s)$

- Step response



$$V_{o,step}(s) = H(s) \frac{V_{in,step}}{s}$$
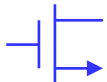
$$v_{o,step}(t) = L^{-1}\{V_{o,step}(s)\} \\ = \dots$$





# Non-Dominant Pole (cont.)

Step response: 
$$v_s(t, K) = -\frac{v_{o,step}(t)|_{\tau=1}}{cV_{in,step}}$$

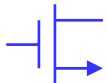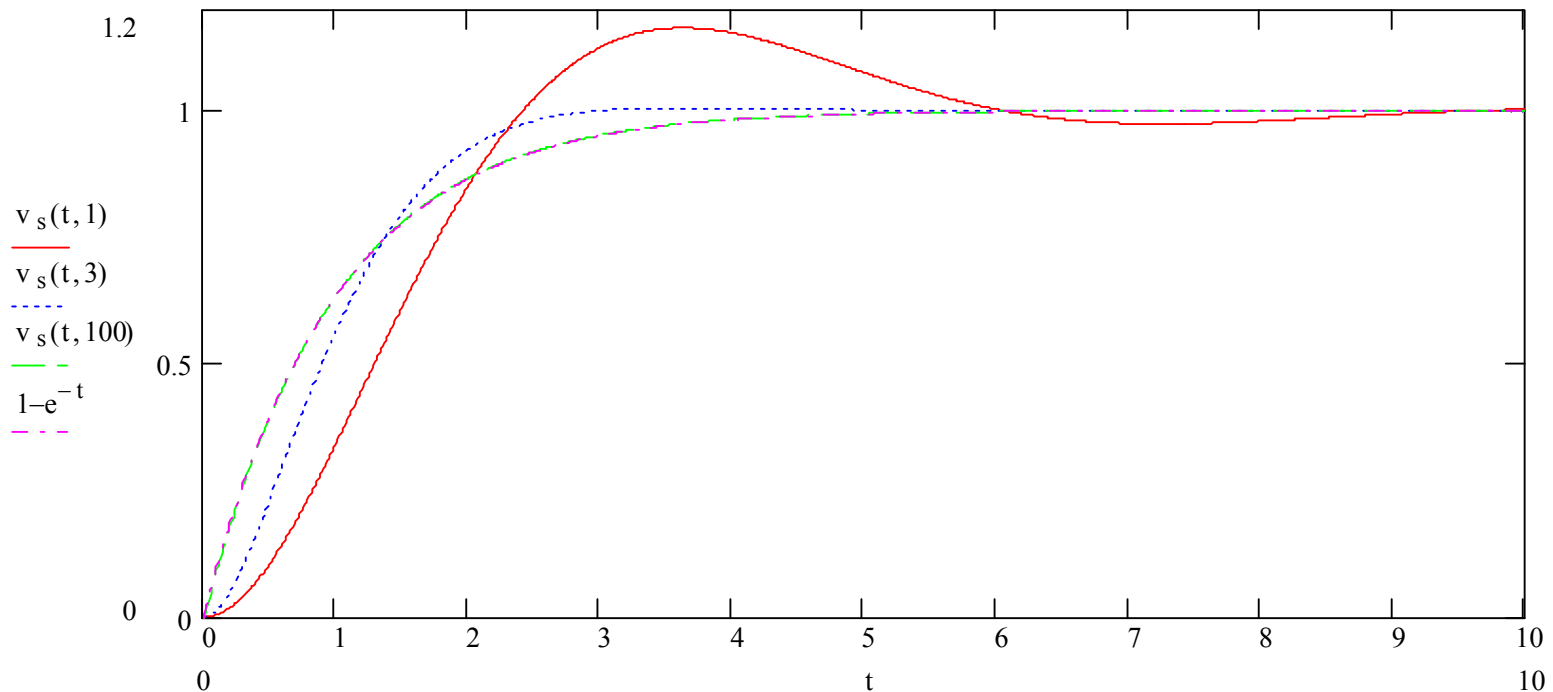

# Non-Dominant Pole (cont.)


Relative error :  $\varepsilon = |1 - v_s(t, K)|$

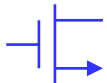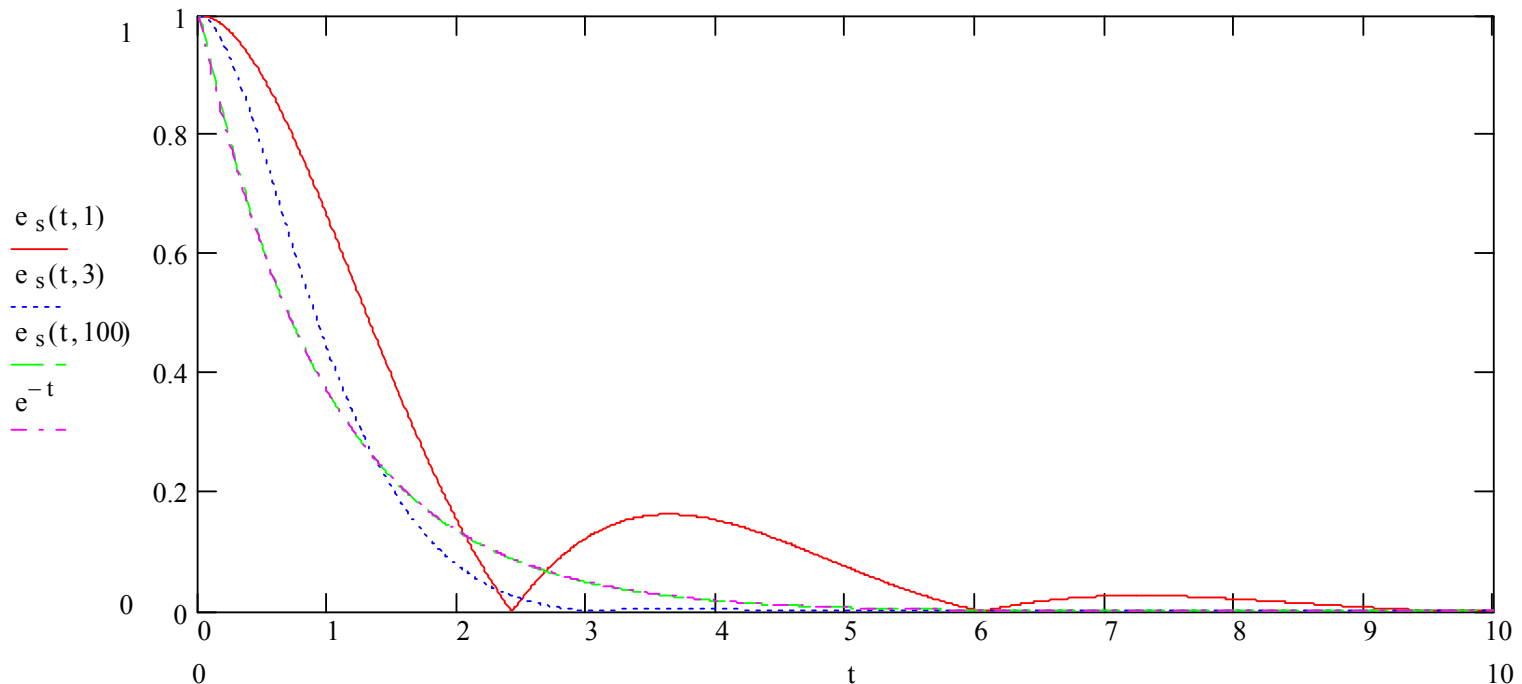




# Non-Dominant Pole (cont.)

Relative error : detail for  $K = 3$

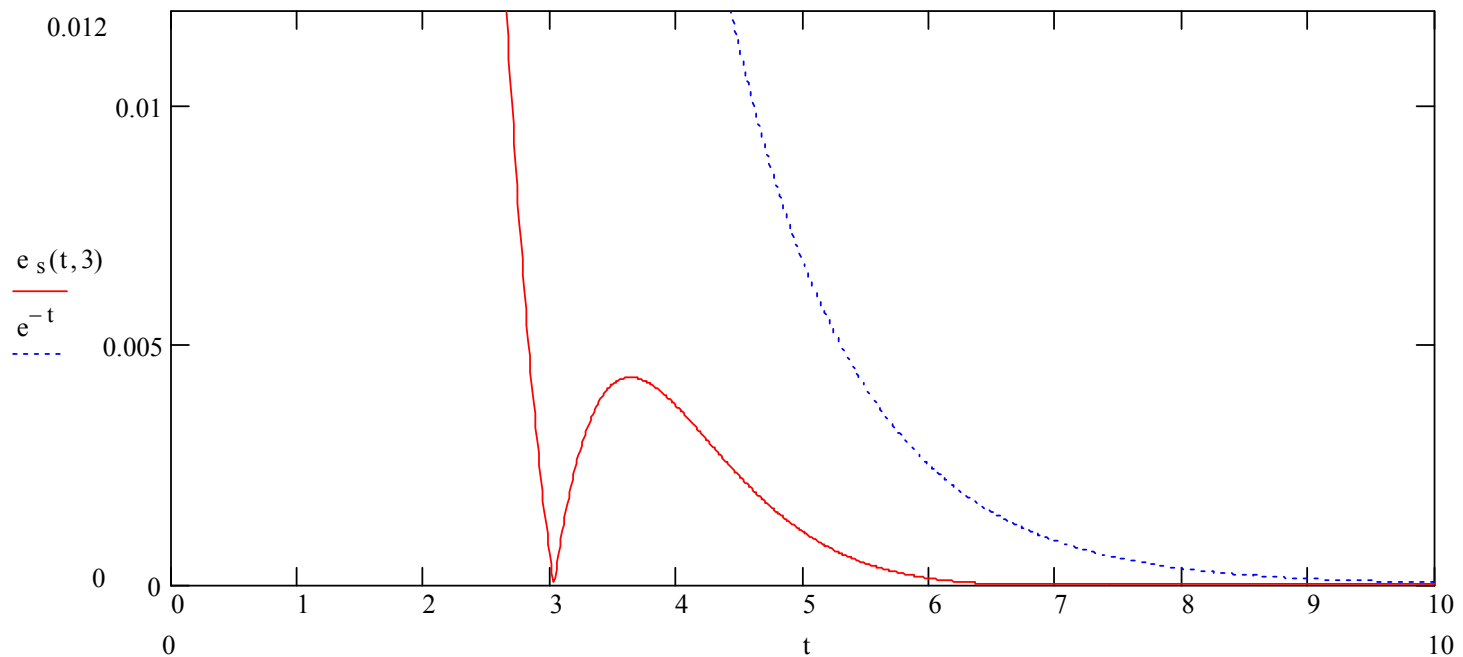


Non-dominant pole can speed up settling!

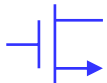

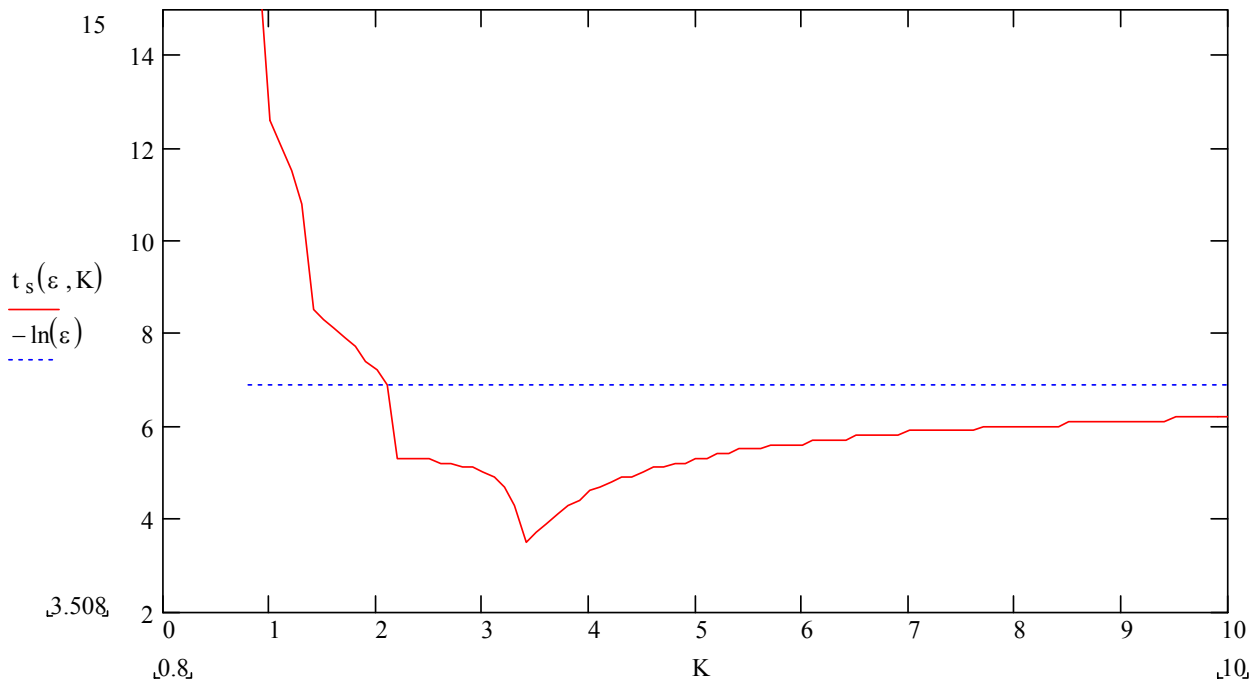
# Non-Dominant Pole (cont.)

Settling time:  $t_s(K)$  for  $\varepsilon = 10^{-3}$ ,  $\tau = 1$




- Optimum for  $K=3.3$
- Avoid  $K < 2$

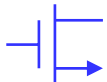
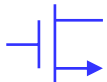
# Doublets

- Doublet = “closely spaced pole/zero pair”
- Origins:
  - Feedforward path (e.g. Miller capacitor)
  - Frequency dependent degeneration (cascode, gain boosting)
  - etc.
- Concerns:
  - Ringing (if high-Q)
  - Slow settling if doublet frequency  $< \omega_{-3\text{dB}}$  of  $T(s)$
  - Hard to see from SPICE output (esp. ac analysis)




# Doublet Analysis

- Amplifier model:

$$G_m(s) = G_{mo} \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_p}} \quad \text{with} \quad \begin{aligned} \omega_p &= \beta \omega_{-3dB}, & \omega_{-3dB} & \text{ is bandwidth of } T(s) \\ \omega_z &= \frac{\omega_p}{\alpha} \\ \alpha &= 1 + \varepsilon & \text{ with } |\varepsilon| & \ll 1 \end{aligned}$$

- Closed-loop gain (ignore feedforward zero):
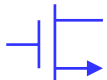
$$\frac{V_o}{V_{in}} = -c \frac{1}{1 + s \frac{C_{Leff}}{FG_m(s)}} \cong -\frac{c}{1 + \frac{s}{\omega_{-3dB}}} \left( \frac{1 + \frac{s}{\omega_z}}{1 + \frac{s}{\omega_{pp}}} \right) \quad \text{with} \quad \begin{aligned} \omega_{-3dB} &= \frac{FG_{mo}}{C_{Leff}} \\ \omega_{pp} &\cong \omega_p \end{aligned}$$



# Doublet Analysis (cont.)

- Step response

$$v_{o,step}(t) = -cV_{step} \left( 1 + Ae^{-t\omega_{-3dB}} + Be^{-t\omega_{pp}} \right)$$

with


$$A \cong -1$$
$$B \cong \varepsilon \frac{\beta}{1 - \beta^2}$$

- Two exponentially decaying errors with time constants



$$\tau_1 = \frac{1}{\omega_{-3dB}} \quad \text{and} \quad \tau_2 = \frac{1}{\omega_{pp}}$$



# Doublet Example

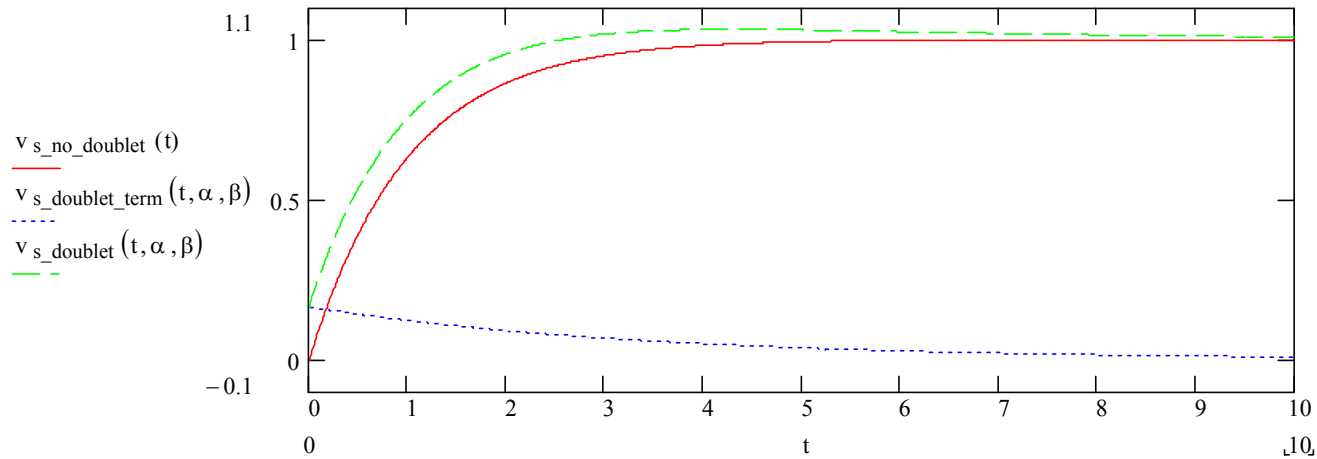


$$\alpha = 1.5$$
$$\beta = 0.3$$

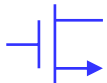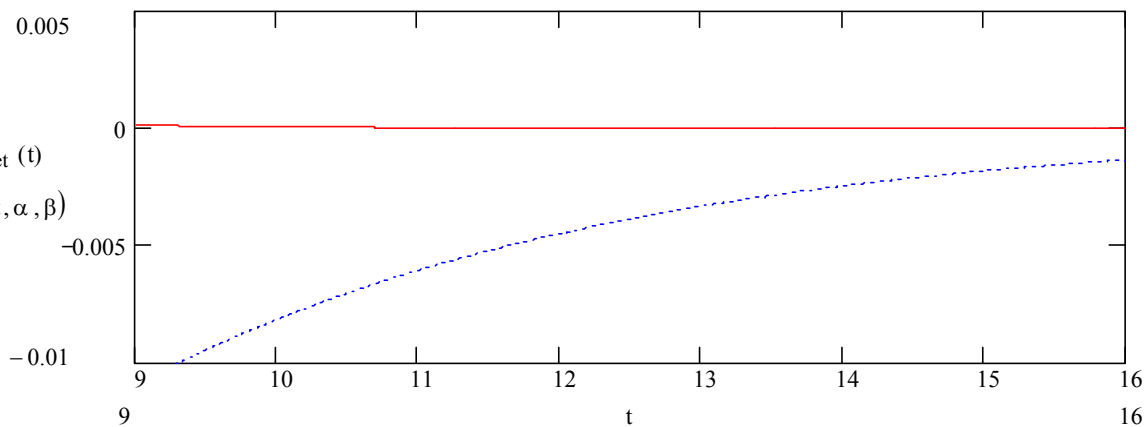

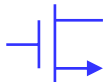
# Doublet Conclusions

- Case A:  $\tau_2 \leq \tau_1$  i.e.  $\beta \geq 1$ 
  - Doublet settles much faster than amplifier
  - Has no impact on overall settling time
- Case B:  $\tau_2 > \tau_1$ 
  - Doublet settles more slowly than amplifier
  - Determines overall settling time  
(unless  $\varepsilon$  within settling accuracy requirements ...  
only met in “low accuracy” situations, cf. scope probes)
- → Avoid “slow” doublets!


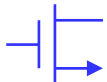
# Slewing



- Transconductor
  - Differential pair
  - Class (A)B input stage
- Model for (nonlinear) slewing amplifier
  - Piecewise linear approximation:
    - Slewing with constant current, followed by
    - Linear settling exponential
    - $t_s = t_{\text{slew}} + t_{\text{lin}}$







# Slewing Analysis

- Circuit model during slewing:

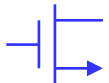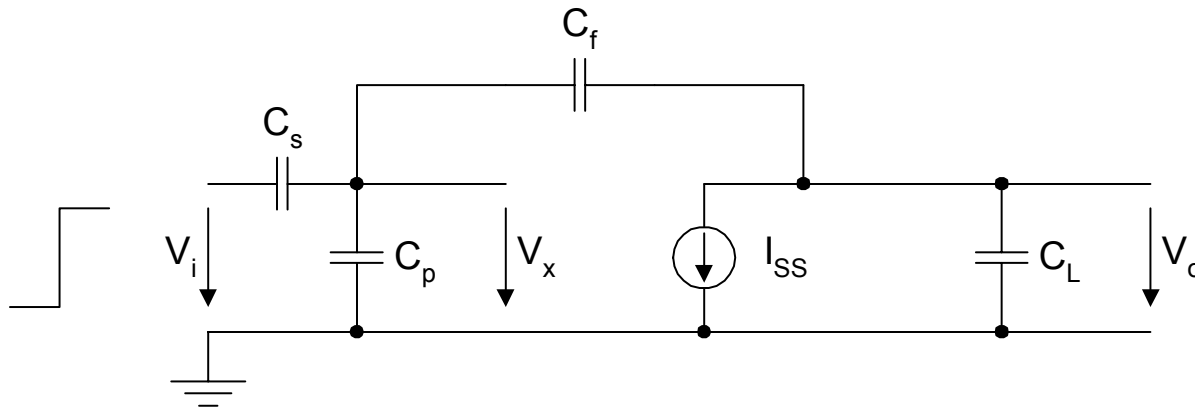

# Slewing Analysis (cont.)

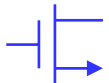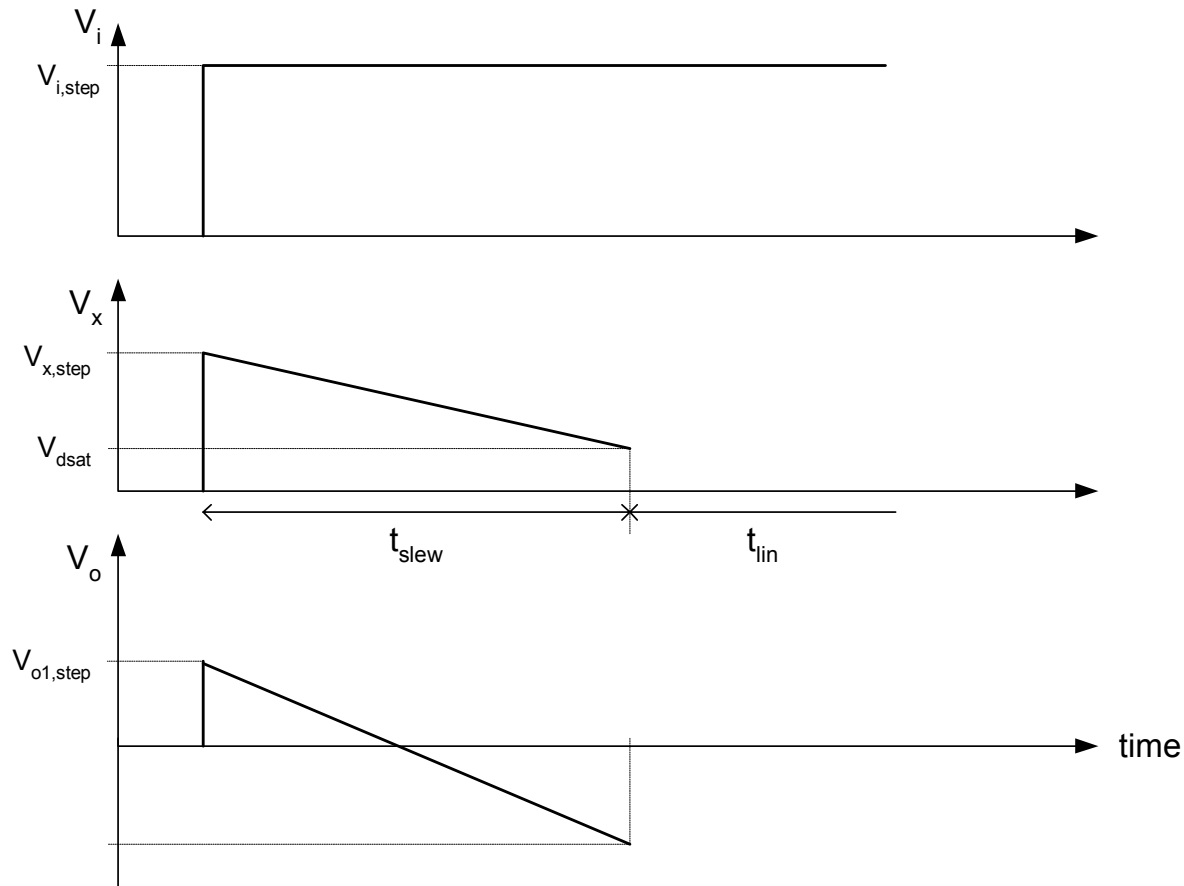

# Slewing Analysis (cont.)

- Slewing period:

$$V_{x,step} = V_{i,step} \frac{C_s}{C_s + C_2} \quad \text{with} \quad C_2 = C_p + \frac{C_f C_L}{C_f + C_L}$$

$$\Delta V_x = V_{x,step} - V_d^{sat}$$

$$\Delta V_o = \frac{\Delta V_x}{F}$$

$$t_{slew} = \frac{\Delta V_o}{SR} \quad \text{with} \quad SR = \frac{I_{SS}}{C_{Leff}}$$

- Linear settling: reduced step size!

- Complete step at output:

$$cV_{i,step}$$

- Step during linear settling:

$$V_d^{sat} / F$$

- Scaled accuracy:

$$\varepsilon_{lin} = \varepsilon \frac{cV_{i,step} F}{V_d^{sat}} > \varepsilon$$

