

EECS 240


Analog Integrated Circuits

Topic 15: Comparators


Ali M. Niknejad and Bernhard E. Boser

© 2006

 
Department of Electrical Engineering and Computer Sciences



Comparator


 


 - Clock rate f_s
- Offset
- Resolution
- Overload Recovery
- Input capacitance (and linearity!)
- Power dissipation
- Common-mode rejection
- Kickback noise
- ...



Flash Converter

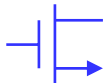 
- Very fast: only 1 clock cycle per conversion
- High complexity: $2^B - 1$ comparators
- High input capacitance




Comparator Gain

 Example:

- 12-Bit / 100MS/s ADC
 - 1V full-scale input
- 1 LSB = $1V / 2^{12} = 240\mu V$
- $A_v > 1V / 120\mu V = 8000$ in 5ns!




Operational Amplifier?


 


$$f_{-3dB} = \frac{f_u}{A_{vo}} \rightarrow \tau = \frac{1}{2\pi f_{-3dB}}$$
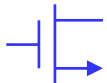
$$\begin{aligned} f_u &= \frac{A_{vo}}{2\pi\tau} \\ &= \frac{8000}{2\pi \times 1\text{ns}} = \underline{1.3\text{THz}} \end{aligned}$$



Open-Loop Amplifier Cascade

 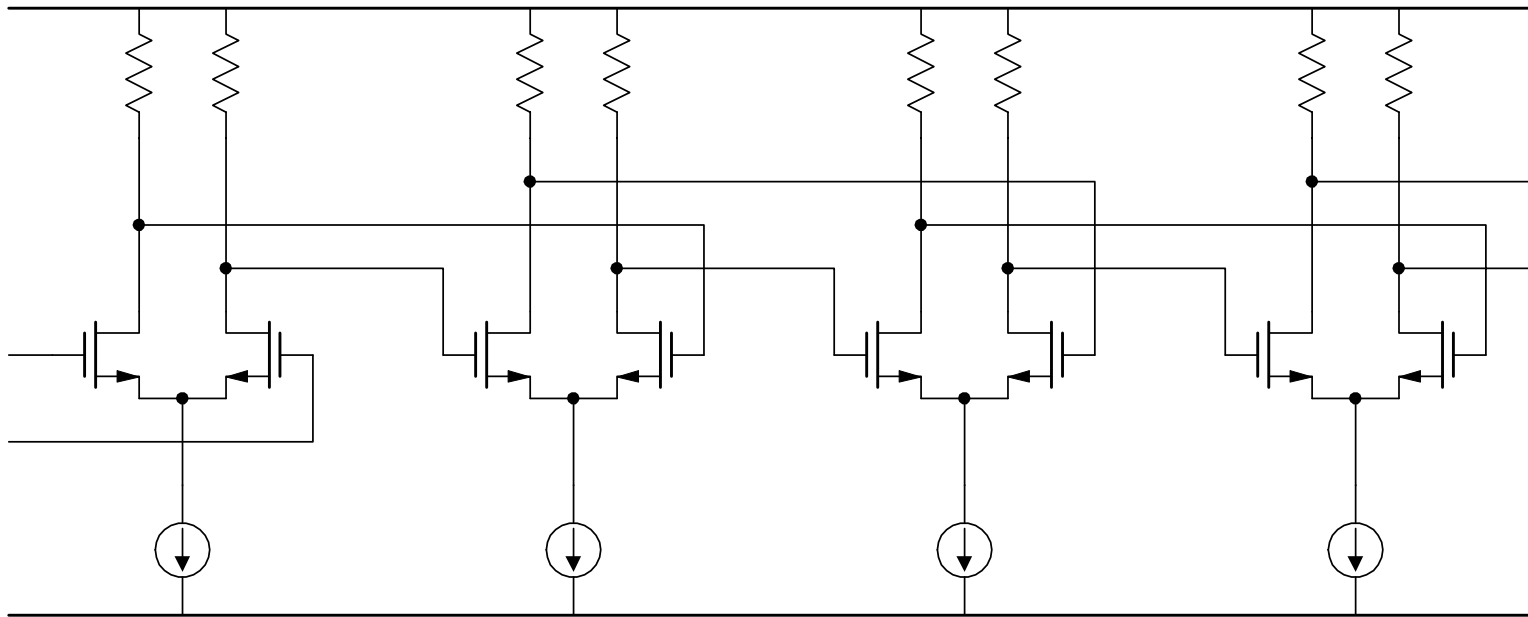

Cascaded Amplifier

- Step response:

$$v_{o1}(t) = \frac{1}{C} \int_0^{T_d} g_m V_{in} dt = \frac{g_m T_d V_{in}}{C}$$


$$v_{o2}(t) = \frac{1}{C} \int_0^{T_d} g_m v_{o1}(t) dt = \frac{1}{2} \left(\frac{g_m}{C} \right)^2 T_d^2 V_{in}$$

$$v_{o3}(t) = \frac{1}{C} \int_0^{T_d} g_m v_{o2}(t) dt = \frac{1}{2} \frac{1}{3} \left(\frac{g_m}{C} \right)^3 T_d^3 V_{in}$$

⋮



$$v_{oN}(t) = \left(\underbrace{\frac{g_m}{C}}_{\sim \omega_T} \right)^N \left(\frac{T_d^N}{N!} \right) V_{in}$$
 
$$T_d = \left(\frac{g_m}{C} \right)^{-1} \sqrt[N]{N! \frac{V_{out}}{V_{in}}} \underbrace{\quad}_{A_{vN}}$$




Gain versus Delay

$$v_o(N, t) := \frac{1}{N!} \cdot t^N$$

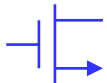 


Optimum Number of Stages
 
$$T_d(A_v N, N) := \lceil A_v N \cdot (N!) \rceil^{\frac{1}{N}} \quad N_x := 2..10$$



Shallow minimum!

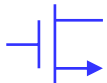

Optimum


$$\frac{dT_d}{dN} = 0 \rightarrow$$

$$N_{opt} \cong 1.2 \ln A_{vN}$$

$$T_{d,opt} \cong 1.2\tau \ln A_{vN}$$



optimum gain/stage: $\sqrt{10} \cong 3.2$

 - Shallow optimum!
- In practice, limit to 4 ... 6 gain stages (area, power, parasitics)
- Can get same speed with single latch ... but higher offset





Practical Considerations


- Overload recovery:

  

Output Common-Mode

  

Latch

 


$t < 0$: initialize C to V_{id}

$t \geq 0$: positive feedback

$$\frac{dv_1}{dt} = \frac{i_1(t)}{C} = \frac{g_m v_2(t)}{C}$$
 
$$\frac{dv_2}{dt} = \frac{i_2(t)}{C} = \frac{g_m v_1(t)}{C}$$




$$T_d = \frac{C}{g_m} \ln \frac{V_{od}}{V_{id}}$$


$$= \tau \ln A_v$$

compare: optimal cascade of amplifiers


$$T_{d,opt} \cong 1.2\tau \ln A_{vN}$$

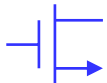


CMOS Comparator Example

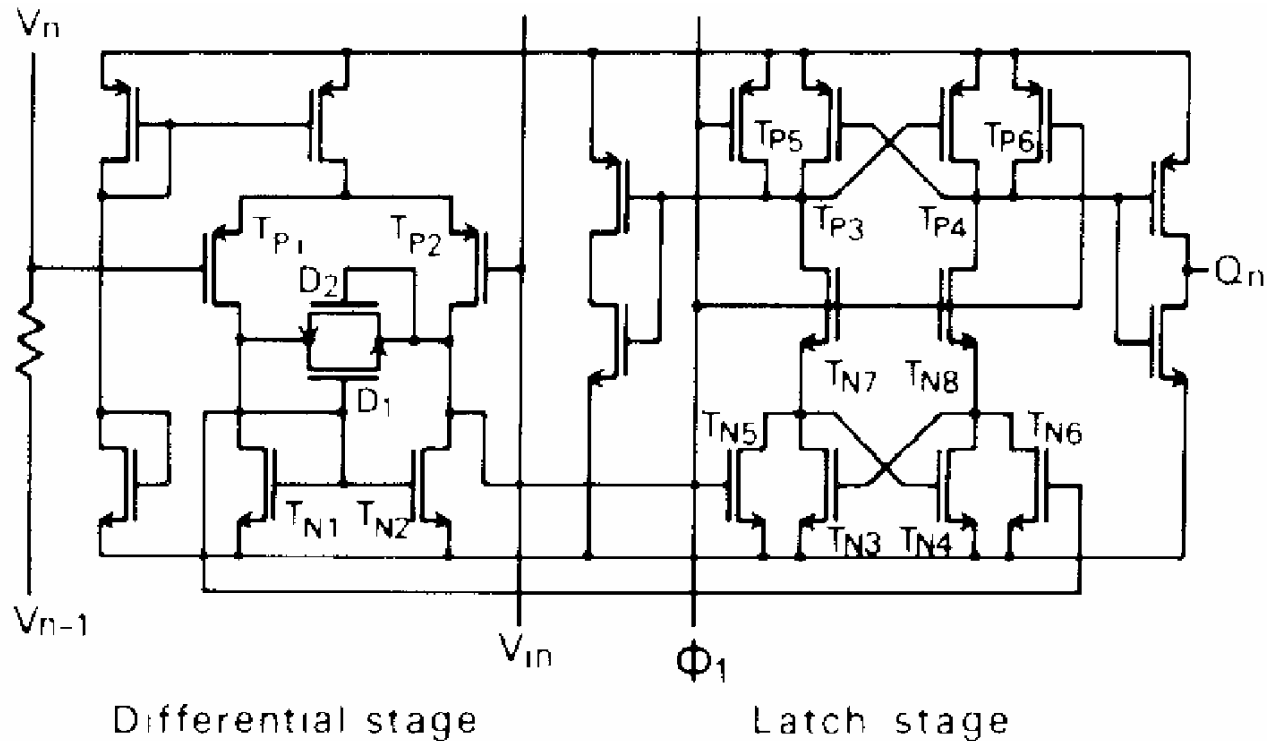

 
A. Yukawa, "A CMOS 8-Bit High-Speed A/D Converter IC," JSSC June 1985, pp. 775-9.




Dynamic Latch

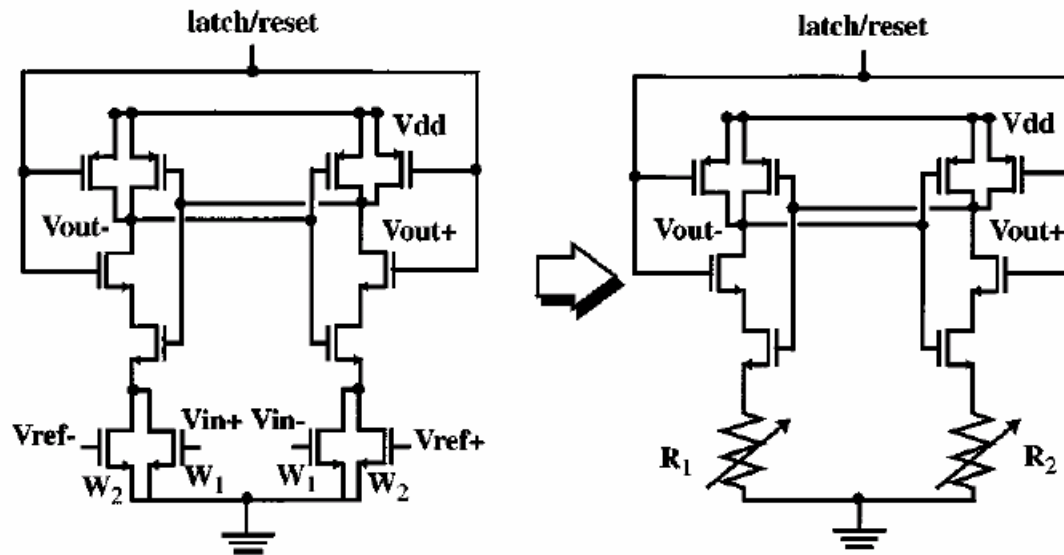

 
T. B. Cho and P. R. Gray, "A 10 b, 20 Msample/s, 35 mW pipeline A/D converter," *IEEE Journal of Solid-State Circuits*, vol. 30, pp. 166 - 172, March 1995.




Latch with Preamp

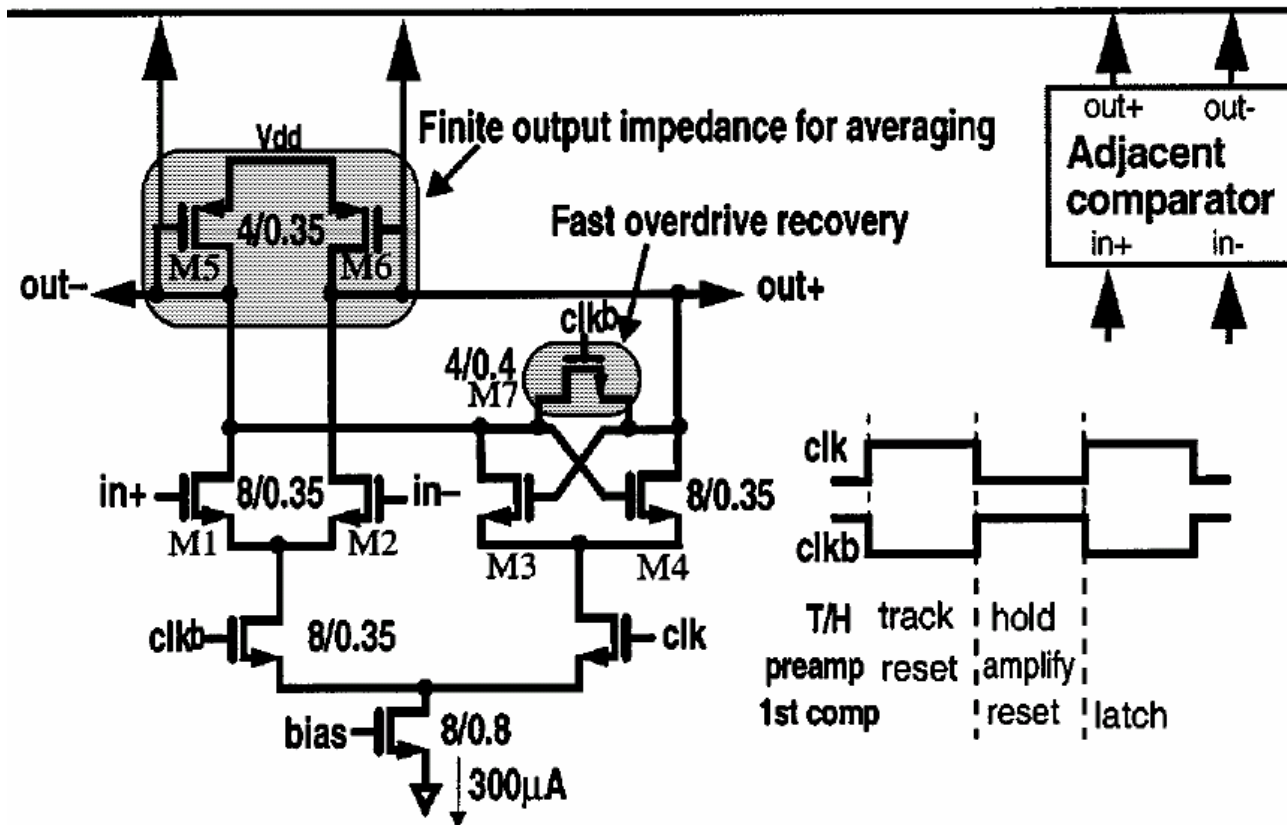

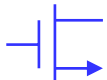
M. Choi and A. A. Abidi, "A 6-b 1.3-Gsample/s A/D converter in 0.35- μm CMOS," *IEEE Journal of Solid-State Circuits*, vol. 36, pp. 1847 - 1858, December 2001 and many others ...




Comparator with Auto-Zero

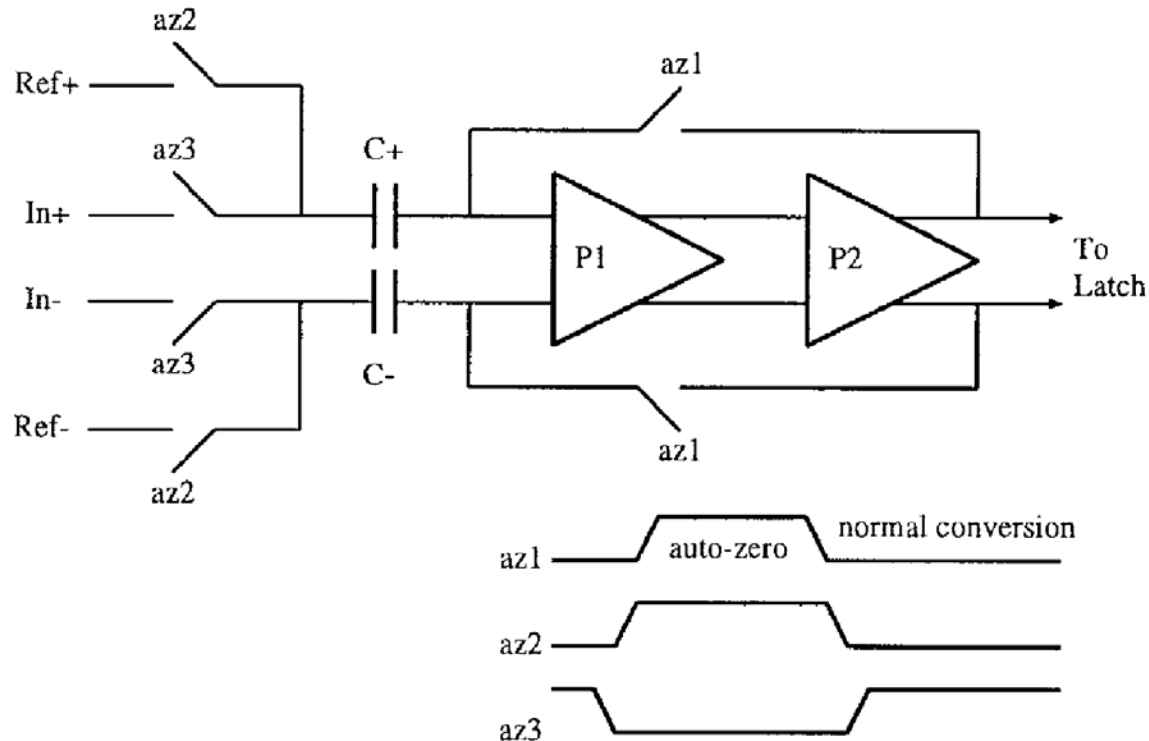

 I. Mehr and L. Singer, "A 500-Msample/s, 6-Bit Nyquist-Rate ADC for Disk-Drive Read-Channel Applications," JSSC July 1999, pp. 912-20.



Auto-Zero Implementation

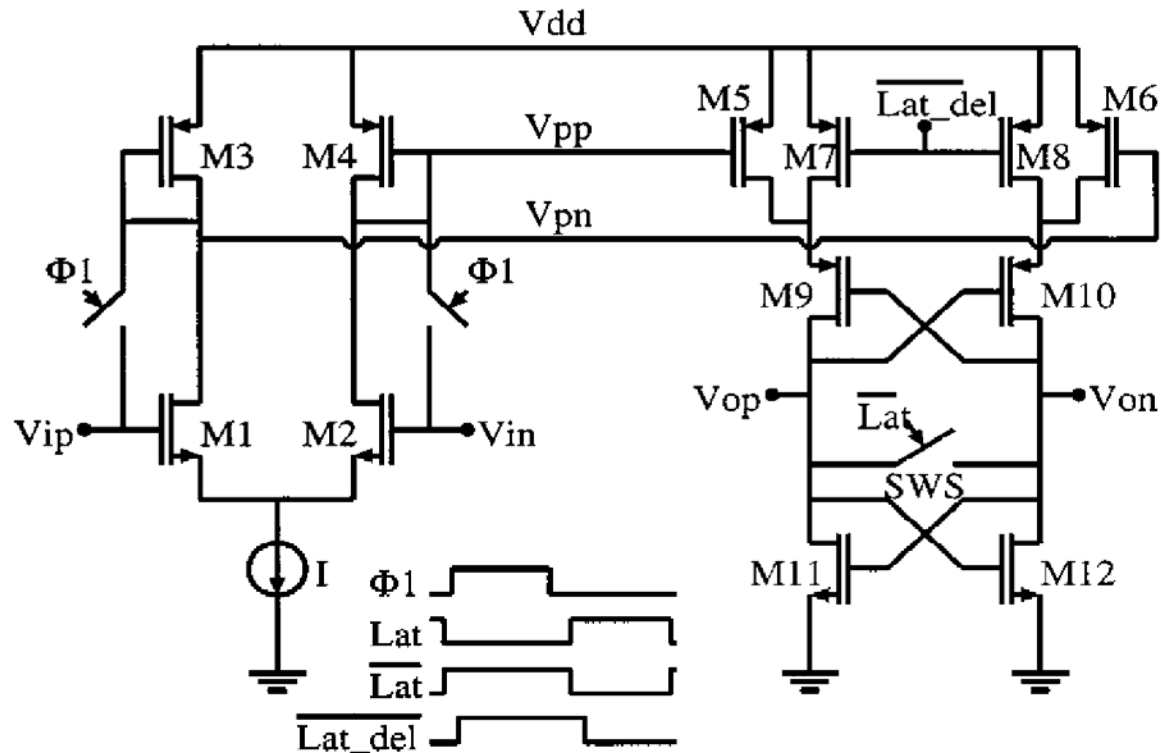

I. Mehr and L. Singer, "A 55-mW, 10-bit, 40-Msample/s Nyquist-Rate CMOS ADC," JSSC March 2000, pp. 318-25.

