


# **EECS 240**

## **Analog Integrated Circuits**

### **Topic 19: Offset Cancellation**


**Ali M. Niknejad and Bernhard E. Boser**  
**© 2006**

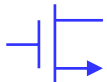**Department of Electrical Engineering and Computer Sciences**



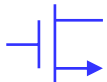
# Offset Cancellation Overview

- Techniques:
  - Correlated double sampling (CDS)
  - Chopper stabilization
- Reject offset and  $1/f$  noise
- Alphabet soup
  - CDS: autozeroing, ping-pong opamp, self-calibrating opamp
  - Chopping: synchronous detection, dynamic element matching
- Reference
  - Ch. Enz and G. C. Temes, “Circuit Techniques for Reducing the Effects of Op-Amp Imperfections,” Proc. IEEE, Nov. 1996, pp. 1584-1614.



# Output Offset Cancellation

 

- Output still corrupted by switch charge injection  
→ bottom plate sampling
- Requires


Phase 1 :

$$V_C = -AV_{os}$$


$$AV_{os} < V_{DD}$$

Phase 2 :

 
$$\begin{aligned} V_{out} &= A(V_{in} - V_{os}) - V_C \\ &= AV_{in} \end{aligned}$$




# Multistage Implementation

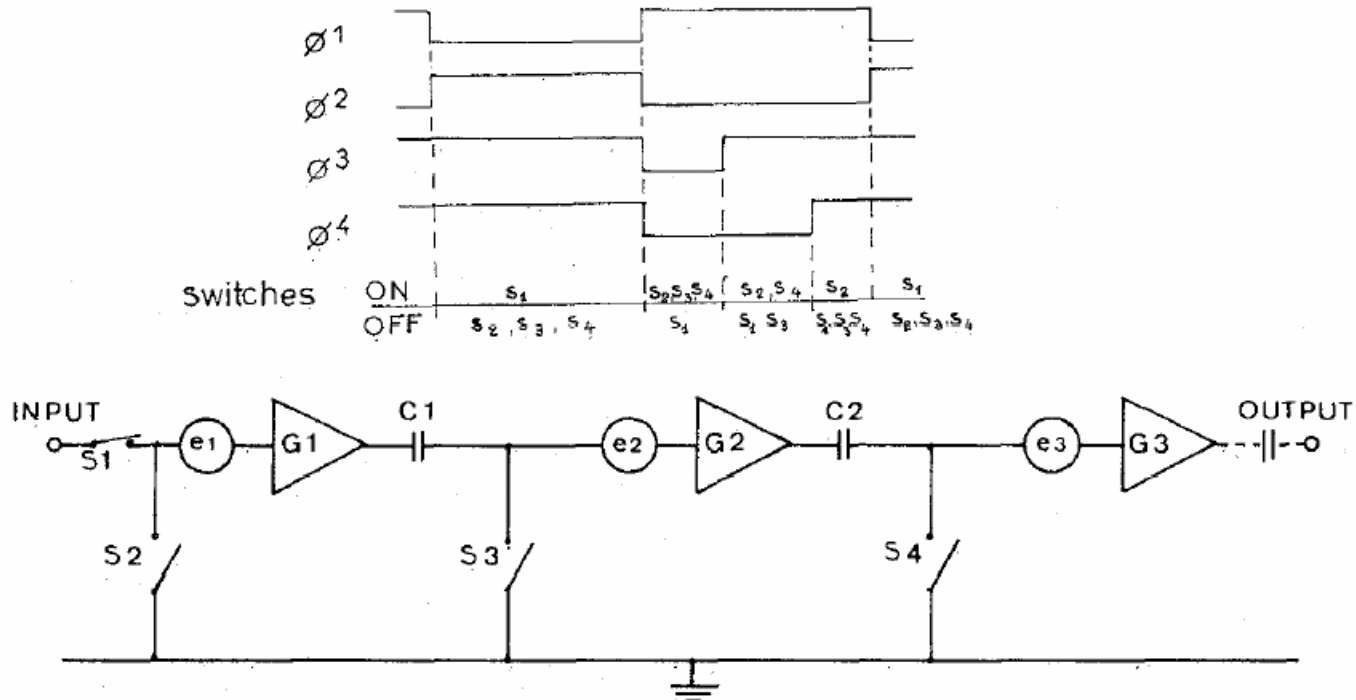

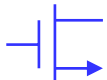R. Poujols and J. Borel, "A low drift fully integrated MOSFET operational amplifier," *IEEE Journal of Solid-State Circuits*, vol. 13, pp. 499 - 503, August 1978.




# Results

 


$$\sigma_{V_{os}} < 5\mu\text{V}$$

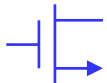Differential implementation also uses chopper stabilization.



# Input Offset Cancellation

 


(a)

Phase (a) :

$$V_o = -A(V_{os} - V_o)$$

$$V_c = -V_o = V_{os} \frac{A}{A+1}$$

 


(b)

Phase (b) :


$$V_o = A(V_{in} - V_{os} + V_c)$$

$$V_o = A \left( V_{in} - \frac{V_{os}}{A+1} \right)$$


$$V_{os,res} = -\frac{V_{os}}{A+1}$$

 



# Multistage Cancellation

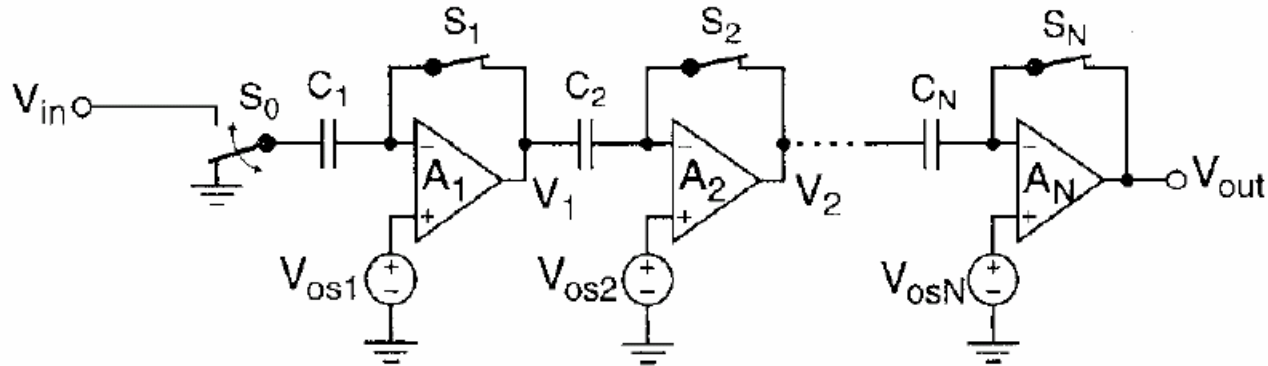

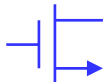- Open switches left to right
- Residual offset from  $S_1 \dots S_{N-1}$  (charge injection?) cancelled by final stage
- Capacitive coupling reduces gain
- Application: comparators




# Offset Compensated SC Gain Stage

 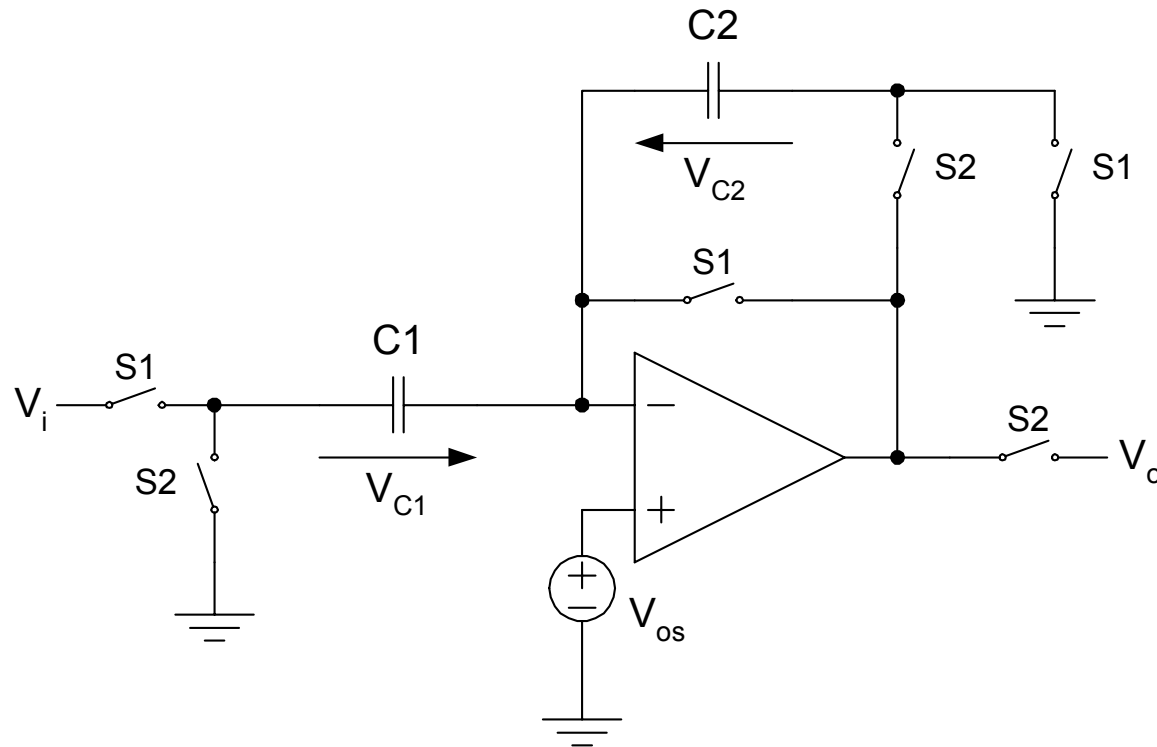



# SC Gain Stage: $\Phi_1$

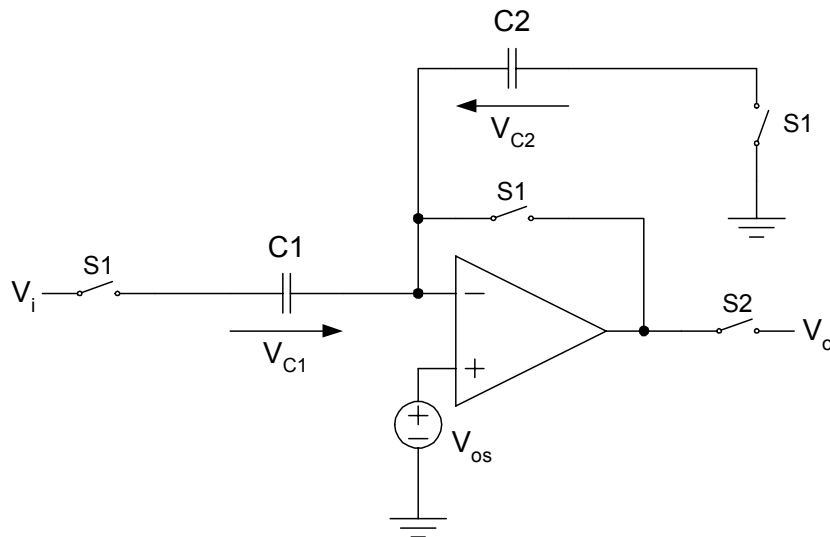


$$V_{C1} = V_i - V_{os}$$

$$V_{C2} = -V_{os}$$


$$\begin{aligned} Q_{tot}^{\Phi_1} &= C_1 V_{C1} + C_2 V_{C2} \\ &= C_1 V_i - (C_1 + C_2) V_{os} \end{aligned}$$

Assuming infinite open-loop gain.

 
 
# SC Gain Stage: $\Phi_2$

- Charge on C1, C2 is redistributed
- Total charge stays same!
- At end of phase 2:



$$V_{C1} = -V_{os}$$


$$V_{C2} = V_o - V_{os}$$

$$Q_{tot}^{\Phi_2} = C_2 V_o - (C_1 + C_2) V_{os}$$


$$Q_{tot}^{\Phi_1} = C_1 V_i - (C_1 + C_2) V_{os}$$

$$Q_{tot}^{\Phi_2} = Q_{tot}^{\Phi_1} \rightarrow$$



$$V_o = \frac{C_1}{C_2} V_i$$

 


# SC Gain Stage Implementation

 

  
- Amplifier must be unity-gain stable
- Output pulled back to  $V_{os}$  in each cycle
- No feedback during clock non-overlap  $\rightarrow C_x$
- Charge injected at input node




# Gain Compensated SC Stage

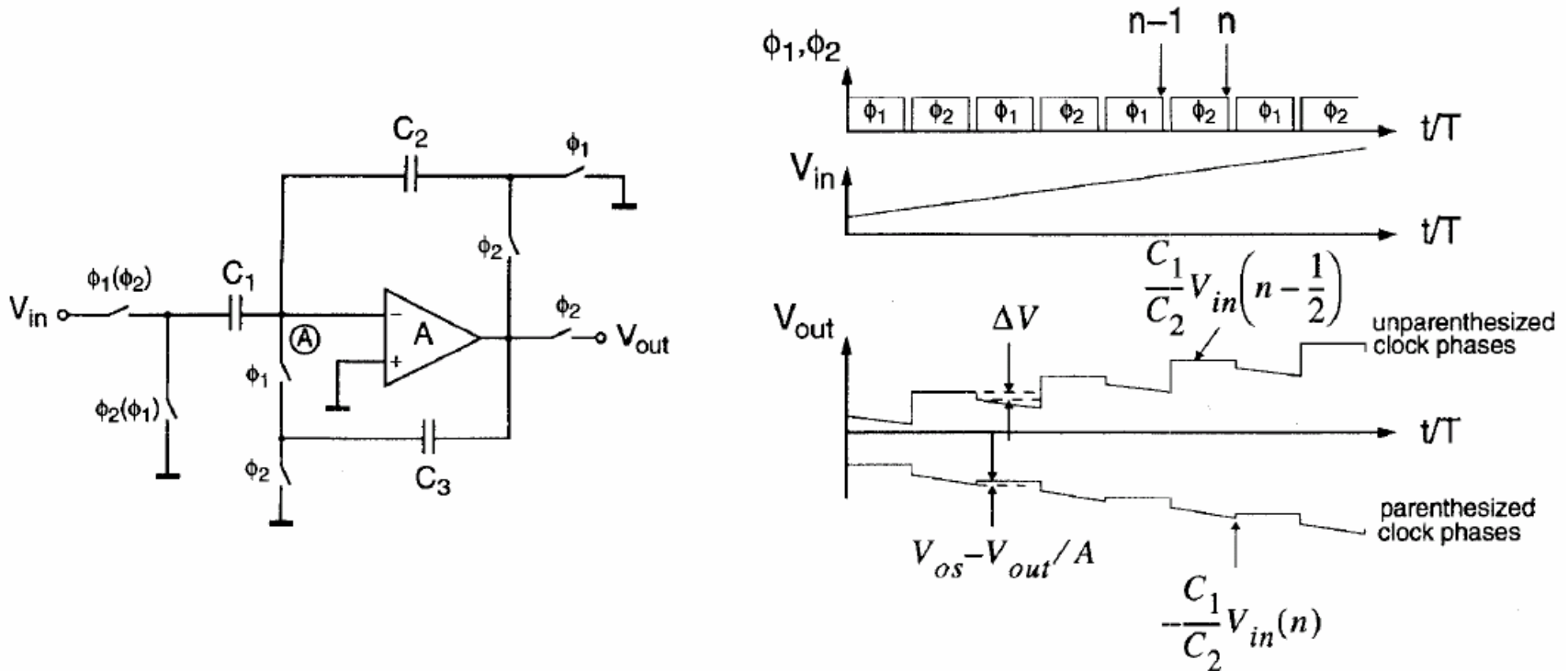

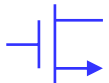Clocks in parentheses are for inverting operation.




# Gain Compensated SC Stage

 


- $C_3$  replaces unity-gain feedback reset
- $C_3$  charged to  $V_{out}$  during  $\Phi_2$
- Output never reset (to zero)
- Reduced slewing requirement
- Reduced static error:

$$\frac{V_{out}}{V_{in}} = \frac{C_1}{C_2} \frac{1}{1 + \frac{C_1}{1 + \frac{C_2}{A^2}}}$$

 - Lowdown: works only for highly oversampled inputs!




# Gain Compensated SC Stage

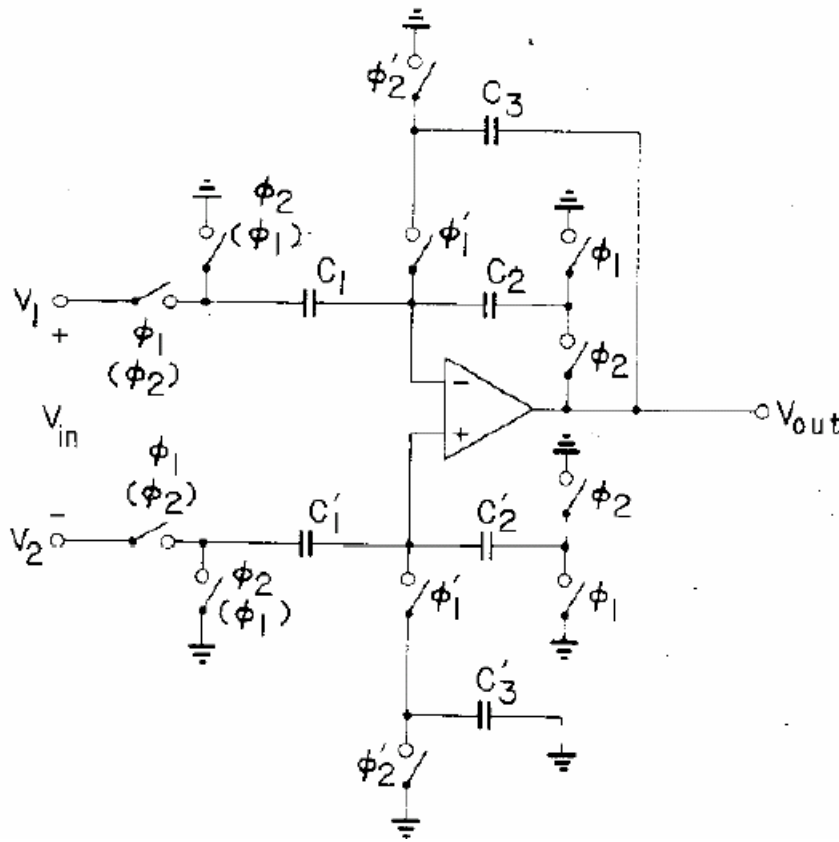


- $V_{os} = 5 \dots 10\text{mV}$
- $\text{CMRR} = 50\text{dB}$
- Distortion:  $0.1 \dots 0.2\%$
  
- Is it worth it?

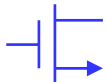K. Martin, L. Ozcolak, Y. S. Lee, and G. C. Temes, "A differential switched-capacitor amplifier," *IEEE Journal of Solid-State Circuits*, Vol. 22, pp. 104 - 106, February 1987.




# Offset Cancellation Comparison


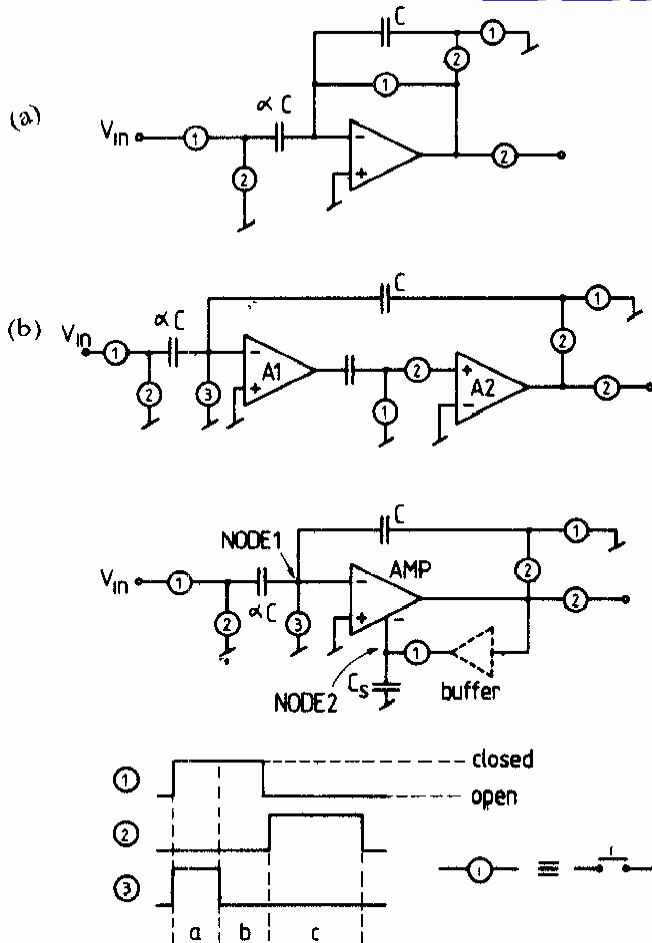


- Offset cancellation options
  - At input
  - At output  
(of first gain stage)
  - At input of auxiliary amp

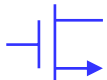M. Degrauwe, E. Vittoz, and I. Verbauwhede, "A micropower CMOS-instrumentation amplifier," *IEEE Journal of Solid-State Circuits*, vol. 20, pp. 805 - 807, June 1985.


  
# Auxiliary Amplifier Offset Cancellation



Switch Charge Injection :

$V_{sw1}$  : phase a, node 1

$V_{sw2}$  : phase b, node 2

$$V_{out} = \underbrace{-A_1(V_1 - V_{OS1})}_{\text{main amp}} - \underbrace{A_2(V_2 - V_{OS2})}_{\text{aux amp}}$$


$$V_2 = V_o = A_1 V_{OS1} - A_2 (V_2 - V_{OS2})$$

$$V_2 = \frac{A_1}{1 + A_2} (V_{OS1} + V_{sw1}) + \frac{A_2}{1 + A_2} V_{OS2} + V_{sw2}$$

$$V_{out} = A_1 V_{OS1} - A_2 V_2 + A_2 V_{OS2}$$



$$= A_1 \left( \underbrace{\frac{V_{OS1} + V_{sw1}}{1 + A_2} + \frac{A_2}{A_1} \frac{A_2}{1 + A_2} V_{OS2} + \frac{A_2}{A_1} V_{sw2}}_{\text{input referred offset}} \right)$$

 → Offset, charge injection attenuated if  $A_1 \gg A_2$






# Aux Amp Options

  


Gain ( $= \alpha C/C$ )	20 dB
Max. clock frequency ( $C_L = 22$ pF)	8 kHz
Offset (at 8 kHz) $\left\{ \begin{array}{l} \bar{x} \\ \sigma \end{array} \right.$	90 $\mu$ V 370 $\mu$ V
Equivalent input noise (0.5 Hz–4 kHz) No 1/f noise was observed above 0.5 Hz (= under limit of measurement equipment)	79 $\mu$ V
CMRR	> 95 dB
Current consumption	7 $\mu$ A
PSRR <sup>-</sup> (at DC)	54 dB
PSRR <sup>+</sup> (at DC)	66 dB

 
M. Degrauwe, E. Vittoz, and I. Verbauwhede, "A micropower CMOS-instrumentation amplifier," *IEEE Journal of Solid-State Circuits*, vol. 20, pp. 805 - 807, June 1985.




# Precision Gain Stage

 

 H. Ohara, H. X. Ngo, M. J. Armstrong, C. F. Rahim, and P. R. Gray, "A CMOS programmable self-calibrating 13-bit eight-channel data acquisition peripheral," *IEEE Journal of Solid-State Circuits*, vol. 22, pp. 930 - 938, December 1987.




# Amplifier with Auxiliary Input




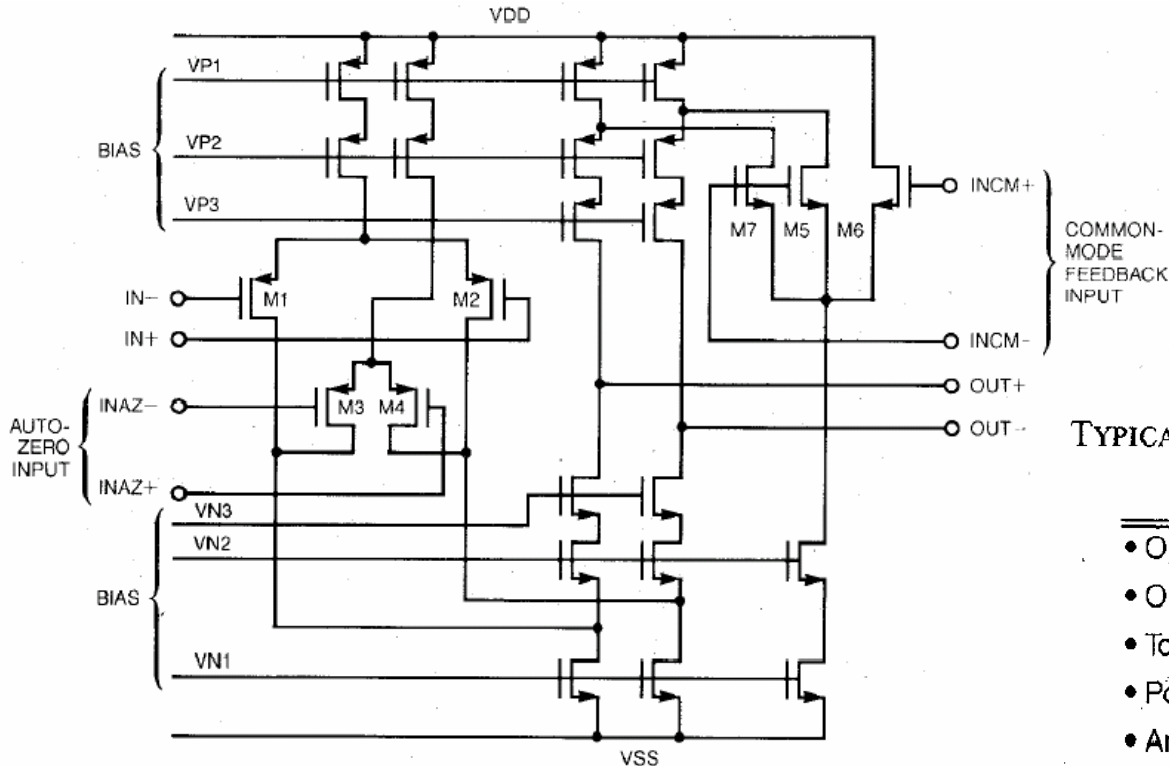

 
## TYPICAL AMPLIFIER PERFORMANCE PARAMETERS ( $\pm 5$ V; $25^\circ\text{C}$ )




- Open loop gain: 125 dB
- Output voltage swing: within 1.5 V of rails
- Total settling time to 0.01%, 6 volt step: 300 ns
- Power dissipation: 30 mW
- Area: 1700 square mils
- Offset:  $300 \mu\text{V}$



# Gain Trimming

   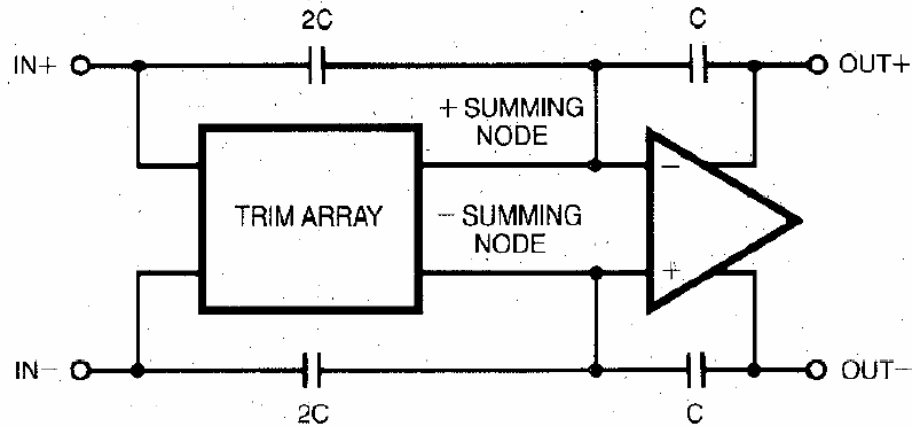

# CDS and Flicker Noise

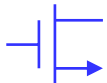 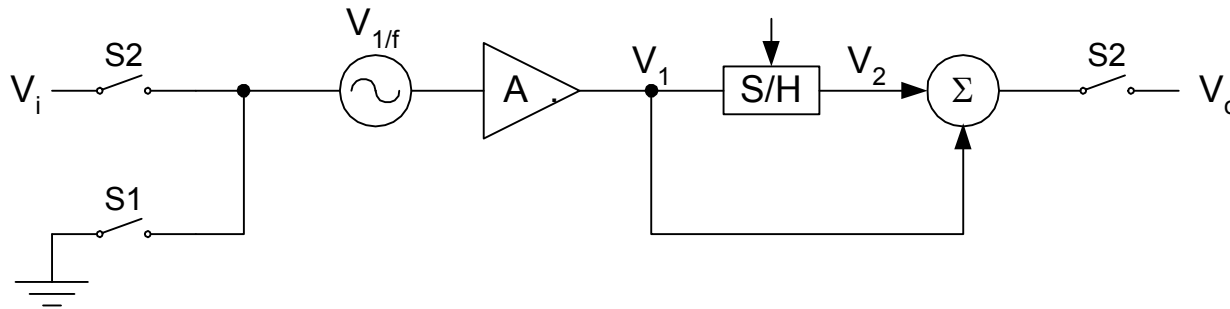


# Flicker Noise Analysis

$$V_o(kT) = A \left\{ \underbrace{V_i(kT)}_{\text{signal}} + \underbrace{V_{1/f}(kT) - V_{1/f}\left(kT - \frac{T}{2}\right)}_{\text{input referred error } V_{nieq}} \right\}$$

Laplace Transform

Delay by  $t_d \rightarrow e^{-st_d}$
 
$$V_{nieq}(s) = V_{1/f}(s) \underbrace{\left\{ 1 - e^{-s\frac{T}{2}} \right\}}_{H_n(s)}$$



# Flicker Noise Frequency Response

$$\begin{aligned}H_n(s) &= 1 - e^{-s\frac{T}{2}} \\ &= 1 - e^{-j\omega\frac{T}{2}} \\ &= 1 - \cos\frac{\omega T}{2} + j \sin\frac{\omega T}{2}\end{aligned}$$

$$\begin{aligned}|H_n(s)|_{s \rightarrow j\omega}^2 &= \left(1 - \cos\frac{\omega T}{2}\right)^2 + \left(\sin\frac{\omega T}{2}\right)^2 \\ &= 1 - 2\cos\frac{\omega T}{2} + \underbrace{\cos^2\frac{\omega T}{2} + \sin^2\frac{\omega T}{2}}_1 \\ &= 2\left(1 - \cos\frac{\omega T}{2}\right) \\ &= 4\sin^2\frac{\omega T}{4}\end{aligned}$$


$$|H_n(s)|_{s \rightarrow j\omega} = \left|2\sin\frac{\omega T}{4}\right| = \left|2\sin\frac{\pi f}{2f_s}\right|$$




# Flicker Noise Spectrum

$$K := 1 \quad f_s := 1$$

$$S_f(f) := \frac{K}{f} \quad H_f(f) := \left| 2 \cdot \sin\left(\frac{\pi \cdot f}{2 \cdot f_s}\right) \right|$$


 


 - Flicker noise is differentiated
- Essentially removed at low frequency
- Choosing  $f_s/2$  sufficiently large effectively removes flicker noise
- Noise above  $f_s/2$  folds to baseband
- Thermal noise folded to  $0 \dots f_s/2$





# Chopper Stabilization

 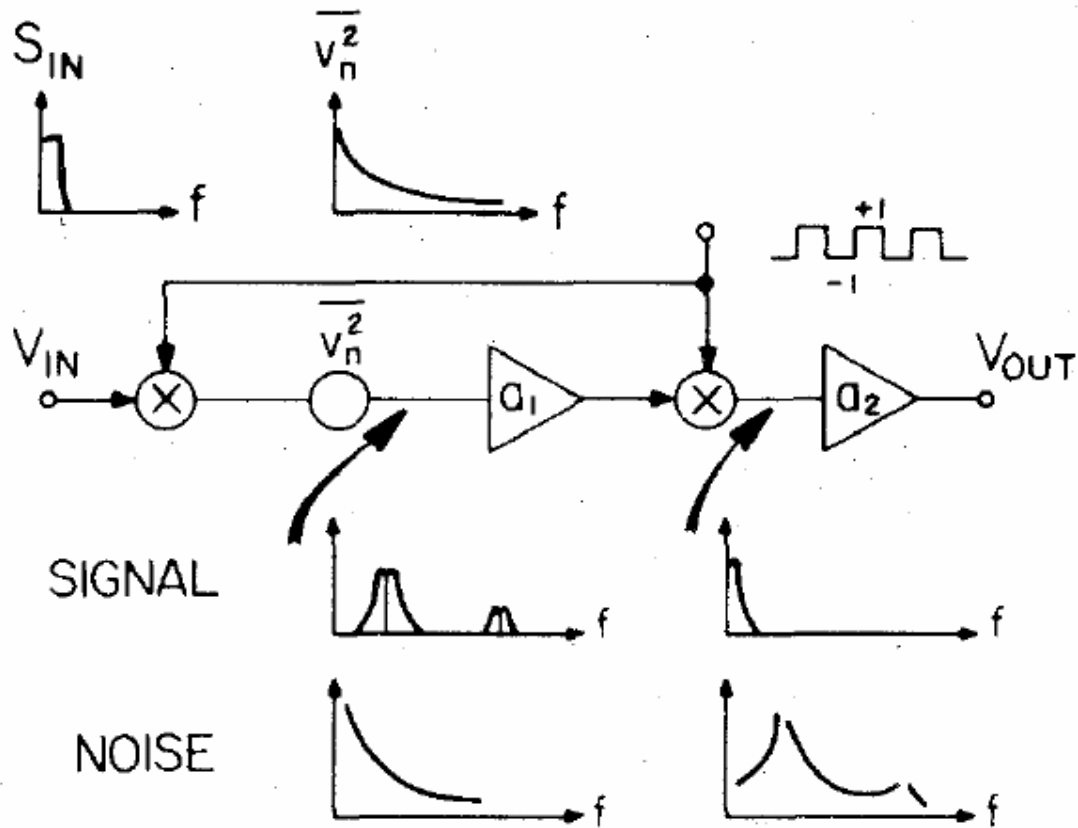

# Chopper Amp Bandwidth & Delay

Example 1:

Amplifier is ideal LPF

- Gain  $A_0$
- BW  $2 f_s$

→ DC gain  $\sim 0.8 A_0$



Example 2:

Amplifier introduces  $90^\circ$  phase shift



→ DC gain is 0

$$\cos x \cos y = \frac{1}{2} [\cos(x - y) + \cos(x + y)]$$

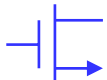 
$$\sin x \cos y = \frac{1}{2} [\sin(x - y) + \sin(x + y)]$$



# Chopper Results

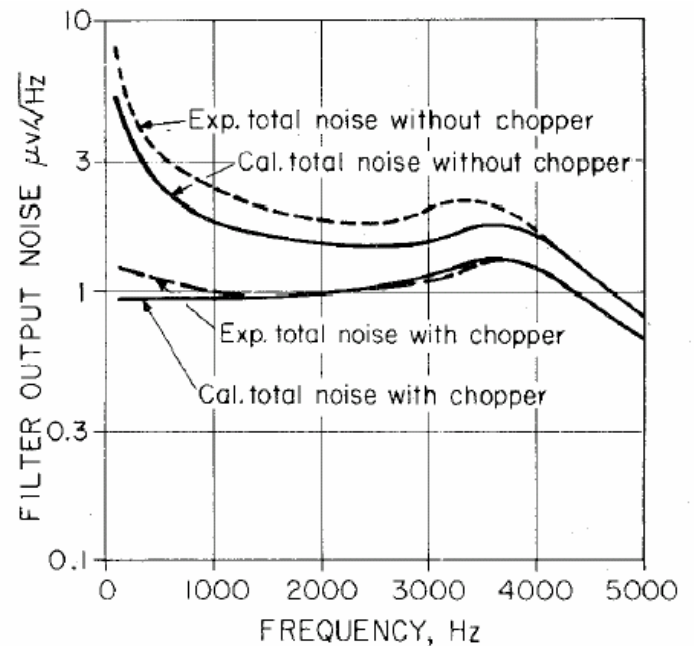 


 
K. Hsieh, P. R. Gray, D. Senderowicz, and D. G. Messerschmitt, "A low-noise chopper-stabilized differential switched-capacitor filtering technique," *IEEE Journal of Solid-State Circuits*, vol. 16, pp. 708 - 715, December 1981.



Precision Zero-Drift  
Operational Amplifier  
with Internal Capacitors


- Offset:  $0.5\mu\text{V}$
- Offset drift:  $0.01\mu\text{V}/^\circ\text{C}$
- Input noise:  $1.5\mu\text{V}_{\text{p-p}}$  DC ... 10Hz  $\rightarrow$   $480\text{nV}/\text{rt-Hz}$  avg
- Open-loop gain: 160dB
- Slew rate:  $4\text{V}/\mu\text{S}$
- Unity-gain bandwidth: 4MHz
- PSRR: 125dB
- CMRR: 120dB

# Chopper Residual Offset

  


Spikes from input chopper due to charge injection mismatch.

 
A. Bakker, K. Thiele, and J. H. Huijsing, "A CMOS nested-chopper instrumentation amplifier with 100-nV offset," *IEEE Journal of Solid-State Circuits*, vol. 35, pp. 1877 - 1883, December 2000.



# Nested Chopper Amplifier

 


 - Inner chopper runs at high frequency to remove  $1/f$  noise
- Outer chopper runs at low frequency to minimize “spiking” and remove residual offset from inner chopper.  $1/f$ -noise is no issue since it has been reduced by inner chopper.



# Results

	Typ	Unit
Supply voltage	5	V
Supply current	200	$\mu\text{A}$
High chopping frequency	2	kHz
Low chopping frequency	16	Hz
Offset	100	nV
Offset temperature coefficient (20-50°C)	3	nV/°C
Noise (input referred, 0.1-3Hz)	27	nV/sqrt(Hz)
CMRR (0.1-3Hz)	140	dB

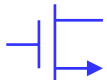

# Comparison

## CDS

- Samples Signal
  - No continuous time operation (except ping-pong)
- Flicker noise removed
  - No need for LPF
- Increased baseband noise due to thermal noise folding
- Can enhance amplifier gain

## Chopper Stabilization

- Modulates Signal
  - Compatible with continuous time operation
- Flicker noise to high frequency
  - Requires LPF to remove noise
- Virtually no thermal noise folding if  $f_{\text{clk}} \gg B$
- Finite BW amp reduces gain

