

EECS 242: RF Mixers

Professor Ali M Niknejad
Advanced Communication Integrated Circuits

University of California, Berkeley



Mixers

The Mixer is a critical component in communication circuits. It translates information content to a new frequency.




Why use a mixer (transmit side)?

- 1) Translate information to a frequency appropriate for transmission

Example: Antennas smaller and more efficient at high frequencies

- 2) Spectrum sharing: Move information into separate channels in order to share spectrum and allow simultaneous use


- 3) Interference resilience

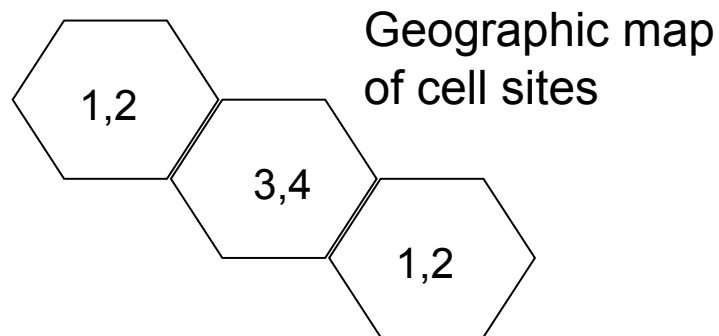

Why use mixer in the receiver?

$$Q \sim \frac{\omega_o}{2\Delta\omega} \quad \text{Q of filter}$$

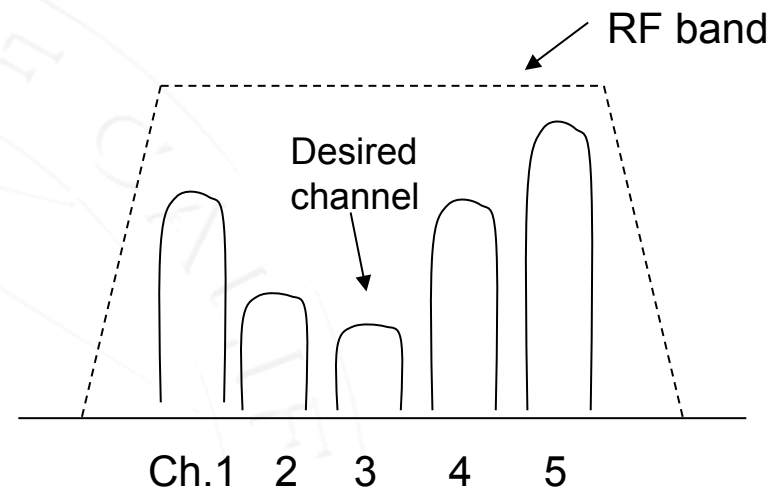Bandpass filter at ω_o
requires a high-Q for
narrowband signals



$\Delta f \sim 200 \text{ kHz (GSM)}$

$f_o \sim 1\text{GHz}$

$$Q = \frac{10^9}{2 \times 200 \times 10^6} = \frac{1000}{0.4} = 2500 \quad \text{High Q}$$

Mixers in Receivers (cont)


High $Q \Rightarrow$ Insertion Loss

Filter center frequency must change to select a given channel \Rightarrow tunable filter difficult to implement

Mixing has big advantage! Translate information down to a fixed (intermediate frequency) or IF.

1 GHz \Rightarrow 10 MHz: 100x decrease in Q required

Don't need a tunable filter

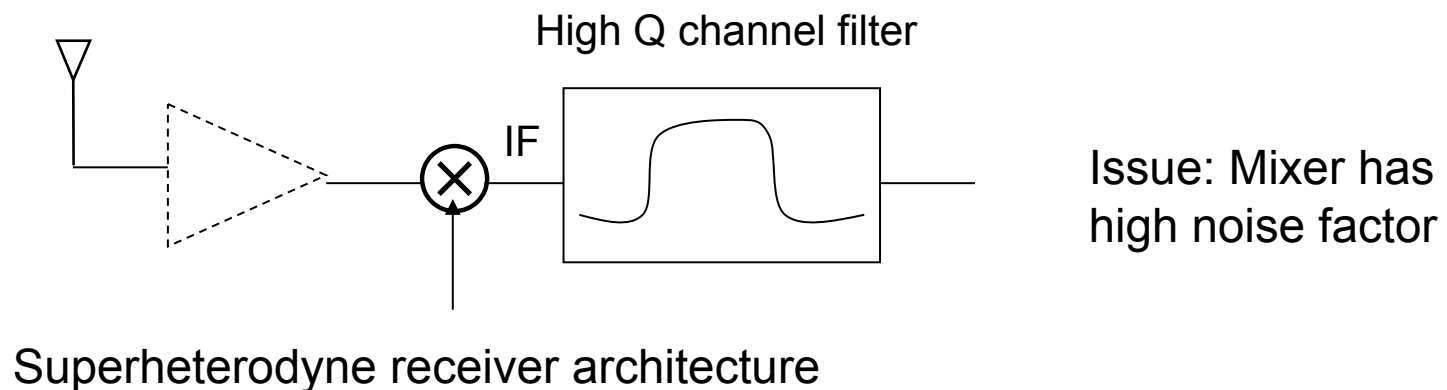


Superheterodyne receiver architecture

Mixers Specifications


- Conversion Gain: Ratio of voltage (power) at output frequency to input voltage (power) at input frequency
 - Downconversion: RF power / IF power
 - Up-conversion: IF power / RF power
- Noise Figure
 - DSB versus SSB
- Linearity
- Image Rejection
- LO Feedthrough
 - Input
 - Output
- RF Feedthrough

Mixer Implementation

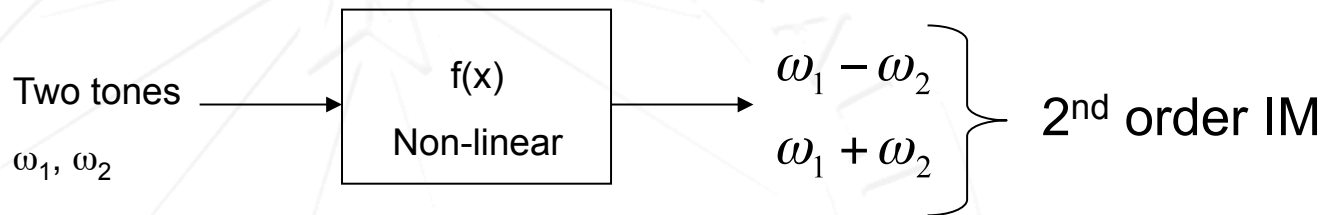We know that any non-linear circuit acts like a mixer




Squarer Example

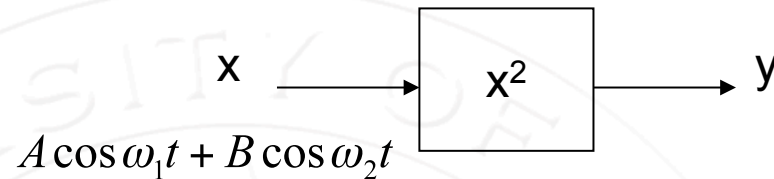

$$y = \underbrace{A^2 \cos^2 \omega_1 t + B^2 \cos^2 \omega_2 t}_{\text{DC \& second harmonic}} + \underbrace{2AB \cos \omega_1 t \cos \omega_2 t}_{\text{Desired mixing}}$$

Product component: $\frac{2AB}{2} \{ \cos(\omega_1 + \omega_2)t + \cos(\omega_1 - \omega_2)t \}$

What we would prefer:

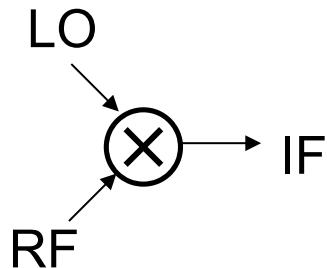


$$v_{IF} = v_{LO} \cdot v_{RF} \cos(\omega_1 \pm \omega_2)t$$


$$v_{RF} = v_{RF} \cos \omega_1 t$$

A true quadrant multiplier with good dynamic range is difficult to fabricate

LTV Mixer

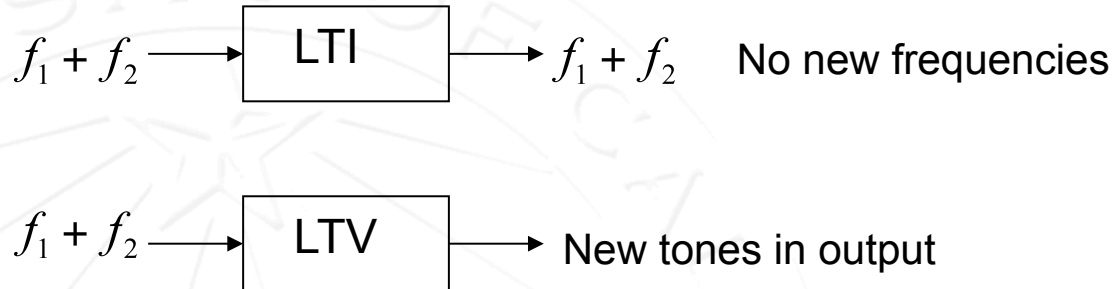

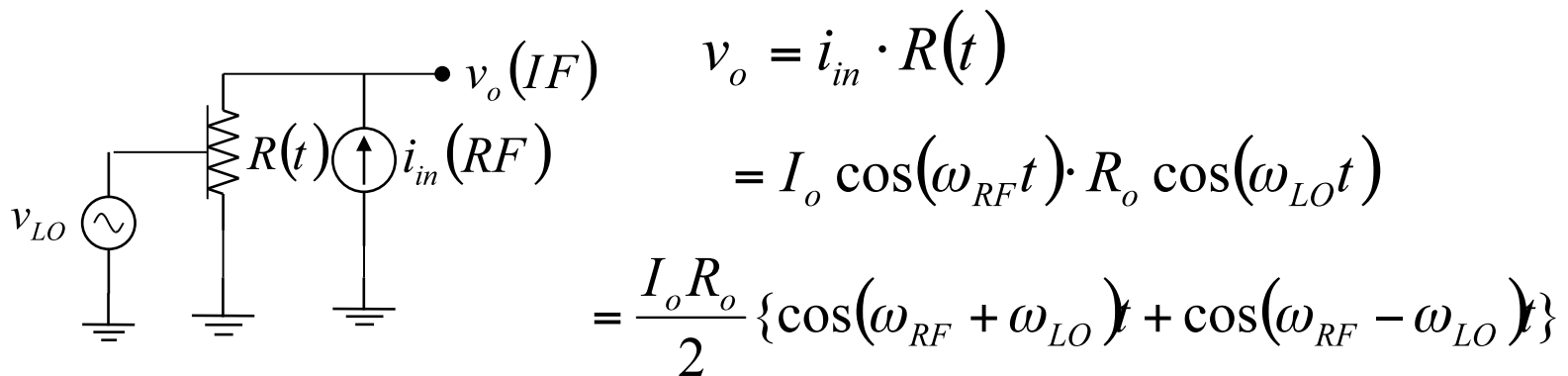Example: Suppose the resistance of an element is modulated harmonically



Time Varying Systems

In general, any periodically time varying system can achieve frequency translation


$$v(t) = p(t)v_i(t) \quad p(t+T) = p(t)$$

$$= \sum_{n=-\infty}^{\infty} c_n e^{j\omega_0 n t} v_i(t)$$

$$c_n = \frac{1}{T} \int_0^T p(t) e^{-j\omega_0 n t} dt \quad v_i(t) = A(t) \cos \omega_1 t = A(t) \left(\frac{e^{j\omega_1 t} + e^{-j\omega_1 t}}{2} \right)$$

$$v_o(t) = A(t) \sum_{n=-\infty}^{\infty} c_n \frac{e^{j(\omega_0 n t + \omega_1 t)} + e^{+j(\omega_0 n t - \omega_1 t)}}{2}$$

consider $n=1$ plus $n=-1$

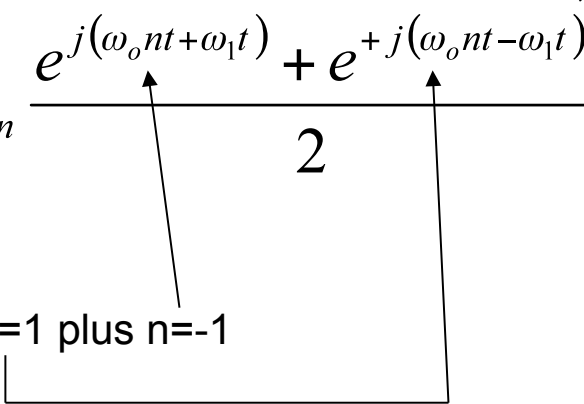

Desired Mixing Product

$$c_1 = c_{-1}$$


$$v_o(t) = \frac{c_1}{2} e^{j(\omega_o t - \omega_1 t)} + \frac{c_{-1}}{2} e^{-j(\omega_o t + \omega_1 t)}$$

$$= c_1 \cos(\omega_o t - \omega_1 t)$$

Output contains desired signal (plus a lot of other signals)
→ filter out undesired components

Convolution in Frequency


Ideal multiplier mixer:

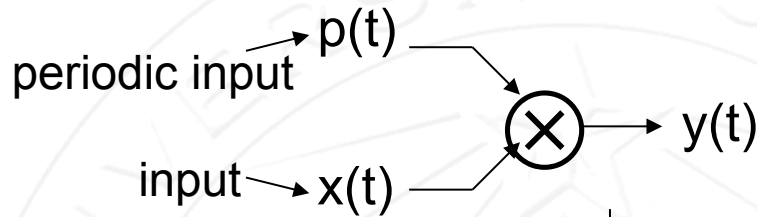

$$y(t) = p(t)x(t)$$


$$Y(f) = X(f) * P(f)$$
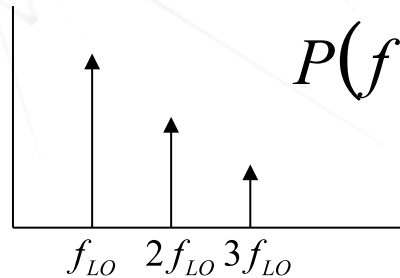
$$P(f) = \sum_{-\infty}^{\infty} c_n \delta(f - nf_{LO})$$




$$\begin{aligned} Y(f) &= \int_{-\infty}^{\infty} \sum_{-\infty}^{\infty} c_n \delta(\sigma - nf_{LO}) X(f - \sigma) d\sigma \\ &= \sum_{-\infty}^{\infty} c_n \left(\int_{-\infty}^{\infty} \delta(\sigma - nf_{LO}) X(f - \sigma) d\sigma \right) \\ &= \sum_{-\infty}^{\infty} c_n X(f - nf_{LO}) \end{aligned}$$

Convolution in Frequency (cont)

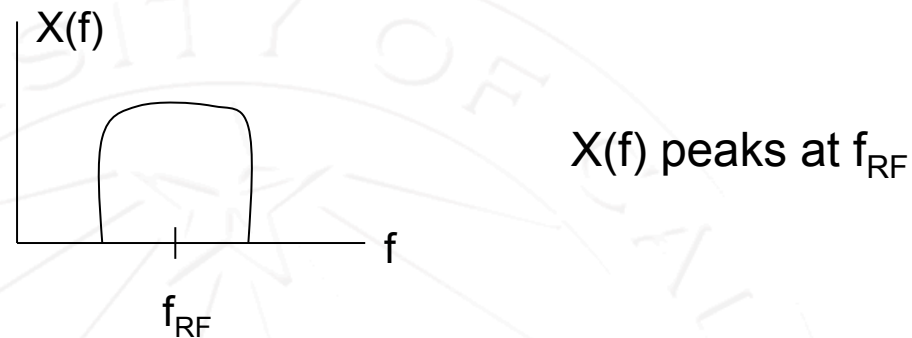

Translated spectrum peaks: $f - nf_{LO} = f_{RF}$

$$f = f_{RF} + nf_{LO}$$


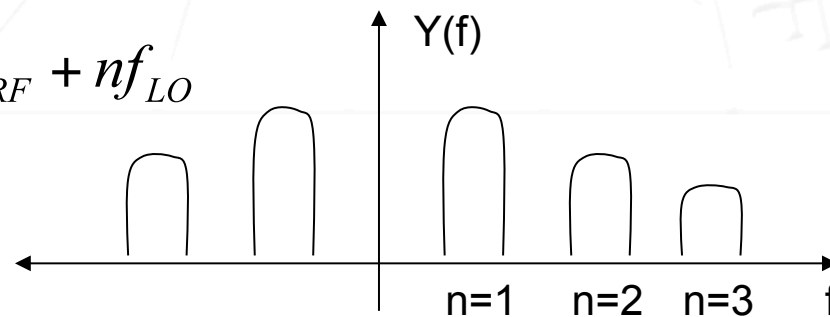


Input spectrum is translated into multiple “sidebands” or “image” frequencies

⇒ Also, the output at a particular frequency originates from multiple input frequency bands

How Low can you LO?

Take the simplest mixer:

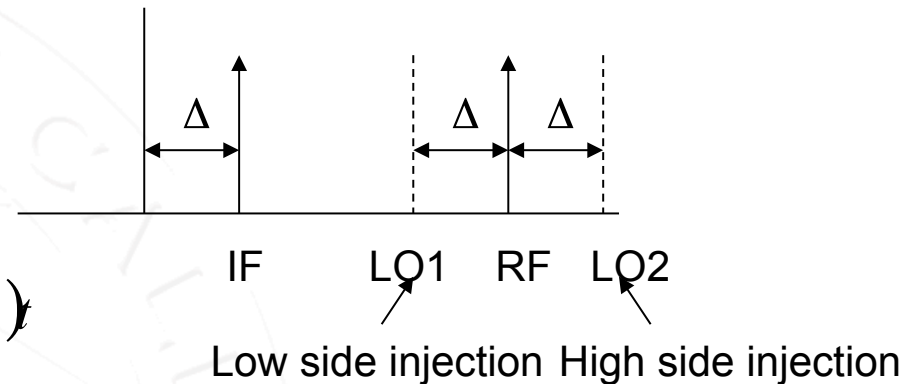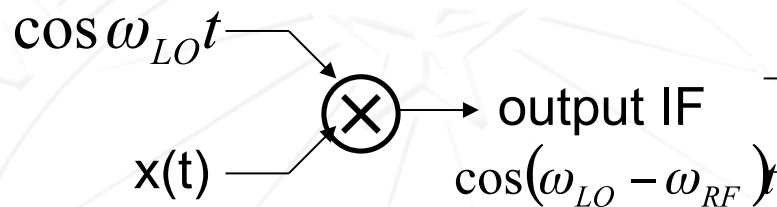

Side note:

Which LO frequency to pick? LO1 or LO2?

$$f_{LO} = f_{LO}' + \frac{n\Delta f}{N}$$

\leftarrow Channel spacing
 \leftarrow No. of channels

Tuning range: $\frac{\Delta f}{f_{LO}} \Rightarrow f_{LO}$ larger implies smaller tuning range


Image Problem

Back to the original problem:




Question: Why filter before mixer in spectrum analyzer?

Answer: Image rejection

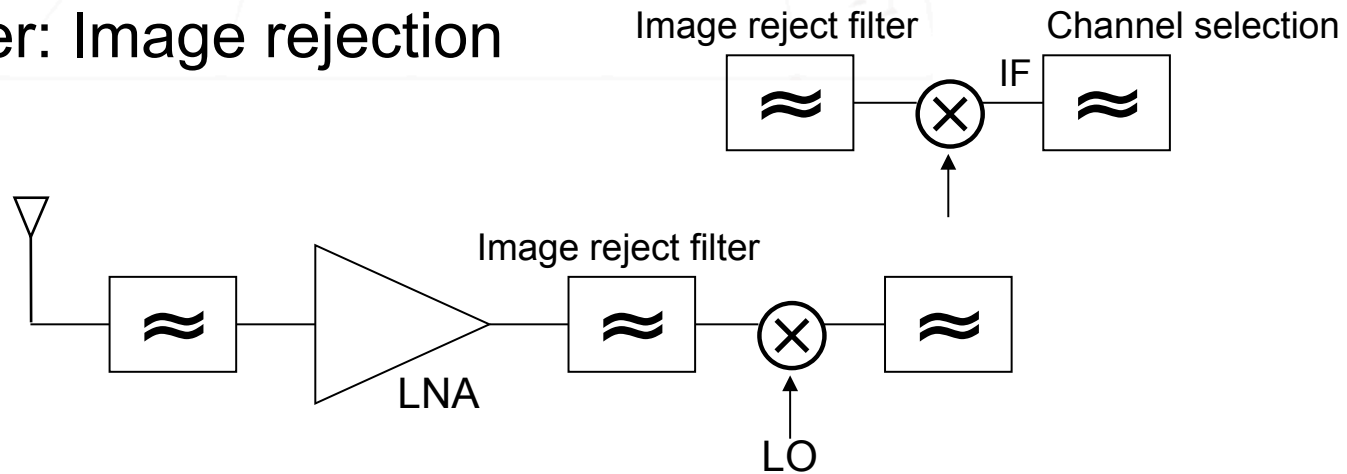

Receiver architecture is getting complicated...

Origin of Image Problem

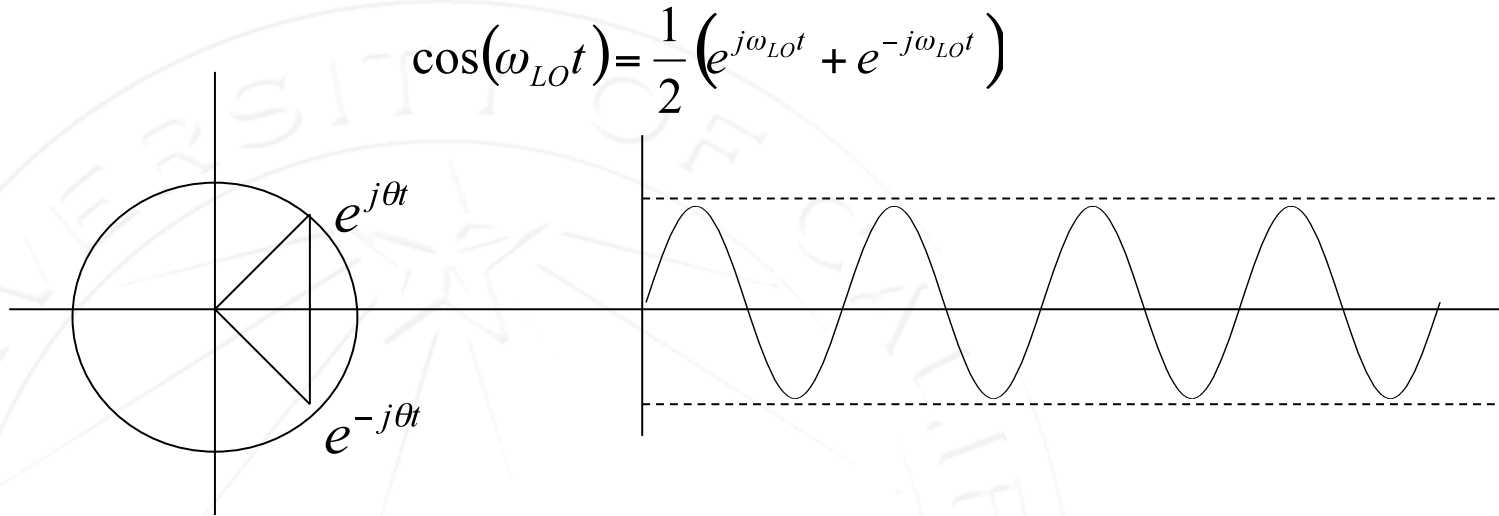

If we could multiply by a complex exponential, then image problem goes away...

$$e^{j\theta_{LO}} \cos(\omega_{RF}t) = e^{j(\theta_{LO} + \theta_{RF})t} + \underbrace{e^{+j(\theta_{LO} - \theta_{RF})t}}_{e^{j\theta_{IF}} \text{ IF frequency}}$$

$$e^{j\theta_{RF}} + e^{-j\theta_{RF}}$$

$$\theta_{RF} = \theta_{LO} - \theta_{IF} \quad \text{High side injection}$$

$$\theta_{IM} = \theta_{LO} + \theta_{IF} \quad \text{(Low side injection) Image Freq.}$$

Review of Linear Systems and PSD

Average response of LTI system:

$$y_1(t) = H_1[x(t)] = \int_{-\infty}^{\infty} h_1(t) x(t - \tau) d\tau$$

$$\overline{y_1(t)} = \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T y_1(t) dt$$

$$= \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T \left(\int_{-\infty}^{\infty} h_1(\tau) x(t - \tau) d\tau \right) dt$$

$$= \int_{-\infty}^{\infty} \underbrace{\left(\lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x(t - \tau) dt \right)}_{\overline{x(t)}} h_1(\tau) d\tau$$

Average Value Property

$$\overline{y_1(t)} = \overline{x(t)} \int_{-\infty}^{\infty} h_1(t) dt$$

$$H_1(j\omega) = \int_{-\infty}^{\infty} h_1(t) e^{-j\omega t} dt$$

$$\overline{y_1(t)} = \overline{x(t)} H_1(0)$$

↑
“DC gain”

Output RMS Statistics

$$\begin{aligned}\overline{y_1^2(t)} &= \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T \left(\int_{-\infty}^{\infty} h_1(\tau_1) x(t - \tau_1) d\tau_1 \right) \left(\int_{-\infty}^{\infty} h_1(\tau_2) x(t - \tau_2) d\tau_2 \right) dt \\ &= \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} h_1(\tau_1) h_1(\tau_2) \left(\lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x(t - \tau_1) x(t - \tau_2) dt \right) d\tau_1 d\tau_2\end{aligned}$$

Recall the definition for the autocorrelation function

$$\begin{aligned}\phi_{xx}(t) &= \overline{x(t)x(t + \tau)} \\ &= \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T x(t)x(t + \tau) dt\end{aligned}$$

Autocorrelation Function

$$\overline{y_1^2(t)} = \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} h_1(\tau_1) h_2(\tau_2) \phi_{xx}(\tau_1 - \tau_2) d\tau_1 d\tau_2$$

$$\phi_{xx}(j\omega) = \int_{-\infty}^{\infty} \phi_{xx}(\tau) e^{-j\omega\tau} d\tau$$

$$\phi_{xx}(\tau) = \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) e^{j\omega\tau} d\omega$$

$\phi_{xx}(j\omega)$ is a real and even function of ω

since $\phi_{xx}(\tau)$ is a real and even function of τ

Autocorrelation Function (2)

$$\overline{y_1^2(t)} = \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} h_1(\tau_1) h_1(\tau_2) \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) e^{j\omega(\tau_1 - \tau_2)} d\omega d\tau_1 d\tau_2$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) \int_{-\infty}^{\infty} \int_{-\infty}^{\infty} h_1(\tau_1) h_1(\tau_2) e^{j\omega(\tau_1 - \tau_2)} d\tau_1 d\tau_2$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) \left(\int_{-\infty}^{\infty} h_1(\tau_1) e^{+j\omega\tau_1} d\tau_1 \right) \left(\int_{-\infty}^{\infty} h_1(\tau_2) e^{-j\omega\tau_2} d\tau_2 \right) d\omega$$


$$H_1^*(j\omega) = \left(\int_{-\infty}^{\infty} h_1(\tau) e^{-j\omega\tau} d\tau \right)^* =$$

$$\overline{y_1^2(t)} = \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) H_1(j\omega) H_1^*(j\omega) d\omega$$

$$= \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) |H_1(j\omega)|^2 d\omega$$

Average Power in X(t)

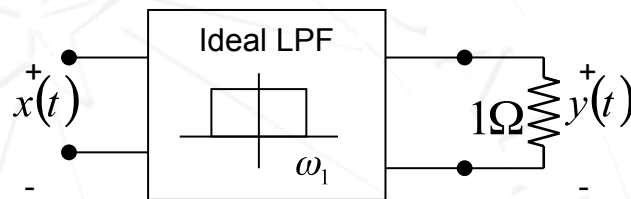Consider $\overline{x(t)}$ as a voltage waveform with total average power $\overline{x^2(t)}$. Let's measure the power in $x(t)$ in the band $0 < \omega < \omega_1$.



The average power in the frequency range $0 < \omega < \omega_1$ is now

$$\begin{aligned} \overline{y_1^2(t)} &= \frac{1}{2\pi} \int_{-\infty}^{\infty} \phi_{xx}(j\omega) |H_1(j\omega)|^2 d\omega \\ &= \frac{1}{2\pi} \int_{-\omega_1}^{\omega_1} \underbrace{\phi_{xx}(j\omega)}_{\text{W/radian}} d\omega \\ &= \int_{-f_1}^{f_1} \underbrace{\phi_{xx}(j2\pi f)}_{\text{W/Hz}} df \end{aligned}$$

Average Power in X(t) (2)

$$= 2 \int_0^{f_1} \phi_{xx}(j2\pi f) df$$

Generalize: To measure the power in any frequency range apply an ideal bandpass filter with passband $\omega_1 < \omega < \omega_2$


$$\overline{y_1^2(t)} = 2 \int_{f_1}^{f_2} \phi_{xx}(j2\pi f) df$$

The interpretation of ϕ_{xx} as the “power spectral density” (PSD) is clear

Spectrum Analyzer

A spectrum analyzer measures the PSD of a signal


Poor man's spectrum analyzer:

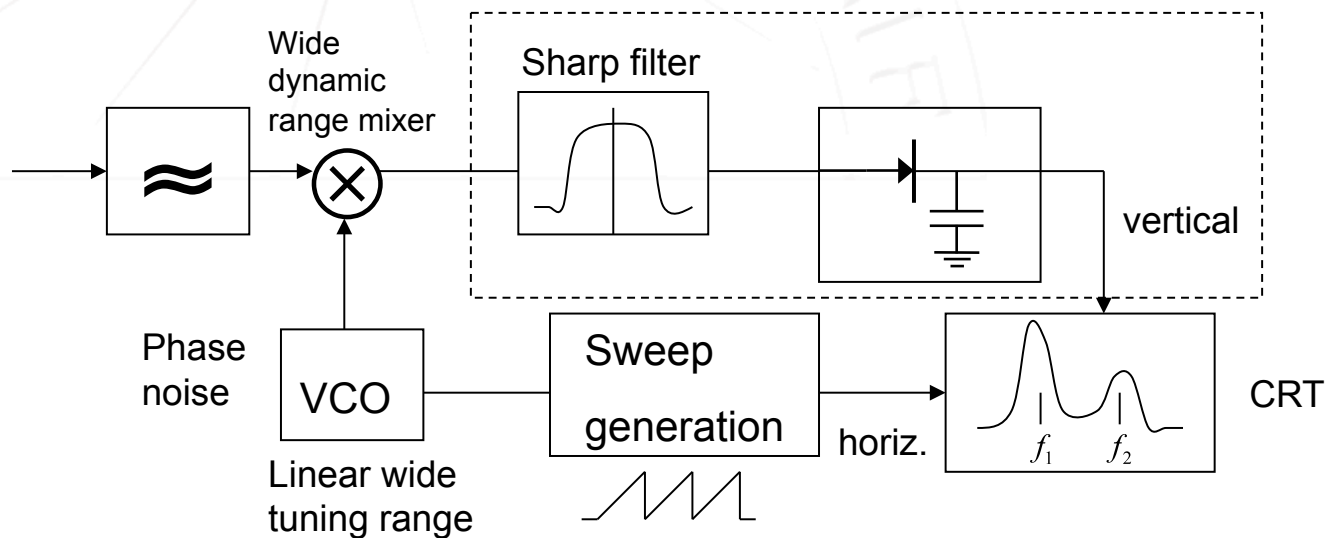

EECS 242: Current Commutating Active Mixers

Professor Ali M Niknejad
Advanced Communication Integrated Circuits

University of California, Berkeley

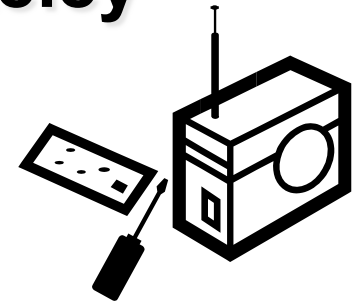

Balanced Mixer

- An unbalanced mixer has a transfer function:

$$y(t) = x(t) \times s(t) = (1 + A(t) \cos(\omega_{RF}t)) \times \begin{Bmatrix} 0 \\ 1 \end{Bmatrix}$$

Has "DC"

- which contains both RF, LO, and IF
- For a single balanced mixer, the LO signal is "balanced" (bipolar) so we have

$$y(t) = x(t) \times s(t) = (1 + A(t) \cos(\omega_{RF}t)) \times \begin{Bmatrix} +1 \\ -1 \end{Bmatrix}$$

Has "DC"


No "DC"

- As a result, the output contains LO but no RF component
- For a double balanced mixer, the LO and RF are balanced so there is no LO or RF leakage

$$y(t) = x(t) \times s(t) = A(t) \cos(\omega_{RF}t) \times \begin{Bmatrix} +1 \\ -1 \end{Bmatrix}$$

Noise in an Ideal Mixers

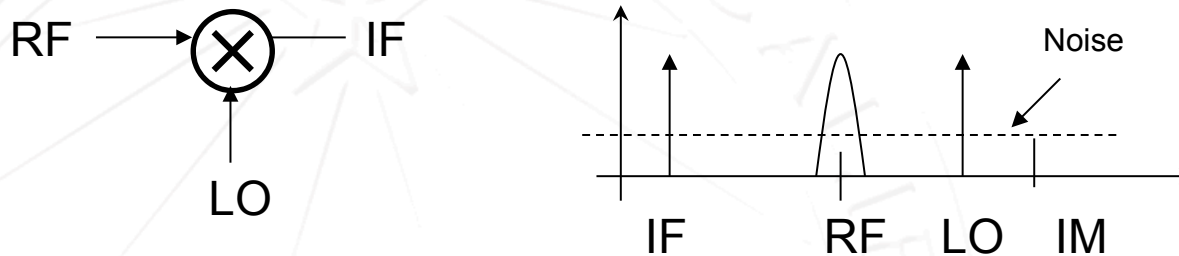Consider the simplest ideal multiplying mixer:



- What's the noise figure for the conversion process?
- Input noise power due to source is kTB where B is the bandwidth of the input signal
- Input signal has power P_s at either the lower or upper sideband

$$SNR_i = \frac{P_s}{kTB}$$

Noise in Ideal Mixers



- At the IF frequency, we have the down-converted signal $G \cdot P_s$ and down-converted noise from two sidebands, LO - IF and LO + IF

$$SNR_o = \frac{G \cdot P_s}{(G' + G'')kTB}$$

For ideal mixer, $G = G' = G''$

$$F = \frac{SNR_i}{SNR_o} = \frac{P_s}{kTB} \frac{2kTB}{P_s} = 2$$


$$NF = 3\text{dB}$$

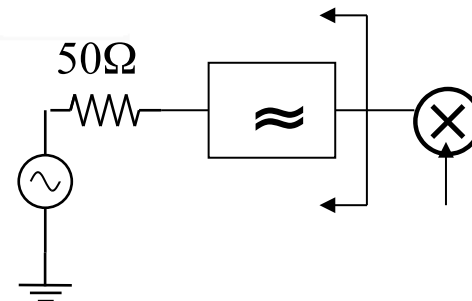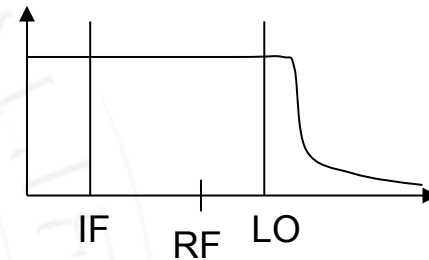

For a real mixer, noise from multiple sidebands can fold into IF frequency & degrade NF

Noise in CMOS Current Commutating Mixer

(After Terrovitis, JSSC)

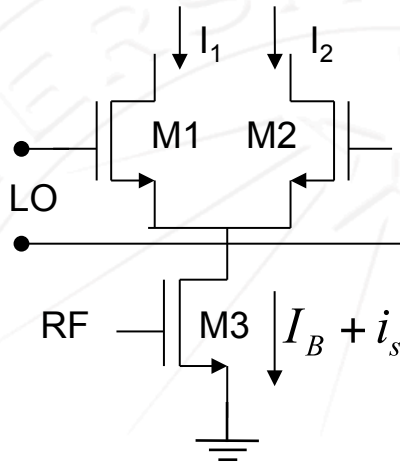


$$I_{o1} = I_1 - I_2 = F(V_{LO}(t), I_B + i_s)$$


Assume i_s is small relative to I_B and perform Taylor series expansion

$$I_{o1} \approx F(V_{LO}(t), I_B) + \frac{\delta F}{\delta I_B}(V_{LO}(t), I_B) \cdot i_s + \dots$$

$$I_{o1} = P_o(t) + P_1(t) \cdot i_s$$

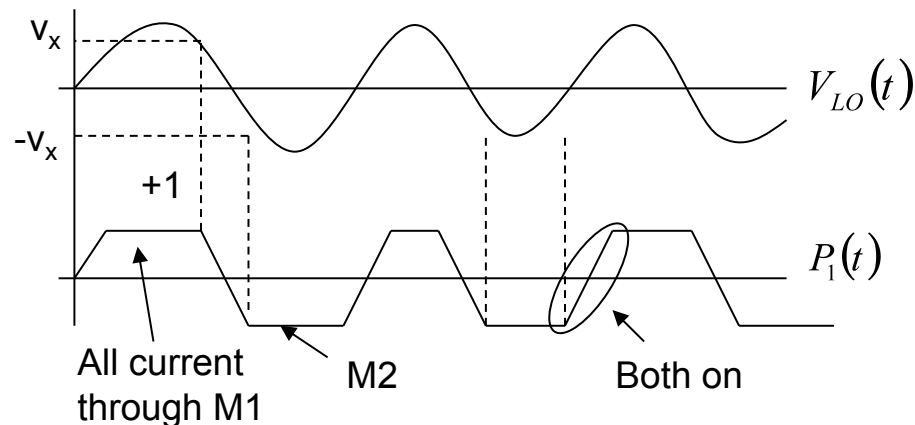

Noise in Current Commutating Mixers

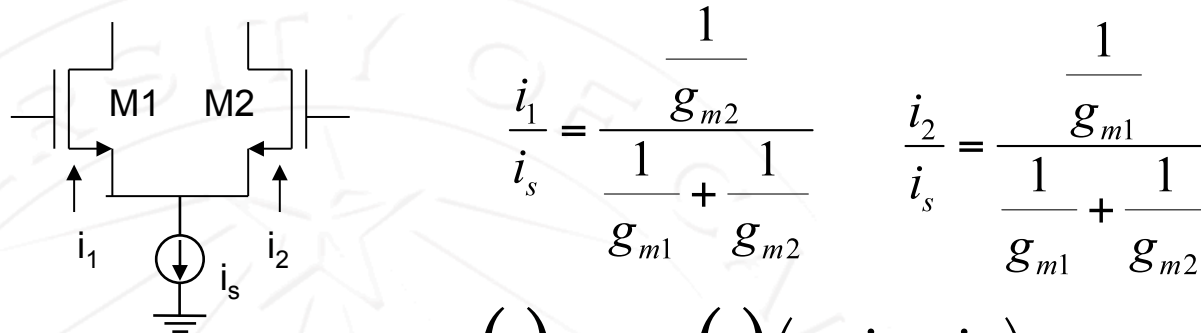

$$\frac{i_1}{i_s} = \frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$\frac{i_2}{i_s} = \frac{\frac{1}{g_{m1}}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}}}$$

$$p_1(t) = \frac{g_{m1}(t) - g_{m2}(t)}{g_{m1}(t) + g_{m2}(t)} \left(= \frac{i_1 - i_2}{i_s} \right)$$

Note that with good device matching


$$p_1(t) = -p_1\left(t + \frac{T_o}{2}\right)$$

Expand $p_1(t)$ into a Fourier series:

$$p_{1,2k} = \frac{1}{T_{LO}} \int_0^{T_{LO}} p_1(t) e^{-j2\pi 2kt/T_{LO}} dt = \int_0^{T_{LO}/2} + \int_{T_{LO}/2}^{T_{LO}} = 0$$

Only odd coefficients of $p_{1,n}$ non-zero

Single Balanced Mixer

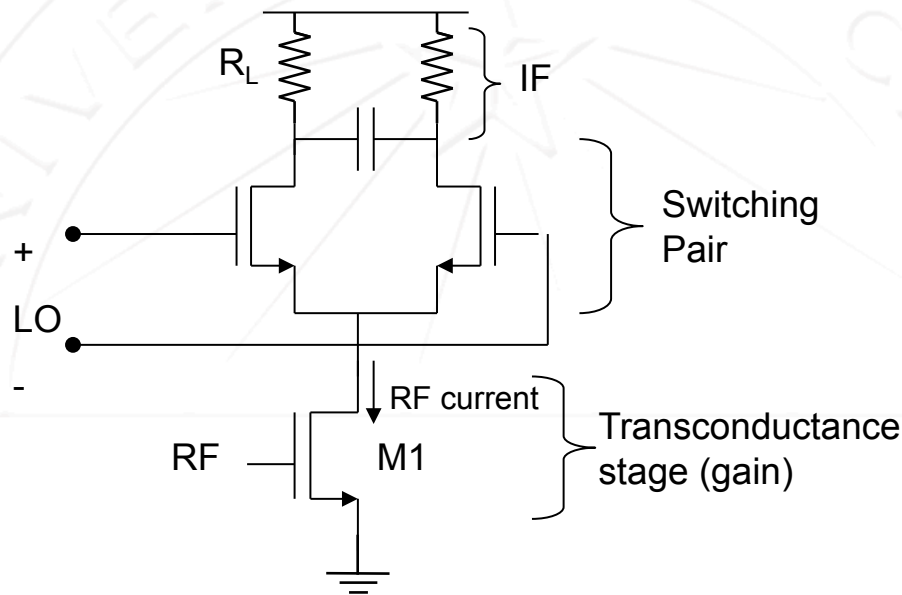

Assume LO signal strong so that current (RF) is alternatively sent to either M₂ or M₃. This is equivalent to multiplying i_{RF} by ± 1 .

$$v_{IF} \approx \text{sign}(V_{LO}) g_m R_L v_{RF} = g(t) g_m R_L v_{RF}$$

Period waveform with period = T_{LO}

Current Commutating Mixer (2)

$$g(t) = \text{square wave} = \frac{4}{\pi} (\cos \omega_{LO} t - \cos 3\omega_{LO} t + \dots)$$

$$\text{Let } v_{RF} = A \cos \omega_{RF} t$$


$$LPF(v_{IF}) = \frac{4}{\pi} \frac{1}{2} \cos(\omega_{RF} - \omega_{LO}) t \cdot g_m R_L \cdot A$$

$$A_v = \frac{\tilde{v}_{IF}}{A} = \frac{2}{\pi} g_m R_L \quad \underline{\text{gain}}$$

LO-RF isolation good, but LO signal appears in output (just a diff pair amp).



Strong LO might desensitize (limit) IF stage (even after filtering).

Double Balanced Mixer

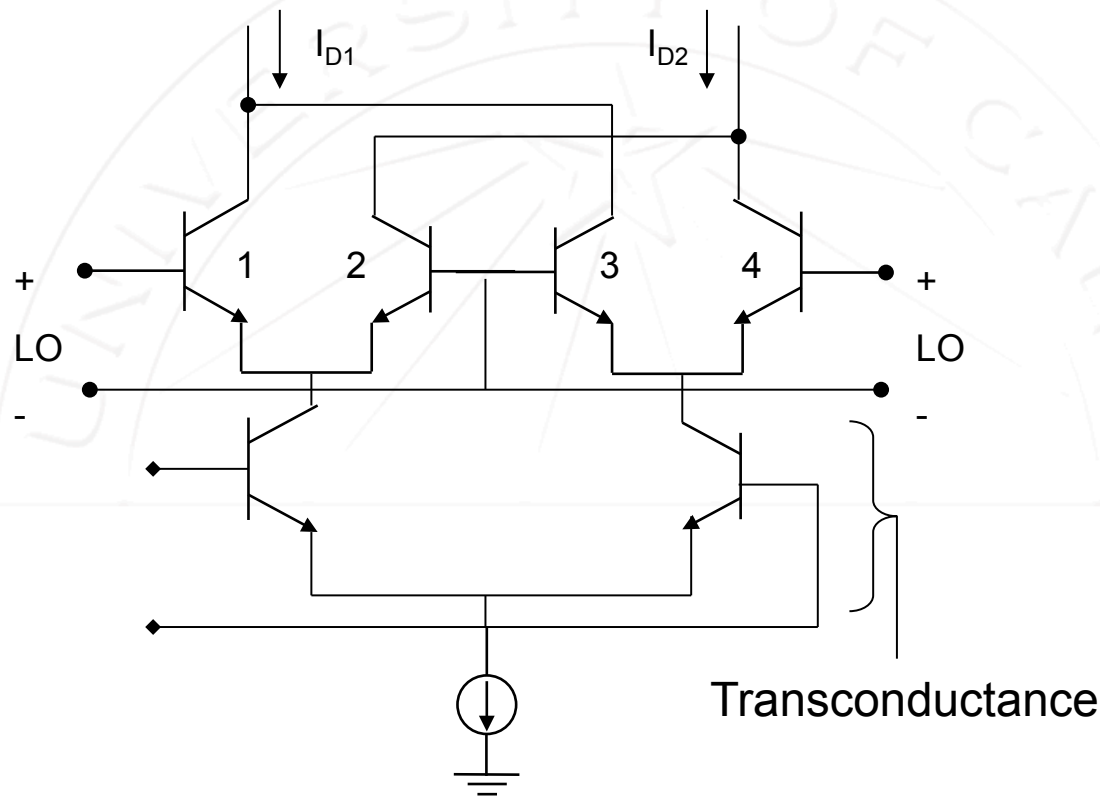


- LO signal is rejected up to matching constraints
- Differential output removes even order non-linearities
- Linearity is improved: Half of signal is processed by each side
- Noise higher than single balanced mixer since no cancellation occurs

Common Gate Input Stage


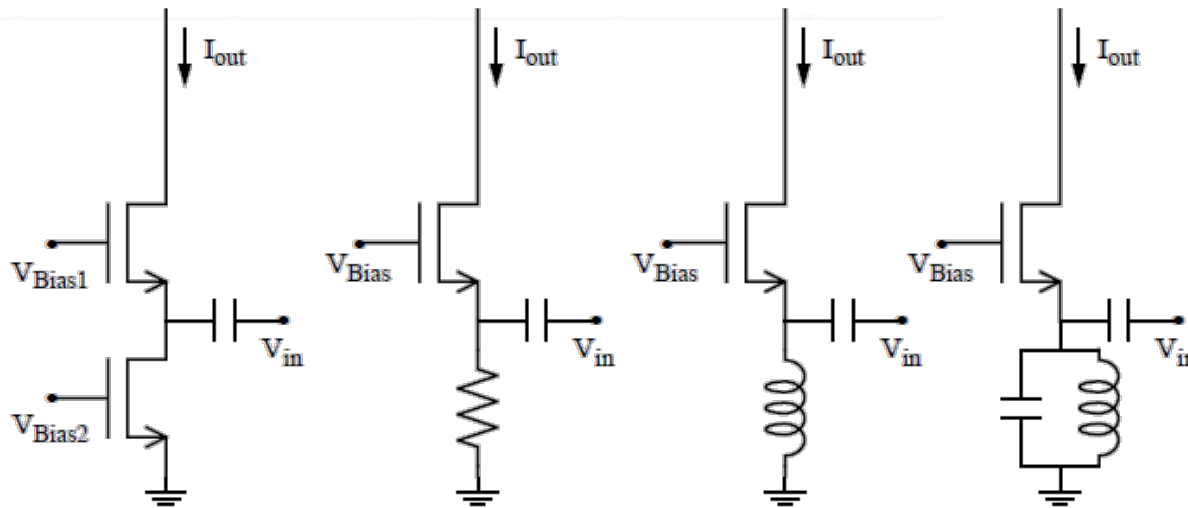
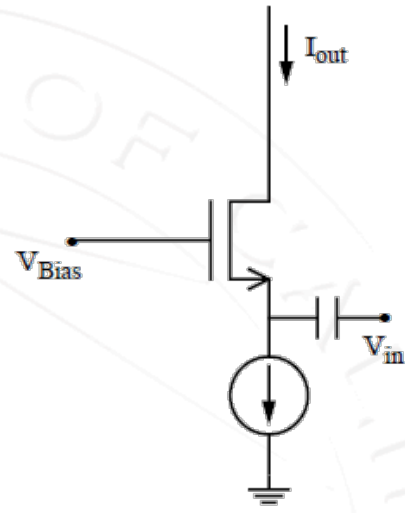


Gilbert Micromixer

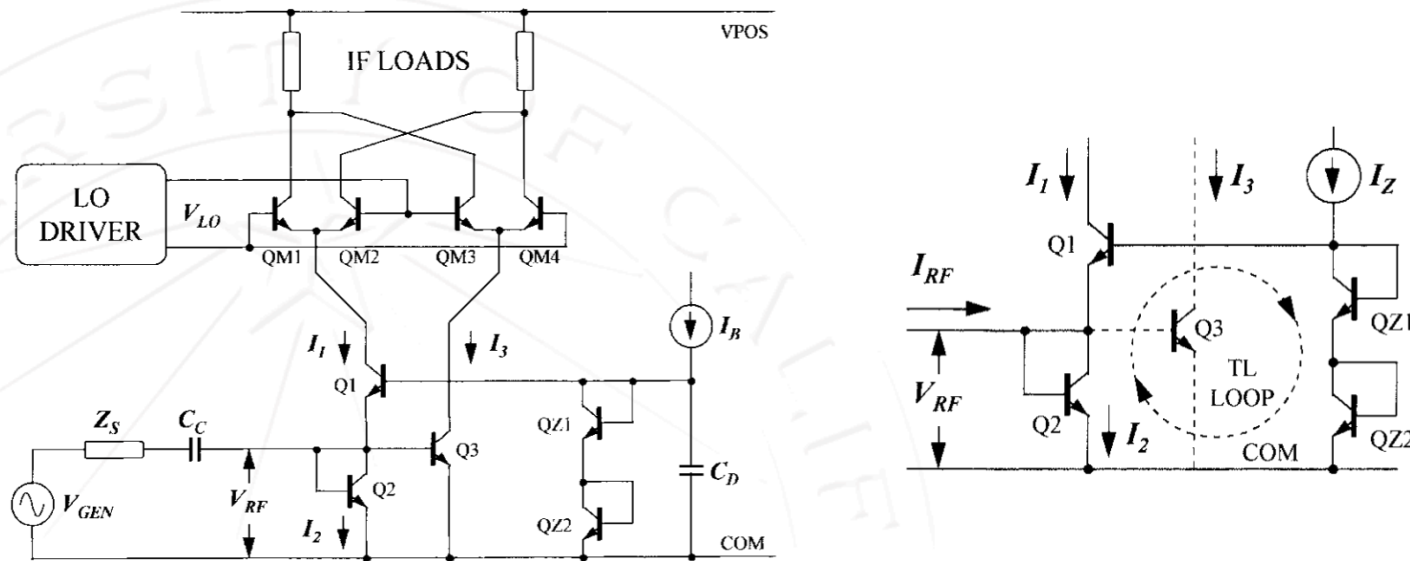


- The LNA output is often single-ended. A good balanced RF signal is required to minimize the feedthrough to the output. LC bridge circuits can be used, but the bandwidth is limited. A transformer is a good choice for this, but bulky and bandwidth is still limited.
- A broadband single-ended to differential conversion stage is used to generate highly balanced signals. Gm stage is Class AB.

Active and Passive Balun

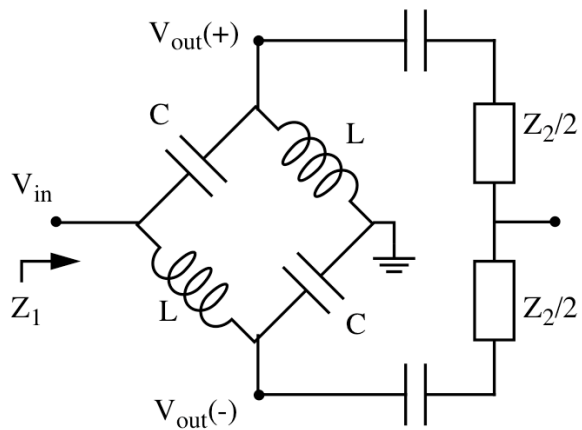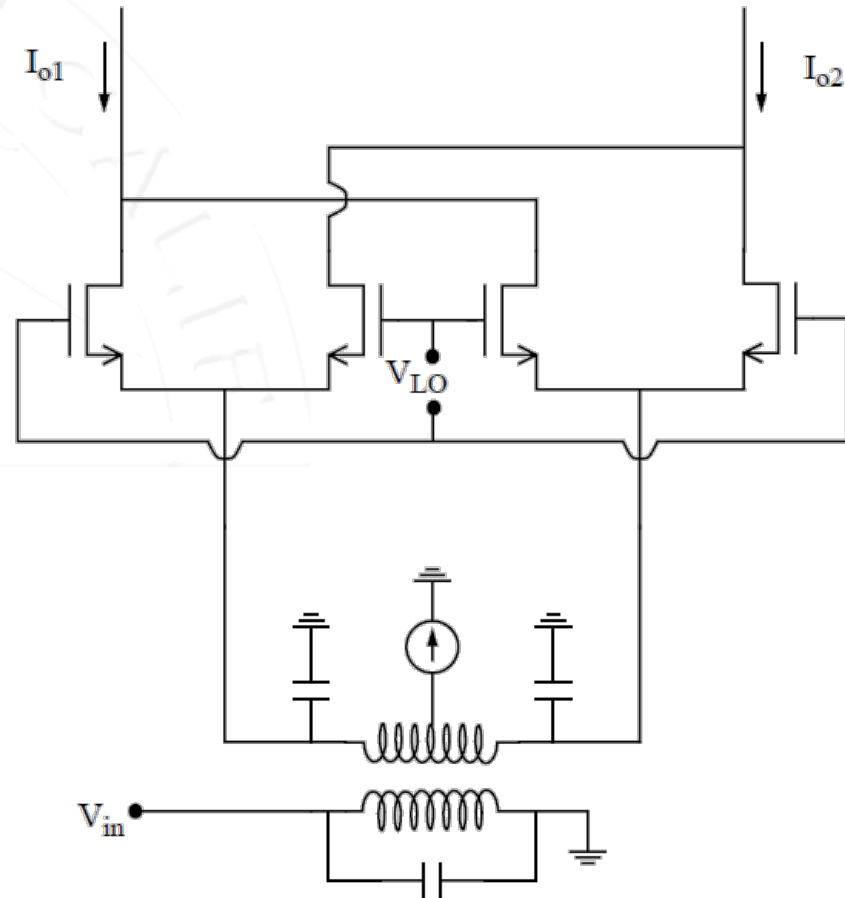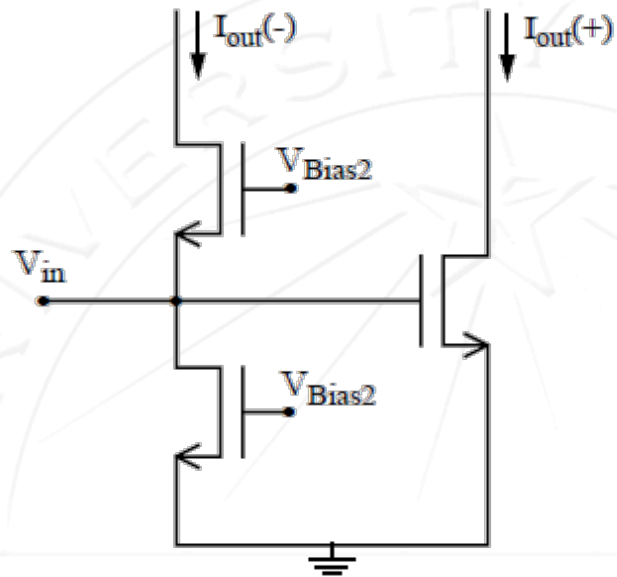


Bleeding the Switching Core

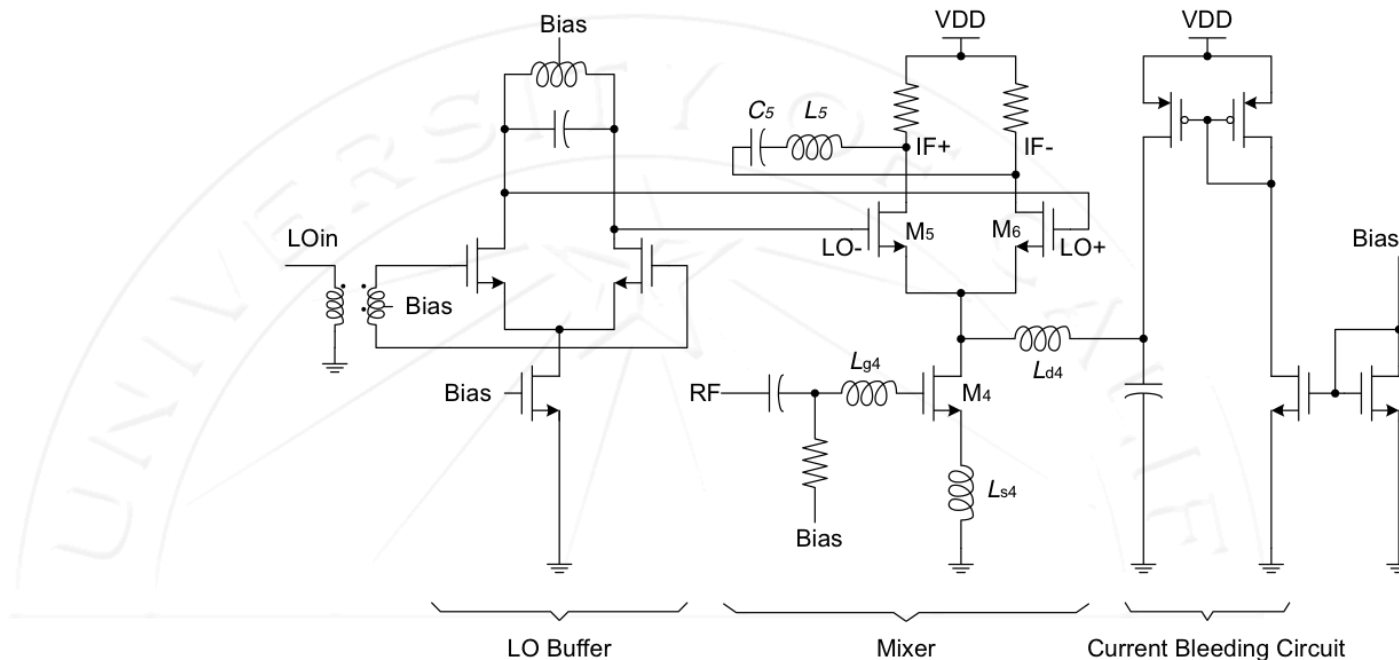


- Large currents are good for the gm stage (noise, conversion gain), but require large devices in the switching core → hard to switch due to capacitance or requires a large LO (large $V_{gs} - V_t$)
- A current source can be used to feed the Gm stage with extra current.

[3] J. Park, C.-H. Lee, B.-S. Kim, J. Laskar, "Design and Analysis of Low Flicker Noise CMOS Mixers for Direct-Conversion Receivers," *IEEE Trans. Microwave Theory Tech.*, vol.54, no.12, pp. 4372-4380, December 2006




Current Re-Use Gm Stage

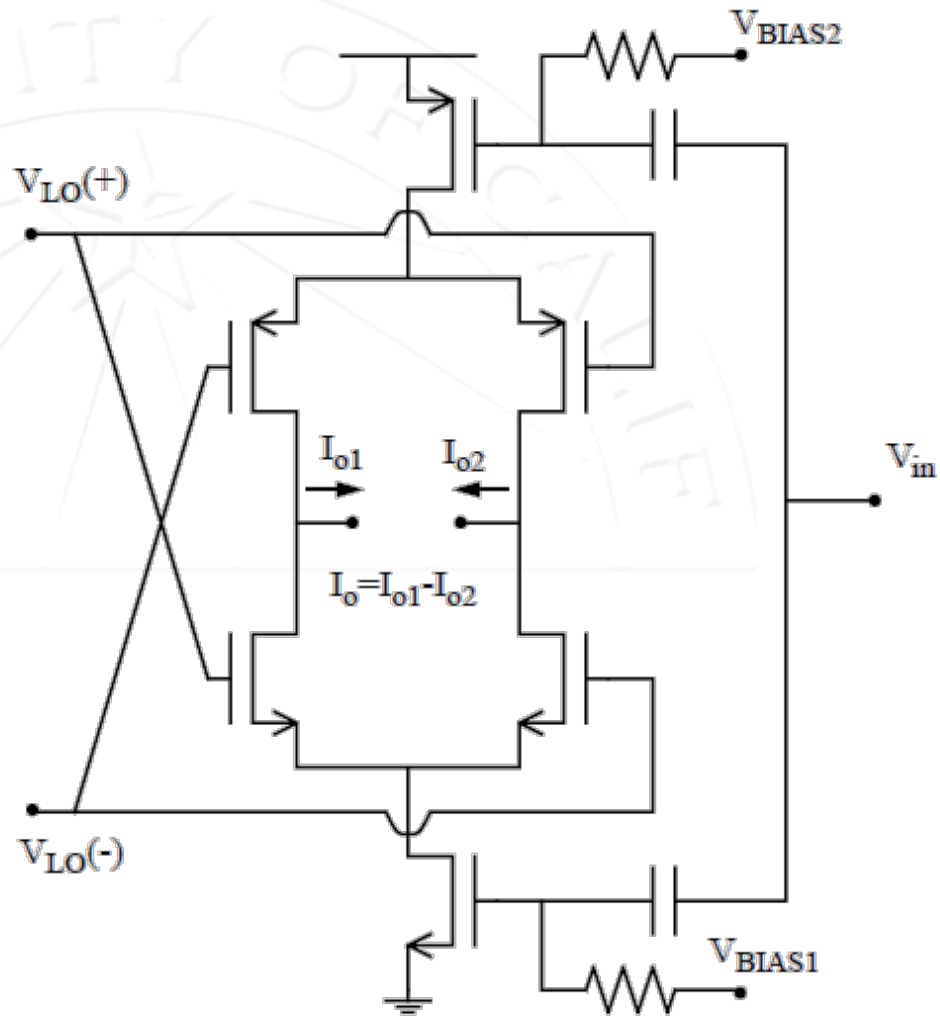


Single, Dual, and Back Gate

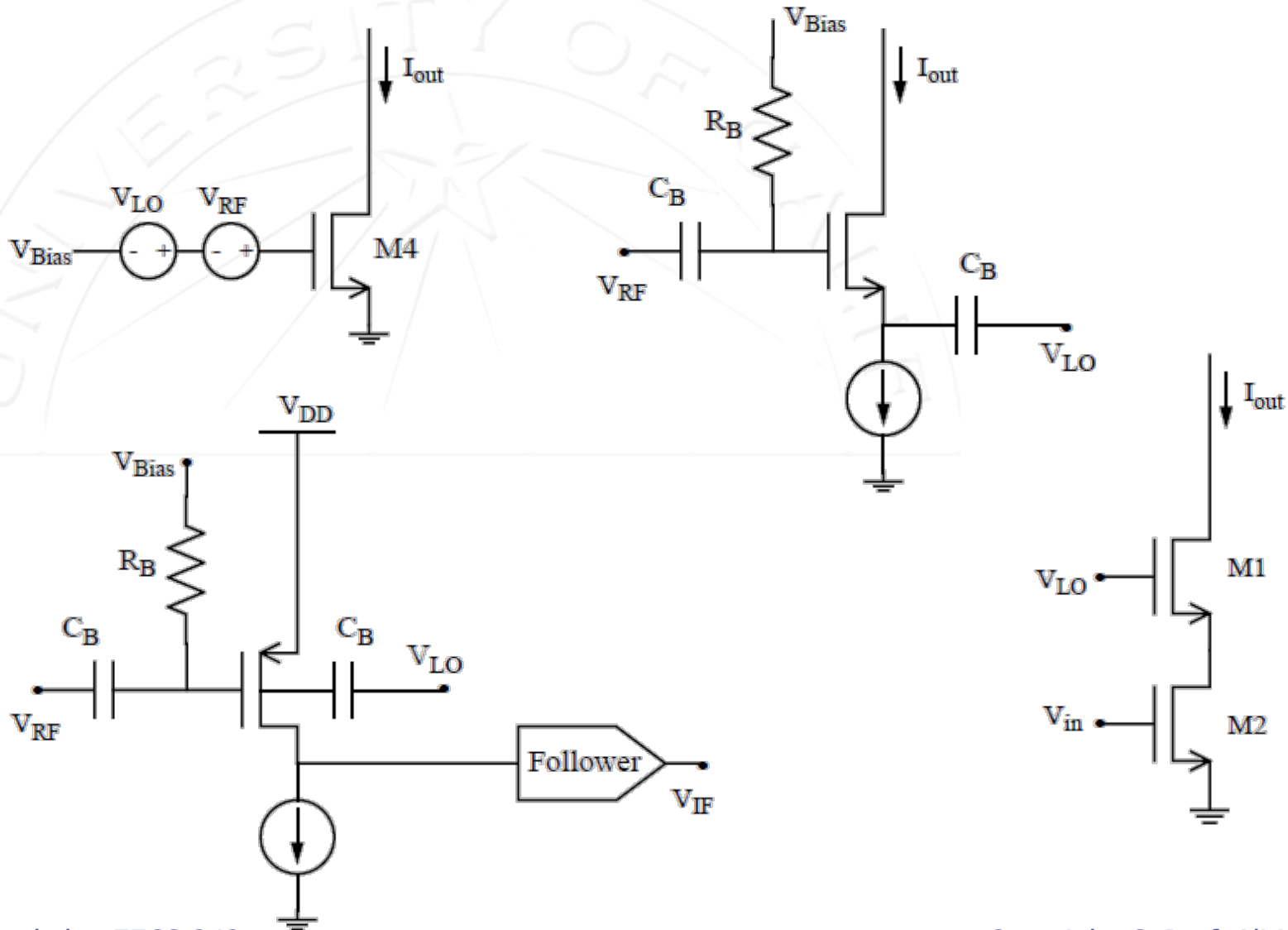


Passive Mixers/Sampling

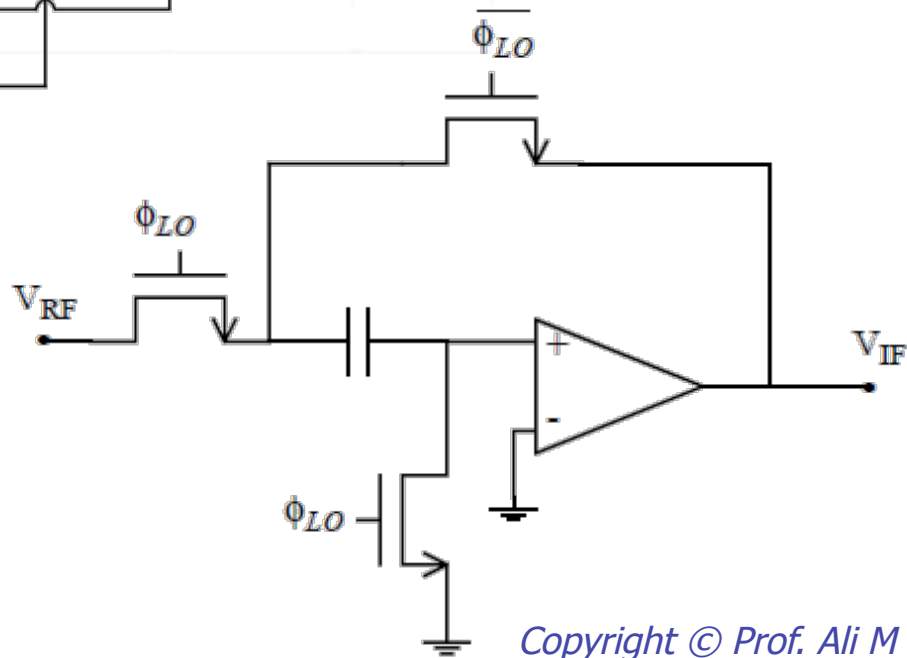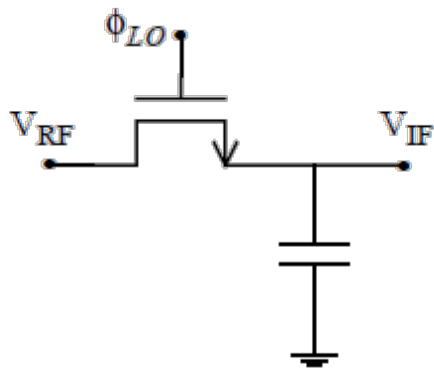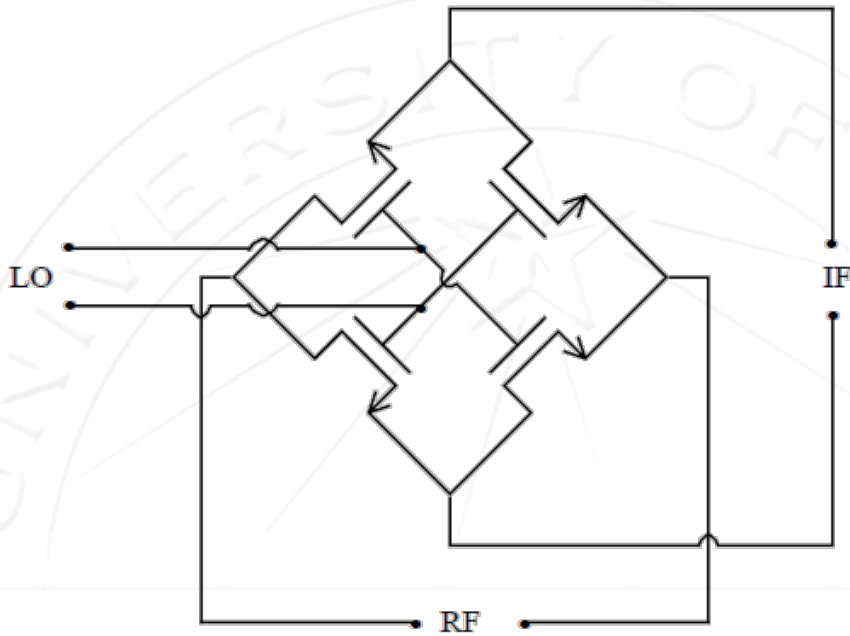


Sub-Sampling Mixers

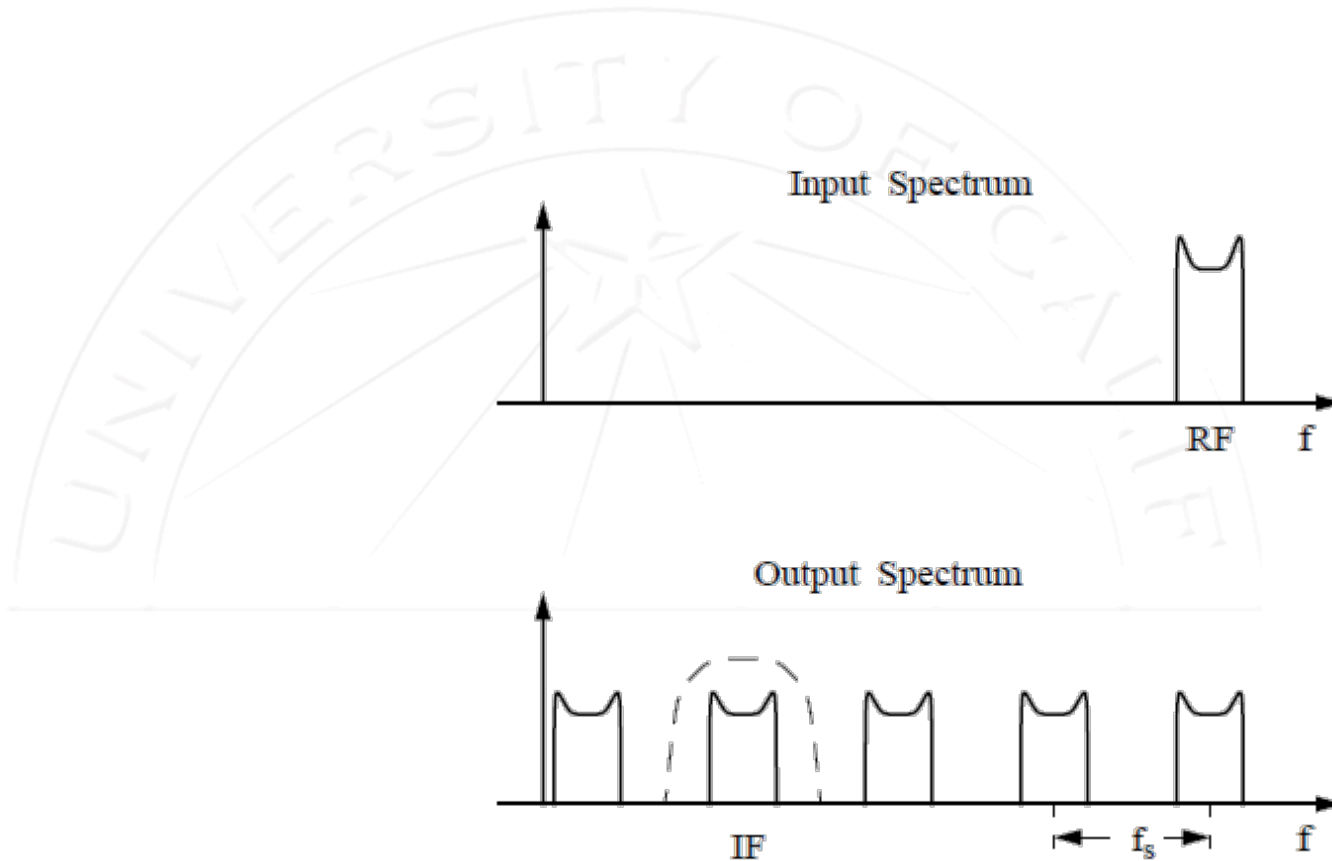

Triode Region Mixer

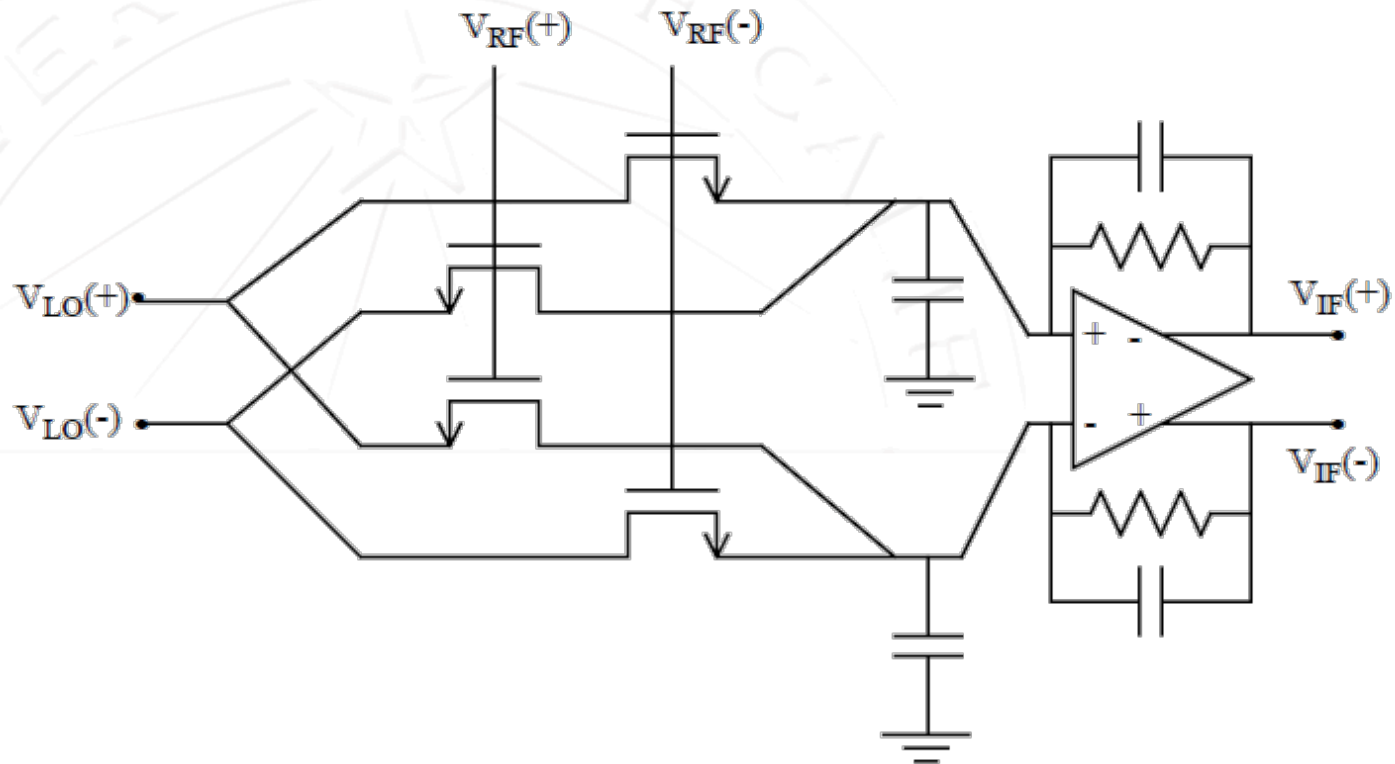

Improved Linearity

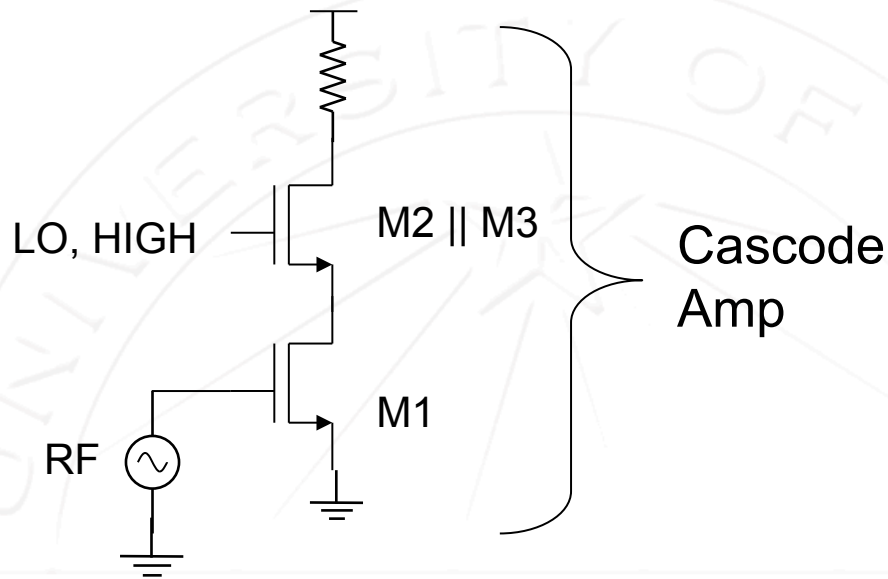


To improve M_1 , apply local series feedback


$$Z_s = j\omega L$$

Provide input matching and feedback

⇒ No DC headroom sacrificed

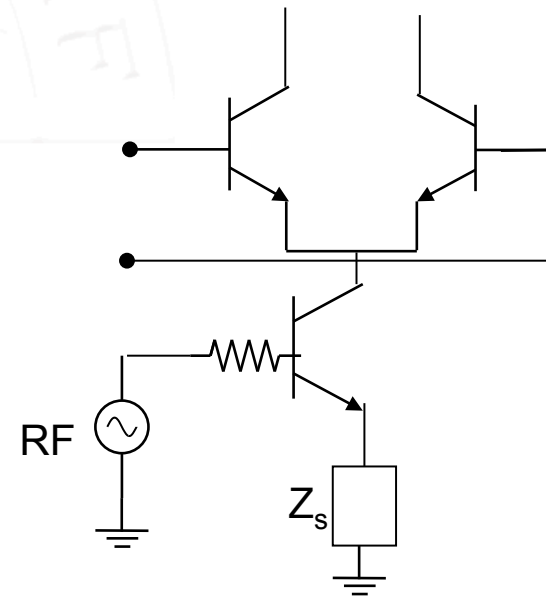

Recap: CMOS Mixer Operation

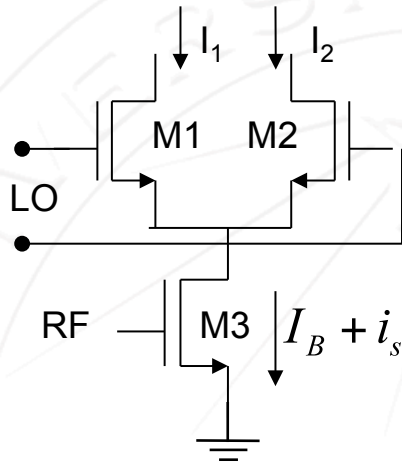

$$\begin{aligned}
 I_{o1} &= I_1 - I_2 = F(V_{LO}(t), I_B + i_s) \\
 &\approx F(V_{LO}(t), I_B) + \frac{\partial F}{\partial I_B}(V_{LO}(t), I_B) \cdot i_s + \dots \\
 &= P_o(t) + P_1(t) \cdot i_s + \dots
 \end{aligned}$$

$$P_1(t) = \frac{g_{m1}(t) - g_{m2}(t)}{g_{m1}(t) + g_{m2}(t)} \quad \text{Periodic}$$

Fourier Series expansion

$$P_{1,2k} \equiv 0 \quad P_1(t) = -P_1\left(t + \frac{T_{LO}}{2}\right)$$

References

- **Noise in current-commutating CMOS mixers**
Terrovitis, M.T.; Meyer, R.G.;
[Solid-State Circuits, IEEE Journal of](#)
Volume 34, Issue 6, June 1999 Page(s):772 - 783
- **Intermodulation distortion in current-commutating CMOS mixers** Terrovitis, M.T.; Meyer, R.G.;
[Solid-State Circuits, IEEE Journal of](#)
Volume 35, Issue 10, Oct. 2000 Page(s):1461 – 1473
- **A systematic approach to the analysis of noise in mixers**
Hull, C.D.; Meyer, R.G.;
[Circuits and Systems I: Fundamental Theory and Applications, IEEE Transactions on \[see also Circuits and Systems I: Regular Papers, IEEE Transactions on\]](#)
Volume 40, Issue 12, Dec. 1993 Page(s):909 - 919