
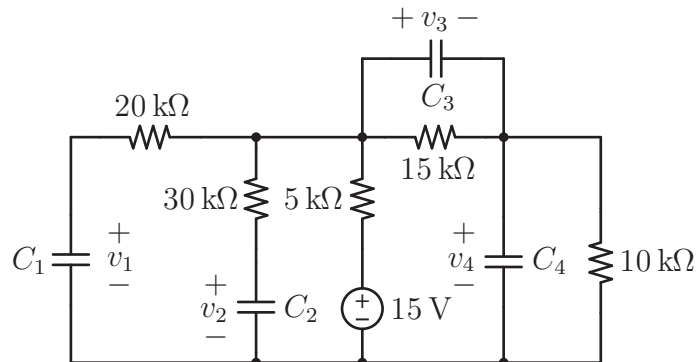


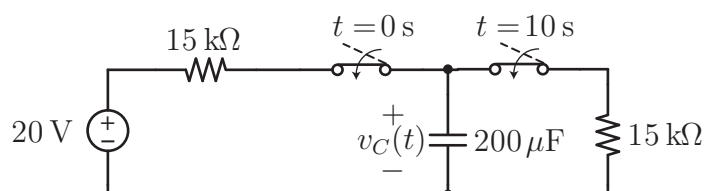Problem Set 5 (rev B)
Due Friday (5pm), March 16, 2012


- The voltage across a 0.2 mF capacitor was 20 V until a switch was opened at $t = 0$, causing the voltage to vary with time as $v(t) = (60 - 40e^{-5t})\text{ V}$ for $t > 0$.
 - Did the switch action result in an instantaneous change in $v(t)$? Why or why not?
 - Did the switch action result in an instantaneous change in the current $i(t)$? Why or why not?
 - How much energy was initially stored in the capacitor at $t = 0$?
 - How much energy will be stored in the capacitor at $t = \infty$?
- Determine the voltages v_1 , v_2 , v_3 , and v_4 for the following circuit under DC conditions.




- Suppose you wanted to store enough energy in a capacitor so that you can run your 1.5 kW oven for 40 minutes. How big is the required capacitance if you can charge it up to 200 V ? How much charge is that? What are the capacitor dimensions if you build it as a parallel plate capacitor with a dielectric whose relative permeability is $\epsilon_r = 15$ and whose thickness is $1\text{ }\mu\text{m}$?
- In the following circuit, suppose that both switches have been open for a long time prior to $t = 0$. Then switch 1 closes at $t = 0$, followed by switch 2 at $t = 10\text{ s}$. Plot $v_C(t)$ for $t \geq 0$, assuming that $v_C(0) = 0$.



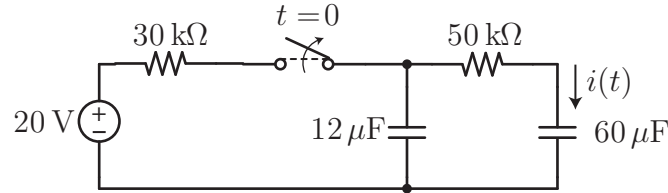
5. In the following circuit, the switch has been closed for a long time before it opens at $t = 0$. Determine $i(t)$ for $t \geq 0$.



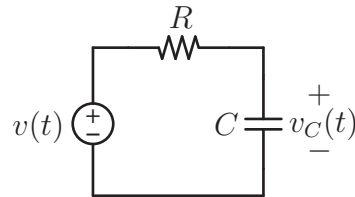
6. Suppose the voltage source in the following circuit is defined by a ramp function, such that $v(t) = 0$ for $t < 0$ and $v(t) = t$ for $t \geq 0$. If $v_C(0) = 0$, derive an expression for $v_C(t)$ for $t \geq 0$ and sketch it to scale versus time. Consider trying a particular solution of the form $v_C(t) = A + Bt$.



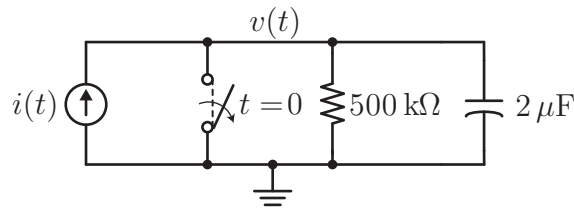
7. In the following circuit, the current source has an exponential characteristic $i(t) = 10e^{-t}\mu\text{A}$. (a) Write the differential equation for the node $v(t)$. (b) What is the time constant? Write the form of the complementary solution. (c) Usually we would want to try a particular solution of the form $v_p(t) = Ke^{-t}$, since the forcing function is exponential. Why won't that work here? (d) Using the form $v_p(t) = Kte^{-t}$ instead, find the particular solution. Then find the complete solution for $v(t)$ by combining your solution with that from (b).



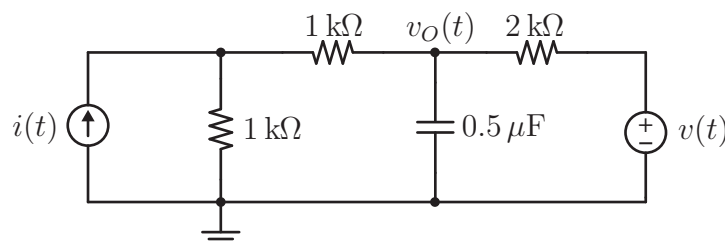8. Suppose that the sources in the following circuit both undergo step transitions at $t = 0$. Prior to this, both sources are off, and the capacitor is uncharged. For $t \geq 0$, $i(t) = 1\text{ mA}$ and $v(t) = 1\text{ V}$. Use superposition to determine $v_O(t)$ for all time.



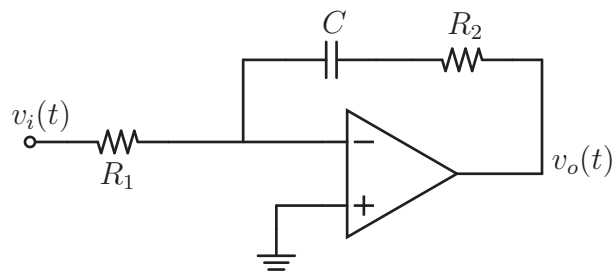9. Relate $v_o(t)$ to $v_i(t)$ in the following circuit. Assume that $v_C = 0$ at $t = 0$.



10. Relate $i_o(t)$ to $v_i(t)$ in the following circuit. Assume that $v_C = 0$ at $t = 0$.

