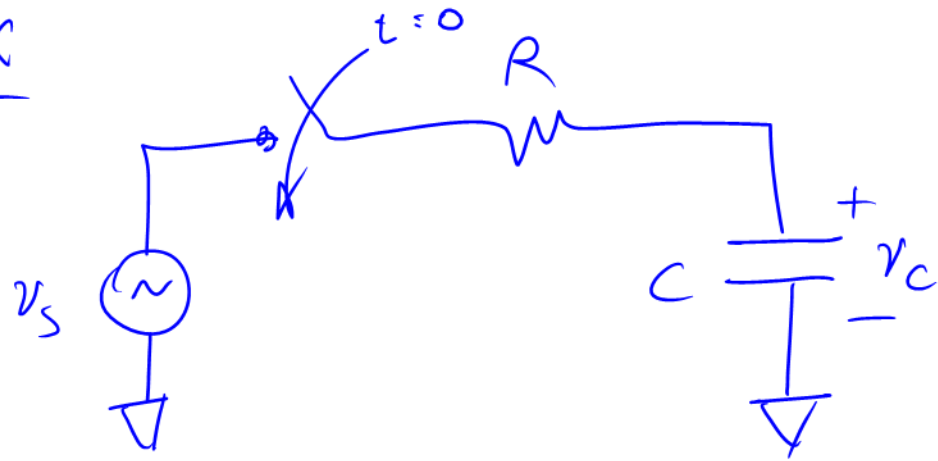


EX



$$V_s = V_0 \cos \omega t$$

$$v_c(0) = 0V$$

STEP 1 SETUP NODAL EQ.

BY INSPECTION

$$v_s = iR + v_c$$

$$v_s = RC \frac{dv_c}{dt} + v_c$$

GOVERNING EQ



KVL

$$i = i_c = C \frac{dv_c}{dt}$$

$$V_c + RC \frac{dV_c}{dt} = V_s$$

STEP 2 : FIND THE HOMOGENEOUS (ZERO INPUT)
SOLUTION

$$V_h + RC \frac{dV_h}{dt} = 0 \quad \text{"NATURAL" RESP}$$

$$V_h = A e^{Bt} \quad V_h' = A \cdot B e^{Bt}$$

$$\cancel{A e^{Bt}} + RC \cancel{A \cdot B \cdot e^{Bt}} = 0$$

$$1 + BRC = 0$$

$$B = -1/RC$$

$$V_h = A e^{-t/\tau}$$

$\tau = RC$
TIME CONSTANT
OF CIRCUIT

STEP 3

FORCED RESPONSE

$$V_f + RC \frac{dV_f}{dt} = v_s = V_0 \cos \omega t$$

TRY

$$V_f = A \cos \omega t$$

$$V_f' = -A \omega \sin \omega t$$

$$A \cos \omega t + RC \cdot (-A \omega \sin \omega t) \neq V_0 \cos \omega t$$

TRY

$$V_f = A \cos \omega t + B \sin \omega t$$

CONST TERM

d/dt TERM

$$V_f' = -A \omega \sin \omega t + B \omega \cos \omega t$$

$$A \cos \omega t + B \sin \omega t + RC (-A \omega \sin \omega t + B \omega \cos \omega t) =$$

cos > $\sum \cos \text{ TERMS} = V_0$
 $A + \tau B \omega = V_0$

$\sum \sin \text{ TERMS} = 0$
 $-A \omega \tau = 0$
 $B = A \omega \tau$

$$B = A \omega \tau$$

$$A + \tau \omega (A \omega \tau) = V_0$$

$$A = \frac{V_0}{1 + (\omega \tau)^2}$$

$$B = \frac{\omega \tau V_0}{1 + (\omega \tau)^2}$$

$$V_f(t) = \frac{V_0}{1 + (\omega \tau)^2} (\cos \omega t + \omega \tau \sin \omega t)$$

$$\cos x \cos y - \sin x \sin y = \cos(x + y)$$

$$V_f(t) = \frac{V_0}{1 + (\omega\tau)^2} (\cos \omega t + \omega\tau \sin \omega t)$$

$$= \frac{V_0}{1 + (\omega\tau)^2} A \cos(\omega t + \phi)$$

$$A = \sqrt{1^2 + \omega^2\tau^2} = \sqrt{1 + (\omega\tau)^2}$$

$$\phi = -\tan^{-1}(\omega\tau)$$

$$V_f(t) = \frac{V_0}{\underbrace{(1 + (\omega\tau)^2)^{1/2}}_{\text{AMPLITUDE}} \cdot \cos(\omega t + \phi)}$$

AMPLITUDE < V_0

$$\cos 2x = \cos^2 x - \sin^2 x$$

$$\sin^2 x = 1 - \cos^2 x$$

$$= \cos^2 x - 1 + \cos^2 x$$

$$\frac{\cos 2x + 1}{2} = \cos^2 x$$

$$I \cos x + Q \sin x = A \cos(x + \theta)$$

$$= \cos x \cos \theta - \sin x \sin \theta$$

$$I = \cos \theta$$

$$\tan \theta = -\frac{Q}{I}$$

$$Q = -\sin \theta$$

$$I^2 + Q^2 = \cos^2 \theta + \sin^2 \theta = 1 \quad \theta = \tan^{-1}\left(-\frac{Q}{I}\right)$$

STEP 4 COMPLETE SOLUTION


$$V_c(t) = V_h(t) + V_f(t)$$

$$= K e^{-t/\tau} + A \cos(\omega t + \phi)$$

STEP 5 USE I.C. TO RESOLVE UNKNOWN


$$V_c(0) = 0V = K + A \cos \phi$$

$$K = -A \cos \phi$$

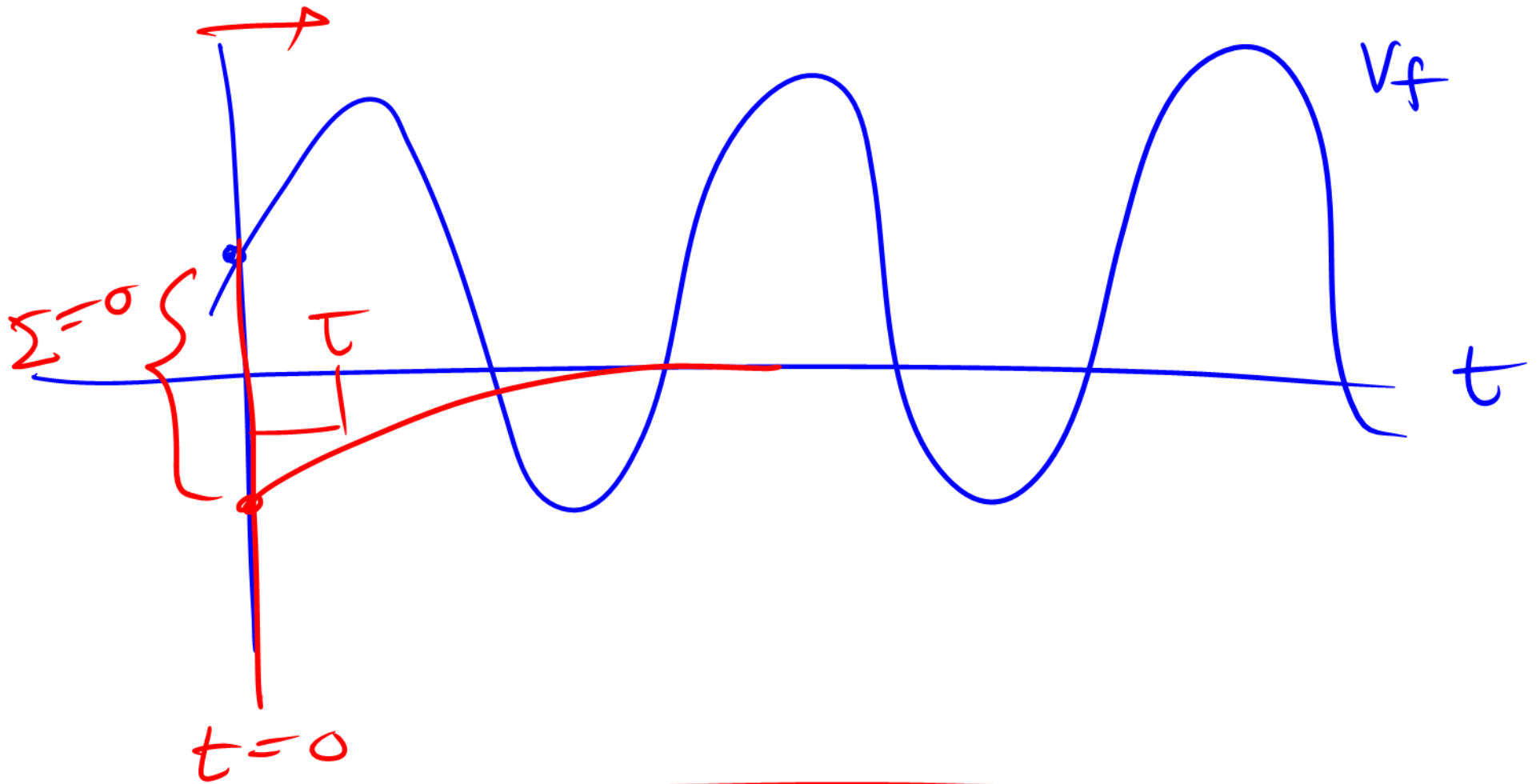

$t=0$
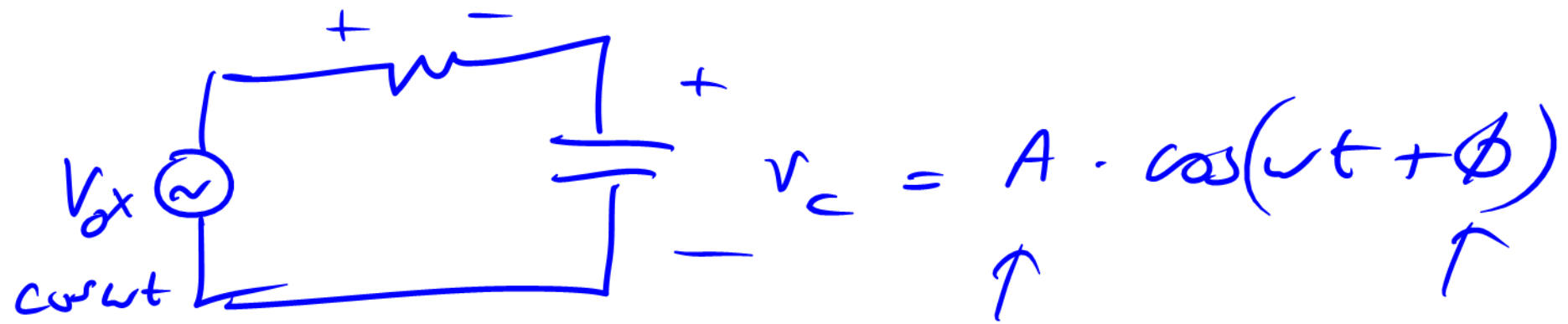
$$A = \frac{V_0}{\sqrt{1 + (\omega\tau)^2}}$$



$$A = \frac{V_0}{\sqrt{1 + (\omega\tau)^2}}$$

ω
 FREQ OF SOURCE
 τ
 TIME CONSTANT OF CIRCUIT

LOWⁿ FREQ INPUT

$$\omega T \ll 1$$

$$\omega \ll 1/\tau$$

SAY

$$R = 1\text{K}\Omega \cdot 2\pi$$

$$C = 1\mu\text{F}$$

$$RC = 1\text{ms}$$



$$\frac{1}{RC} = 2\pi \text{K rad/s}$$

$$\omega_c = 2\pi f_c = 2\pi \text{K rad/s}$$

$$f_c = 1\text{KHz}$$

\Rightarrow

$$A = V_o$$

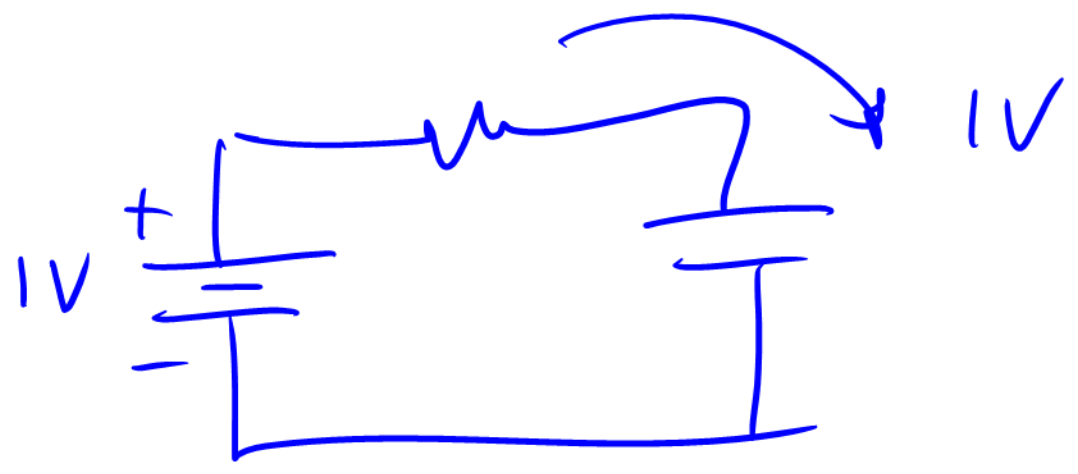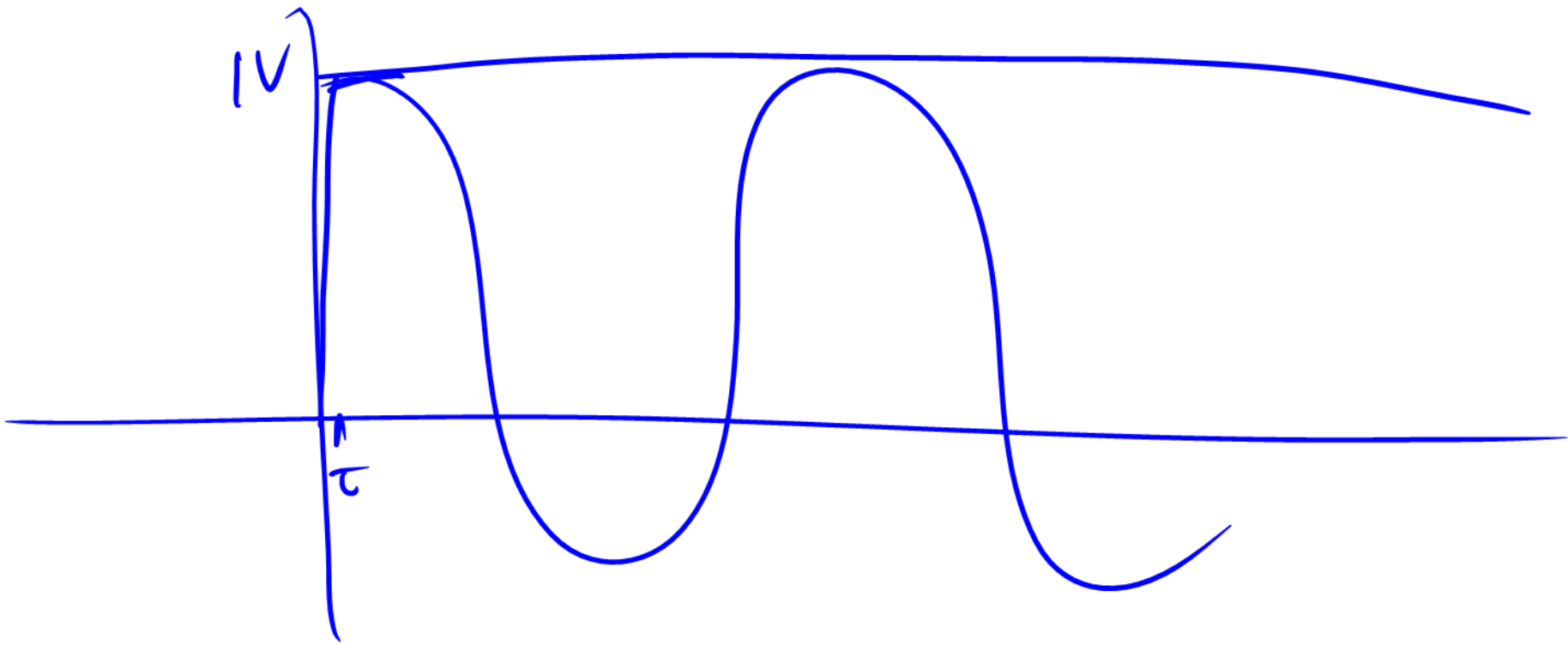

$\omega\tau \gg 1$

HIGH

FREQ

$$f > f_c = 1 \text{ kHz} = \frac{1}{2\pi RC}$$


$$A = \frac{V_o}{\sqrt{1 + (\omega\tau)^2}} \approx \frac{V_o}{\omega\tau}$$


$\gg 1$

$\omega\tau = 1$


CRITICAL FREQ
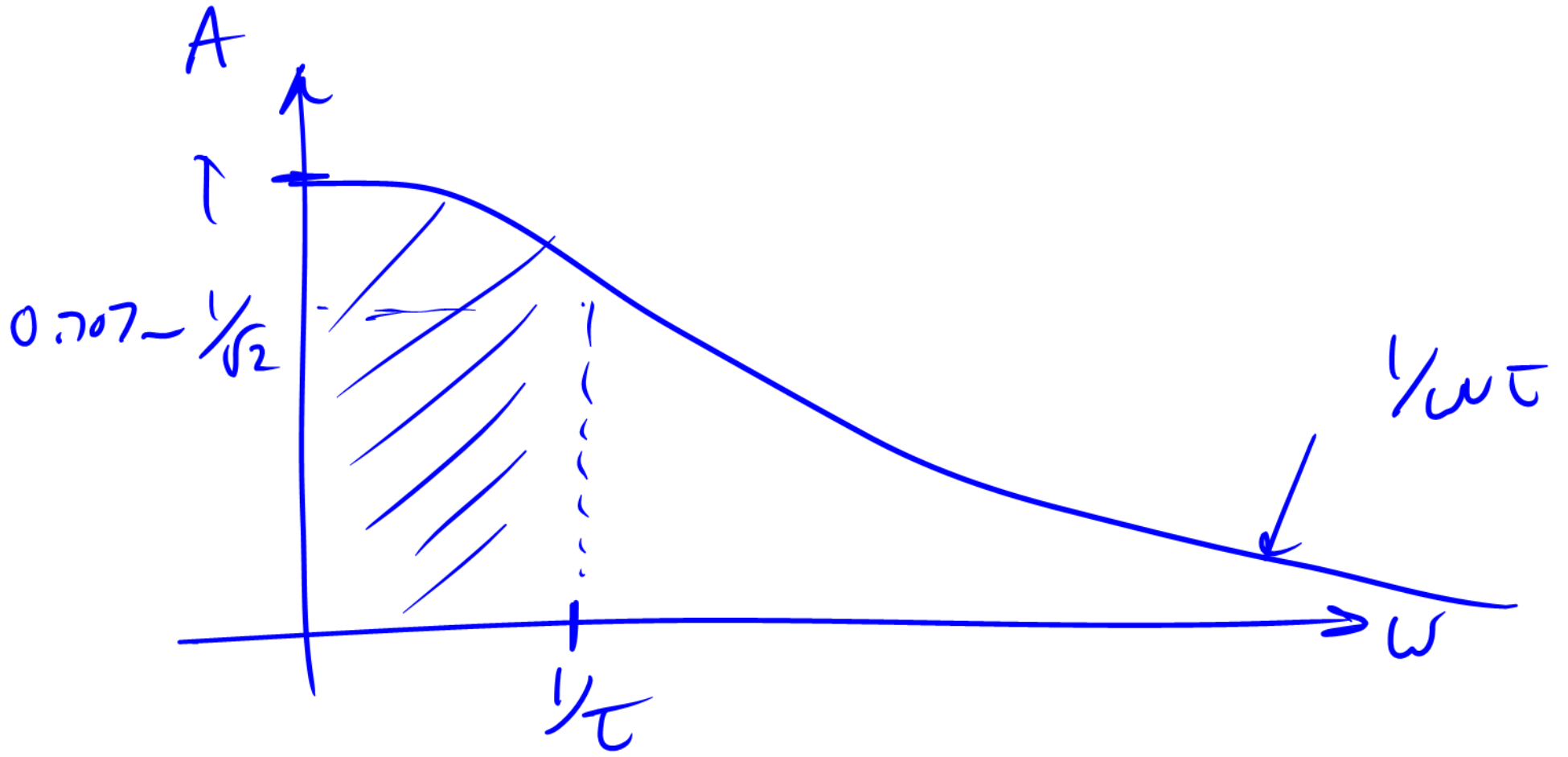
$$A = \frac{V_o}{\sqrt{1+1}} = \frac{V_o}{\sqrt{2}}$$



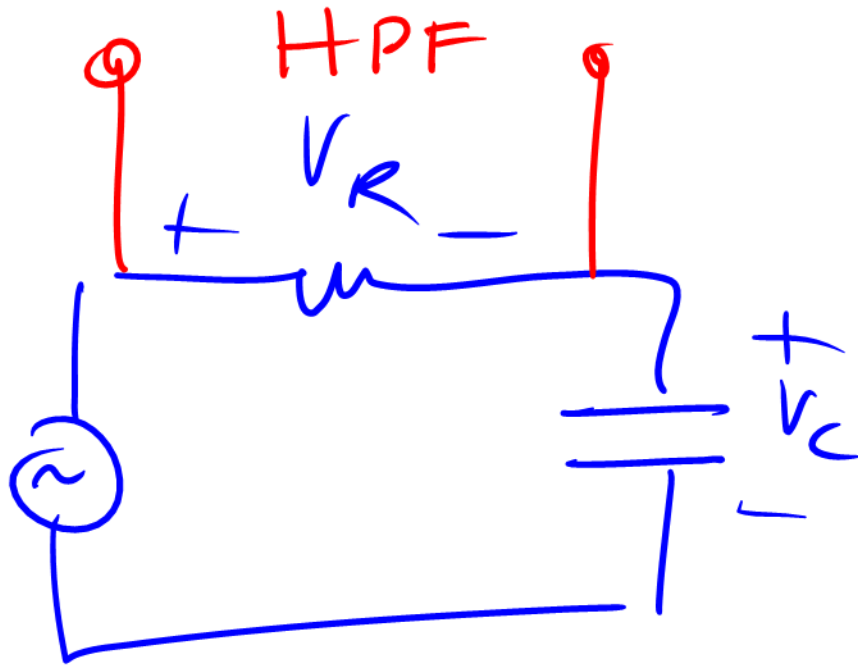

HIGH-PASS
FILTER


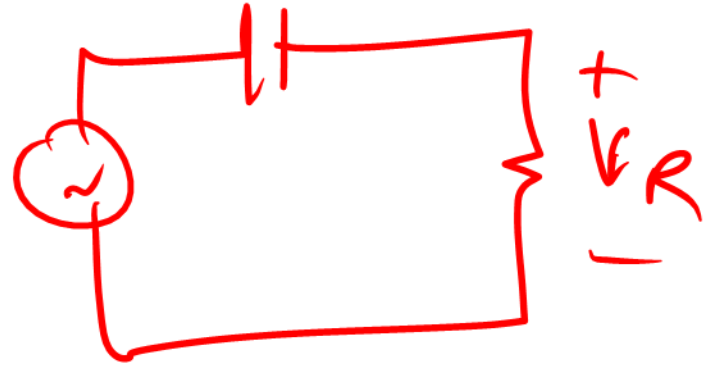


$$V_R + V_C = V_S$$



≈ 0 $\approx V_S$
 $\approx V_S$ ≈ 0

LOW FREQ

HIGH FREQ

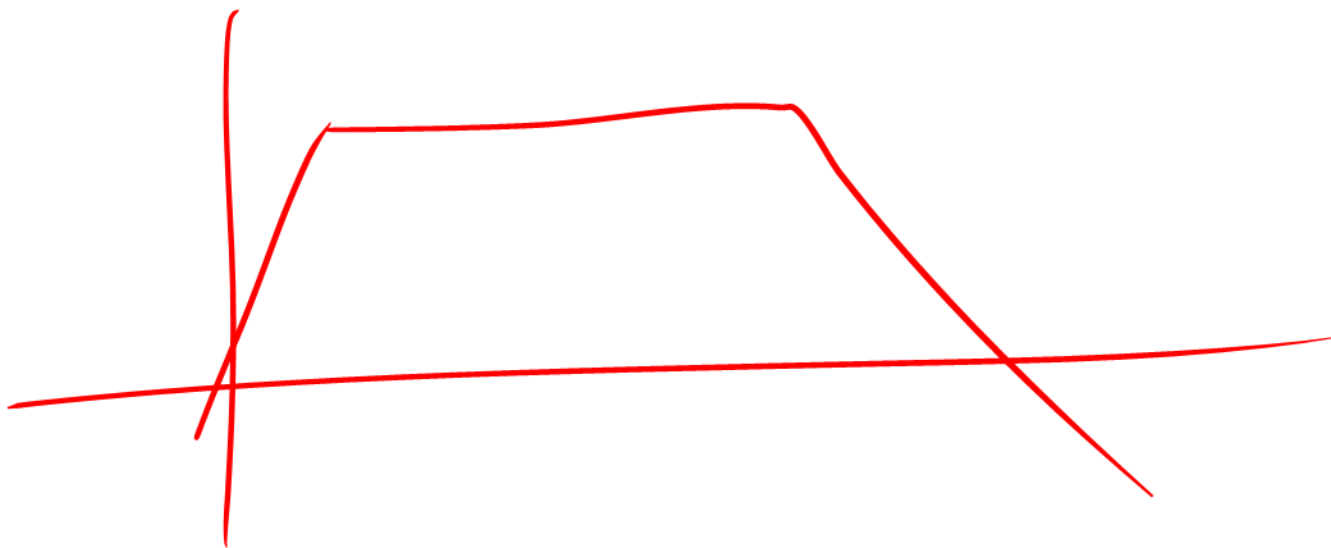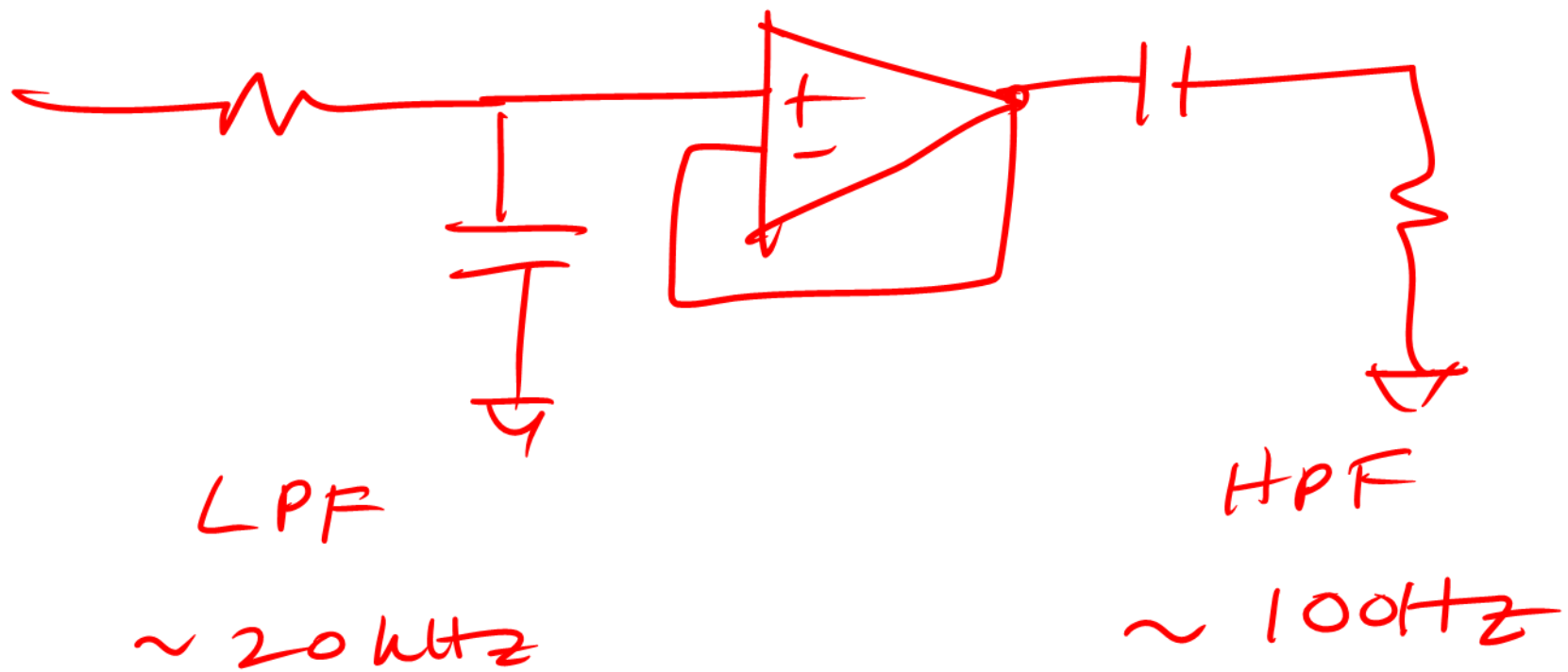

CASCADE FILTER

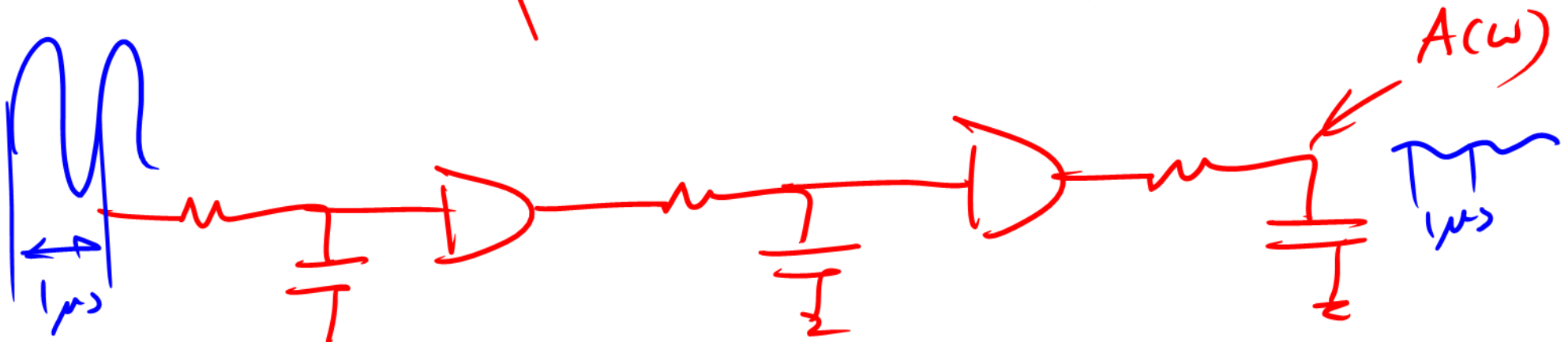
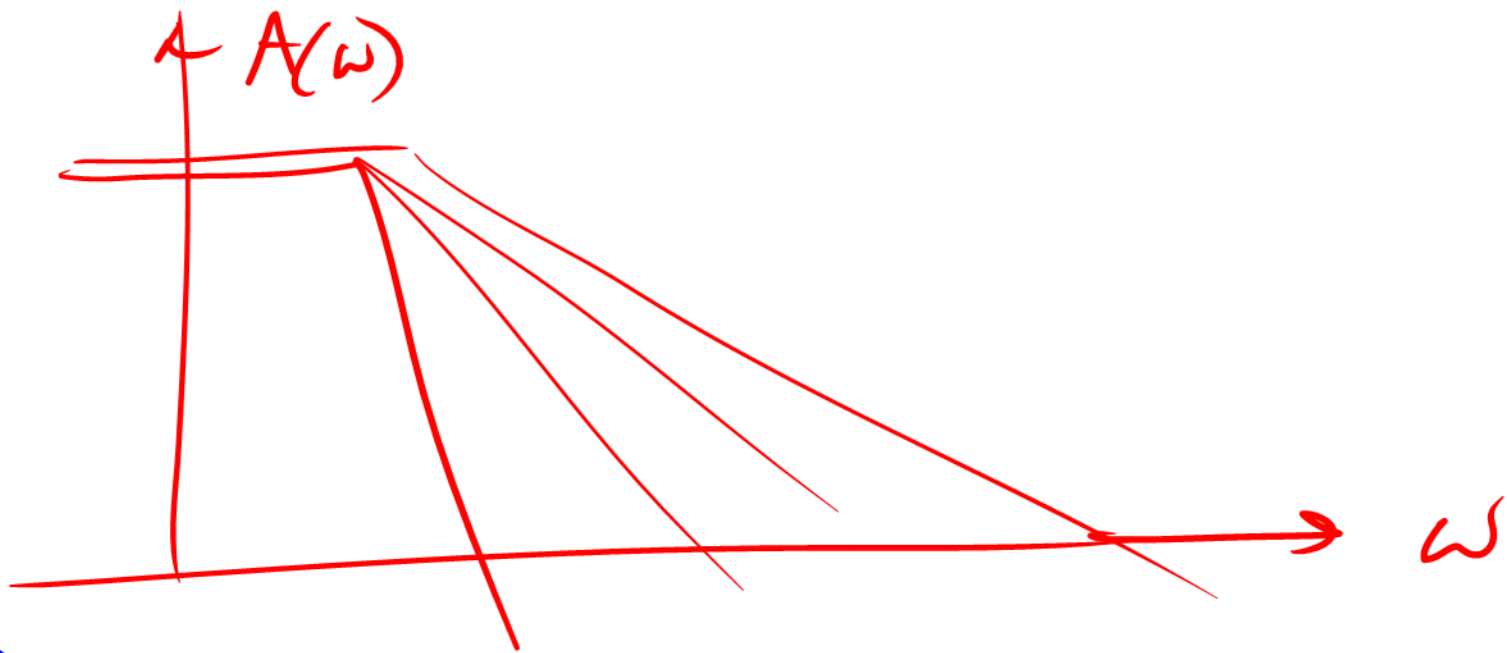


$$\tau = 1\mu s$$

$$\omega\tau = 2\pi \cdot \frac{1}{\mu s} \cdot 1\mu s = \frac{2\pi}{1000}$$

INPUT

+

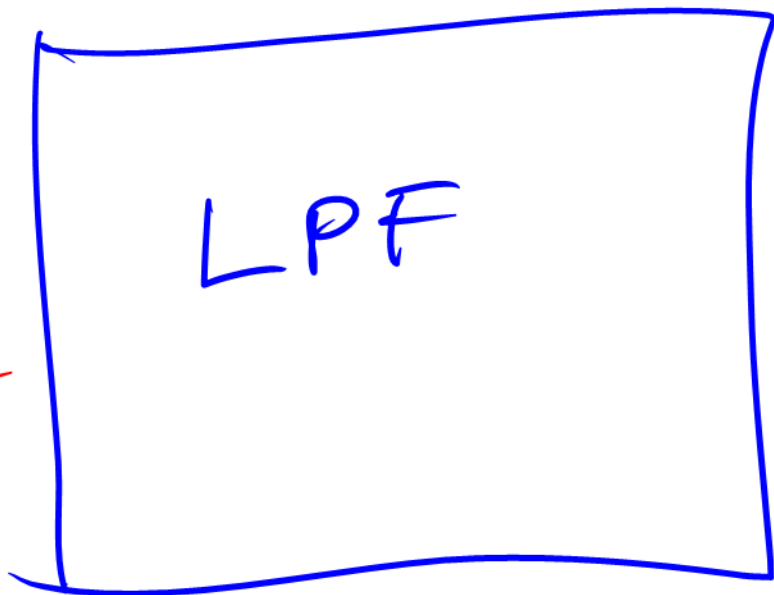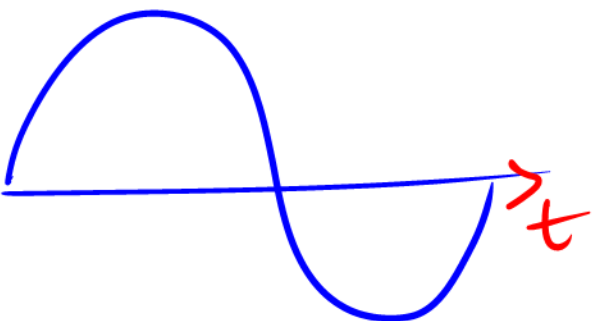

OUTPUT

