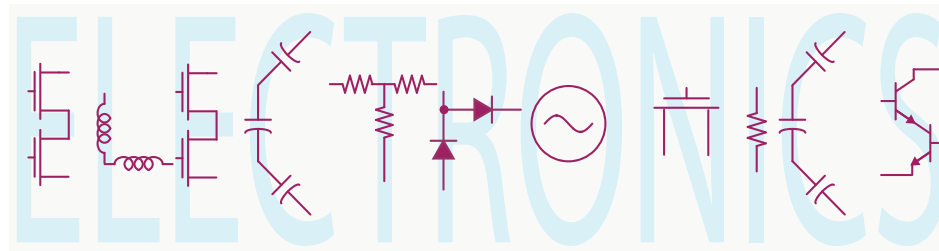


EE 42/100

Lecture 16: Sinusoidal Steady-State and Linear Systems




Rev B 3/13/2012 (2:23 PM)

Prof. Ali M. Niknejad

University of California, Berkeley

Copyright © 2012 by Ali M. Niknejad

The Magic of Sinusoids

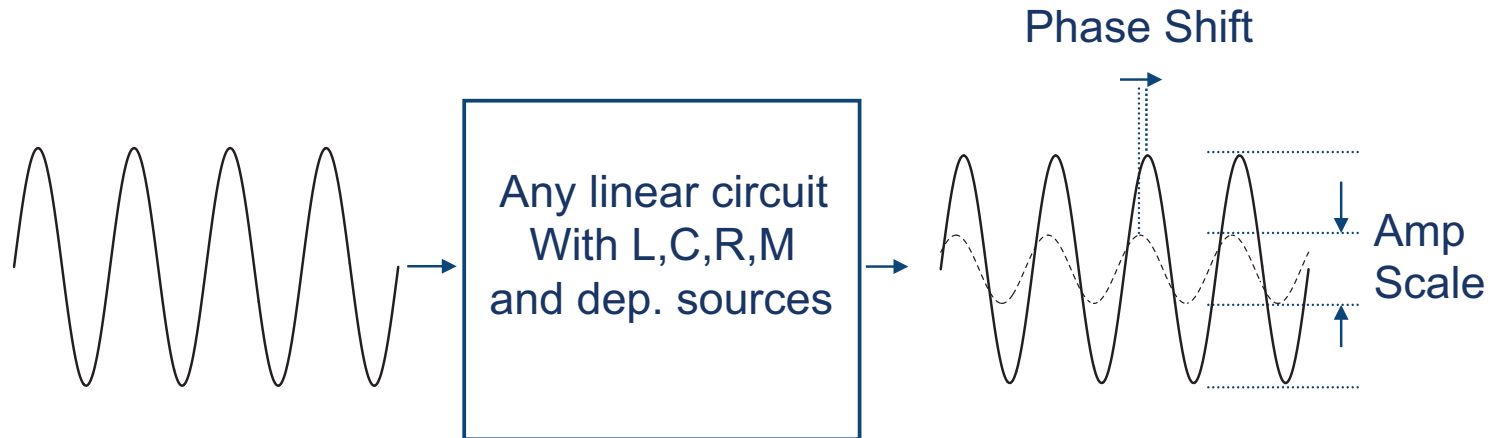

- When a linear, time invariant (LTI) circuit is excited by a sinusoid, its output is a sinusoid at the *same* frequency. Only the magnitude and phase of the output differ from the input. Sinusoids are very special functions for LTI systems.
- The “Frequency Response” is a characterization of the input-output response for sinusoidal inputs at all frequencies.
- Since most periodic (non-periodic) signals can be decomposed into a summation (integration) of sinusoids via Fourier Series (Transform), the response of a LTI system to virtually any input is characterized by the frequency response of the system.

Example: Low Pass Filter (LPF)


- Input signal: $v_s(t) = V_s \cos(\omega t)$
- We know that in SS the amplitude and phase will change:
$$v_o(t) = \underbrace{K \cdot V_s}_{V_o} \cos(\omega t + \phi)$$
- The governing equations are:

$$v_o(t) = v_s(t) - i(t)R$$

$$i(t) = C \frac{dv_o(t)}{dt}$$

$$v_o(t) = v_s(t) - RC \frac{dv_o(t)}{dt}$$
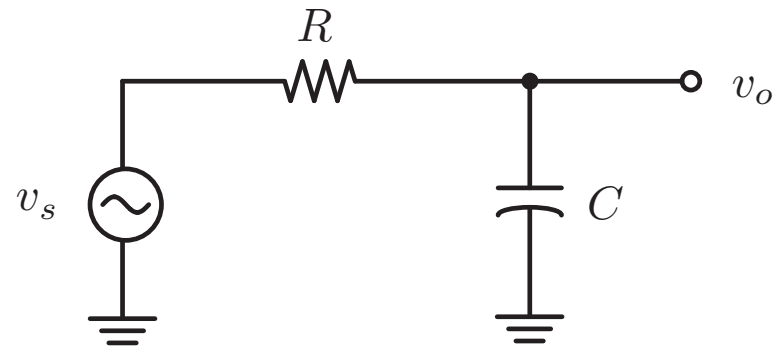
$$v_o(t) = v_s(t) - \tau \frac{dv_o(t)}{dt}$$



LPF the “hard way”

- Plug the known form of the output into the equation and verify that it can satisfy KVL and KCL

$$V_s \cos(\omega t) = V_o \cos(\omega t + \phi) - \tau\omega V_o \sin(\omega t + \phi)$$

Use the following identities:

$$\cos(x + y) = \cos x \cos y - \sin x \sin y$$

$$\sin(x + y) = \sin x \cos y + \cos x \sin y$$

$$V_s \cos(\omega t) = V_o \cos(\omega t)(\cos \phi - \tau\omega \sin \phi) - V_o \sin(\omega t)(\sin \phi + \tau\omega \cos \phi)$$

- Since sine and cosine are linearly independent functions:

$$a_1 \sin(\omega t) + a_2 \cos(\omega t) = 0$$

implies that $a_1 = 0$ and $a_2 = 0$.

LPF: Solving for response

- Applying the linear independence gives us

$$-V_o \sin \phi - V_o \tau \omega \cos \phi = 0$$

this can be converted into

$$\tan \phi = -\tau \omega$$

- The phase response is therefore

$$\phi = -\tan^{-1} \tau \omega$$

Likewise we have

$$V_o \cos \phi - V_o \tau \omega \sin \phi - V_s = 0$$


$$V_o(\cos \phi - \tau \omega \sin \phi) = V_s \quad V_o \cos \phi(1 + (\tau \omega)^2) = V_s$$

$$V_o \cos \phi(1 - \tau \omega \tan \phi) = V_s \quad V_o(1 + (\tau \omega)^2)^{1/2} = V_s$$


- The amplitude response is therefore given by

$$\frac{V_o}{V_s} = \frac{1}{\sqrt{1 + (\tau \omega)^2}}$$

LPF Magnitude Response

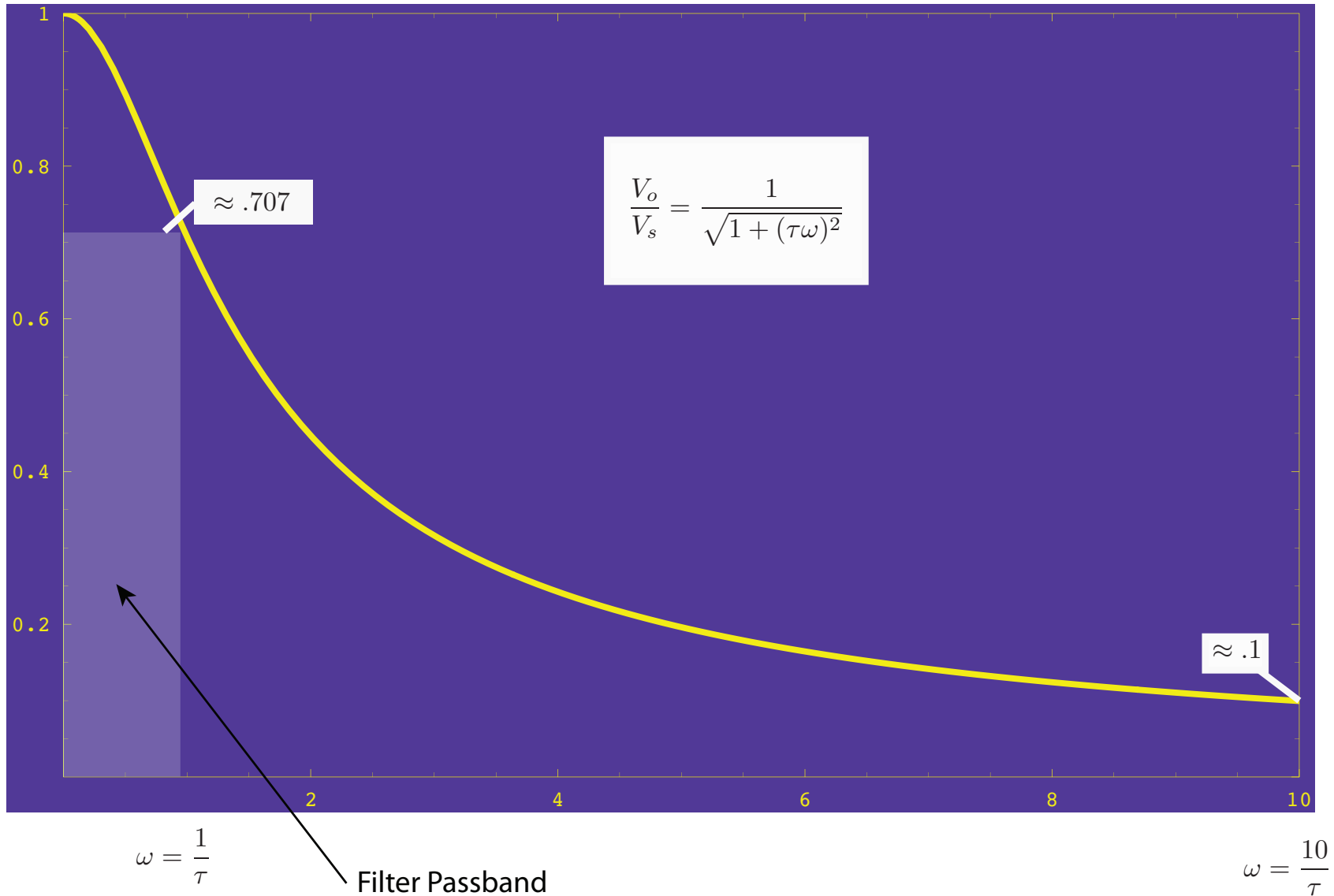


LPF Phase Response

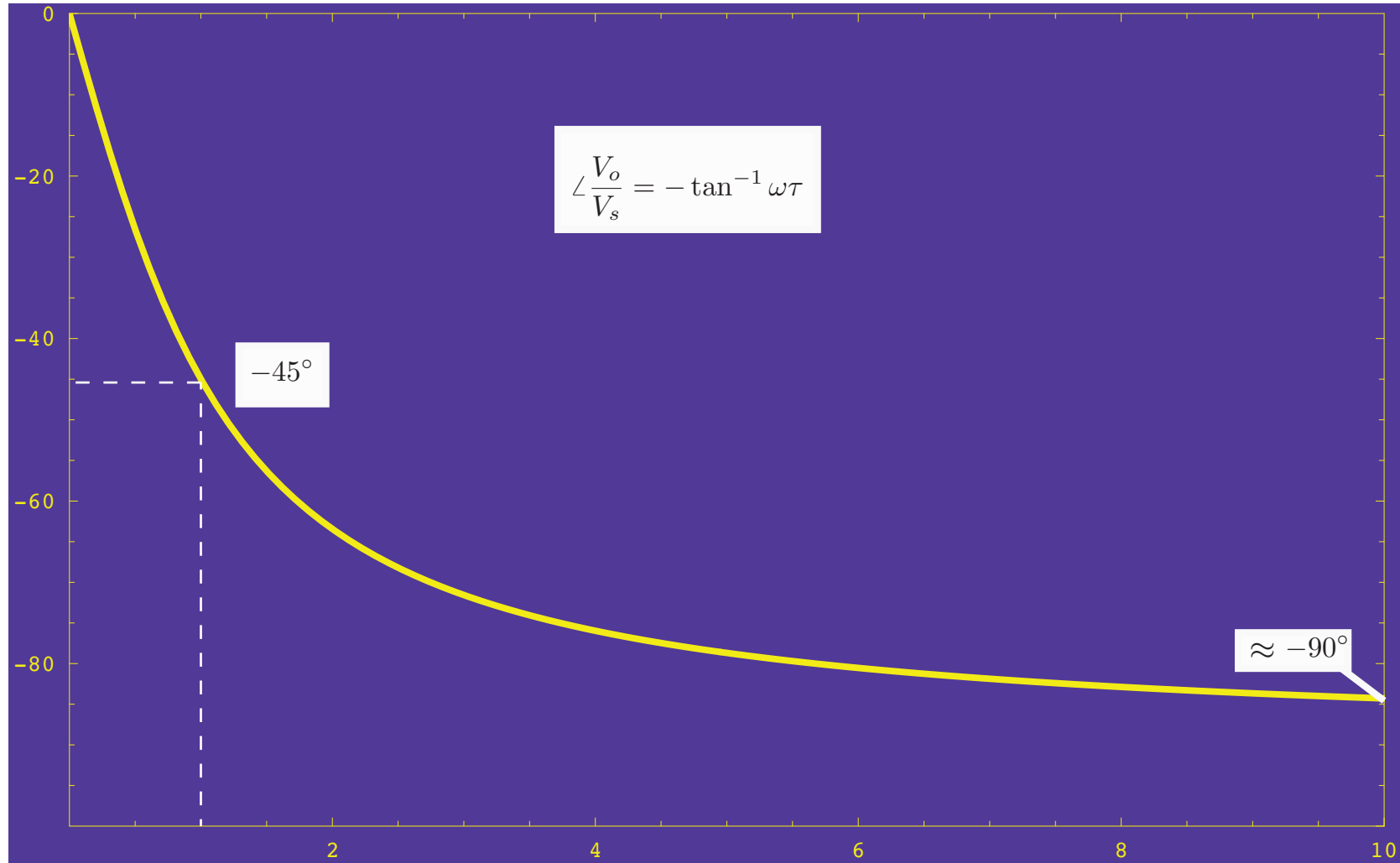

$$\omega = \frac{1}{\tau}$$

$$\omega = \frac{10}{\tau}$$

dB: Honor the inventor of the phone...

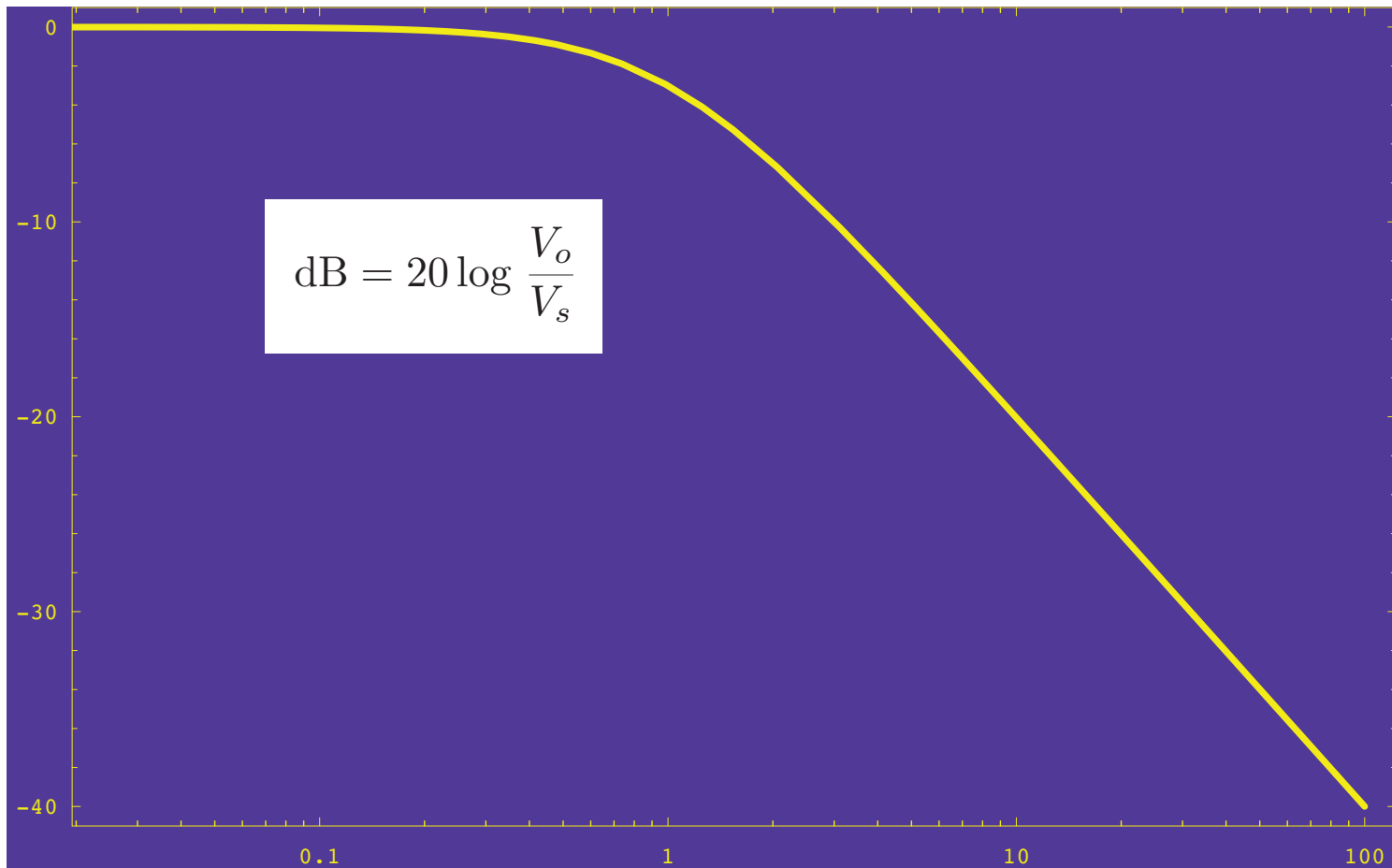

- The LPF response quickly decays to zero
- We can expand range by taking the log of the magnitude response
- dB = deciBel (deci = 10)

Why 20? Power!

- Why multiply log by “20” rather than “10”?
- Power is proportional to voltage squared:

$$\text{dB} = 10 \log \left(\frac{V_o}{V_s} \right)^2 = 20 \log \left(\frac{V_o}{V_s} \right)$$

- At various frequencies we have:

$$\omega = 1/\tau \rightarrow \left(\frac{V_o}{V_s} \right)_{\text{dB}} = -3\text{dB}$$

$$\omega = 100/\tau \rightarrow \left(\frac{V_o}{V_s} \right)_{\text{dB}} = -40\text{dB}$$

$$\omega = 1000/\tau \rightarrow \left(\frac{V_o}{V_s} \right)_{\text{dB}} = -60\text{dB}$$

- Observe: slope of Signal attenuation is 20 dB/decade in frequency.
- Alternatively, if you double the frequency, the attenuation changes by 6 dB, or 6 dB/octave.

Complex Exponential

- Euler's Theorem says that

$$e^{jx} = \cos x + j \sin x$$


- This can be derived by expanding each term in a power series.
- If take the magnitude of this quantity, it's unity

$$|e^{jx}| = \sqrt{\cos^2 x + \sin^2 x} = 1$$

- That means that $e^{j\phi}$ is a point on the unit circle at an angle of ϕ from the x -axis.

Any complex number z , expressed as have a real and imaginary part $z = x + jy$, can also be interpreted as having a magnitude and a phase. The magnitude $|z| = \sqrt{x^2 + y^2}$ and the phase $\phi = \angle z = \tan^{-1} y/x$ can be combined using the complex exponential

$$x + jy = |z|e^{j\phi}$$

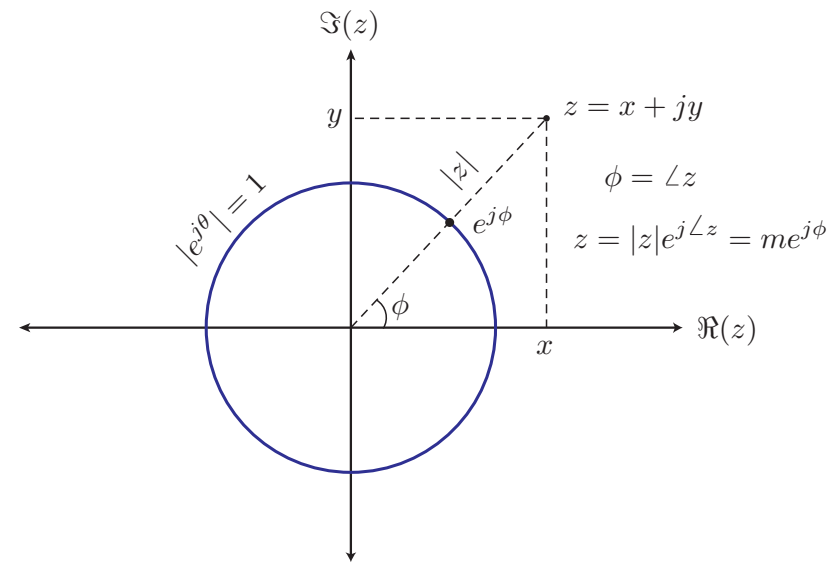

Euler's Theorem and The Circle

- This implies that $e^{j\omega t}$ is nothing but a point rotating on a circle on the complex plane. The real part and imaginary parts are just projections of the circle, which by trigonometry we know equal the cosine and sine functions.
- We can also express \cos and \sin in terms of e as follows

$$\cos x = \frac{e^{jx} + e^{-jx}}{2}$$

$$\sin x = \frac{e^{jx} - e^{-jx}}{2j}$$

- To see an animation of these equations, click below:

$e^{j\omega t}$ rotating around circle^a $e^{-j\omega t}$ rotating around circle^b
 $e^{j\omega t} + e^{-j\omega t}$ oscillates on the real axis^c

^a<http://rfic.eecs.berkeley.edu/ee100/pdf/exp1.gif>

^b<http://rfic.eecs.berkeley.edu/ee100/pdf/exp2.gif>

^c<http://rfic.eecs.berkeley.edu/ee100/pdf/exp3.gif>

Why introduce complex numbers?

- They actually make things easier!
- Integration and differentiation are trivial with complex exponentials:


$$\frac{d}{dt} e^{j\omega t} = j\omega e^{j\omega t}$$

$$\int e^{j\omega x} dx = \frac{1}{j\omega} e^{j\omega t}$$

- Any ODE is now trivial algebraic manipulations ... in fact, we'll show that you don't even need to directly derive the ODE by using phasors (phasor is essentially a shorthand notation for a complex number)
- The key is to observe that the current/voltage relation for any element can be derived for complex exponential excitation

Complex Exponential is Powerful

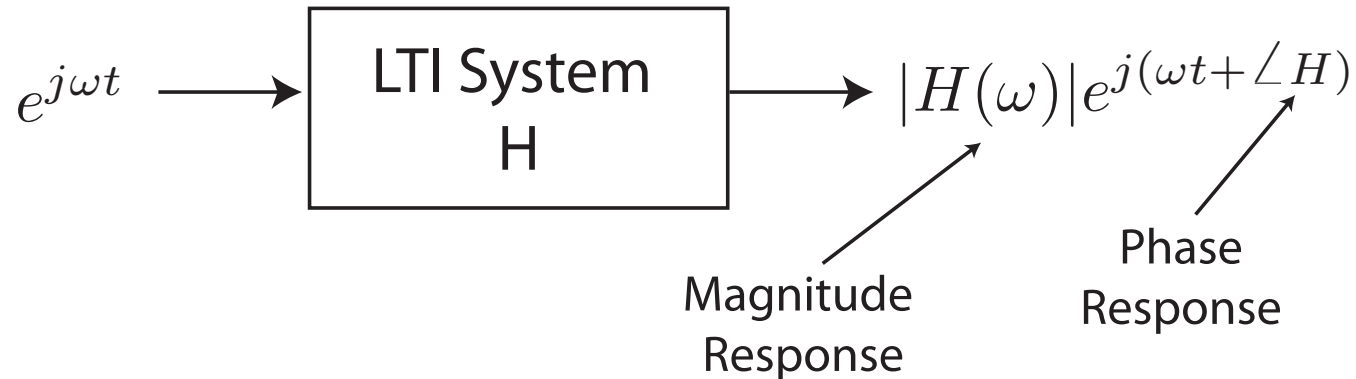- To find steady state response we can excite the system with a complex exponential



- At any frequency, the system response is characterized by a single complex number H :
 - The magnitude response is given by $|H(\omega)|$
 - The phase response is given by $\angle H$
- We see that the complex exponential is an "eigenfunction" of the system. It is used to probe the system.
- Since a sinusoid is a sum of complex exponentials (and because of linearity!), we can also probe a system by applying a real sinusoidal input.

LPF Example: The “soft way”

- Let's excite the system with a complex exponential

$$v_s(t) = v_o(t) + \tau \frac{dv_o}{dt}$$

$$v_s(t) = V_s e^{j\omega t}$$

$$v_o(t) = |V_o| e^{j(\omega t + \phi)} = V_o e^{j\omega t}$$

- Now substitute into the original equation

$$V_s e^{j\omega t} = V_o e^{j\omega t} + \tau \cdot j\omega \cdot V_o e^{j\omega t}$$

divide out the non-zero common factors

$$V_s = V_o(1 + j\omega \cdot \tau)$$

$$\frac{V_o}{V_s} = \frac{1}{1 + j\omega \cdot \tau}$$

Magnitude and Phase Response

- The system is characterized by the complex function

$$H(\omega) = \frac{V_o}{V_s} = \frac{1}{1 + j\omega \cdot \tau}$$

- The magnitude and phase response match our previous calculation

$$|H(\omega)| = \left| \frac{V_o}{V_s} \right| = \frac{1}{\sqrt{1 + (\omega\tau)^2}}$$

$$\angle H(\omega) = -\tan^{-1} \omega\tau$$

Why did it work?

- The system is linear:

$$\Re[y] = \mathbf{L}(\Re[x]) = \Re[\mathbf{L}(x)]$$


- If we excite system with a sinusoid:

$$v_s(t) = V_s \cos(\omega t) = V_s \Re[e^{j\omega t}]$$

- If we push the complex exponential through the system first and take the real part of the output, then that's the “real” sinusoidal response

$$v_o(t) = V_o \cos(\omega t + \phi) = V_o \Re[e^{j(\omega t + \phi)}]$$

And yet another perspective

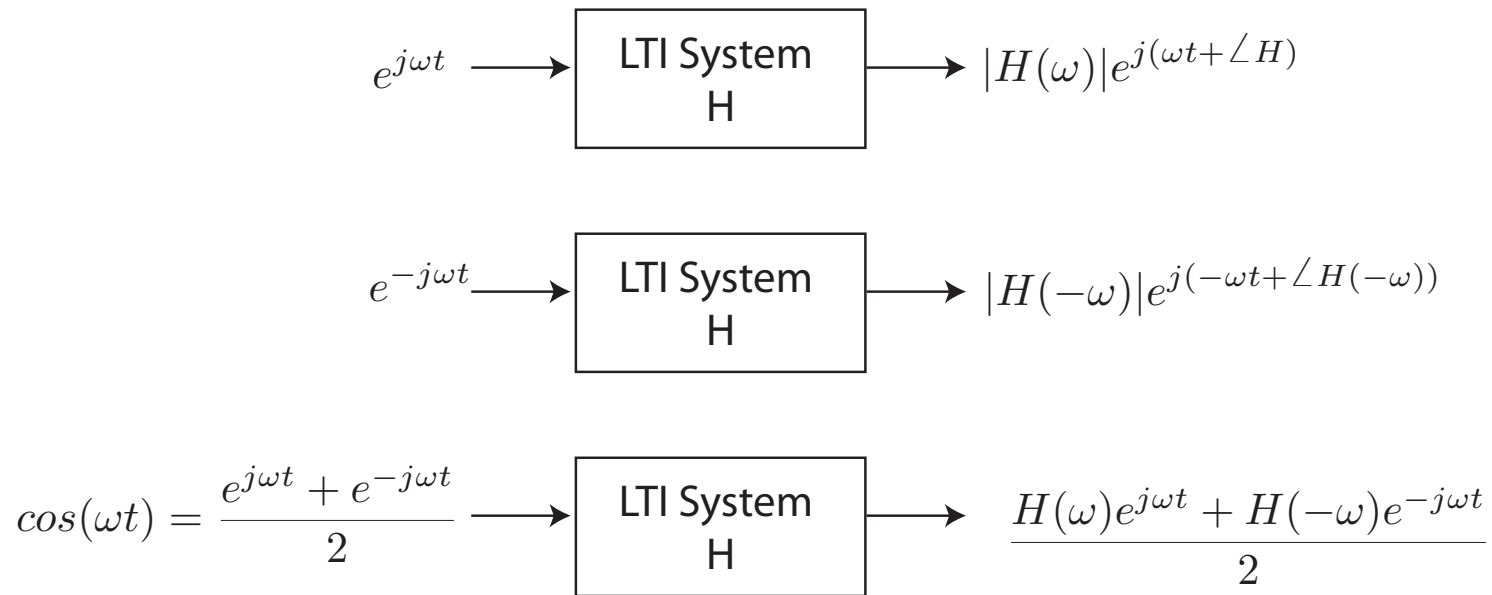

- Another way to see this is to observe the system is linear so that

$$y = \mathbf{L}(x_1 + x_2) = \mathbf{L}(x_1) + \mathbf{L}(x_2)$$

- To find the response to a sinusoid, we can find the response to $e^{j\omega t}$ and $e^{-j\omega t}$ and sum the results.

Another perspective (cont.)

- Since the input is real, the output has to be real:

$$y(t) = \frac{H(\omega)e^{j\omega t} + H(-\omega)e^{-j\omega t}}{2}$$

- That means the second term is the conjugate of the first:

$$|H(-\omega)| = |H(\omega)|$$

(even function)

$$\angle H(-\omega) = -\angle H(\omega) = -\phi$$

(odd function)

- Therefore the output is:

$$\begin{aligned} y(t) &= \frac{|H(\omega)|}{2} \left(e^{j(\omega t + \phi)} + e^{-j(\omega t + \phi)} \right) \\ &= |H(\omega)| \cos(\omega t + \phi) \end{aligned}$$

“Proof” for Linear Systems

- For an arbitrary linear circuit (L, C, R, M , and linear dependent sources), decompose it into linear sub-operators, like multiplication by constants, time derivatives, or integrals:

$$y = \mathbf{L}(x) = ax + b_1 \frac{d}{dt}x + b_2 \frac{d^2}{dt^2}x + \dots + \int x + \iint x + \dots$$

- For a complex exponential input this simplifies to:

$$y = \mathbf{L}(e^{j\omega t}) = ae^{j\omega t} + b_1 \frac{d}{dt}e^{j\omega t} + b_2 \frac{d^2}{dt^2}e^{j\omega t} + \dots + \int e^{j\omega t} + \iint e^{j\omega t} + \dots$$

$$y = ae^{j\omega t} + b_1 j\omega e^{j\omega t} + b_2 (j\omega)^2 e^{j\omega t} + \dots + \frac{e^{j\omega t}}{j\omega} + \frac{e^{j\omega t}}{(j\omega)^2} + \dots$$

- Note that every term is of the form $e^{j\omega t}$ times a constant, which when grouped together gives

$$y = e^{j\omega t} \underbrace{\left(a + b_1 j\omega + b_2 (j\omega)^2 + \dots + \frac{1}{j\omega} + \frac{1}{(j\omega)^2} + \dots \right)}_H$$

“Proof” (cont.)

- The amplitude of the output is the magnitude of the complex number and the phase of the output is the phase of the complex number

$$y = e^{j\omega t} \underbrace{\left(a + b_1 j\omega + b_2 (j\omega)^2 + \cdots + \frac{1}{j\omega} + \frac{1}{(j\omega)^2} + \cdots \right)}_H$$

or

$$y = e^{j\omega t} |H(\omega)| e^{j\angle H(\omega)}$$

$$\Re[y] = |H(\omega)| \cos(\omega t + \angle H(\omega))$$

Phasors

- With our new confidence in complex numbers, we go full steam ahead and work directly with them ... we can even drop the time factor $e^{j\omega t}$ since it will cancel out of the equations.
- When a circuit is excited by a sinusoidal input, we assign the source a “phasor” with magnitude and phase equal to the source. Then we analyze the circuit assuming all voltages/currents are sinusoidal, which can be represented by the shorthand phasor form.
- Excite system with a phasor: $\widetilde{V}_1 = V_1 e^{j\phi_1} = V_1 \angle \phi_1$
- Response will also be phasor: $\widetilde{V}_2 = V_2 e^{j\phi_2} = V_2 \angle \phi_2$
- We see that a phasor is nothing more than a complex number which represents the complex exponential form of the voltage/current where we divide out the time dependence.

Capacitor I - V Phasor Relation

- Find the phasor relation for current and voltage in a capacitor:

$$i_c = C \frac{dv_c(t)}{dt}$$

- Assume the current/voltage can be written in a complex exponential form

$$i_c(t) = I_c e^{j\omega t}$$

$$v_c(t) = V_c e^{j\omega t}$$

- Substitute in the governing equation

$$I_c e^{j\omega t} = C \frac{d}{dt} V_c e^{j\omega t} = j\omega C V_c e^{j\omega t}$$

$$I_c e^{j\omega t} = j\omega C V_c e^{j\omega t}$$

or directly in Phasor form

$$I_c = j\omega C V_c$$