
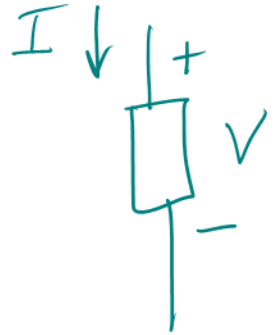


EXAM REVIEW TOPICS:

Lecture 2:

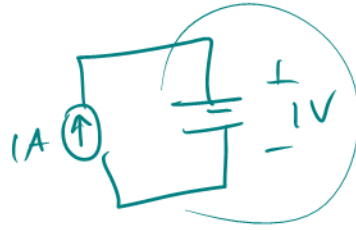- * What is current?
 - * Sign convention
 - * Positive and negative charge
 - * AC versus DC



- * What is voltage?
 - * How is it related to energy?
 - * What is the "ground" potential?
 - * What is the physical ground "plane" versus the reference node?

- * Power?
 - * Passive sign convention
 - * Energy



$$P = I \cdot V$$

$$P \geq 0$$

- * Components
 - * Sign convention of voltage/current
 - * Sign convention of power


- * Voltage Source
 - * Ideal voltage source
 - * Real battery
 - * Internal resistance/ source resistance



$$I = \frac{V}{R}$$

- * Ideal switch
 - * voltage/current /power

- * From Physics: KCL/KVL
- * Battery packs (homework)

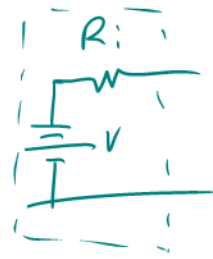

Lecture 3:

- * Conductors
 - * Ideal conductors
 - * Real conductors
 - * Ohm's law
 - * Calculating resistance
 - * Conductance
 - * Power loss in conductors
 - * Strain gauge as an example

$$V = I \cdot R$$

$$I = G \cdot V$$

$$P = I^2 \cdot R$$

$$= V^2 \cdot G$$



$$R = \rho \cdot \frac{l}{w \cdot T}$$


$$G = 1/R$$

- * Resistors as modeling elements
 - * Light bulb




$$V_{oc} = V_{int} = 1.2V$$

$$R_i = 0.6\Omega$$

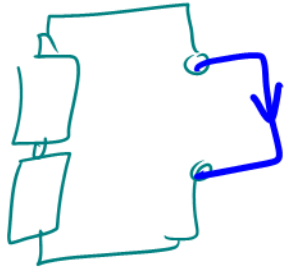


$$I_{MAX} = ?$$

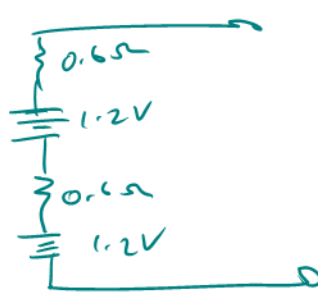


$$V'_{oc} = 2.4V$$

$$R'_i = 0.6\Omega + 0.6\Omega = 1.2\Omega$$

$$I_{max} = \frac{V'_{oc}}{R'_i} = 2A$$

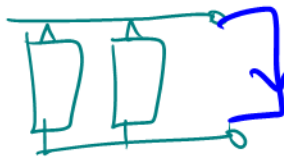

$$V'_{oc} = 1.2V$$

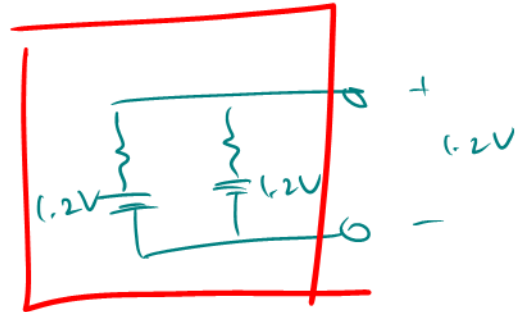

Thevenin :

• ZERO OUT INDEPENDENT SOURCES


• FIND Req (RTH)

$$R'_i = 0.3\Omega$$



$$I_{max} = \frac{V'_{oc}}{R'_i} = \frac{1.2V}{0.3\Omega} = 4A$$

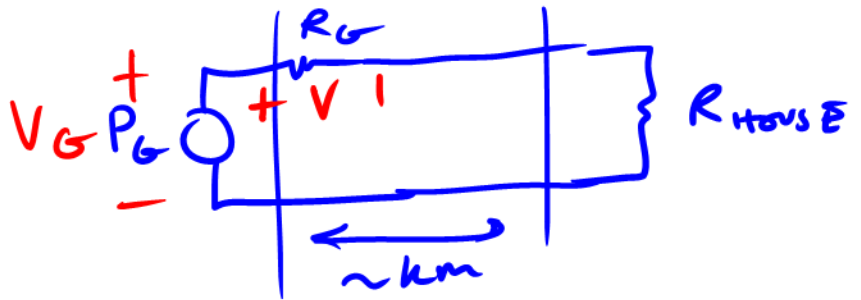- * Motor
- * Antenna
- * Speakers
- * Anything passive!




- * Energy loss in power delivery
 - * High voltage versus high current
 - * Need for transformers / AC

$$P_{\text{loss}} \propto I^2 R_G \quad V \uparrow$$


$$P_{\text{loss}} \propto V^2 \frac{1}{R_G} \quad V \downarrow ??$$

- * Resistors
 - * Series resistors
 - * Parallel resistors

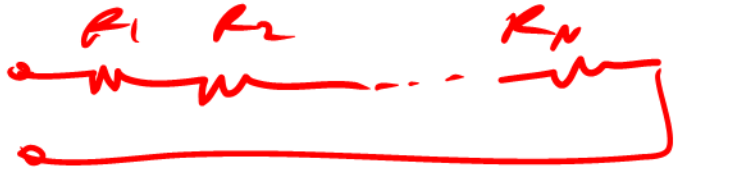

Lecture 4:

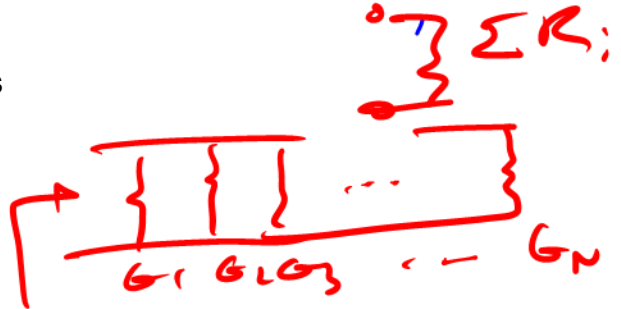- * Current source
- * Dependent sources versus independent sources
- * Resistive dividers
 - * Voltage dividers
 - * Current dividers
 - * Shorts and opens / Winners and losers




- * Variable resistors/Pots
- * Efficiency of divider circuits

$$G = \sum G_i$$

Lecture 5:

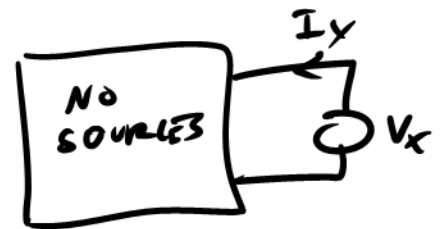- * Nodal analysis
 - * counting nodes
 - * reference node
 - * eliminating nodes
 - * super nodes
 - * trivial nodes
 - * Nodal without dependent sources
 - * Nodal with dependent sources
 - * Knowns versus unknowns
 - * Setting up equations in standard format (LHS = RHS)
 - * LHS = unknowns
 - * RHS = knowns




$$R_{TH} = \frac{V_x}{I_x}$$

Lecture 6:

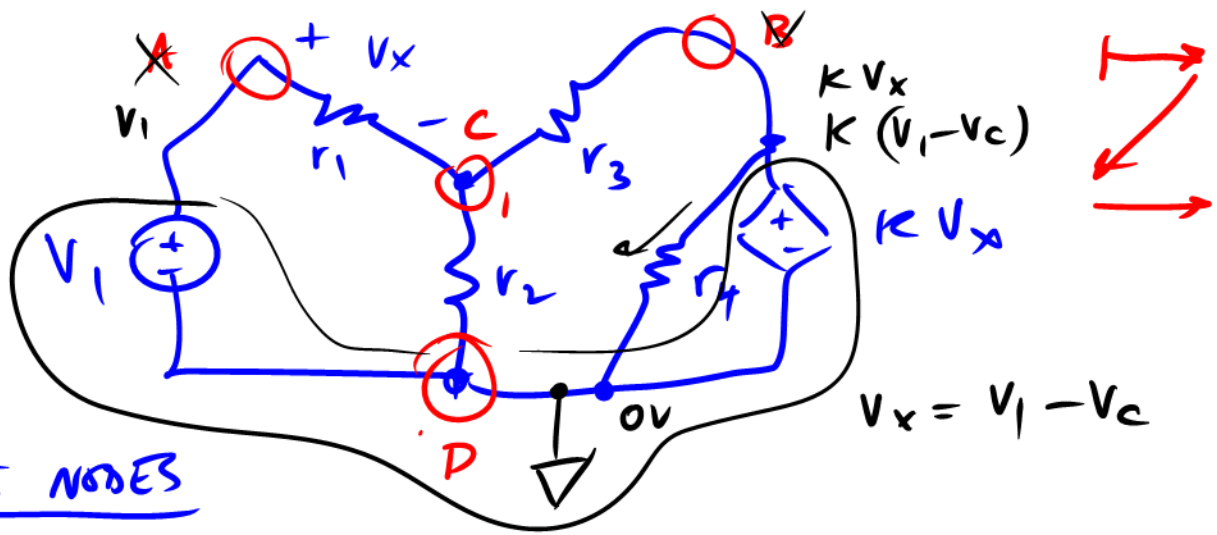- * Linearity and Superposition
- * Thevenin Equivalent
 - * Voc and Isc
 - * "Req" approach without internal sources





COUNT NODES

A, B, C, D

DEFINE A REF NODE

: NODE D \Rightarrow RESULTS IN ELIMINATING 2 OTHER NODES


UNK V_c

IDENTIFY SUPER NODES:


- FLOATING VOLTAGE SOURCE

- GROUP OF CONNECTED VOLTAGE SOURCES

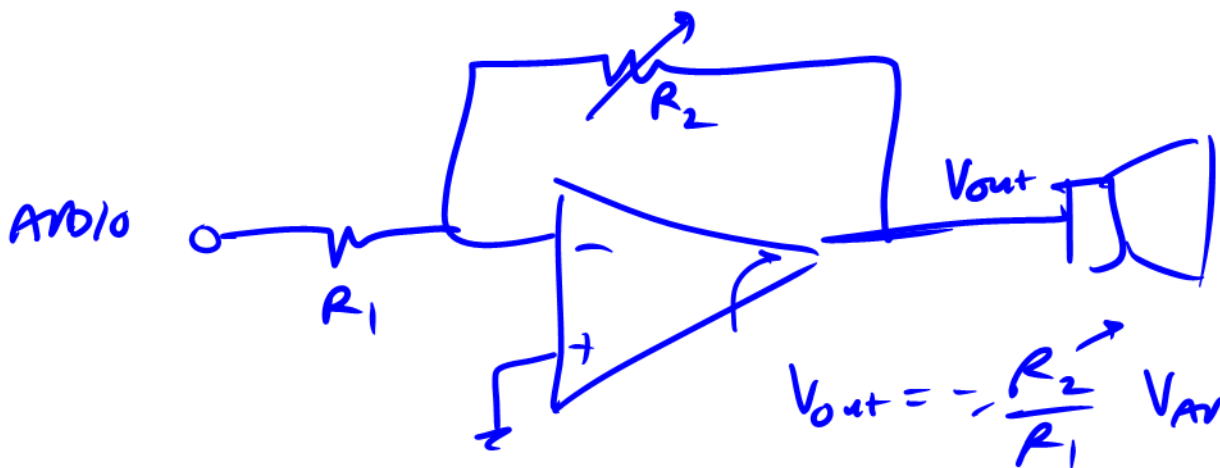
WRITE KCL EQ \Rightarrow FOR EVERY UNK NODE






$$V_{out} = -\frac{R_2}{R_1} V_{AUDIO}$$

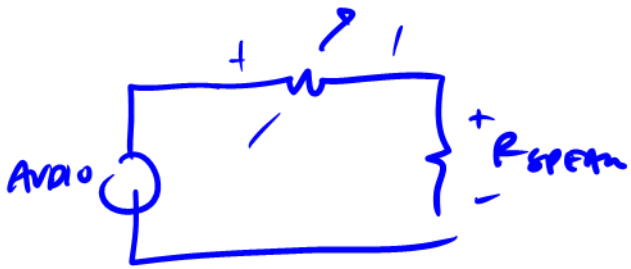

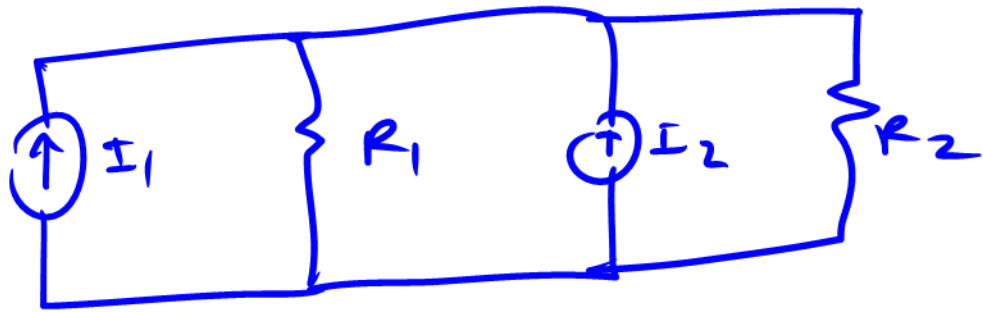
$$\eta = \frac{R_{speaker}}{R_{speaker} + R_{pot}}$$




|||

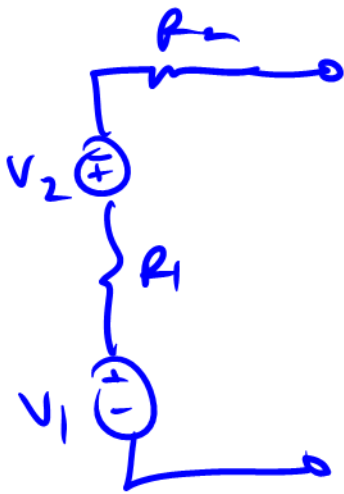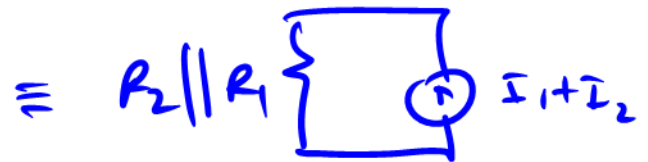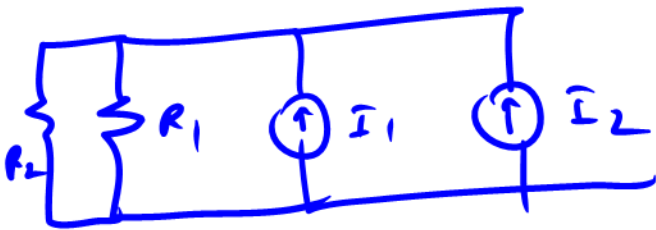


≡

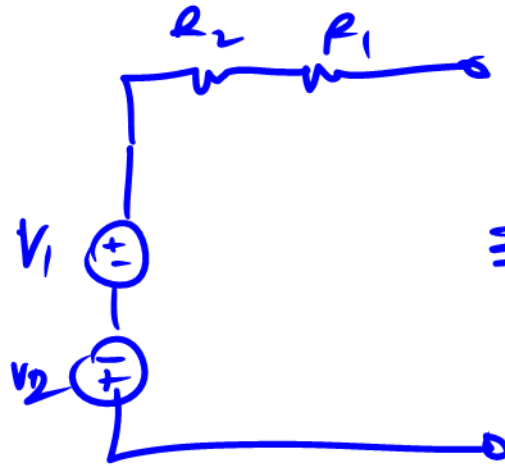

≡

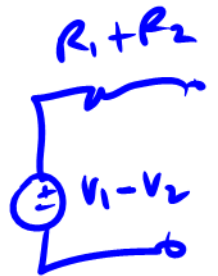



$$V_x = ?$$

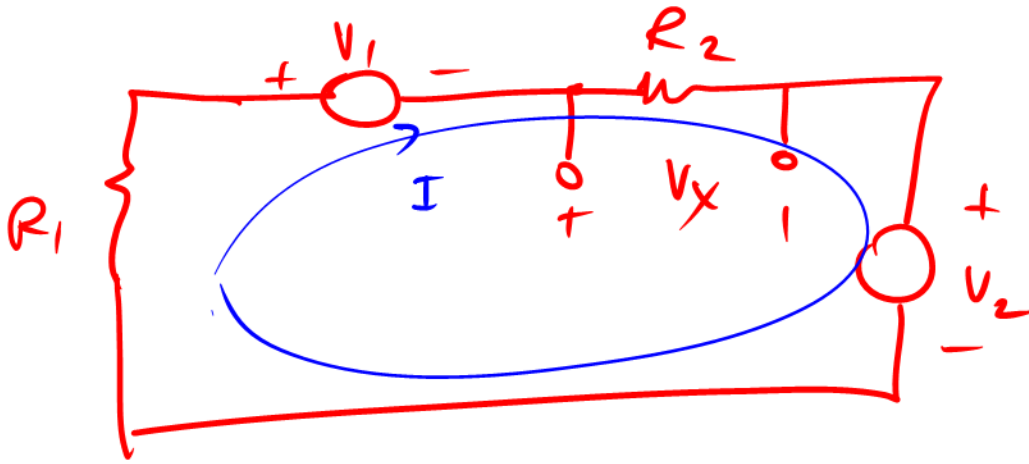


$$V_1 + IR_2 + V_2 + IR_1 = 0 \quad I = \frac{-(V_1 + V_2)}{R_1 + R_2}$$
$$V_x = IR_2 = -\frac{(V_1 + V_2) R_2}{R_1 + R_2}$$

SUPERPOSITION


$$V_2 = 0$$


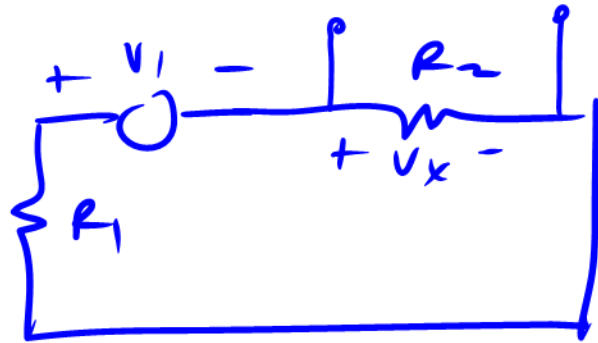
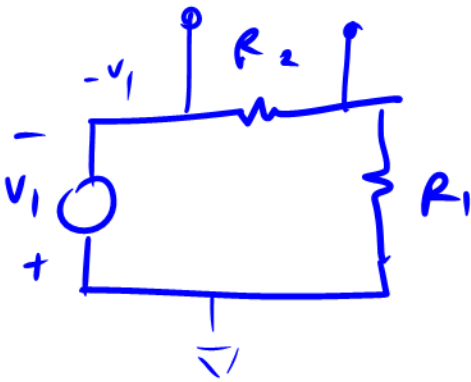

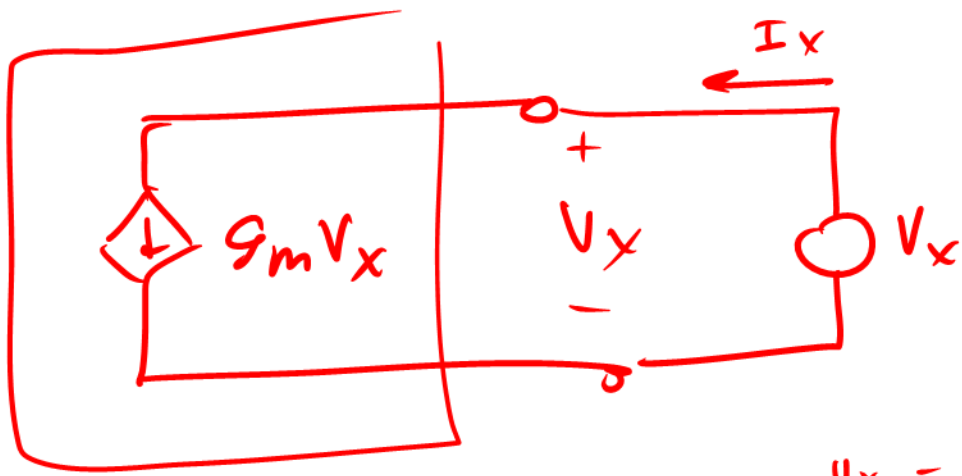
$$V_x = -V_1 \cdot \frac{R_2}{R_1 + R_2}$$




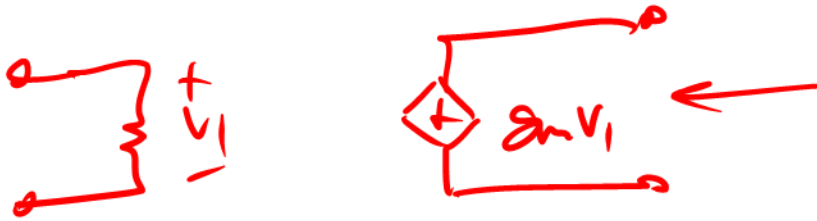
$$I_x = g_m V_x \quad R_{Th} = \frac{V_x}{I_x} = \frac{1}{g_m}$$



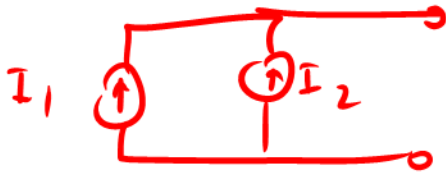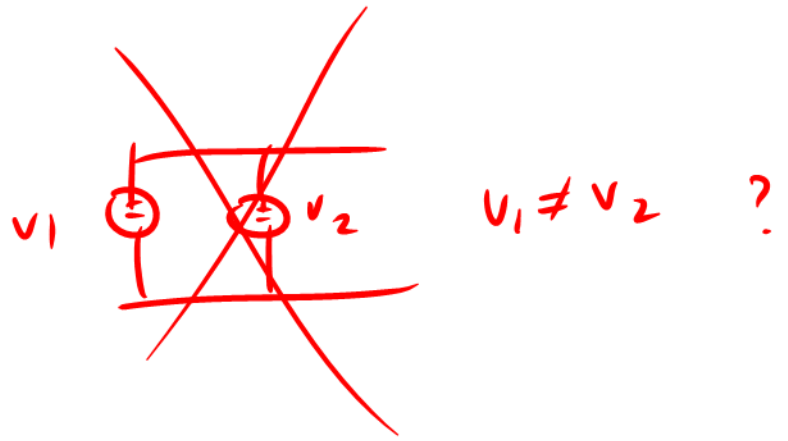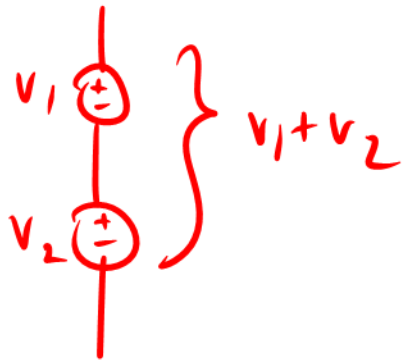

\equiv

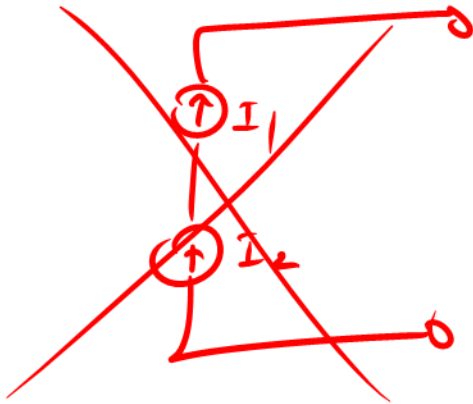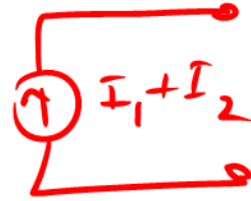

$I_1 \neq I_2$


- * "Req" with independent sources
- * Norton Equivalent
- * Maximum power transfer theorem
- * Wheatstone Bridge (homework)

2 PRO
OUT
SOURCES

Lecture 7:

- * Amplifiers
 - * Terminals
 - * Signal pins versus power pins
 - * Gain
 - * Ideal vs. Real
 - * Input R / Output R
 - * Equivalent circuit
 - * Loading
 - * Dividers at input / output
 - * Effective gain
 - * Cascade
 - * Dynamic Range
 - * Clipping
- * Types: CC, VV, CV, VC
 - * Most common is voltage/voltage

|

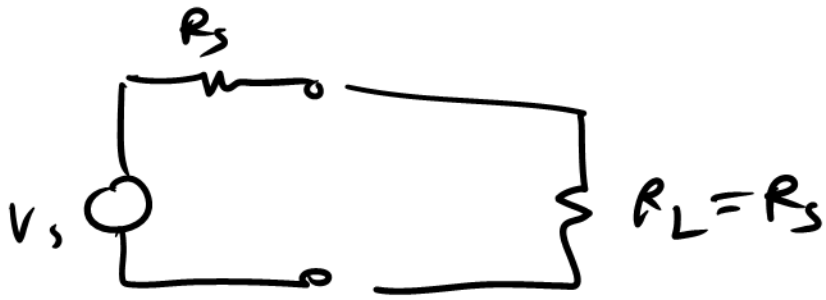

$$\eta = \frac{P_L}{P_L + P_s}$$

$$= \frac{I^2 R_L}{I^2 R_s + I^2 R_L}$$

\Rightarrow MAXIMUM POWER EXTRACTED

$$= \frac{R_L}{R_s + R_L}$$

$$= \frac{R_s}{2R_s} = 50\%$$