

*EECS 217*

*Lecture 18: Two-Port Power Gain*

Prof. Niknejad

University of California, Berkeley

# Two-Port Power and Scattering Parameters

- The power flowing into a two-port can be represented by

$$P_{in} = \frac{|V_1^+|^2}{2Z_0} (1 - |\Gamma_{in}|^2)$$

- The power flowing to the load is likewise given by

$$P_L = \frac{|V_2^-|^2}{2Z_0} (1 - |\Gamma_L|^2)$$

- We can solve for  $V_1^+$  using circuit theory

$$V_1^+ + V_1^- = V_1^+ (1 + \Gamma_{in}) = \frac{Z_{in}}{Z_{in} + Z_S} V_S$$

- In terms of the input and source reflection coefficient

$$Z_{in} = \frac{1 + \Gamma_{in}}{1 - \Gamma_{in}} Z_0 \qquad Z_S = \frac{1 + \Gamma_S}{1 - \Gamma_S} Z_0$$

## Two-Port Incident Wave

- Solve for  $V_1^+$

$$V_1^+(1 + \Gamma_{in}) = \frac{V_S(1 + \Gamma_{in})(1 - \Gamma_S)}{(1 + \Gamma_{in})(1 - \Gamma_S) + (1 + \Gamma_S)(1 - \Gamma_{in})}$$

$$V_1^+ = \frac{V_S}{2} \frac{1 - \Gamma_S}{1 - \Gamma_{in}\Gamma_S}$$

- The voltage incident on the load is given by

$$V_2^- = S_{21}V_1^+ + S_{22}V_2^+ = S_{21}V_1^+ + S_{22}\Gamma_L V_2^-$$

$$V_2^- = \frac{S_{21}V_1^+}{1 - S_{22}\Gamma_L}$$

$$P_L = \frac{|S_{21}|^2 |V_1^+|^2}{|1 - S_{22}\Gamma_L|^2} \frac{1 - |\Gamma_L|^2}{2Z_0}$$

# Operating Gain and Available Power

- The operating power gain can be written in terms of the two-port s-parameters and the load reflection coefficient

$$G_p = \frac{P_L}{P_{in}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{|1 - S_{22}\Gamma_L|^2 (1 - |\Gamma_{in}|^2)}$$

- The available power can be similarly derived from  $V_1^+$

$$P_{avs} = P_{in}|_{\Gamma_{in}=\Gamma_S^*} = \frac{|V_{1a}^+|^2}{2Z_0} (1 - |\Gamma_S^*|^2)$$

$$V_{1a}^+ = V_1^+|_{\Gamma_{in}=\Gamma_S^*} = \frac{V_S}{2} \frac{1 - \Gamma_S^*}{1 - |\Gamma_S|^2}$$

$$P_{avs} = \frac{|V_S|^2}{8Z_0} \frac{|1 - \Gamma_S|^2}{1 - |\Gamma_S|^2}$$

# Transducer Gain


- The transducer gain can be easily derived

$$G_T = \frac{P_L}{P_{avs}} = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)(1 - |\Gamma_S|^2)}{|1 - \Gamma_{in}\Gamma_S|^2 |1 - S_{22}\Gamma_L|^2}$$

- Note that as expected,  $G_T$  is a function of the two-port s-parameters and the load and source impedance.
- If the two port is connected to a source and load with impedance  $Z_0$ , then we have  $\Gamma_L = \Gamma_S = 0$  and

$$G_T = |S_{21}|^2$$

# Unilateral Gain

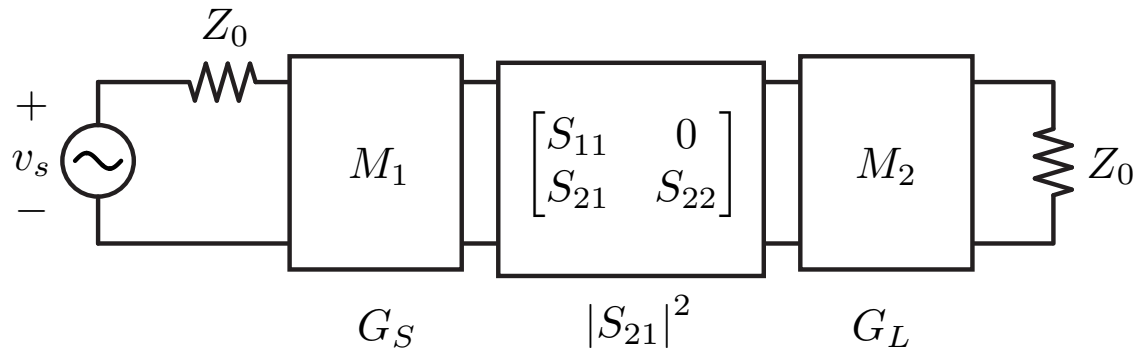

- If  $S_{12} \approx 0$ , we can simplify the expression by just assuming  $S_{12} = 0$ . This is the *unilateral* assumption

$$G_{TU} = \frac{1 - |\Gamma_S|^2}{|1 - S_{11}\Gamma_S|^2} |S_{21}|^2 \frac{1 - |\Gamma_L|^2}{|1 - S_{22}\Gamma_L|^2} = G_S |S_{21}|^2 G_L$$

- The gain partitions into three terms, which can be interpreted as the gain from the source matching network, the gain of the two port, and the gain of the load.
- In reality the source/load matching network are passive and hopefully lossless, so the power gain is 1 or less, but by virtue of the matching network we can change the gain of the two-port.

# Maximum Unilateral Gain

- We know that the maximum gain occurs for the biconjugate match

$$\Gamma_S = S_{11}^*$$

$$\Gamma_L = S_{22}^*$$


$$G_{S,max} = \frac{1}{1 - |S_{11}|^2}$$

$$G_{L,max} = \frac{1}{1 - |S_{22}|^2}$$

$$G_{TU,max} = \frac{|S_{21}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

- Note that if  $|S_{11}| = 1$  or  $|S_{22}| = 1$ , the maximum gain is infinity. This is the unstable case since  $|S_{ii}| > 1$  is potentially unstable.


# Ideal MOSFET

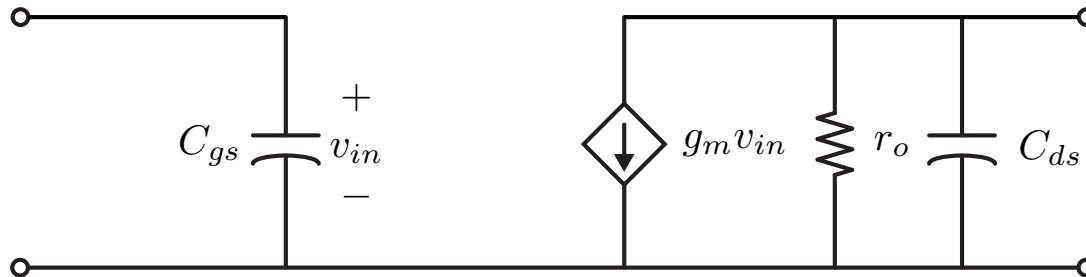

- The AC equivalent circuit for a MOSFET at low to moderate frequencies is shown above. Since  $|S_{11}| = 1$ , this circuit has infinite power gain. This is a trivial fact since the gate capacitance cannot dissipate power whereas the output can deliver real power to the load.



# Real MOSFET

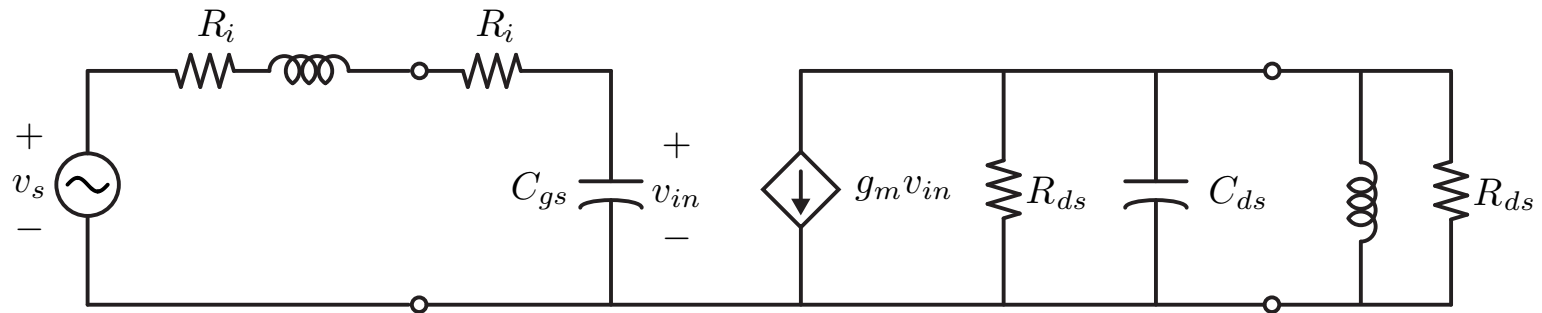

- A more realistic equivalent circuit is shown above. If we make the unilateral assumption, then the input and output power can be easily calculated. Assume we conjugate match the input/output

$$P_{avs} = \frac{|V_S|^2}{8R_i}$$

$$P_L = \Re\left(\frac{1}{2} I_L V_L^*\right) = \frac{1}{2} \left| \frac{g_m V_1}{2} \right|^2 R_{ds}$$

$$G_{TU,max} = g_m^2 R_{ds} R_i \left| \frac{V_1}{V_S} \right|^2$$

## Real MOSFET (cont)

- At the center resonant frequency, the voltage at the input of the FET is given by

$$V_1 = \frac{1}{j\omega C_{gs}} \frac{V_S}{2R_i}$$

$$G_{TU,max} = \frac{R_{ds}}{R_i} \frac{(g_m/C_{gs})^2}{4\omega^2}$$

- This can be written in terms of the device unity gain frequency  $f_T$

$$G_{TU,max} = \frac{1}{4} \frac{R_{ds}}{R_i} \left( \frac{f_T}{f} \right)^2$$

- The above expression is very insightful. To maximum power gain we should maximize the device  $f_T$  and minimize the input resistance while maximizing the output resistance.

# *Design for Gain*

- So far we have only discussed power gain using bi-conjugate matching. This is possible when the device is unconditionally stable. In many cases, though, we'd like to design with a potentially unstable device.
- Moreover, we would like to introduce more flexibility in the design. We can trade off gain for
  - bandwidth
  - noise
  - gain flatness
  - linearity
  - etc.
- We can make this tradeoff by identifying a range of source/load impedances that can realize a given value of power gain. While maximum gain is achieved for a single point on the Smith Chart, we will find that a lot more flexibility if we back-off from the peak gain.

# Unilateral Design

- No real transistor is unilateral. But most are predominantly unilateral, or else we use cascades of devices (such as the cascode) to realize such a device.
- The *unilateral figure of merit* can be used to test the validity of the unilateral assumption

$$U_m = \frac{|S_{12}|^2 |S_{21}|^2 |S_{11}|^2 |S_{22}|^2}{(1 - |S_{11}|^2)(1 - |S_{22}|^2)}$$

- It can be shown that the transducer gain satisfies the following inequality

$$\frac{1}{(1 + U)^2} < \frac{G_T}{G_{TU}} < \frac{1}{(1 - U)^2}$$

- Where the actual power gain  $G_T$  is compared to the power gain under the unilateral assumption  $G_{TU}$ . If the inequality is tight, say on the order of 0.1 dB, then the amplifier can be assumed to be unilateral with negligible error.

# Gain Circles

- We now can plot gain circles for the source and load. Let

$$g_S = \frac{G_S}{G_{S,max}}$$


$$g_L = \frac{G_L}{G_{L,max}}$$

- By definition,  $0 \leq g_S \leq 1$  and  $0 \leq g_L \leq 1$ . One can show that a fixed value of  $g_S$  represents a circle on the  $\Gamma_S$  plane

$$\left| \Gamma_S - \frac{S_{11}^* g_S}{|S_{11}|^2 (g_S - 1) + 1} \right| = \left| \frac{\sqrt{1 - g_S} (1 - |S_{11}|^2)}{|S_{11}|^2 (g_S - 1) + 1} \right|$$

- More simply,  $|\Gamma_S - C_S| = R_S$ . A similar equation can be derived for the load. Note that for  $g_S = 1$ ,  $R_S = 0$ , and  $C_S = S_{11}^*$  corresponding to the maximum gain.

## Gain Circles (cont)

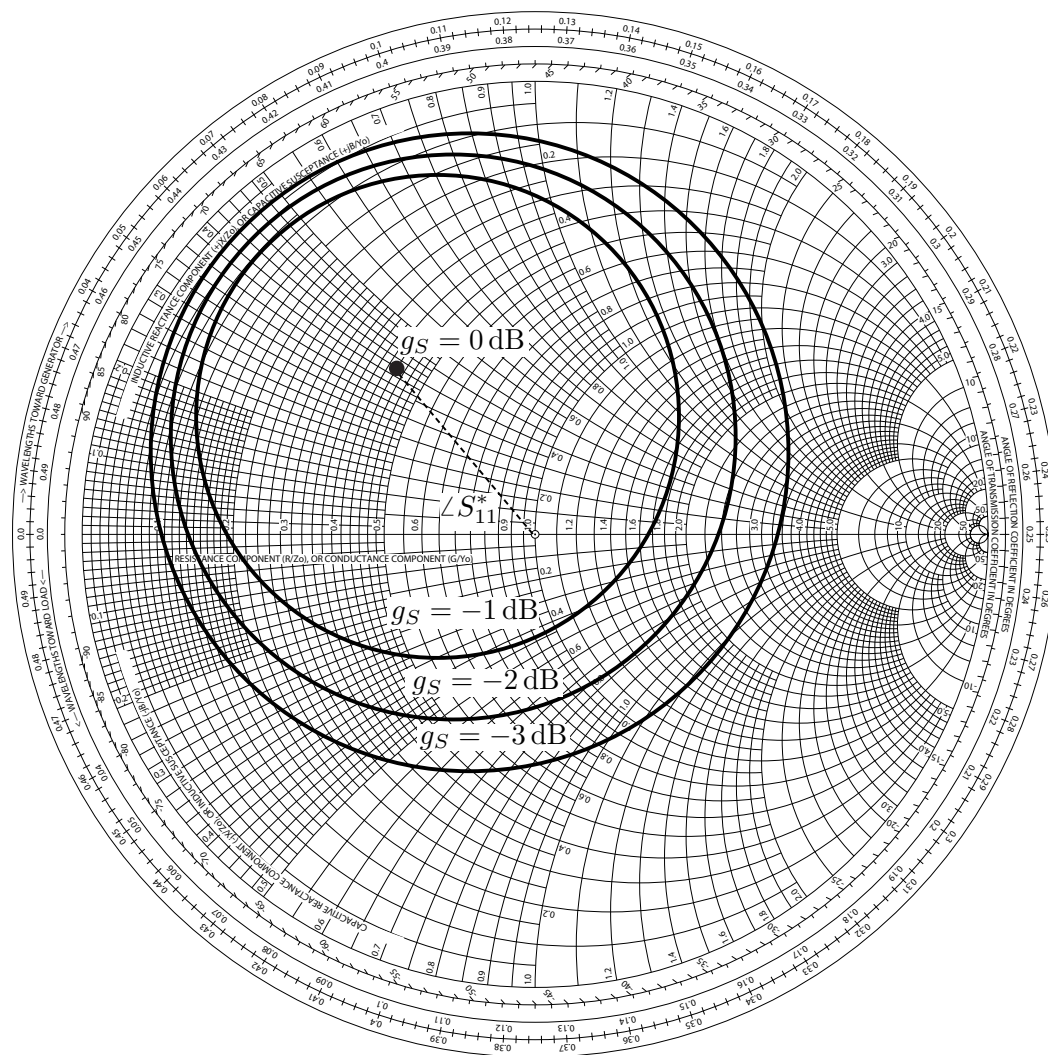

- All gain circles lie on the line given by the angle of  $S_{ii}^*$ . We can select any desired value of source/load reflection coefficient to achieve the desired gain. To minimize the impedance mismatch, and thus maximize the bandwidth, we should select a point close to the origin.

## Extended Smith Chart

- For  $|\Gamma| > 1$ , we can still employ the Smith Chart if we make the following mapping. The reflection coefficient for a negative resistance is given by

$$\Gamma(-R + jX) = \frac{-R + jX - Z_0}{-R + jX + Z_0} = \frac{(R + Z_0) - jX}{(R - Z_0) - jX}$$

$$\frac{1}{\Gamma^*} = \frac{(R - Z_0) + jX}{(R + Z_0) + jX}$$

- We see that  $\Gamma$  can be mapped to the unit circle by taking  $1/\Gamma^*$  and reading the resistance value (and noting that it's actually negative).

## Potentially Unstable Unilateral Amplifier

- For a unilateral two-port with  $|S_{11}| > 1$ , we note that the input impedance has a negative real part. Thus we can still design a stable amplifier as long as the source resistance is larger than  $\Re(Z_{in})$

$$\Re(Z_S) > |\Re(Z_{in})|$$

- The same is true of the load impedance if  $|S_{22}| > 1$ . Thus the design procedure is identical to before as long as we avoid source or load reflection coefficients with real part less than the critical value.



# Pot. Unstable Unilateral Amp Example


- Consider a transistor with the following  $S$ -Parameters

$$S_{11} = 2.02 \angle -130.4^\circ$$

$$S_{12} = 0$$

$$S_{22} = 0.50 \angle -70^\circ$$

$$S_{21} = 5.00 \angle 60^\circ$$

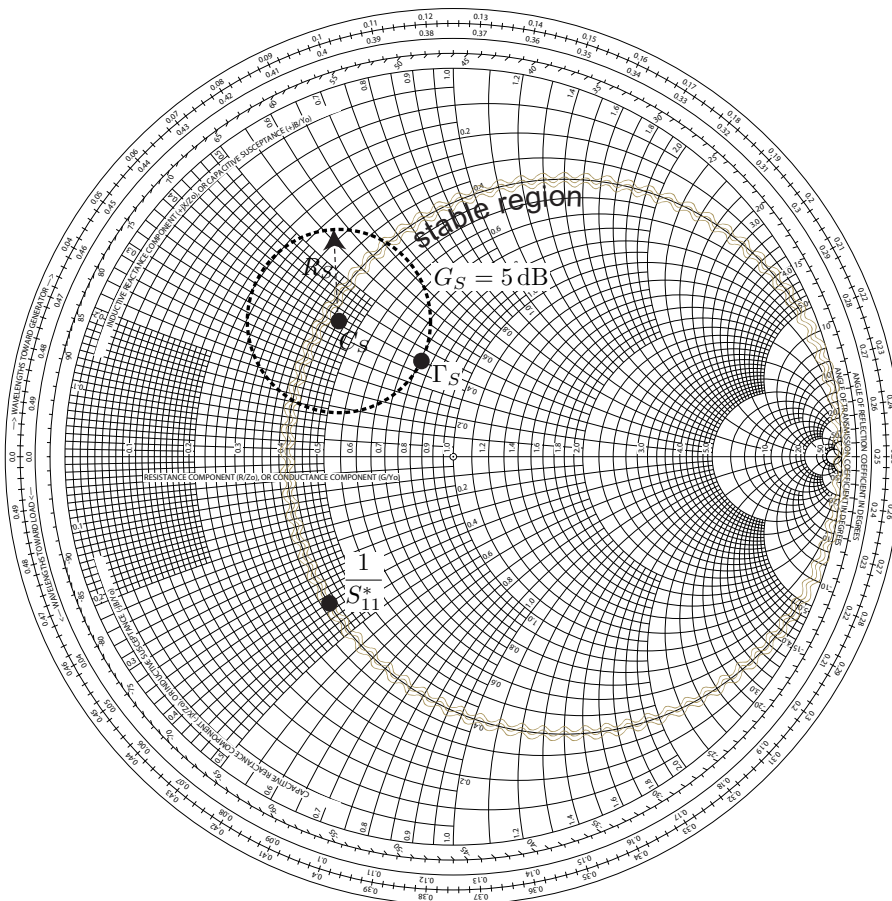

- Since  $|S_{11}| > 1$ , the amplifier is potentially unstable. We begin by plotting  $1/S_{11}^*$  to find the negative real input resistance.
- Now any source inside this circle is stable, since  $\Re(Z_S) > \Re(Z_{in})$ .
- We also draw the source gain circle for  $G_S = 5$  dB.

## Amp Example (cont)

- The input impedance is read off the Smith Chart from  $1/S_{11}^*$ . Note the real part is interpreted as negative

$$Z_{in} = 50(-0.4 - 0.4j)$$

- The  $G_S = 5$  dB gain circle is calculated as follows

$$g_S = 3.15(1 - |S_{11}|^2)$$

$$R_S = \frac{\sqrt{1 - g_S}(1 - |S_{11}|^2)}{1 - |S_{11}|^2(1 - g_S)} = 0.236$$

$$C_S = \frac{g_S S_{11}^*}{1 - |S_{11}|^2(1 - g_S)} = -.3 + 0.35j$$

- We can select any point on this circle and obtain a stable gain of 5 dB. In particular, we can pick a point near the origin (to maximize the BW) but with as large of a real impedance as possible:

$$Z_S = 50(0.75 + 0.4j)$$

# Bilateral Amp Design

- In the bilateral case, we will work with the power gain  $G_p$ . The transducer gain is not used since the source impedance is a function of the load impedance.  $G_p$ , on the other hand, is only a function of the load.

$$G_p = \frac{|S_{21}|^2 (1 - |\Gamma_L|^2)}{\left(1 - \left|\frac{S_{11} - \Delta \Gamma_L}{1 - S_{22} \Gamma_L}\right|^2\right) |1 - S_{22} \Gamma_L|^2} = |S_{21}|^2 g_p$$

- It can be shown that  $g_p$  is a circle on the  $\Gamma_L$  plane. The radius and center are given by

$$R_L = \frac{\sqrt{1 - 2k|S_{12}S_{21}|g_p - |S_{12}S_{21}|^2g_p^2}}{\left|-1 - |S_{22}|^2g_p + |\Delta|^2g_p\right|^2}$$

$$C_L = \frac{g_p(S_{22}^* - \Delta^* S_{11})}{1 + g_p(|S_{22}|^2 - |\Delta|^2)}$$

## Bilateral Amp (cont)

- We can also use this formula to find the maximum gain. We know that this occurs when  $R_L = 0$ , or

$$1 - 2k|S_{12}S_{21}|g_{p,max} + |S_{12}S_{21}|^2g_{p,max}^2 = 0$$

$$g_{p,max} = \frac{1}{|S_{12}S_{21}|} \left( K - \sqrt{K^2 - 1} \right)$$

$$G_{p,max} = \left| \frac{S_{21}}{S_{12}} \right| \left( K - \sqrt{K^2 - 1} \right)$$

- The design procedure is as follows
  1. Specify  $g_p$
  2. Draw operation gain circle.
  3. Draw load stability circle. Select  $\Gamma_L$  that is in the stable region and not too close to the stability circle.
  4. Draw source stability circle.
  5. To maximize gain, calculate  $\Gamma_{in}$  and check to see if  $\Gamma_S = \Gamma_{in}^*$  is in the stable region. If not, iterate on  $\Gamma_L$  or compromise.