

# 21

4/17/03

14

## BROADBAND AMP DESIGN

FREQ VARIATIONS DUE TO

- (1)  $|S_{21}|$  AS A FUNCT OF FREQ  
 $|S_{12}|$  AS A FUNCT OF FREQ


$S_{21} \downarrow$  6dB/OCTAVE

$S_{12} \uparrow$  6dB/OCTAVE

- (2)  $S_{11}$  &  $S_{22}$  FREQ DEPENDENT

### SOLUTION

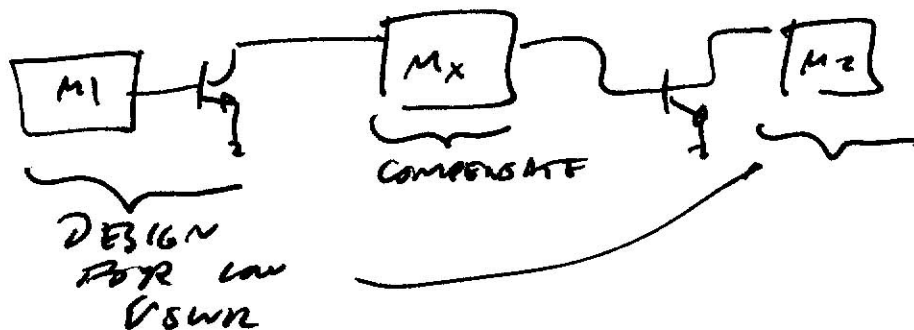- (1) COMPENSATION : MAKE  $M_1$  &  $M_2$   
MATCHING NETWORKS THAT COMPENSATE  
FOR VARIATIONS IN  $S_{21}$




→ NETWORK SYNTHESIS

→ IMPERATION LOSS TECHNIQUE "ACTIVE FILTER"

- (2) BALANCED AMPLIFIERS  
(3) FEEDBACK  
(4) DISTRIBUTED AMPS

# BALANCED AMPS (MIDTERM)

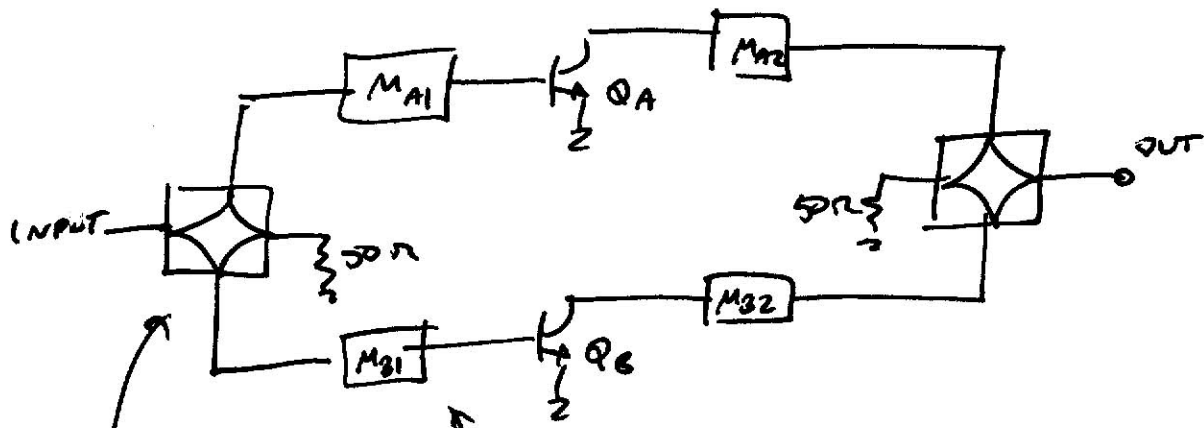

USE BROADBAND COUPLER

MATCH FOR OPTIMIZED NOISE!

$$|S_{11}| = \frac{1}{2} (S_{11A} - S_{11B}) \approx 0$$

$$|S_{21}| = \frac{1}{2} (S_{21A} + S_{21B}) \approx S_{21A}$$

$$|S_{12}| = \frac{1}{2} (S_{12A} + S_{12B})$$

$$|S_{22}| = \frac{1}{2} (S_{22A} - S_{22B}) \approx 0$$

$$NF = \frac{1}{2} (NFA + NFB)$$


USE MATCHED AMPS

ADVANTAGES:

- GOOD STABILITY
- OIP POWER TRICE
- IF ONE AMP FAILS, UNIT STILL OPERATES
- EACH INDIVIDUAL AMP DESIGNED FOR FLAT-GAIN, NOISE FIGURE ... AND IIP & OIP MATCH PROVIDED BY COUPLER


→ HIGHER COST (HIGHER POWER) LARGER AREA

### 3-dB WILKINSON POWER DIVIDER

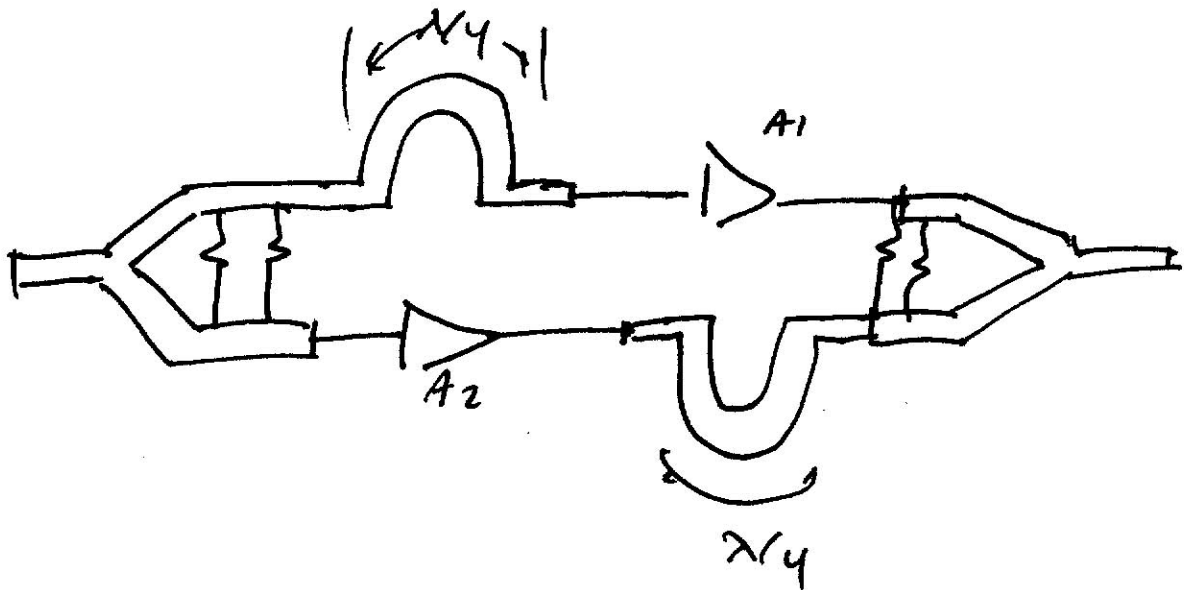

POWER SPLIT IN PHASE &  $\lambda/4$  LINE PROVIDES  $90^\circ$  SHIFT

### ISOLATOR<sup>2</sup> ANOTHER CHOICE

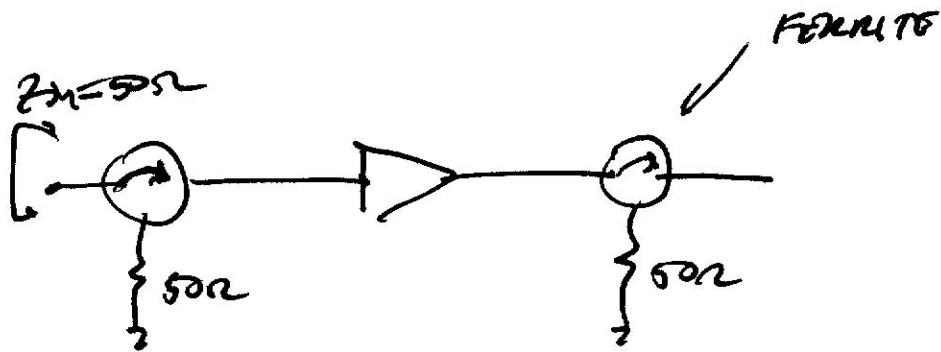


OFTEN USED TO ISOLATE THE PA FROM CHANGING LOAD ENVIRONMENT

# DISTRIBUTED AMPLIFIERS

→ ALSO CALLED A TRAVELING WAVE AMPLIFIER

FANCY NAME BUT A VERY SIMPLE CONCEPT...

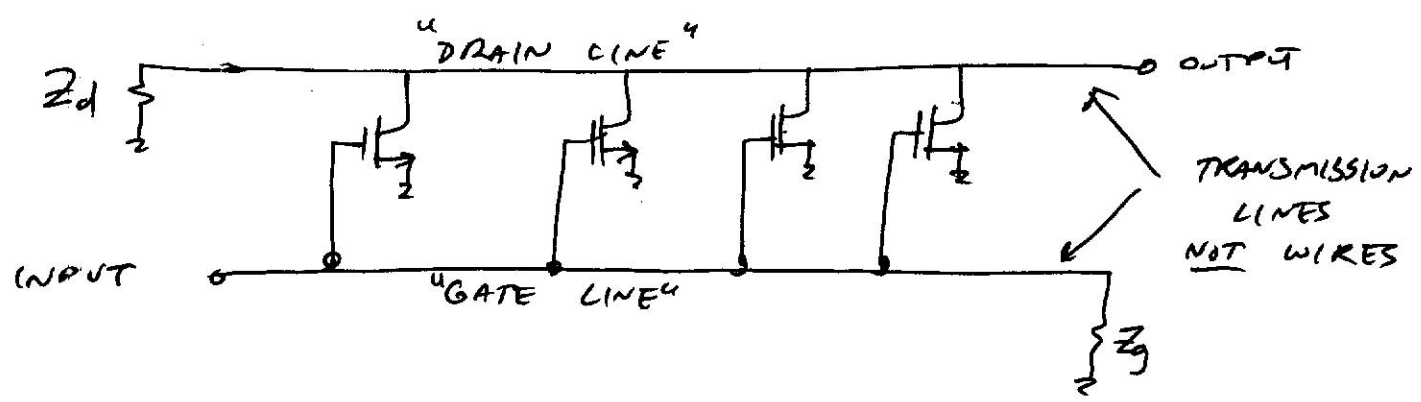

- ASSUME IDEAL TRANSISTORS WITH NO PARASITICS

$$i_d = g_m v_{gs}$$

→ GATE & DRAIN DO NOT LOAD LINES

- NOW EXCITE A WAVE ON THE GATE LINE (SINUSOID OR NON-SINUSOID)


- THE GATE LINE IS TERMINATED IN ITS CHAR IMP  $Z_g$  & THE INPUT IS DRIVEN WITH A GENERATOR OF IMPEDANCE  $Z_g$

→ SAME AT OUTPUT ( $Z_d$ )

- IDEAL TEM TRANSMISSION LINE HAS A INFINITE CUTOFF FREQ

- ASSUME GATE AND DRAIN LINE HAVE EQUAL PROPAGATION VELOCITY  $\beta_g = \beta_d$  AND ZERO LOSS  $\alpha = 0$
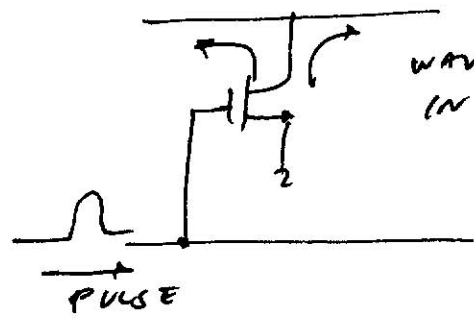
$$V_g(z) = e^{-j\beta z} \frac{V_s}{2} \qquad V_{gn} = \frac{V_s}{2} e^{-(n-1)j\beta_g l_g}$$



$n=1$   
"NO DELAY  
"FIRST GUY"

Q1  $V_o = I_d Z_d$

$$I_d = + \frac{1}{2} \sum_{n=1}^N i_{dn} e^{-(N-n)j\beta_d l_d}$$

$n=N \Rightarrow$  "NO DELAY  
"LAST GUY"

$$i_{dn} = -g_m V_{gs}$$

$$I_d = - \frac{g_m V_s}{4} \sum_{n=1}^N e^{-(n-1)j\beta_g l_g} \cdot e^{-(N-n)j\beta_d l_d}$$

$$= - \frac{g_m V_s}{4} e^{-Nj\beta_d l_d} e^{j\beta_g l_g} \sum_{n=1}^N e^{-nj(\beta_g l_g - \beta_d l_d)}$$

ENFORCE SYNCHRONIZATION

$$\rightarrow \beta_g l_g = \beta_d l_d = \beta l$$

$$I_d = - \frac{g_m V_s}{4} e^{-Nj\beta l} e^{j\beta l} \cdot N$$

↑  
CURRENT  
SUM (IN  
PHASE

$$G = \frac{P_{out}}{P_{in}} = \frac{\frac{1}{2} |I_d|^2 Z_d}{\frac{1}{2} |V_s|^2 / Z_g} = \frac{g_m^2 Z_d Z_g N^2}{4}$$

FOR THIS SIMPLE CASE THE GAIN INCREASES LIKE  $N^2$  AND THE BW IS INFINITE!


THIS IS AN ENCOURAGING START ---

① GAIN INC IS MILD; CASCADE GIVES  $G_0^N$

PRACTICAL CASE: - TRANSISTOR HAS LOSSES


- TRANSMISSION LINE HAS LOSSES

SIMPLE TRANSISTOR MODEL

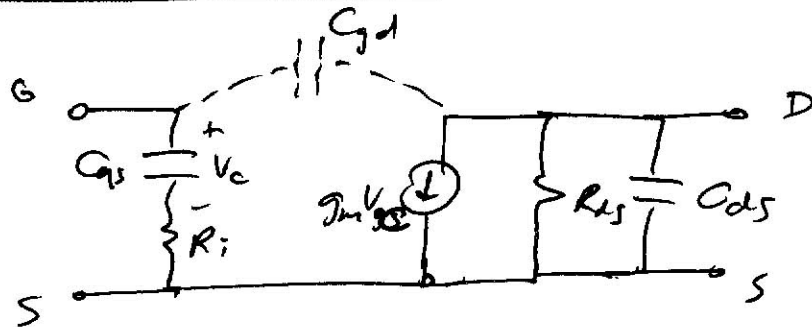


- TRANSISTOR WILL LOAD LINE
- LOSSES WILL INCREASE T-LINE LOSSES

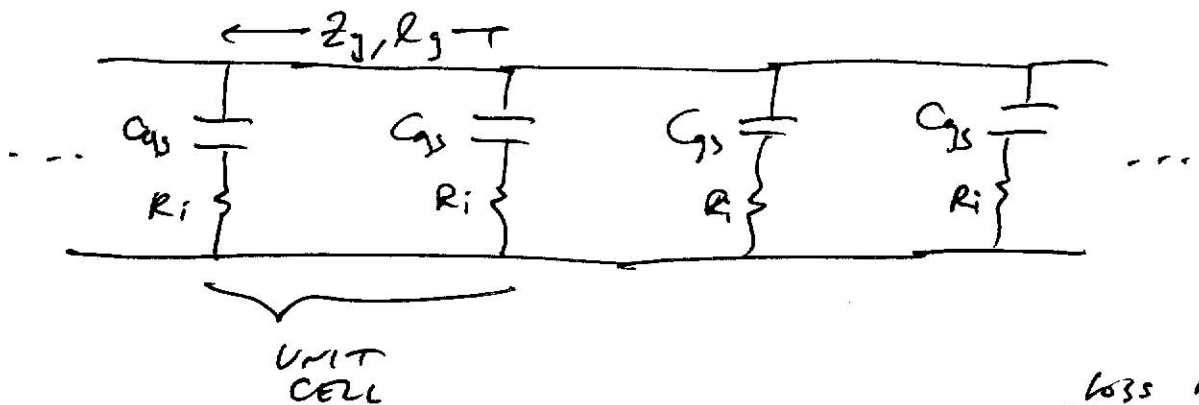ASSUME TRANSISTOR IS UNILATERAL  $C_{gd} = 0$   
GATE LINE:




EQ CIRCUIT

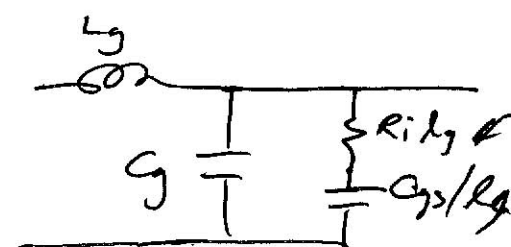


LOSSES PER UNIT CELL

DRAIN LINE

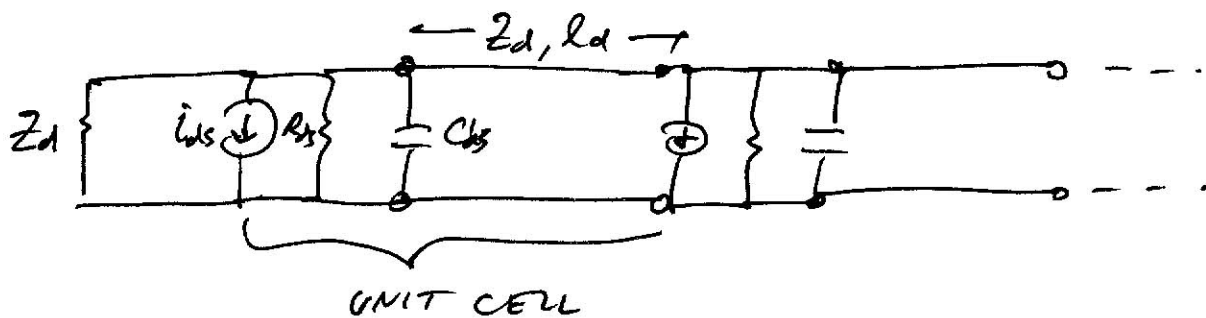

DIST  
EQV CIRCUIT OF UNIT CELL

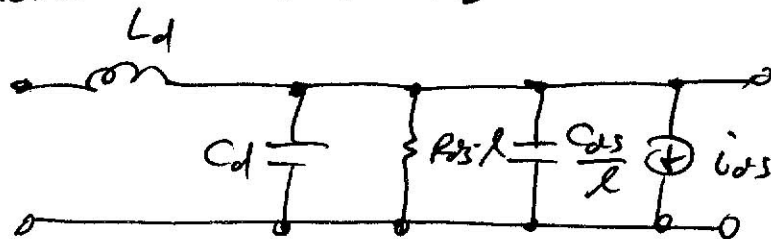

GATE

$$Z = j\omega L_g$$

$$Y = j\omega C_g + \frac{j\omega C_{gs}/l_g}{1 + j\omega R_i C_{gs}}$$

$$Z_g = \sqrt{\frac{Z}{Y}} \approx \sqrt{\frac{L_g}{C_g + C_{gs}/l_g}}$$

low loss

$$\gamma_g = \alpha_g + j\beta_g = \sqrt{ZY}$$

$$= \sqrt{j\omega L_g \left( j\omega C_g + \frac{j\omega C_{gs}/l_g}{1 + j\omega R_i C_{gs}} \right)}$$

$$\approx \sqrt{-\omega^2 L_g \left( C_g + C_{gs} (1 - j\omega R_i C_{gs})/l_g \right)}$$

DRAIN

$$Z = j\omega L_d$$

$$Y = \frac{1}{R_{ds} L_d} + j\omega (C_d + C_{ds}/L_d)$$

$$Z_0 = \sqrt{\frac{Z}{Y}} \approx \sqrt{\frac{L_d}{C_d + C_{ds}/L_d}}$$

$$\begin{aligned} \gamma_d &= \alpha_d + j\beta_d = \sqrt{(j\omega L_d) \left( \frac{1}{R_{ds} L_d} + j\omega (C_d + C_{ds}/L_d) \right)} \\ &\approx \frac{Z_d}{2R_{ds} L_d} + j\omega \sqrt{L_d (C_d + C_{ds}/L_d)} \quad \uparrow \text{dominates} \end{aligned}$$

REDO GAIN CALC

$$V_{gsn} = \frac{V_s}{2} e^{-(n-1)\tau_g L_g} \underbrace{\left( \frac{1}{1 + j\omega R_i C_{gs}} \right)}_{\text{VOLTAGE DIV } \approx 1}$$

$$I_d = -\frac{g_m V_s}{4} e^{-N\tau_d L_d} e^{\tau_g L_g} \underbrace{\sum_{n=1}^N e^{-n(\tau_g L_g - \tau_d L_d)}}_{\text{SUM}}$$

$$I_d = -\frac{g_m V_s}{4} \frac{e^{-N\tau_g L_g} - e^{-N\tau_d L_d}}{e^{-\tau_g L_g} - e^{-\tau_d L_d}}$$

$$G = \frac{g_m^2 Z_d Z_g}{4} \frac{\left( e^{-N\alpha_g L_g} - e^{-N\alpha_d L_d} \right)^2}{\left( e^{-\alpha_g L_g} - e^{-\alpha_d L_d} \right)^2} \approx \alpha_g L_g - \alpha_d L_d$$



GAIN IS NO LONGER A MONOTONIC FUNC OF N BUT PEAKS AT A FINITE N

PHYSICAL EXPLANATION: ADDING AN EXTRA STAGE WILL ONLY IMPROVE GAIN IF THE

PRODUCT OF  $\frac{g_m V_{GS} (A+1) Z_d}{2} > |e^{T_d \omega_d}|$

EXTRA GAIN

ATTEN ON DRAIN LINE

DECREASING EXP.

EVENTUALLY THE POLYNOMIAL INC IN GAIN DUE TO EXTRA STAGE WILL NOT OUTWEIGHT THE EXPONENTIAL LOSS!


TAKE DERIVATIVE

$$N_{opt} = \frac{\ln(\alpha_g l_g / \alpha_d l_d)}{\alpha_g l_g - \alpha_d l_d}$$

GAIN IS NOT FLAT WITH FREQ DUE FREQ DEPENDENCE OF  $\alpha_g$  &  $\alpha_d$

MORE DETAILED CALC... (MY CLASS PROJECT)

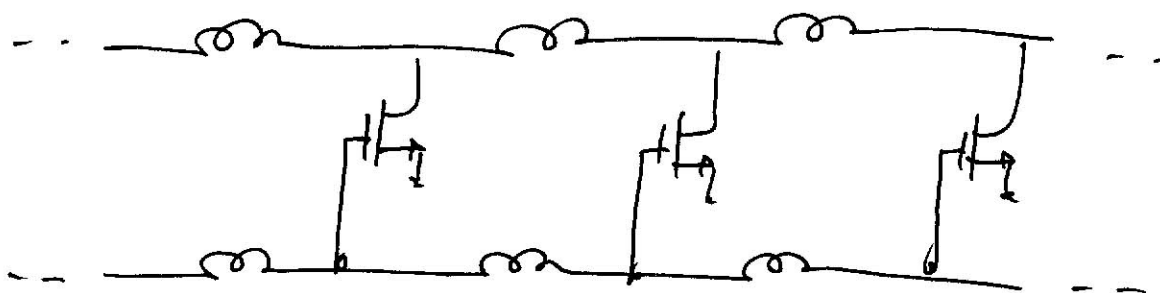
- ANALYZE CIRCUIT AS AN ARTIFICIAL TRANSMISSION LINE USING IMAGE PARAMETER METHOD
- TAKE INTO ACCOUNT LOSSES IN <sup>LUMPED</sup> INDUCTORS



- USE ~~B~~BISECTED-TO  $n$ -DERIVED MATCHING NETWORKS TO COMPENSATE FOR FREQ DEP OF T-LINE

$$G = \frac{\text{Re}(Z_{id})}{\text{Re}(Z_{i0}')} |Z_{i0}|^2 \frac{g_m^2 |S|^2 \sinh^2 \left[ \frac{n}{2} (\alpha_d - \alpha_g) \right] e^{\dots}}{4 \left( 1 + \left( \frac{\omega}{\omega_0} \right)^2 \right) \sinh^2 \left( \frac{1}{2} (\alpha_d - \alpha_g) \right)}$$

$- n(\alpha_d + \alpha_g)$

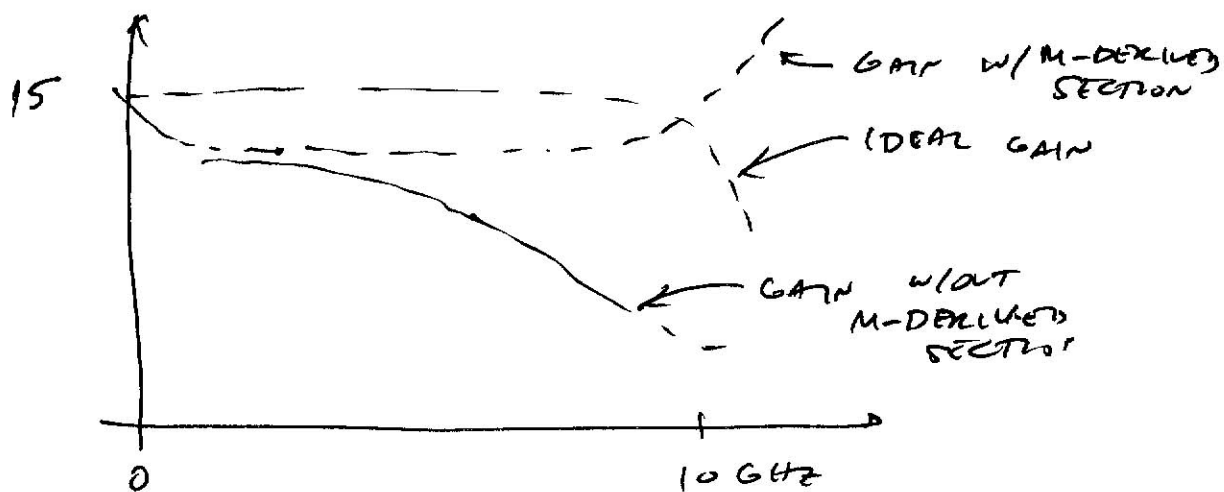

## ZERO LOSS ATTENUATION FACTOR

$$Z_1 = \sqrt{\frac{L}{C} \left( 1 - \left( \frac{\omega}{\omega_c} \right)^2 \right)}$$

$$e^{\gamma} = 1 - \frac{2\omega^2}{\omega_c^2} + \frac{2\omega}{\omega_c} \sqrt{\frac{\omega^2}{\omega_c^2} - 1}$$

$$\omega_c = \frac{2}{\sqrt{LC}}$$

$\omega_c$  IS CUTOFF FREQ  
OF ARTIFICIAL LINE

## 'BEYER' DESIGN METH. FOR LOW LOSS

$$\alpha_g = \frac{2a X_k^2}{n \sqrt{1 + \left( \frac{4a^2}{n^2} - 1 \right) X_k^2}}$$

$$\alpha_d = \frac{2b}{n \sqrt{1 - X_k^2}}$$

$$X_k = \frac{\omega}{\omega_c}$$

$$a = \frac{n \omega_c}{2 \omega_g}$$

$$b = \frac{n \omega_d}{2 \omega_c}$$

NORMAL  
PARAM

$$\omega_g = \frac{1}{R_i C_{gs}}$$

$$\omega_d = \frac{1}{C_{ds} R_{ds}}$$

$$A_N = \frac{\sinh\left(\frac{b}{n}\right) e^b \sinh \eta_- e^{-\eta_+}}{\sinh(b) \left( 1 + \frac{4a^2}{n^2} X_k^2 \right)^{1/2} \sqrt{1 - X_k^2} \sinh \frac{1}{n} \eta_-}$$

$$\eta_{\pm} = \frac{b}{\sqrt{1 - X_k^2}} \pm \frac{a X_k^2}{\sqrt{1 + \left( \frac{4a^2}{n^2} - 1 \right) X_k^2}}$$

$$A_0 = \text{LF GAIN} = \frac{g_m \sqrt{R_{o1} R_{o2}} \sinh b e^{-b}}{2 \sinh \left( \frac{b}{u} \right)}$$

⇒ THREE PARAM DETERMINE PERF:  $a, b, u$

$$\frac{A_0 f_c}{4 f_{\max}} = \sqrt{ab} e^{-b} = K$$

$$A_0 f_c = 4K X f_{\max}$$

$$f_{\max} \cong \frac{g_m}{4\pi C_D} \sqrt{\frac{R_{o2}}{R_i}}$$

$$X = \frac{f_{-10\text{dB}}}{f_c} \quad \text{FRAC BANDWIDTH}$$

$KX$  IS GAIN BW PRODUCT NORMALIZED TO  $4 f_{\max}$


$$KX \approx 0.2 \Rightarrow A_0 f_{10\text{dB}} \approx 0.8 f_{\max}$$

↑  
LIMIT OF BROADBAND DESIGN!

$$A_0 = 10 \Rightarrow f_{10\text{dB}} = \underbrace{0.08 f_{\max}}_{100\text{kHz}} \\ \underbrace{\hspace{10em}}_{86\text{kHz}}$$
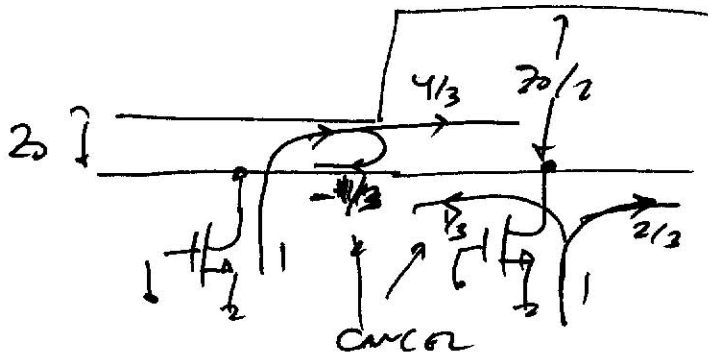
## TAPERED DRAIN LINE $\frac{1}{2}$ OF POWER

ON DRAIN LINE IS WASTED INTO TERMINATION RESISTANCE, BY TAPERING LINE WE CAN REDUCE CURRENT IN "BACKWARD" DIRECTION



$$\frac{Z_0}{Z_0/2 + Z_0} = \frac{2}{3}$$

$$\frac{Z_0/2 - Z_0}{Z_0/2 + Z_0} = \frac{2-1}{2+1} = -\frac{1}{3}$$

DESIGN SO ALL CURRENT GOING INTO  $Z_0$

CANCEL  $\Rightarrow$  EACH SECTION HAS IMPEDANCE  $Z_0/K$