

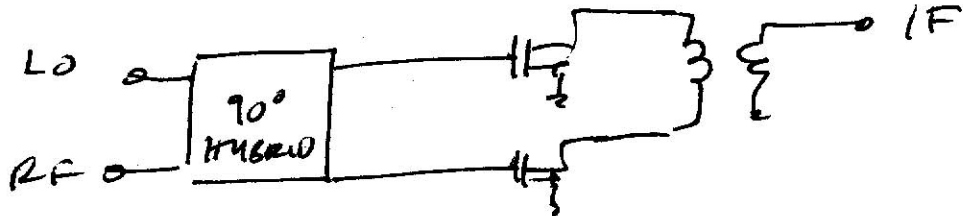
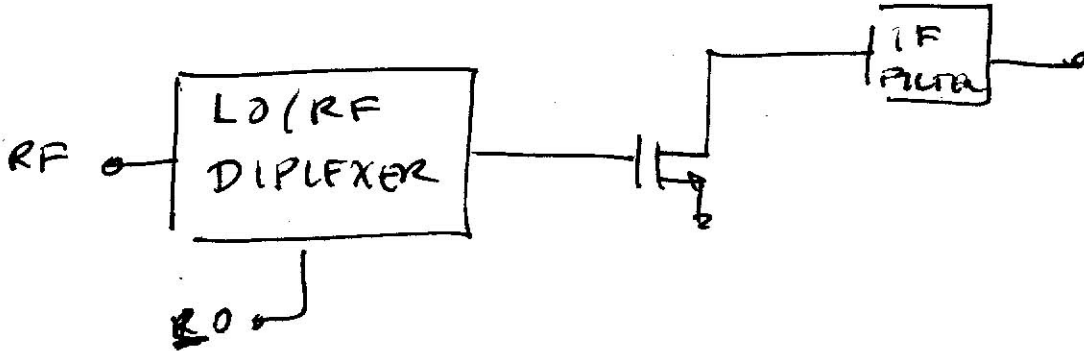


GATE DRIVEN MIXER

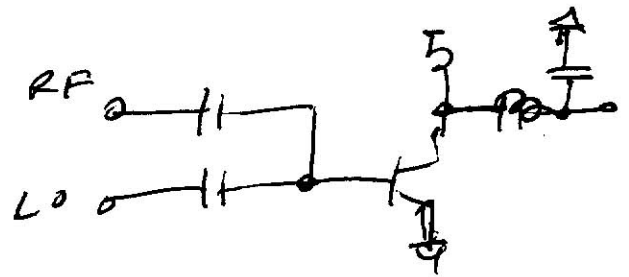

QUADRATURE BALANCED MIXER


SOURCE DRIVEN MIXER

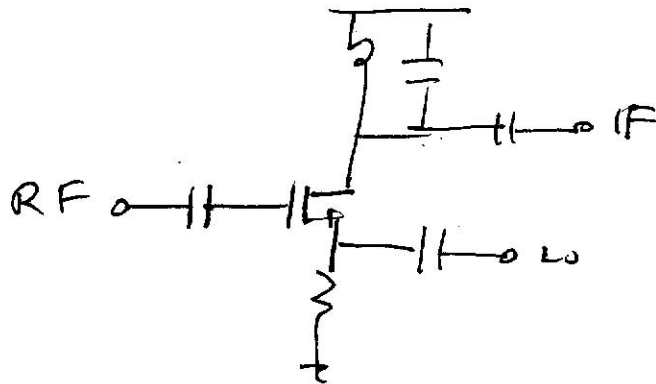

BETTER LO/RF ISOLATION BUT NOT GREAT



DUAL GATE MIXER

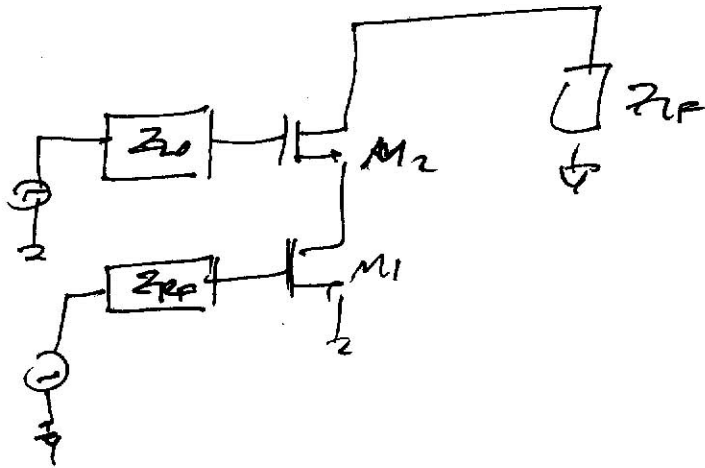


LO MODULATES THE
Gm OF M1 BY
CHANGING Vds

LO/RF ISOLATION GOOD

DON'T NEED TO COMBINE LO/RF SIGNALS

CONVERSION GAIN FROM M1

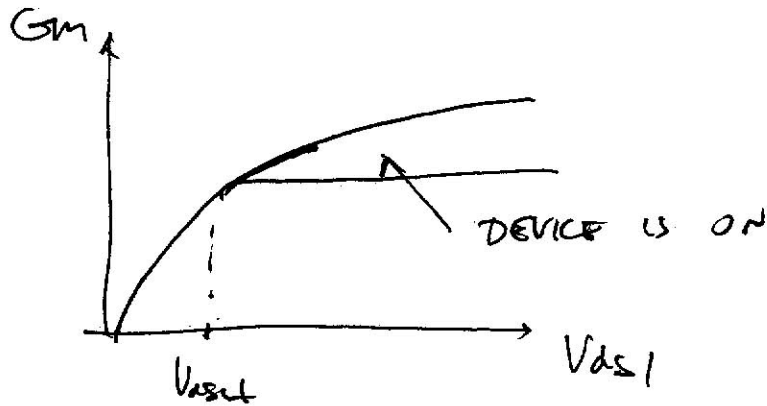


$$I_{ds} = \left\{ \mu_{cox} \left(\frac{w}{L} \right) \left\{ (V_{gs} - V_t) V_{ds} - \frac{V_{ds}^2}{2} \right\} (1 + \lambda V_{ds}) \right.$$

$$\left. \mu_{cox} \left(\frac{w}{L} \right) \frac{1}{2} (V_{gs} - V_t)^2 (1 + \lambda V_{ds}) \right.$$

$$G_m \approx \begin{cases} \mu_{cox} \left(\frac{w}{L} \right) (V_{gs} - V_t) V_{ds} \\ \mu_{cox} \left(\frac{w}{L} \right) (V_{gs} - V_t) (1 + \lambda V_{ds}) \end{cases}$$

CURRENT COMMUTATING MIXERS (GAIN)

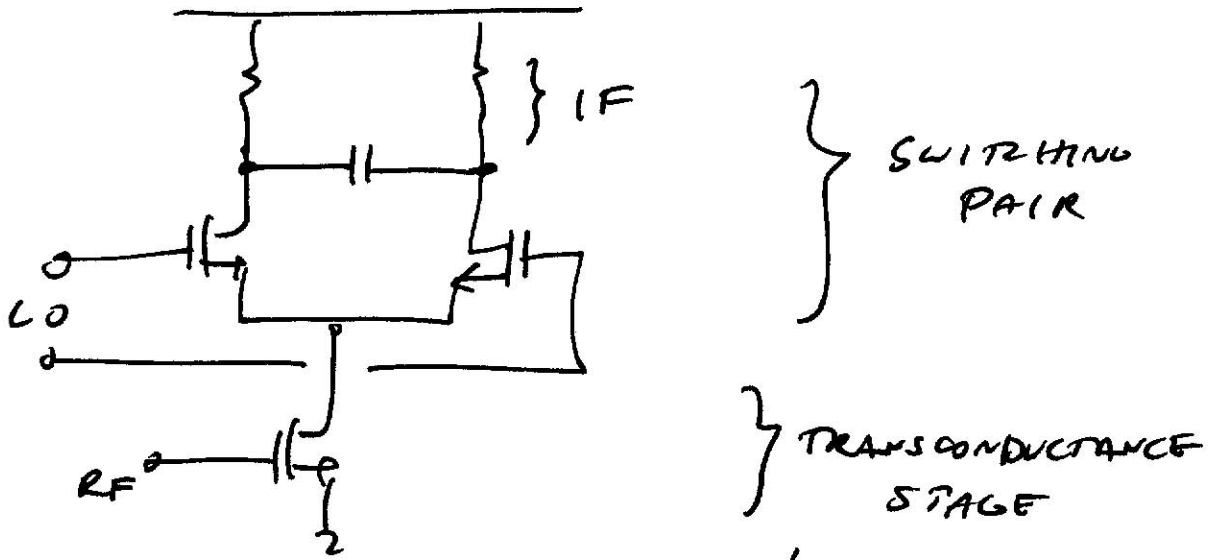


MULTIPLY SIGNAL $2k \approx \frac{1}{2} + 1$ + HAVE DC CONTENT
 $A_V < \frac{2}{\pi} g_m R_L$ STRONG SWITCHING ASSUMP

LO & RF ISOLATION PRETTY GOOD
 BUT LO APPEARS IN O/P

STRONG LO COULD SATURATE IF AMP
 (EVEN AFTER FILTERING)

DOUBLE BALANCED MIXER

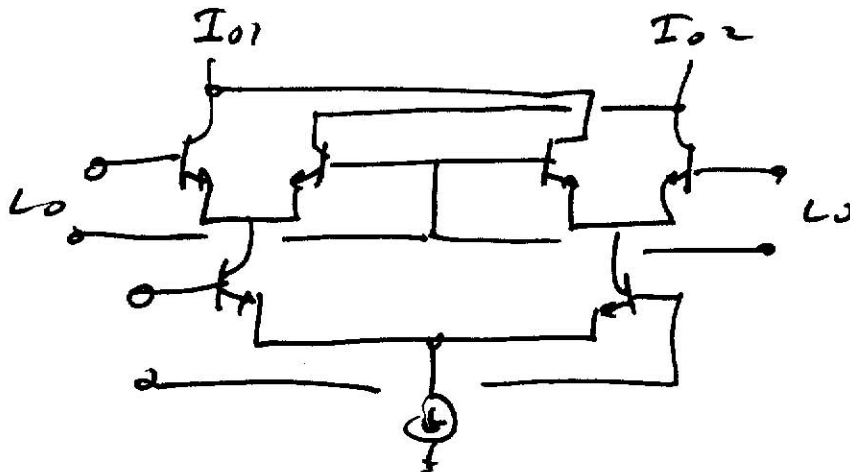


$$I_0 = I_{D1} - I_{D2} = (I_1 + I_3) - (I_2 + I_4)$$

→ LO REJECTED UP TO MATCHING

CAN SHOW THAT FLICKER NOISE OF INPUT DEVICES IS UP-CONVERTED BUT FLICKER NOISE OF SWITCHING DEVICES CAN DEGRADATE SNR AT IF.

OPTION 1: USE PMOS SWITCHING PAIR

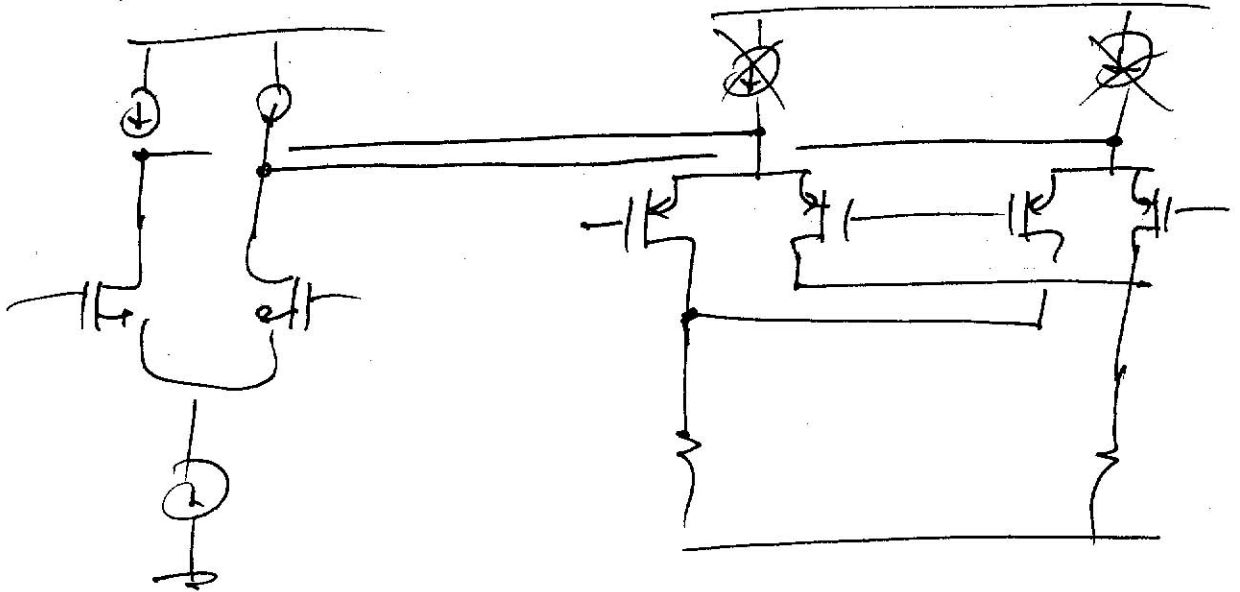


PROPOSED DESIGN

NMOS INPUT \Rightarrow HIGH G_m


PMOS SWITCH \Rightarrow LOW FN

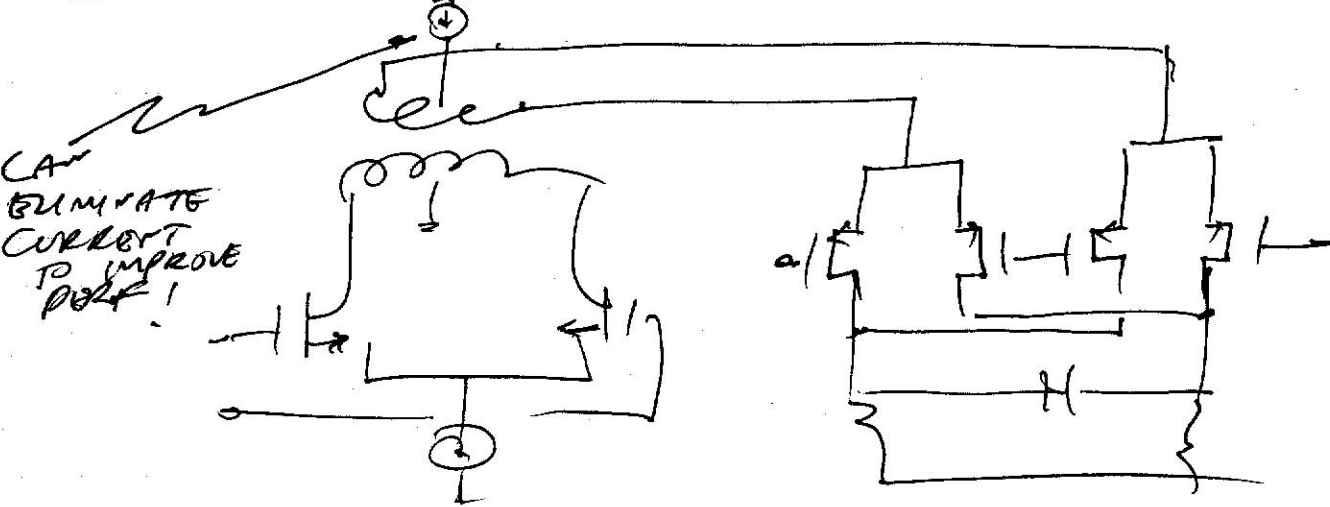OR TRANSFORMER COUPLE: IMPROVED HEAD ROOM




CAN ELIMINATE CURRENT TO IMPROVE PSRR!


PASSIVE OR ACTIVE ?

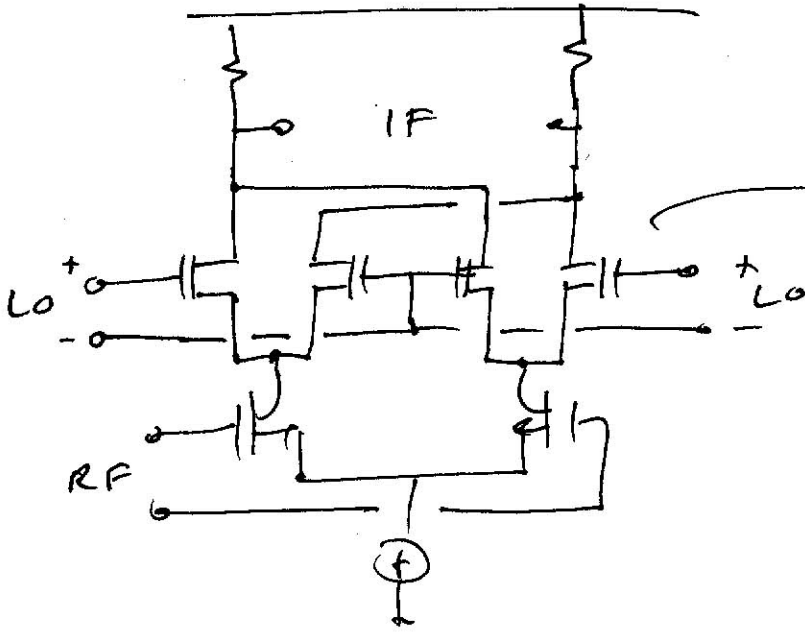

REDRAW

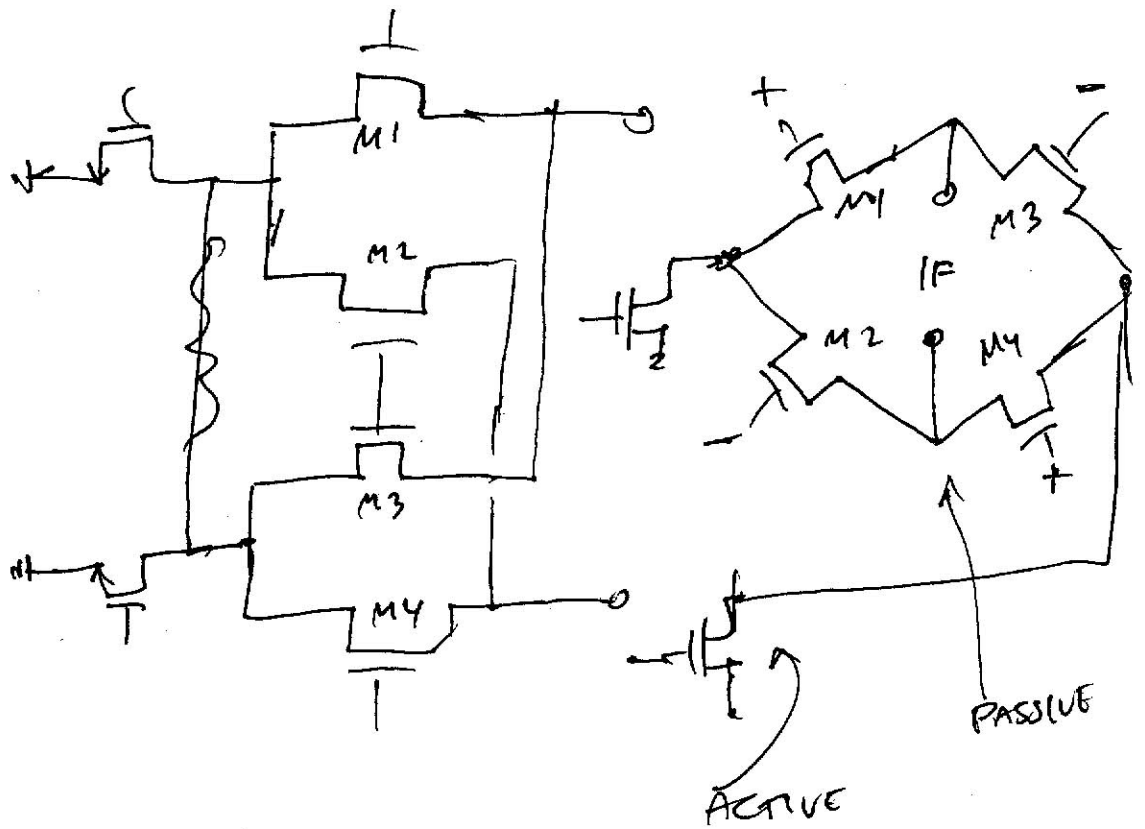

IMPROVED HEADROOM #2: USE CURRENT D/P

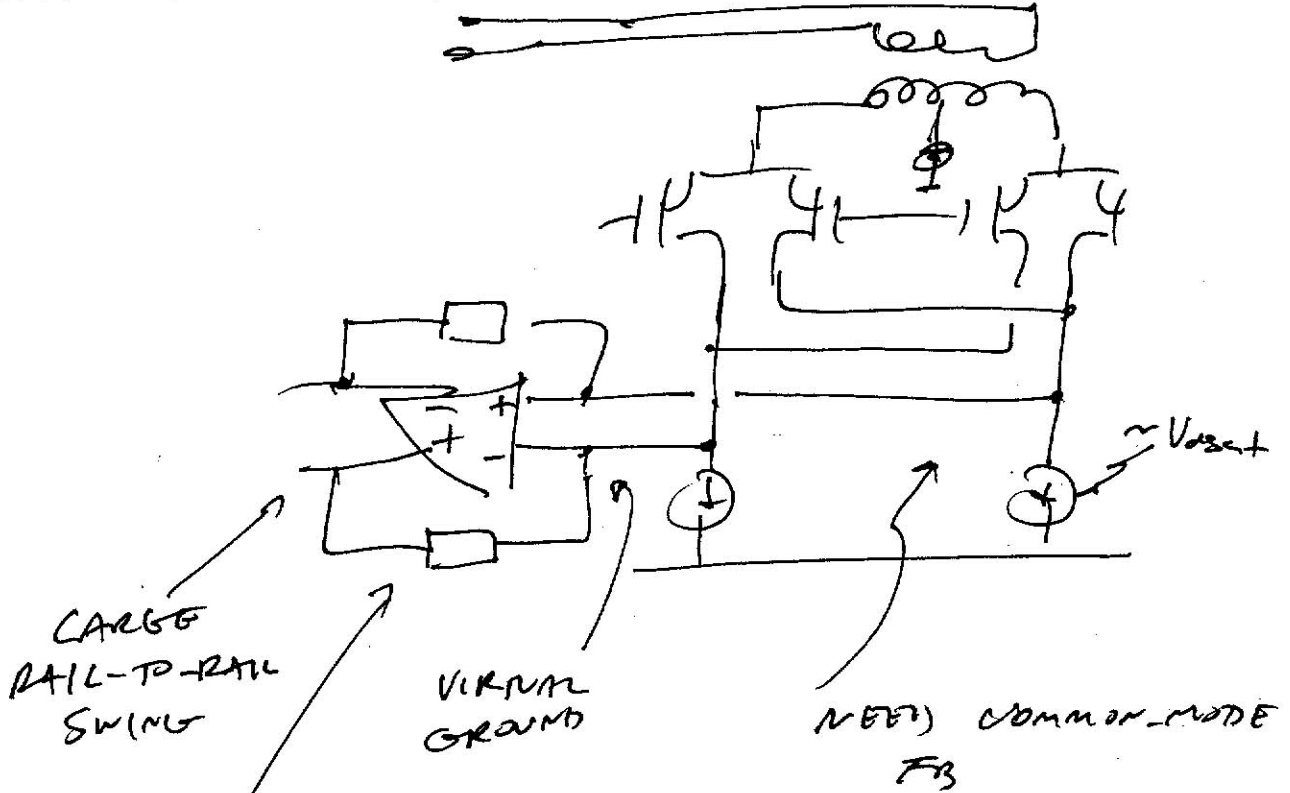


CARRY RAIL-TO-RAIL SWING

VIRTUAL GROUND

NEED COMMON-MODE FB


CAN FORM FIRST STAGE OF LPF (IF)

IMAGE REJECT MIXERS

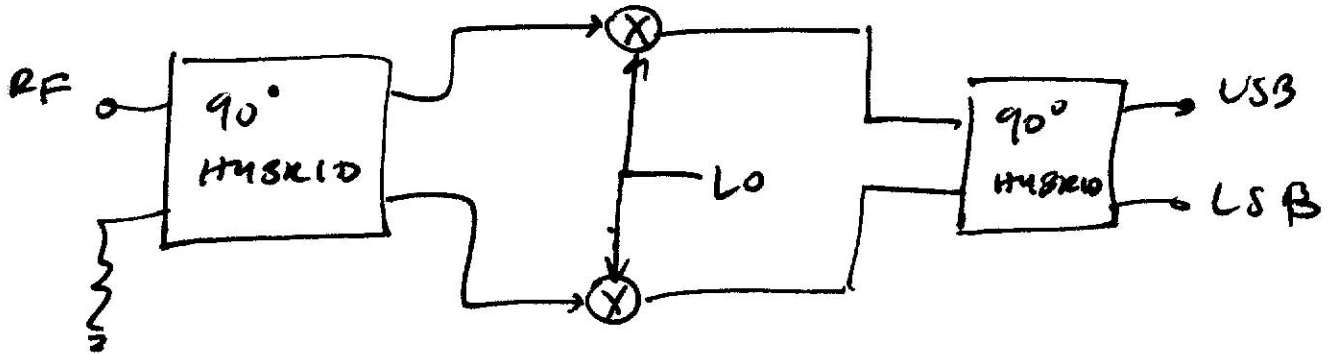


MIXER IS INHERENTLY SENSITIVE TO IMAGE
FREQ :

$$\omega_{IF} = |\omega_{LO} \pm \omega_{RF}|$$

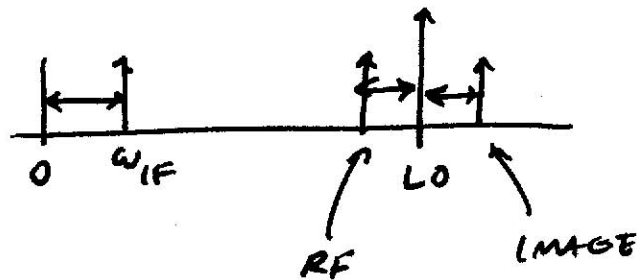

ONE OPTION IS TO FILTER THE IMAGE

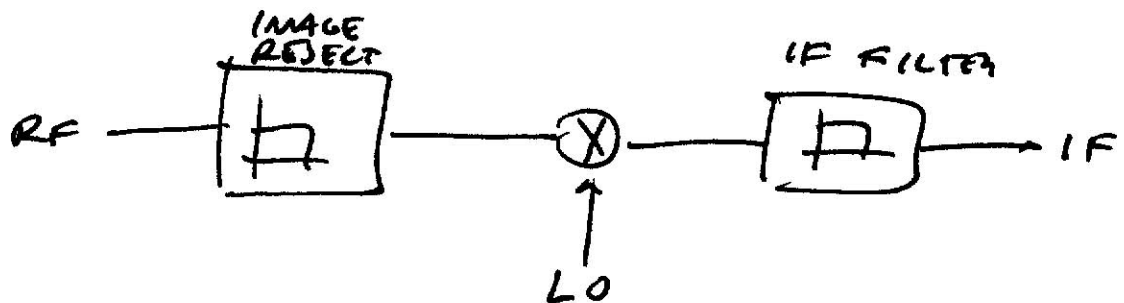


BUT THE FREQ MIGHT BE TOO CLOSE

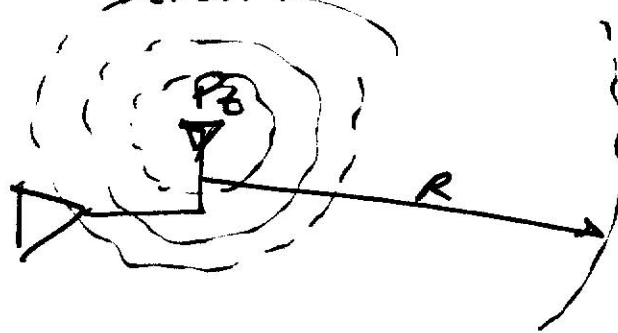(3)

CONSERVATION OF ENERGY ARGUMENT:

IDEAL ISOTROPIC ANT RADIATES
POWER RADially WITH UNIFORM
DENSITY



AT A DISTANCE R FROM SOURCE THE
TOTAL POWER OVER SOLID ANGLE IS THE
SAME AS TRANSMITTED \Rightarrow

$$4\pi R_1^2 S_{R_1} = S_{R_2} 4\pi R_2^2$$

\rightarrow POWER DENSITY DROPS LIKE $1/R^2$

STATIC FIELDS DROP LIKE $1/R^2$ SO POWER
DROPS LIKE $1/R^4$. MUCH FASTER THAN
THE RADIATED FIELD.


AT A DISTANCE $d \gg \lambda$ THE ACCIDENT ENERGY
RADIATION IS DOMINATED BY ELECTRODYNAMIC
RADIATION

ON A TRANSMISSION LINE:

$$\frac{P_2}{P_1} = e^{-\alpha(R_2 - R_1)}$$

MUCH FASTER THAN RADIATION!

POZAR PLOT

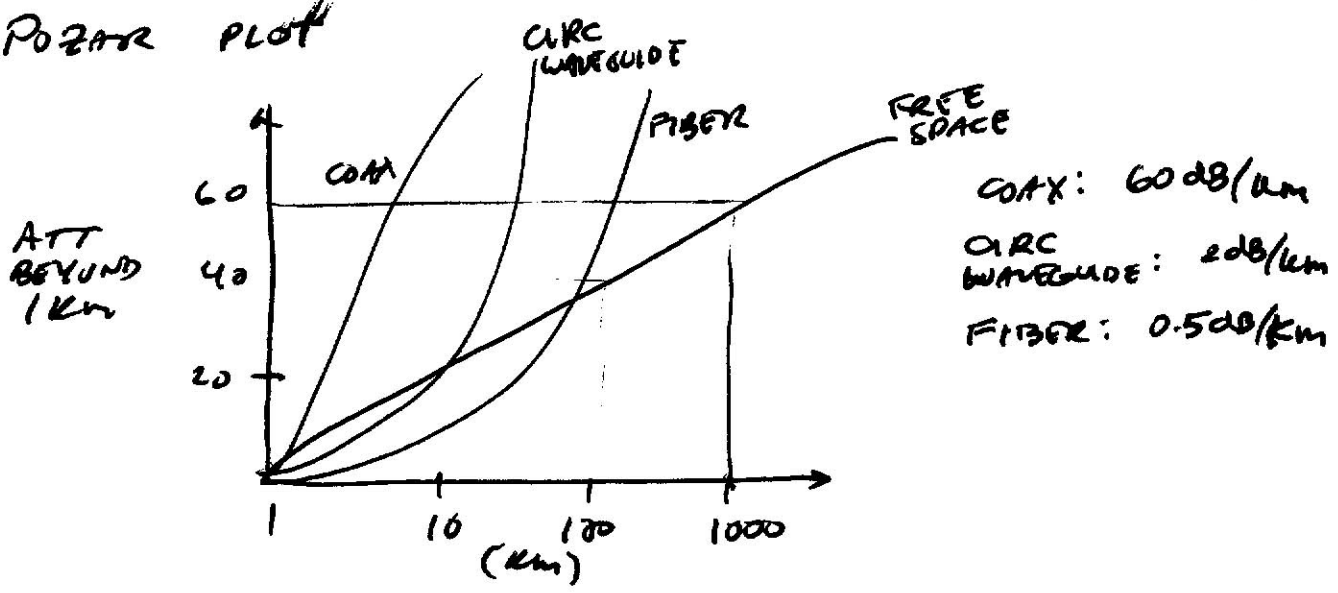


FOR 1000 dB ATTENUATION :

- COAX HAS FEW KM RANGE
- WAVEGUIDE HAS ~ 100 km
- FIBER ~ 1000 km
- FREE SPACE ~ 100,000 km !


LINE OF SITE PROPAGATION LIMITED BY CURV. OF EARTH

$$d \approx \sqrt{15h} \quad (\text{km})$$

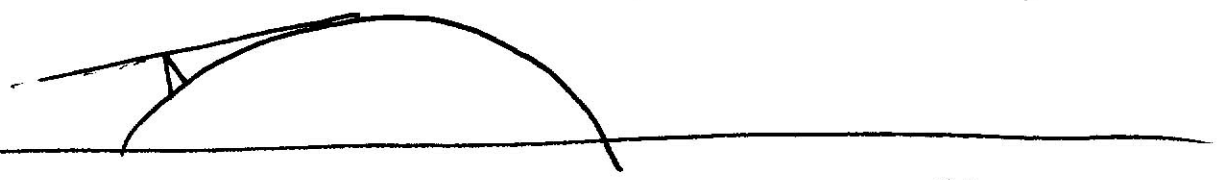- REFL (GROUND)
- DIFF (EDGES)
- SCATT (FOLIAGE)
- ATTEN (RAIN)
- DOPPLER (MOVING)



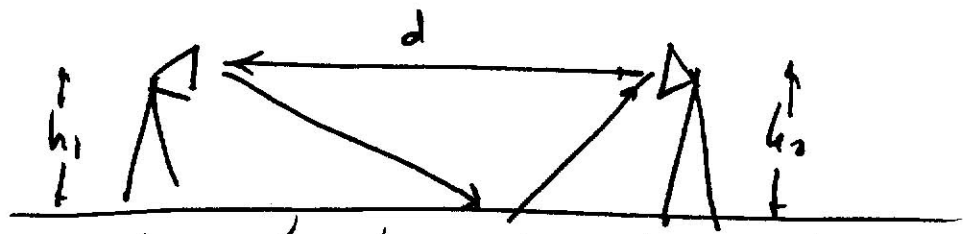REFLECTIONS FROM EARTH INCREASE PROP LOSS :



PROP FACTOR $F = 2 \sin \left(\frac{k_0 h_1 h_2}{d} \right)$

OUT OF PHASE → $0 \leq F \leq 2$ IN PHASE

FOR $d \gg \lambda$ THE FORMULA GIVES THE FOLLOWING SURPRISING RESULT


$$\frac{P_r}{P_t} \propto \frac{1}{R^4}$$

RECALL THAT FREE SPACE $\propto 1/R^2$

REALISTIC PROP. FACTOR PATH LOSS

FREE SPACE	2
URBAN	2.7-3.5
SHADOW URBAN	3-5
IN-BUILDING LOS	1.6-1.8
IN-BUILDING SHADOWED	4-6
FACTORY SHADOWED	2-3
RETAIL STORE	2.2
OFFICE - SOFT PARTITION	2-4

OTHER EFFECTS: LOSS TO ATMOSPHERE

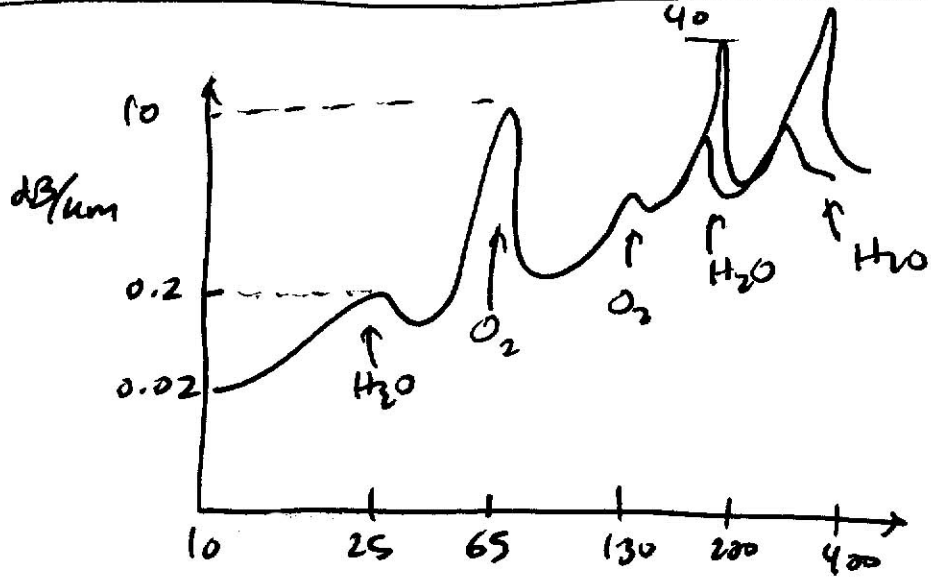

BELOW 10 GHz NO PROBLEM!



ATTENUATION DUE TO MATERIALS

CONCRETE BLOCK WALL	1.3GHz	13dB
SHEET ROCK	9.6GHz	2dB
PLYWOOD	9.6GHz	4dB
CONCRETE WALL	1.3	8-15
CHAIN LINK FENCE	1.3	5-12
LOSS BETWEEN FLOORS	1.3	20-30
CORNER IN CORRIDOR	1.3	10-15

~~FADING~~

MULTI-PATH PROPAGATION

TIME VARYING "CHANNEL"

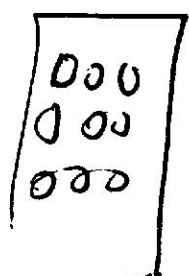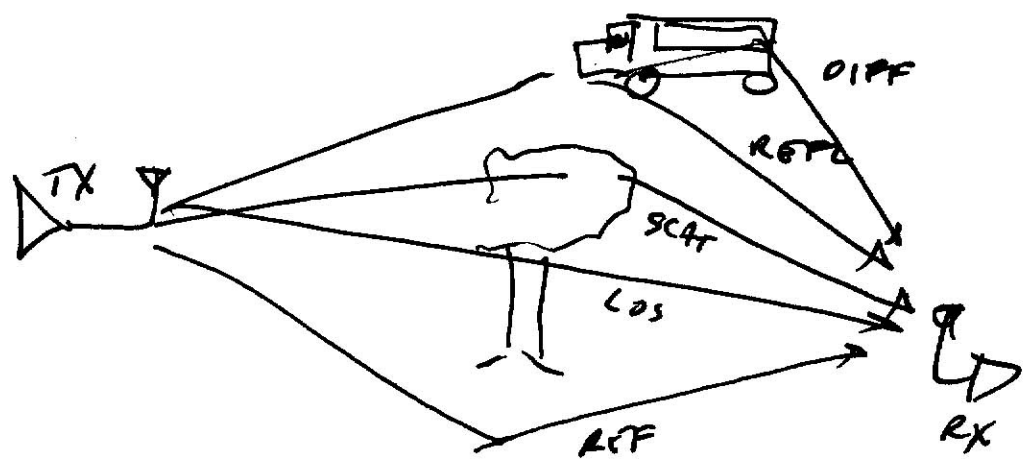

SINCE SIGNALS ARRIVE WITH APPARENTLY RANDOM PHASE, SIGNAL IS SUBJECT TO FADING

RAYLEIGH FADING

$$v(t) = \sum V_n \cos(\omega t + \phi_n)$$

$$= x(t) \cos \omega t - y(t) \sin \omega t$$


$$x(t) = \sum V_n \cos \phi_n \quad y(t) = \sum V_n \sin \phi_n$$

\uparrow \uparrow
 GAUSSIAN WITH ZERO MEAN

$$v(t) = r(t) \cos(\omega t + \theta(t))$$


$$f_{r\theta}(r, \theta) = \frac{e^{-r^2/2\sigma^2}}{2\sigma^2} \quad \begin{array}{l} 0 \leq r < \infty \\ 0 \leq \theta < 2\pi \end{array}$$
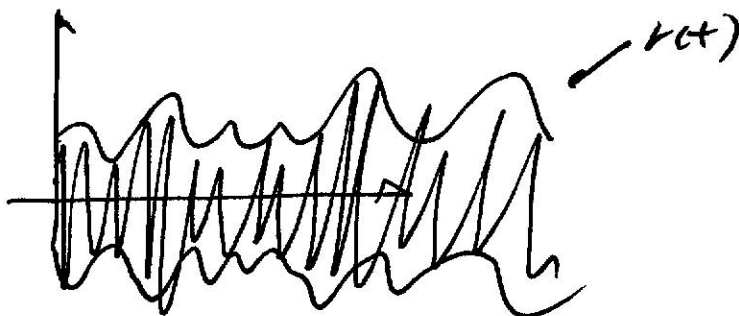
$$f_r(r) = \frac{r e^{-r^2/2\sigma^2}}{\sigma^2} \quad 0 \leq r < \infty$$



FOR ANTENNAS

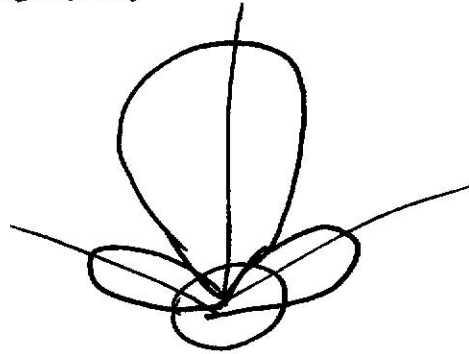RADIATION PATTERN : ~~GAIN~~ NORMALIZE GAIN
AS A FUNCTION OF (θ, ϕ) ... OR FAR-ZONE
FIELD STRENGTH



DIRECTIVITY :

$$D = \frac{U_{max}}{U_{av}}$$

↑
RAD INTENSITY
IN MAIN
BEAM

RADIATION EFFICIENCY :


$$\eta = \frac{P_{rad}}{P_{in}} = 1 - \frac{P_{loss}}{P_{in}}$$

←
OHMIC
LOSSES


EFFECTIVE AREA :

$$P_r = S \cdot A_{eff}$$

$$A_{eff} = \frac{D \lambda^2}{4\pi}$$

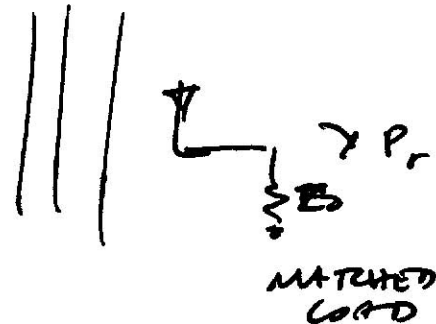

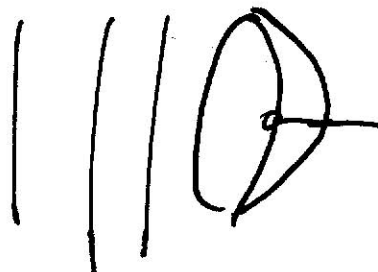$A_{eff} \approx$ PHYSICAL APERTURE AREA IF ANTENNA IS
LARGE ... BUT FOR ELECTRICALLY SMALL
ANTENNAS IT'S A MATH. QUANTITY



FRISS EQ:


$$S_{avg} = \frac{P_t}{4\pi R^2} \quad W/m^2$$

$$P_r = A_{eff} S_{avg} = \frac{G_t P_t A_e}{4\pi R^2} \quad W$$

$$= \frac{G_t G_r \lambda^2}{(4\pi R)^2} P_t$$

VERY PHYSICAL EXPLANATION: $A_{eff} \propto \lambda^2$

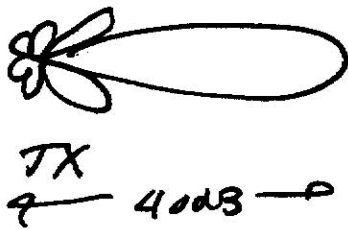
FOR A DISTANCE R, SURFACE AREA IS $\propto R^2$
SO WE INTERCEPT $(\lambda/R)^2$ FRACTION OF ENERGY X GAIN FACTORS:



DIRECTIVE ANTENNAS DIRECT ENERGY IN DESIRED DIRECTION.

NOISE: ANTENNA NOISE TEMP DEPENDS ON WHAT ITS LOOKING AT! (AND FREQ)

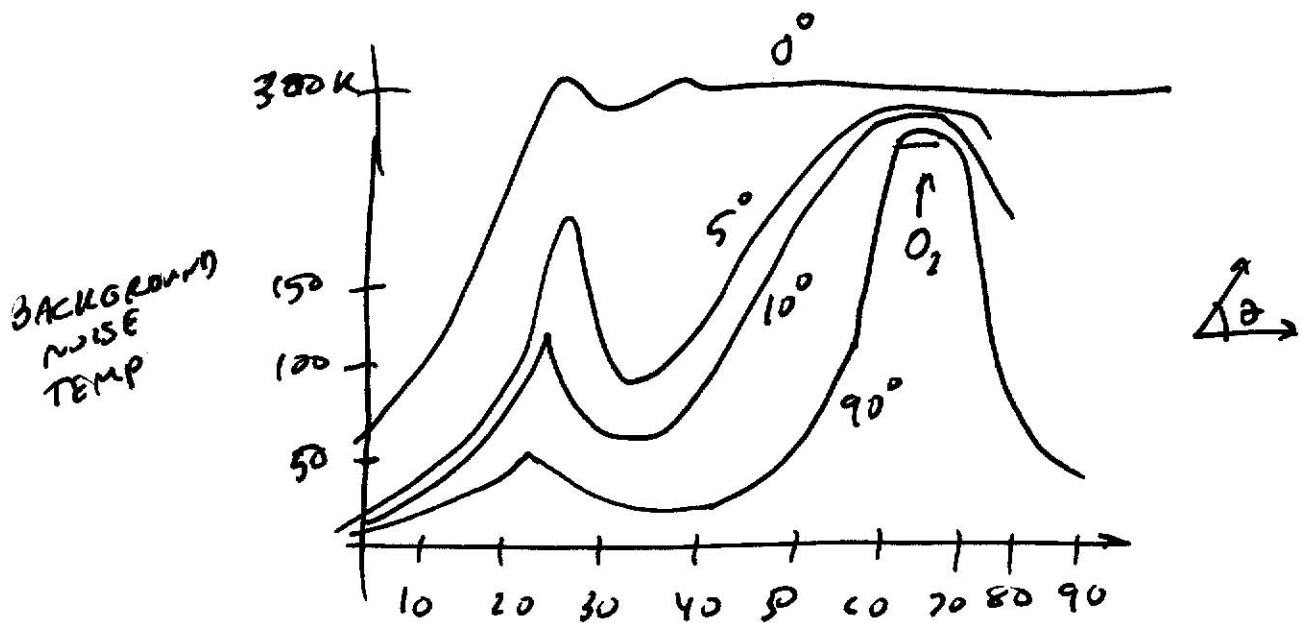- SKY 3-5K (ZENITH)
- SKY 50-100K (TOWARDS HORIZON)
- GROUND 290-300K



SNR AT RECEIVER INPUT:

$$S_i = \frac{G_r G_t P_t \lambda^2}{(4\pi R)^2}$$

$$N_i = k T_A B$$

$$\left(\frac{S}{N}\right)_i = \left(\frac{G_r}{T_A}\right) \frac{G_t P_t \lambda^2}{k B (4\pi R)^2}$$

GOOD METRIC
FOR ANTENNA

RADIATION RESISTANCE:

$$P_r = \frac{1}{2} I_0^2 R_r$$

SMALL DIPOLE $R_r = 20\pi^2 \left(\frac{L}{\lambda}\right)^2$

$$X = \frac{-60\lambda}{\pi L} \left(\ln\left(\frac{L}{a}\right) - 1 \right)$$

$$R_{loss} = \frac{R_s L}{6\pi a}$$

- WANT BIGGER ANTENNA TO INCREASE
 R_r → EASIER TO POWER MATCH
 → MORE EFFICIENT RADIATOR
 → LESS NOISY RX

SAY WE USE A 1cm ANTENNA TO COMM AT
 10 MHz. $Q = 0.01 \text{ cm}$
 $\sigma = 5.8 \times 10^7 \text{ Cu}$

$$R_s = \sqrt{\frac{\omega \mu}{2\sigma}} = \sqrt{\frac{F \cdot 4\pi \times 10^{-7} \cdot 10 \times 10^6}{2 \cdot 5.8 \times 10^7}} = 1.6 \text{ m}\Omega$$

$$R_{\text{loss}} = \frac{R_s L}{6\pi a} = 3 \text{ m}\Omega$$

$$R_{\text{rad}} = 20\pi^2 \left(\frac{L}{\lambda}\right)^2 = 22 \mu\Omega$$

$$\eta = 0.7 \%$$

→ MUST USE HIGHER FREQ FOR EFF COMM


→ IF WE INPUT MATCH ANTENNA (LNA

$R_{in} \approx 0$ CAPACITIVE (OR INDUCTIVE)
 OR LOOP


NOISE DOMINATED BY LOSS RESISTOR

∴ INPUT REFER NOISE OF AMP
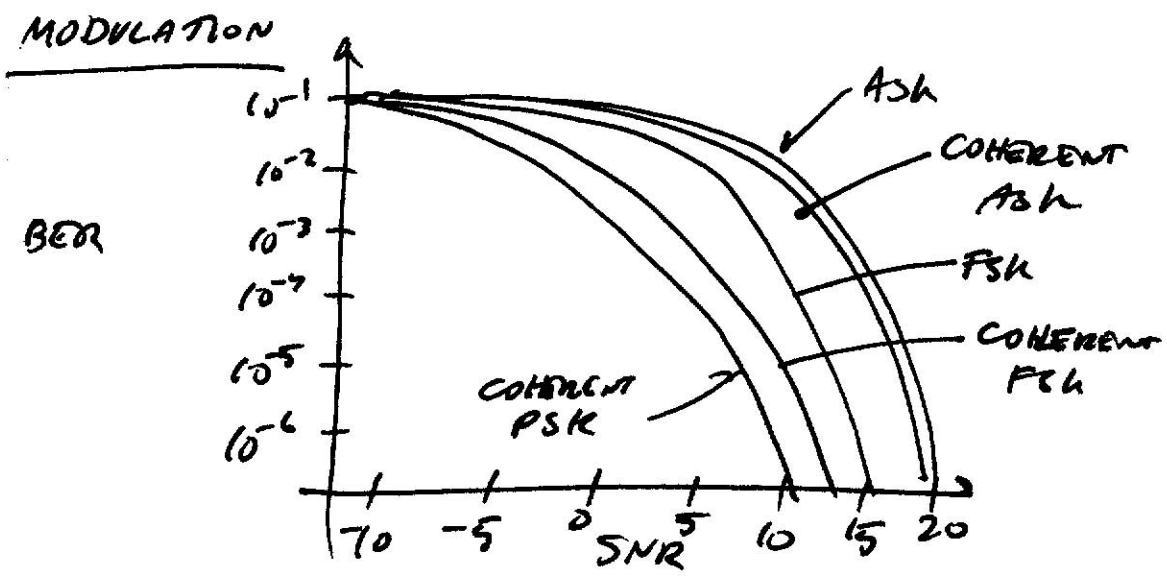
$$R_n \sim 100\Omega \gg R_{\text{LOSS}} \\ \gg \frac{R_{\text{ANT}}}{R_r}$$



THIS ASSUMES NO FADING!

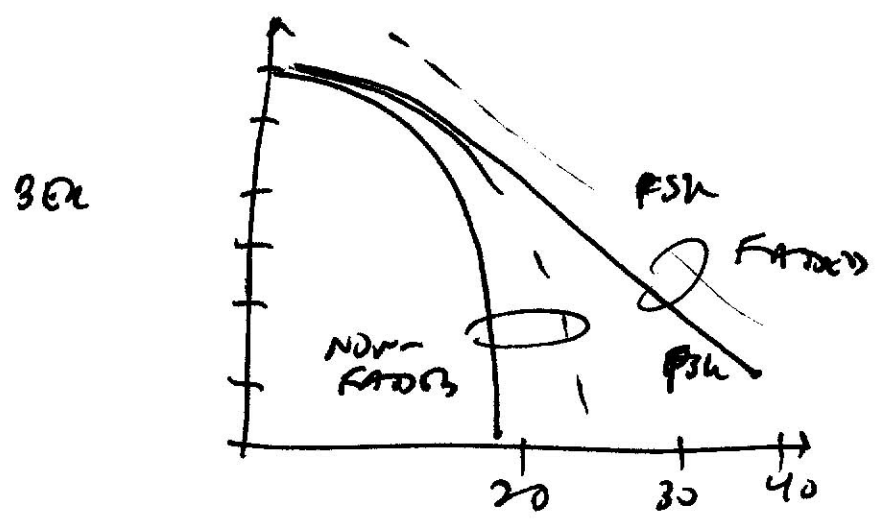

THIS LIMITS RANGE OF WIRELESS SYSTEM!

CELL PHONE LINK BUDGET

20 kHz, 1 km


$$\text{TX POWER} = 25 \text{ dBm} \quad (300 \text{ mW})$$

$$\text{ANT GAIN} = 2.4 \text{ dB}$$

1 km LINK PATH LOSS

$$L = \frac{\Delta^2}{(4\pi R)^2} = +98.5 \text{ dB}$$

URBAN PATH LOSS: 120.8 dB
(INDOOR)

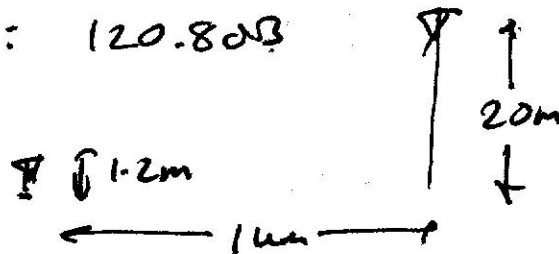

$$\begin{aligned} \text{RX SIG} &= G_{\text{RX}} + 30 \text{ dBm} - 12 \text{ dB} + \text{SHADOW LOSS} \\ &= -99 \text{ dBm} - 103.5 \end{aligned}$$

$$\text{NOISE POWER} = -174 \text{ dB/Hz}$$

$$\text{BW} = 20 \text{ kHz} = 53$$

$$\text{RX NOISE} = -121 + 5 \text{ dB} = -116 \text{ dBm}$$

$$\text{NF} = 5 \text{ dB}$$

$$\text{SNR} = 12 \text{ dB}$$