

# MT SOLUTIONS

---

1) MAIN LOOP M2/M3 SHUNT FB PAIR

$$\text{LOOP GAIN} \simeq g_{m3} r_{o3} \quad | \simeq 10$$

~  
FOLLOWER  
GAIN

SERIES FB OF M1 A SECOND LOOP...

---

2)  $A_v = G_m R_o = g_m R_o$

$$R_o \simeq r_{o1} (1 + g_{m2} r_{o2}) g_{m3} r_{o3}$$

$$A_v \simeq (g_m r_o)^3 \simeq 1000$$

---


3)  $a_1 \simeq 1$     3<sup>rd</sup> INSPECTION

$a_2 \simeq 0$     DUE TO CASCODE / AWD GAIN BOOSTING

$a_3 = ?$

↘ CALC

### 3) NOISE CALC

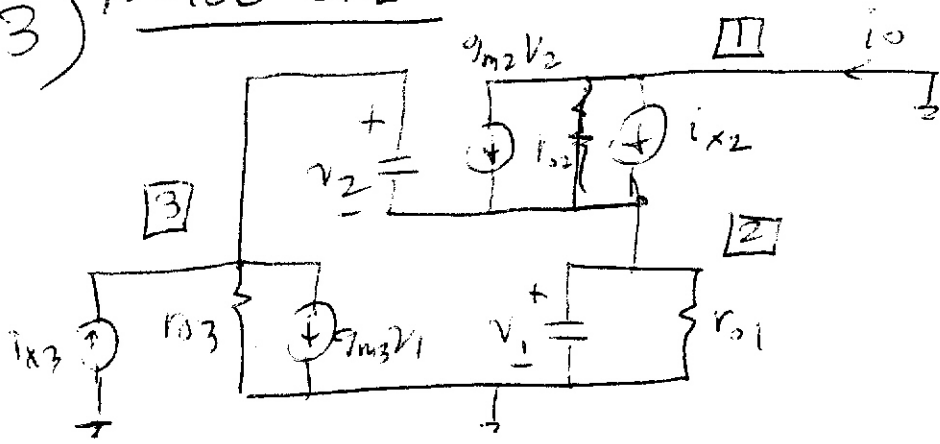

1  $i_o = i_{x2} + g_{m2} v_2 - v_1 / r_{o2}$

2  $v_1 / r_{o1} \parallel r_{o2} = i_{x2} + g_{m2} v_2$

3  $(i_{x3} - g_{m3} v_1) r_{o3} = v_1 + v_2$

$$i_{x3} r_{o3} - A_v v_1 = v_1 + v_2$$

$$v_2 = i_{x3} r_{o3} - (A_v + 1) v_1$$

FROM 2  $\frac{v_1}{r_{o1} \parallel r_{o2}} = i_{x2} + g_{m2} r_{o3} i_{x3} - g_{m2} (A_v + 1) v_1$

$$v_1 \left( \frac{1}{r_{o1} \parallel r_{o2}} + g_{m2} (A_v + 1) \right) = i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3}$$

D

FROM 1  $i_o = i_{x2} - g_{m2} (A_v + 1) v_1 - v_1 / r_{o2} + g_{m2} r_{o3} i_{x3}$

$$= i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} - \left( g_{m2} (A_v + 1) + \frac{1}{r_{o2}} \right) v_1$$

$$= i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} - \frac{\left( g_{m2} (A_v + 1) + \frac{1}{r_{o2}} \right) \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right)}{D}$$

$$= \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right) \left( 1 - \frac{g_{m2} (A_v + 1) + \frac{1}{r_{o2}}}{D} \right)$$

$$\begin{aligned}
i_o &= \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right) \left( \frac{D - g_m(A_v+1) + \frac{1}{r_{o2}}}{D} \right) \\
&= \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right) \left( \frac{\frac{1}{r_{o1}r_{o2}} - \frac{1}{r_{o2}}}{D} \right) \\
&= \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right) \left( \frac{1 - \frac{r_{o1}r_{o2}}{r_{o2}}}{1 + g_{m2} r_{o1}r_{o2}(A_v+1)} \right) \\
&= \left( i_{x2} + A_v \frac{r_{o3}}{r_{o2}} i_{x3} \right) \left( \frac{1 - 1/2}{1 + A_v \frac{1}{2}(A_v+1)} \right) \\
&= \left( \frac{1}{2 + A_v(A_v+1)} \right)
\end{aligned}$$

$$a_2 \approx \frac{1}{A_v^2}$$

$$a_3 \approx \frac{r_{o3}}{r_{o2} A_v}$$

DOMINATES NOISE AFTER  
M1

$$a_1 \approx 1$$

$$4) \text{ DOM POLE } R_o C_L = r_{o1} (1 + g_{m2} r_{o2}) g_{m3} r_{o3}$$

$$= 2.5 \text{ k}\Omega \cdot 100 = 250 \text{ k}\Omega$$

$$C_L = 1 \text{ pF}$$

$$\frac{1}{C_o R_L} = \frac{1}{250 \times 10^{-12} \times 10^3} = \frac{10^9}{250} = 4 \times 10^6$$

$$f_{-3dB} \approx 636 \text{ kHz}$$

$$\omega_{p2} = \frac{1}{C_x \frac{r_{o3}}{A_v}} \quad \left. \vphantom{\frac{1}{C_x \frac{r_{o3}}{A_v}}} \right\} \begin{array}{l} \text{RESISTANCE} \\ \text{LOWERED BY} \\ \text{LOOP GAIN} \end{array}$$

$$\omega_{p2} = \frac{A_v}{C_x r_{o3}} = \frac{10}{20 \text{ f} \cdot 20 \text{ k}} = 25 \times 10^9$$

$$f_{p2} \approx 4 \text{ GHz}$$

$$3) \quad \tau = \frac{C_{\text{eff}}}{F \cdot G_m} \quad C_{\text{eff}} = C_L + (1-F)C_F$$

$$= \frac{1 \text{ p} + (1 - 1/5) 0.5 \text{ p}}{\frac{1}{5} 4 \text{ mA}} = \frac{5 \times 1.4 \cdot 10^{-12}}{4}$$

$$f = 1/\tau_{20} = 91 \text{ MHz} \quad \text{PM} \approx 90^\circ$$