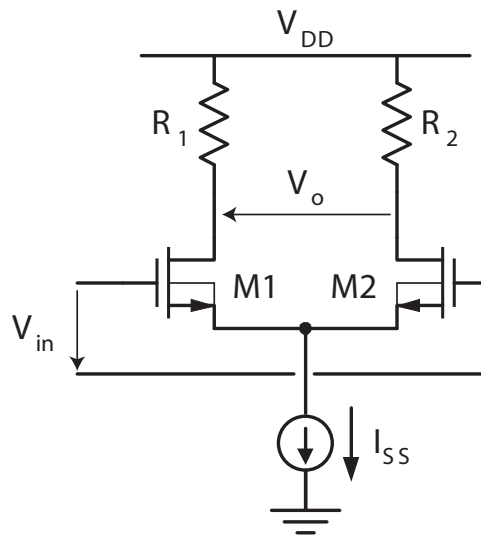


Problem Set 5 Solutions

- The offset voltage V_{os} of an amplifier is defined as the input required to satisfy $V_o = 0V$. Calculate the variance of the offset voltage of the differential amplifier below as a function of $\sigma_{V_{th}}$, $\sigma_{\frac{\Delta R}{R}}$, I_{SS} , and V^* . Use the square-law approximation (i.e. $V_{od} = V^*$) and assume infinite transistor output resistance.



The solution is found by adjusting the output currents for zero output offset

$$I_{D1}R_{D1} = I_{D2}R_{D2}$$

This is equivalent to

$$\frac{\Delta I_D}{I_D} = \frac{\Delta R_D}{R_D}$$

Under this condition, assuming the offset voltage is small, the input voltage is given by

$$V_{os} = V_{GS1} - V_{GS2} = \Delta V_T + \frac{\Delta I_D}{g_m}$$

Substitution of the output trim condition yields

$$V_{os} = V_{GS1} - V_{GS2} = \Delta V_T + \frac{\Delta R_D}{R_D} \frac{I_D}{g_m}$$

or

$$V_{os} = V_{GS1} - V_{GS2} = \Delta V_T + \frac{\Delta R_D}{R_D} \frac{V^*}{2}$$

The variance of the offset voltage is therefore given by

$$\sigma_{V_{os}}^2 = \sigma_{V_{th}}^2 + \left(\frac{V^*}{2}\right)^2 \sigma_{\left(\frac{\Delta R}{R}\right)}^2$$

EECS 240, Spring 2004, Midterm Solution

1) Noise

$$S_{ieq} = 4 \cdot k_B \cdot T \cdot \gamma \cdot \frac{V_{1star}}{I_{SS}} \cdot \left(1 + 2 \cdot \frac{V_{1star}}{V_{5star}} + \frac{V_{1star}}{V_{9star}} \right)$$

(ignoring flicker noise)

2) Offset

- Systematic offset is result of different VDS of M9 and M10
- Solution: cascode M9 with a device with same size and bias as M11. Make sure it won't go into triode (due to M9 diode connection).

3) Bandwidth

$$H(s) = \frac{C_s}{C_f} \cdot \frac{1 + s \cdot \frac{C_f}{g_{m1}}}{1 + \frac{s}{\omega_o}}$$

$$\omega_o = F \frac{g_{m1}}{C_L + C_f \cdot (1 - F)}$$

$$g_{m1} = \frac{I_{SS}}{V_{1star}}$$

$$F = \frac{C_f}{C_f + C_s + C_i}$$

usually the zero is at a much higher frequency than the pole and can be ignored.

$$|H(s)| = 1$$

$$\omega_u = \omega_o \cdot \left(\frac{C_s}{C_f} - 1 \right) = \frac{g_{m1}}{C_L + C_f \cdot (1 - F)} \cdot \frac{C_s}{C_f + C_s + C_i} \quad (\text{approx})$$

4) Fast settling

Optimal settling for 2-pole response occurs for $p_2 = -K\omega_o$ $K = 3.3$

$$p_2 = -\frac{g_{m7}}{C_{x1}}$$

$$C_{x1} = \frac{g_{m7}}{K \cdot \omega_o} = \frac{1}{K \cdot F} \cdot \frac{V_{1star}}{V_{7star}} \cdot C_{Leff}$$

5) Slewing

$$V_{1\text{star}} = V_{\text{istep_max}} \cdot \frac{C_s}{C_s + C_a} \quad C_a = C_i + \text{ser}(C_f, C_L)$$

$$V_{\text{istep_max}} = V_{1\text{star}} \cdot \left(1 + \frac{C_a}{C_s} \right)$$

$$V_{\text{istep_max}} = V_{1\text{star}} \cdot \frac{(C_f \cdot C_s + C_f \cdot C_i + C_L \cdot C_s + C_L \cdot C_i + C_f \cdot C_L)}{C_s \cdot (C_f + C_L)}$$

6) Slewing time

initial step at amplifier input:

$$V_{x0} = V_{\text{istep}} \cdot \frac{C_s}{C_s + C_a}$$

slew rate at output:

$$SR_o = \frac{I_{SS}}{C_c} \quad C_c = C_L + \text{ser}(C_f, C_s + C_i)$$
$$C_c = C_L + F \cdot (C_s + C_i)$$

slew rate at amp input:

$$SR_i = F \cdot SR_o$$
$$SR_i = F \cdot \frac{I_{SS}}{C_L + F \cdot (C_s + C_i)}$$

slewing time:

$$t_{\text{slew}} = \frac{V_{x0} - V_{1\text{star}}}{SR_i}$$

$$t_{\text{slew}} = \frac{V_{x0} - V_{1\text{star}}}{I_{SS}} \cdot \left(\frac{C_L}{F} + C_s + C_i \right)$$

Given

$$v_o \cdot s \cdot (C_f + C_L) - v_x \cdot (s \cdot C_f + g_m) = 0$$

$$v_x \cdot C_T - v_i \cdot C_s - v_o \cdot C_f = 0$$

$$\text{Find}(v_o, v_x) \rightarrow \left[\begin{array}{l} -v_i \cdot C_s \cdot \frac{(s \cdot C_f + g_m)}{\left(-s \cdot C_f \cdot C_T - s \cdot C_L \cdot C_T + s \cdot C_f^2 + g_m \cdot C_f\right)} \\ -s \cdot v_i \cdot C_s \cdot \frac{(C_f + C_L)}{\left(-s \cdot C_f \cdot C_T - s \cdot C_L \cdot C_T + s \cdot C_f^2 + g_m \cdot C_f\right)} \end{array} \right]$$

$$v_o = -v_i \cdot \frac{C_s}{C_f} \cdot \frac{1 + s \cdot \frac{C_f}{g_m}}{1 - s \cdot \frac{C_f \cdot C_T + C_L \cdot C_T - C_f^2}{g_m \cdot C_f}}$$

$$\frac{C_f \cdot C_T + C_L \cdot C_T - C_f^2}{g_m \cdot C_f} = \frac{C_T + \frac{C_L}{F} - C_f}{g_m} = \frac{C_L}{F \cdot g_m} \cdot \left(\frac{C_T \cdot F}{C_L} - C_f \cdot \frac{F}{C_L} + 1 \right)$$

$$C_T + \frac{C_L}{F} - C_f = \frac{F \cdot (C_s + C_i) + C_L}{F}$$

$$\frac{C_s}{C_f} \cdot \frac{1 + s \cdot \frac{C_f}{g_m}}{1 + \frac{s}{\omega_o}} \quad \omega_o = F \frac{g_m}{C_L + C_f \cdot (1 - F)}$$

usually the zero is at much higher frequency than the pole --> ignore