
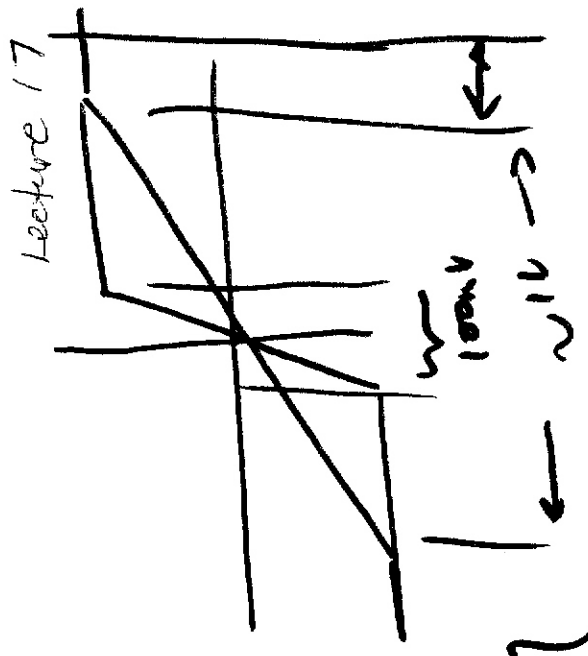


IMPROVING SLEW RATE

- DEGENERATE INPUT STAGE
- BIAS CURRENT SCALING
- PMOS I/P STAGE
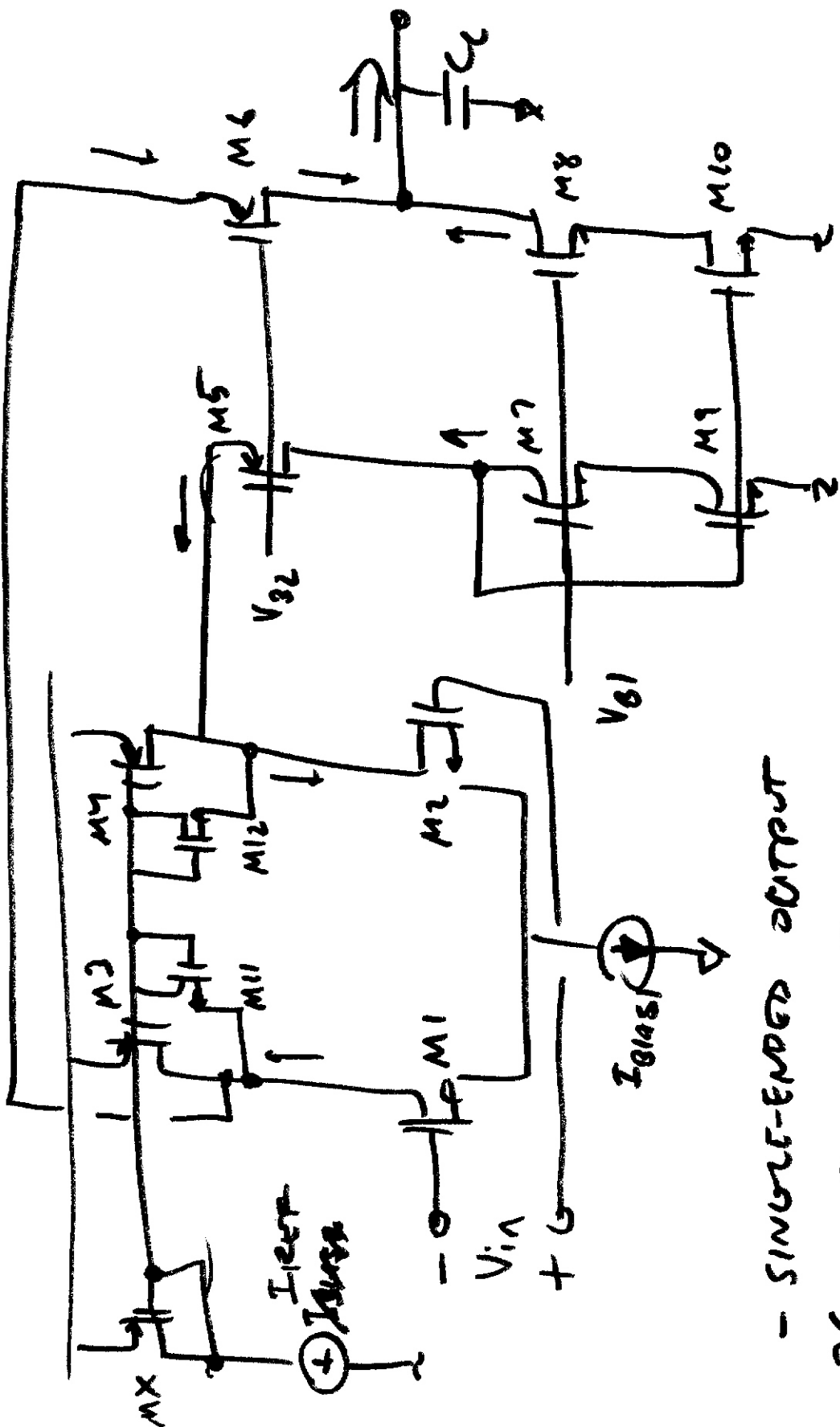
$$g_m \downarrow \left\{ \begin{array}{l} 1/f_{11} \\ \text{COVER} \end{array} \right\}$$






- SINGLE-ENDED OUTPUT

$$DC \quad I_{DS} = I_{D3} - I_{D1}$$

$$= M I_{BIAS} - \frac{I_{BIAS}}{2} = \left(M - \frac{N}{2}\right) I_{REF}$$

APPLY LARGE STEP INPUT

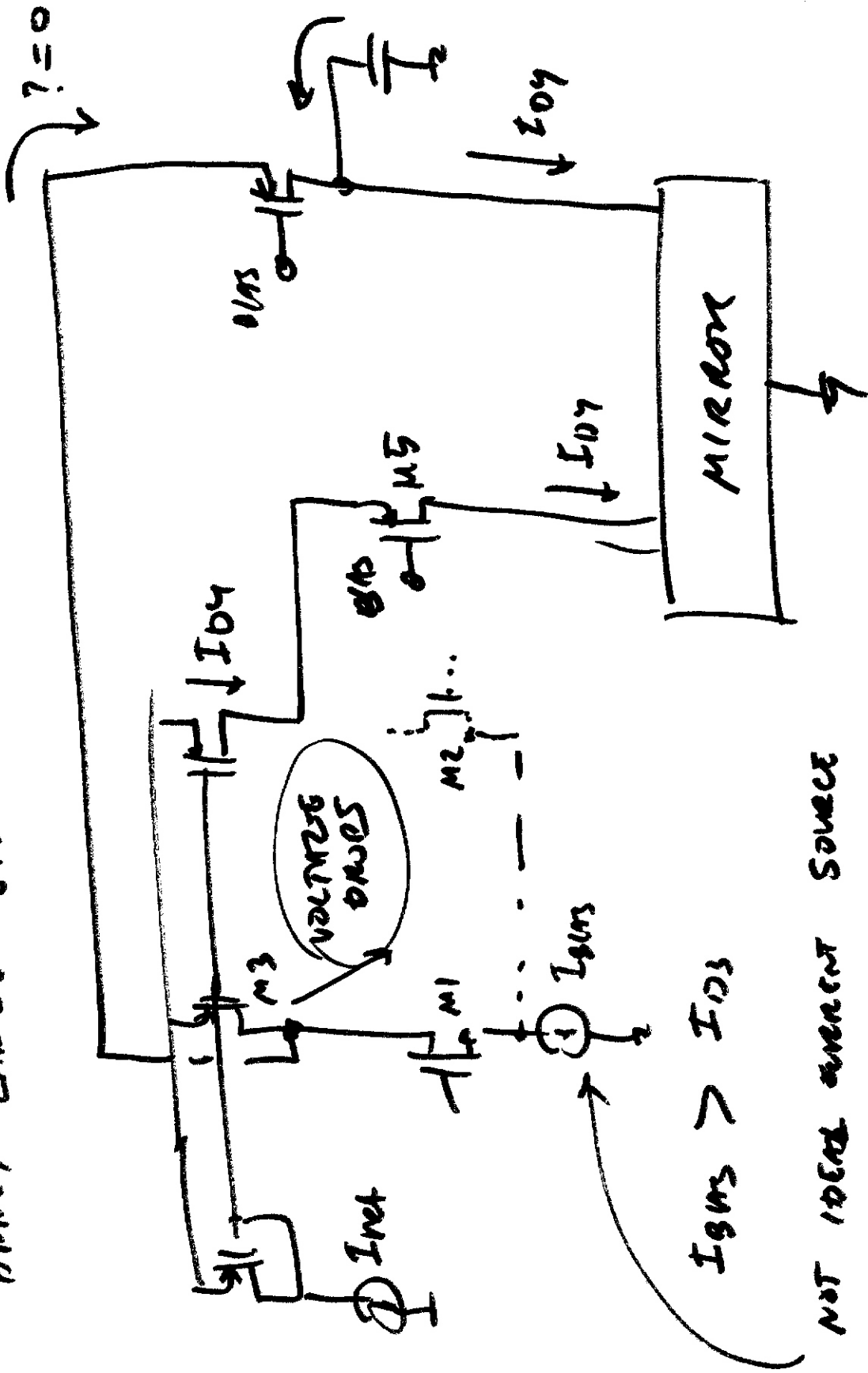

$$I_{BIAS} > I_{D3}$$

NOT IDEAL CURRENT SOURCE

TRANSISTORS M11 & M12 ARE VOLTAGE
CLAMP TO LIMIT THE CHANGE IN
VOLTAGE DURING SLEWING.

↪ IMPROVE RECOVERY TIME!!!

ALSO EXTRA CURRENT OF M11 (SAY DURING



A NEGATIVE STEP INPUT) IS DRAWN

FROM TRANSISTOR M4 \Rightarrow ~~ARE~~ M4


CURRENT ALSO INCREASES \Rightarrow

MORE SLEWING CURRENT

CLASS A/B INPUT STAGE

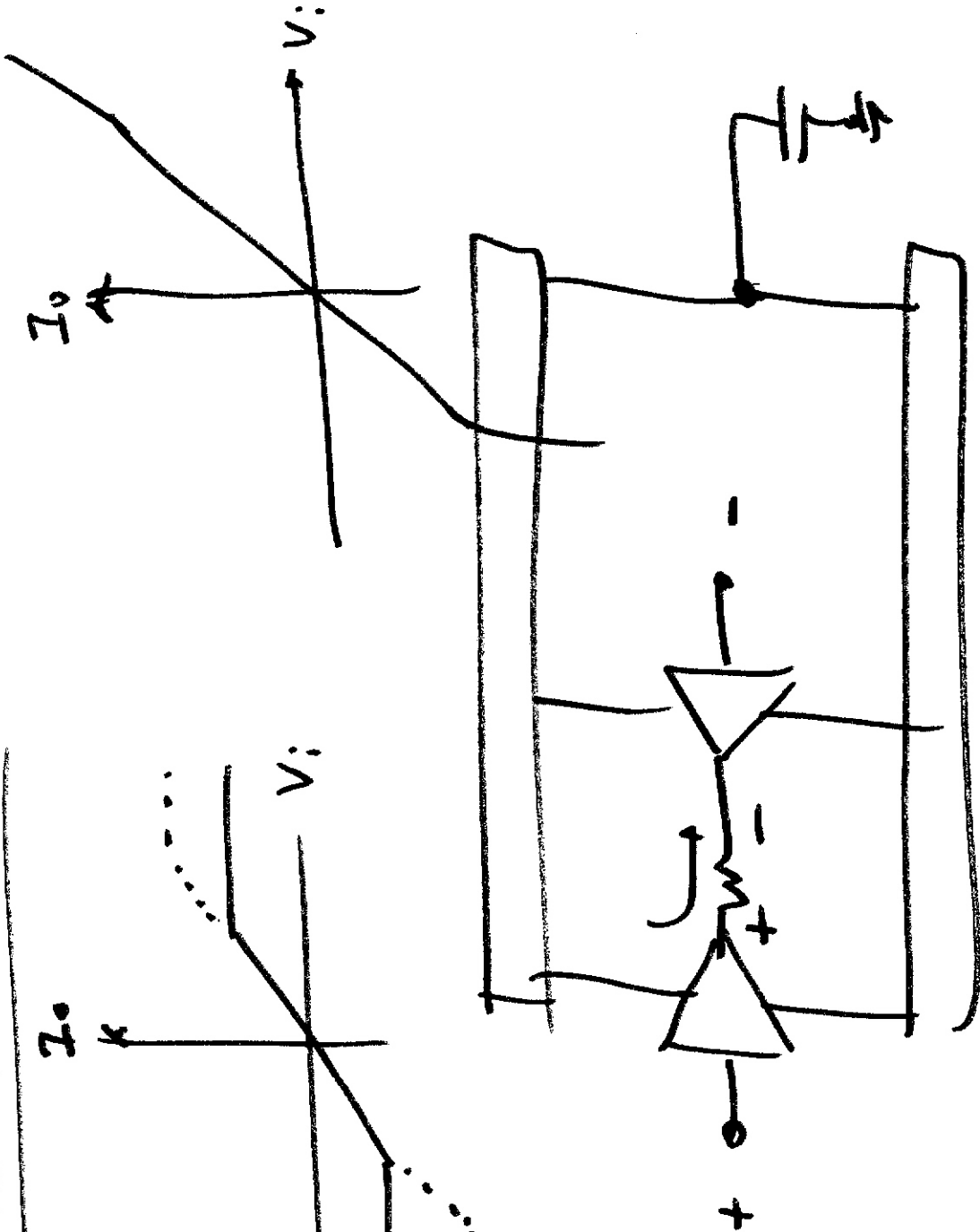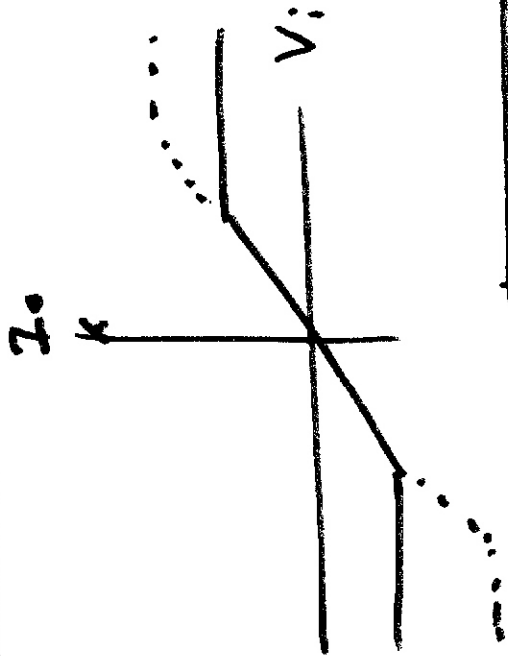


BJT CLASS AB INPUT STAGE

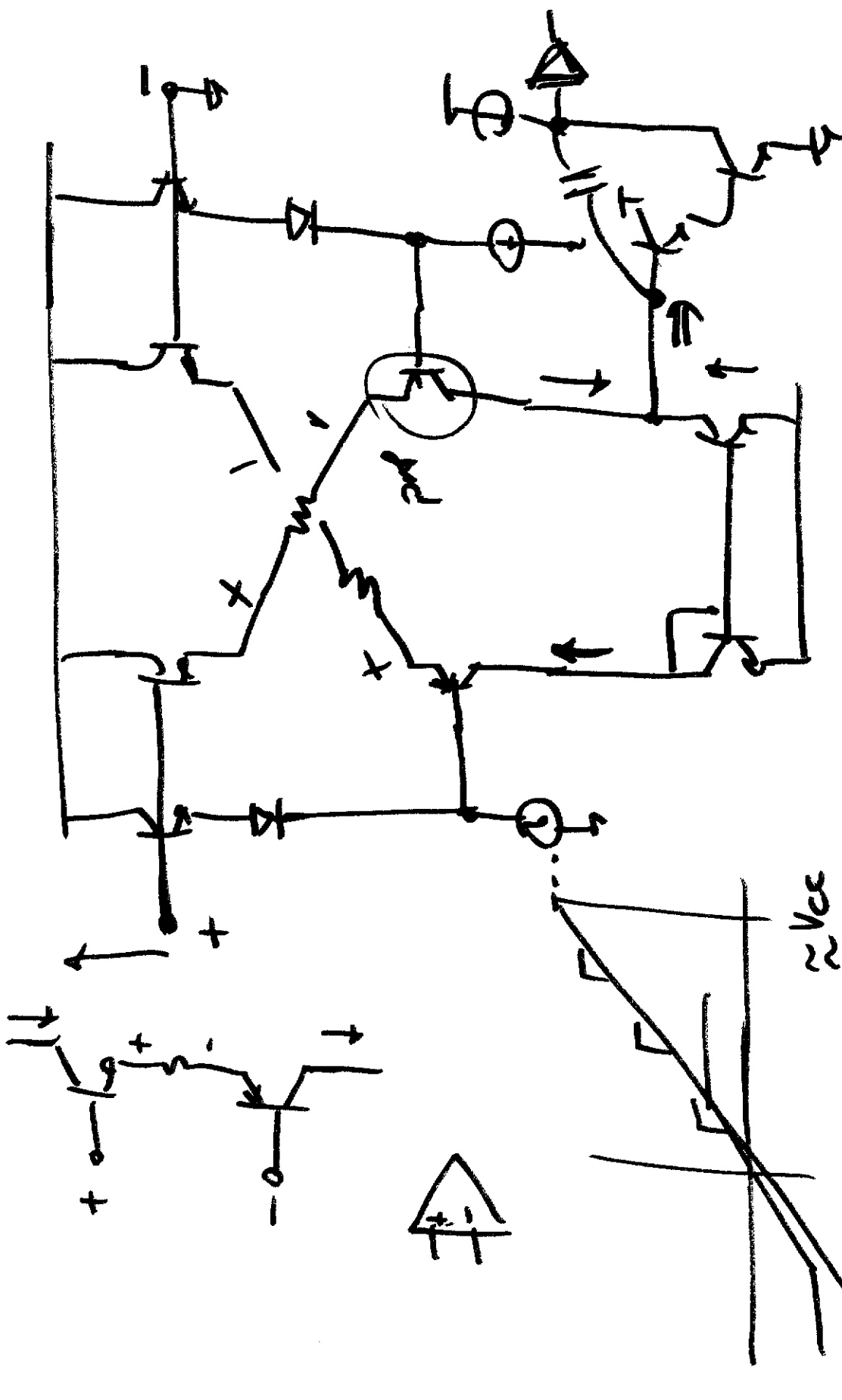


— NEED A FAST PNP

— BAD INPUT OFFSET VOLTAGE

CLASS AB INPUT STAGE

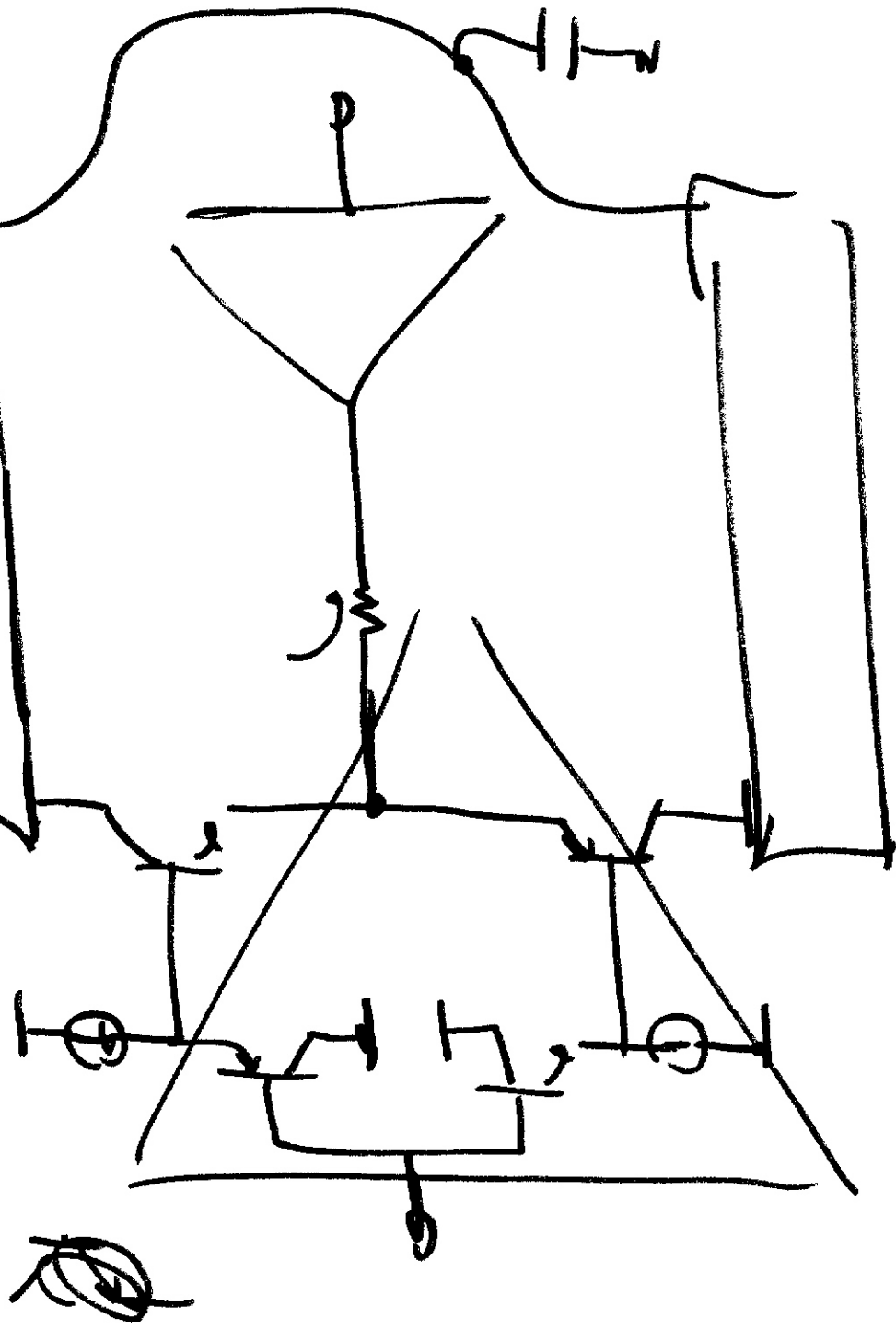


HIGHER INPUT IMPEDANCE

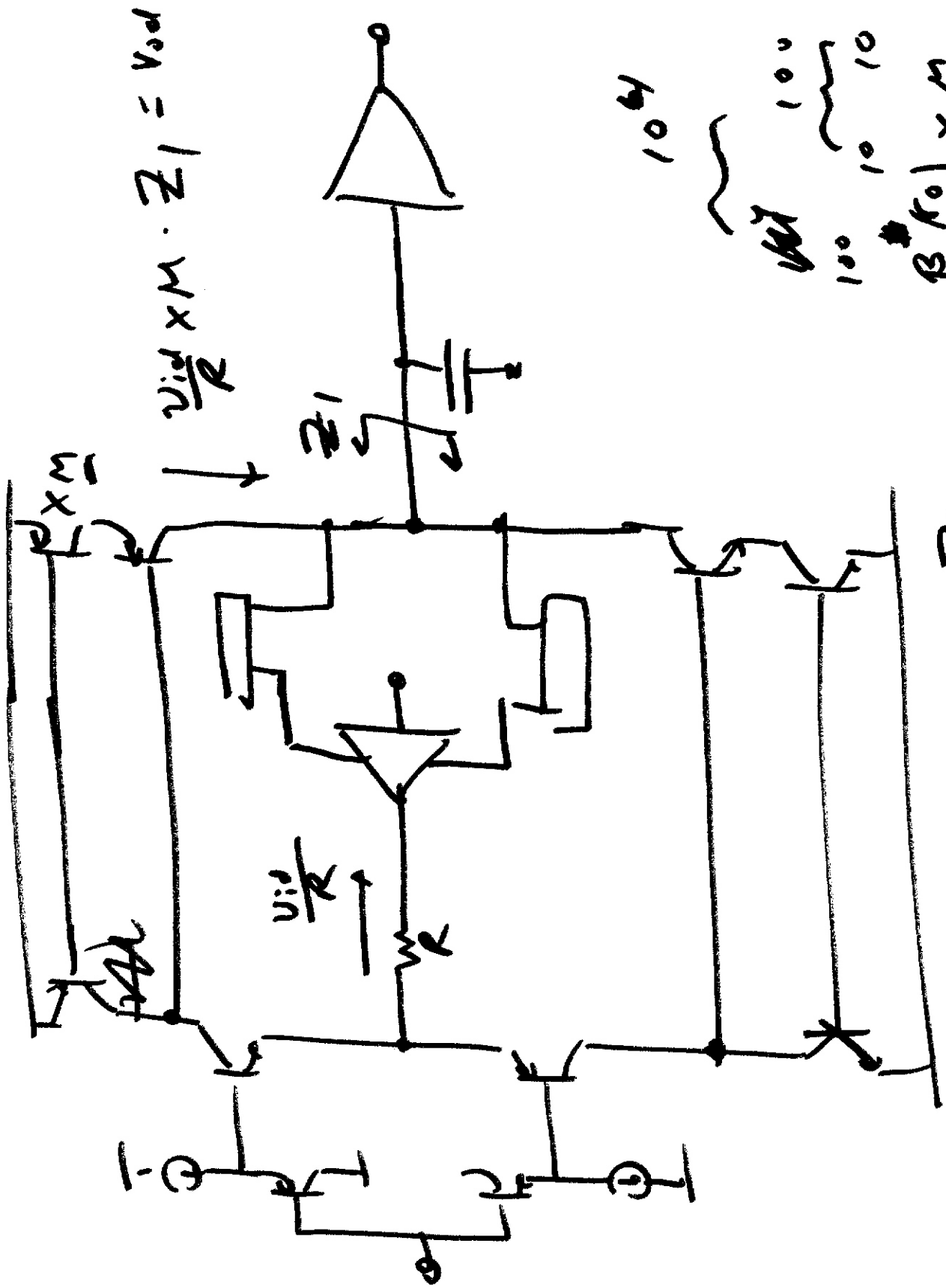

10^4
 $100 \times 100 \times 10 = 10^4$
 $\frac{\beta(r_o)}{R} \times M$

$OPEN\ LOOP\ GAIN = \frac{Z_1}{R} \times M =$

CURRENT FB² AMPLIFIERS

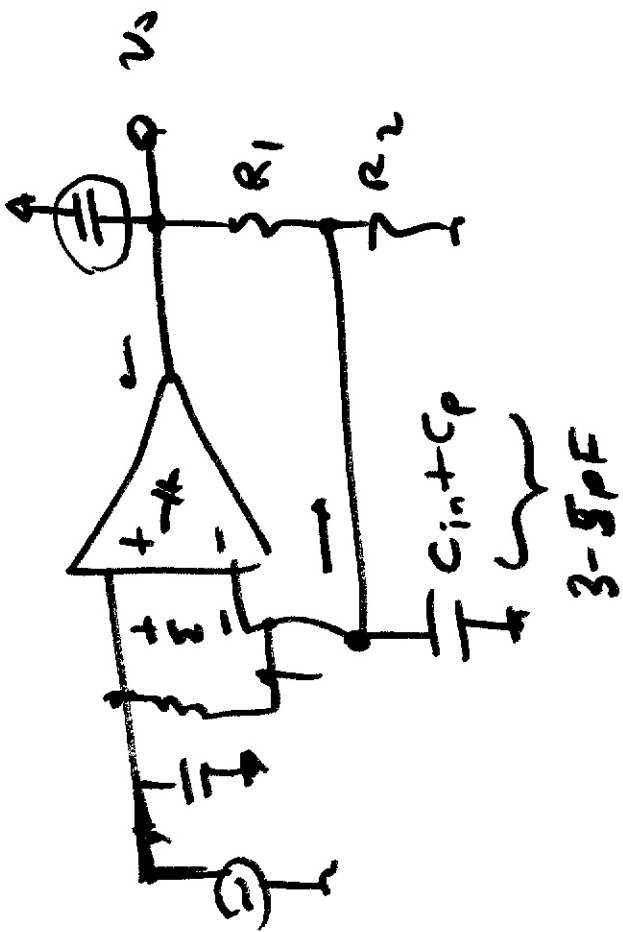

$R_1 || R_2 \sim 1k\Omega$


SIZE 1J SET 87
DRIVE CURRENT

NOISE

$$\tau = 50 \times 10^{-9} \text{ s}$$


$$f = 1/\tau = 50 \text{ MHz}$$

LOW IMPEDANCE SUMMING MODE

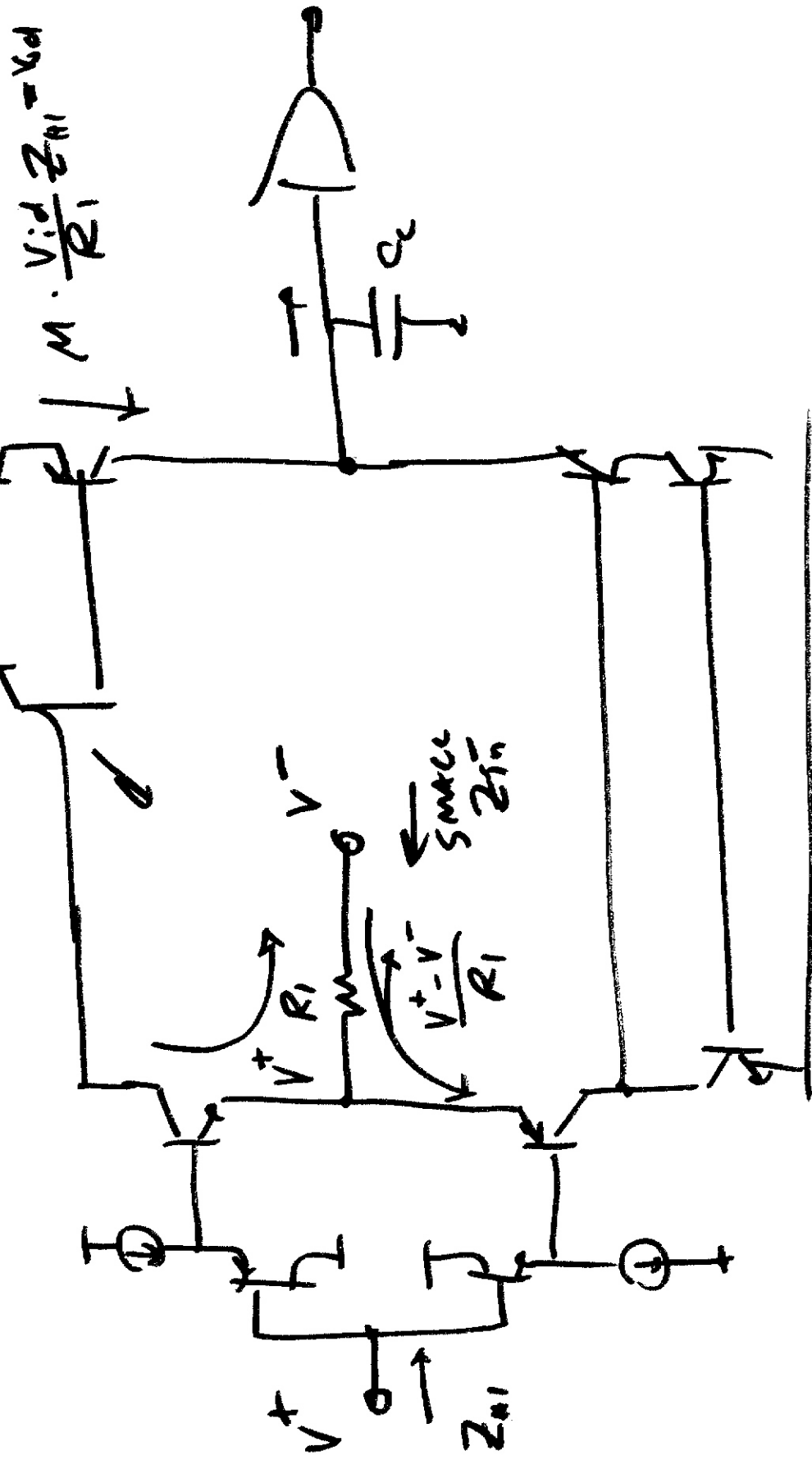


$$G = \frac{Z_{H1}}{R_1} = \frac{\beta r_o}{2R} = \frac{500}{2} \cdot \frac{r_o}{R} = \frac{500}{2} \cdot \frac{40k\Omega}{40k\Omega} = 250,000$$

EQ circuit

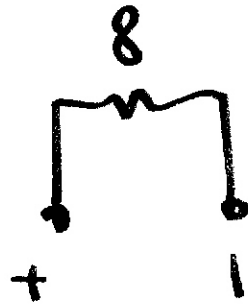


IDEAL
OP-AMP

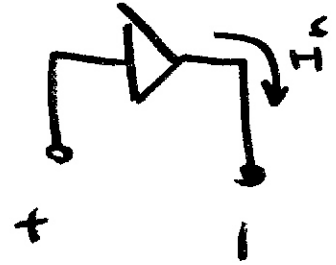

"CURRENT"
OP-AMP

EX

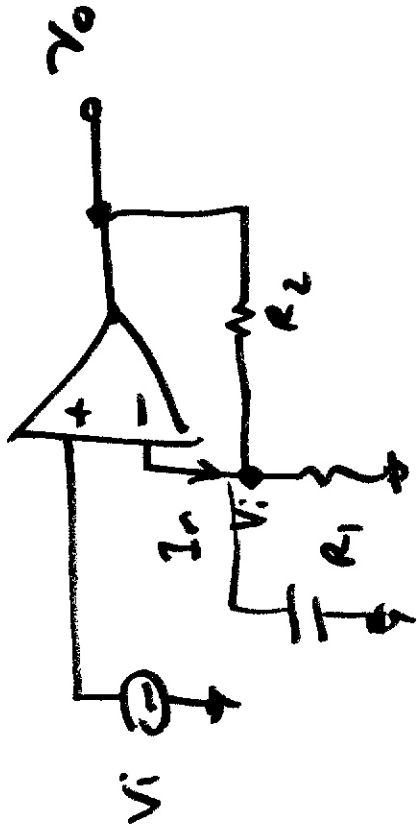

$$I_n = \frac{V_i}{R_1} + \frac{V_i - V_o}{R_2} = V_i \left(\frac{1}{R_1} + \frac{1}{R_2} \right) - \frac{V_o}{R_2}$$

CURRENT
FB SIGNAL

ERROR
SIGNAL

$$V_o = Z I_n$$


$$\frac{V_o}{Z} + \frac{V_o}{R_2} = \frac{V_i}{R_1 \parallel R_2} = \frac{V_i}{Z \parallel R_2}$$

$$\frac{V_o}{V_i} = \frac{Z \parallel R_2}{R_1 \parallel R_2} \approx \frac{R_2}{R_1} \left(\frac{R_1 + R_2}{R_2} \right)$$

$$= 1 + \frac{R_2}{R_1} \quad \checkmark$$

IDEAL \Rightarrow LOOP GAIN $\Rightarrow \infty$
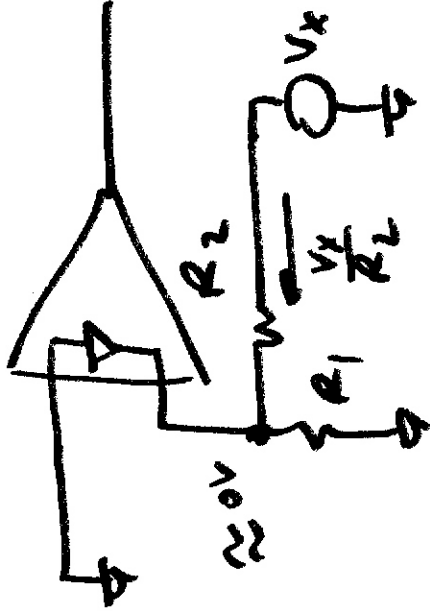
$$v_r = Z \cdot I_n = Z \cdot \left(-\frac{v_x}{R_2} \right)$$



$$T = -\frac{v_r}{v_x} = \frac{Z}{R_2}$$

LOOP GAIN

$$V_o \left(\frac{1}{Z} + \frac{1}{R_2} \right) = \frac{V_i}{R_1 \| R_2}$$

$$\frac{V_o}{Z} \left(1 + \frac{Z}{R_2} \right) = \frac{V_i}{R_1 \| R_2}$$

$$\frac{V_o}{V_i} = \frac{\cancel{Z} (R_1 + R_2)}{R_1 R_2 (1 + \tau)}$$

$$= \underbrace{\left(1 + \frac{R_2}{R_1} \right)}_{\text{IDEAL GAIN}} \underbrace{\frac{\tau}{1 + \tau}}_{\text{ERROR}} \approx 1$$

GAIN/BANDWIDTH TRADEOFF

$$Z = \frac{Z_0}{1 + j \frac{\omega}{\omega_0}} \quad T = \frac{Z}{R_2}$$

$$A = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + j\omega/\omega_0}$$
$$= \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \frac{R_2}{Z_0} \left(1 + j \frac{\omega}{\omega_0}\right)}$$

$$= \frac{\left(1 + \frac{R_2}{R_1}\right)}{1 + j \frac{\omega}{\omega_0} \frac{R_2}{Z_0}}$$

$\omega_a = \frac{Z_0 \omega_0}{R_2}$ CLOSED LOOP BANDWIDTH!
 R_2 DEPENDS ON R_2

↑ $G \times BW \downarrow = \text{CONSTANT}$

$$= \left(1 + \frac{R_2}{R_1}\right) \times \frac{Z_0 \omega_0}{R_2} = \frac{Z_0 \omega_0}{R_1}$$