


EECS 240

Analog Integrated Circuits

Topic 10: Folded Cascode OTA

Ali M. Niknejad and Bernhard E. Boser
© 2006

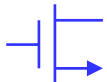Department of Electrical Engineering and Computer Sciences




Folded Cascode


- Good general purpose single-stage OTA
- Analysis
 - Bias
 - Gain
 - Input capacitance
 - Frequency response
 - Feedback, stability
 - Settling time
 - Noise
 - Common-Mode Feedback
- Design
 - Specifications
 - Circuit parameters




Schematic

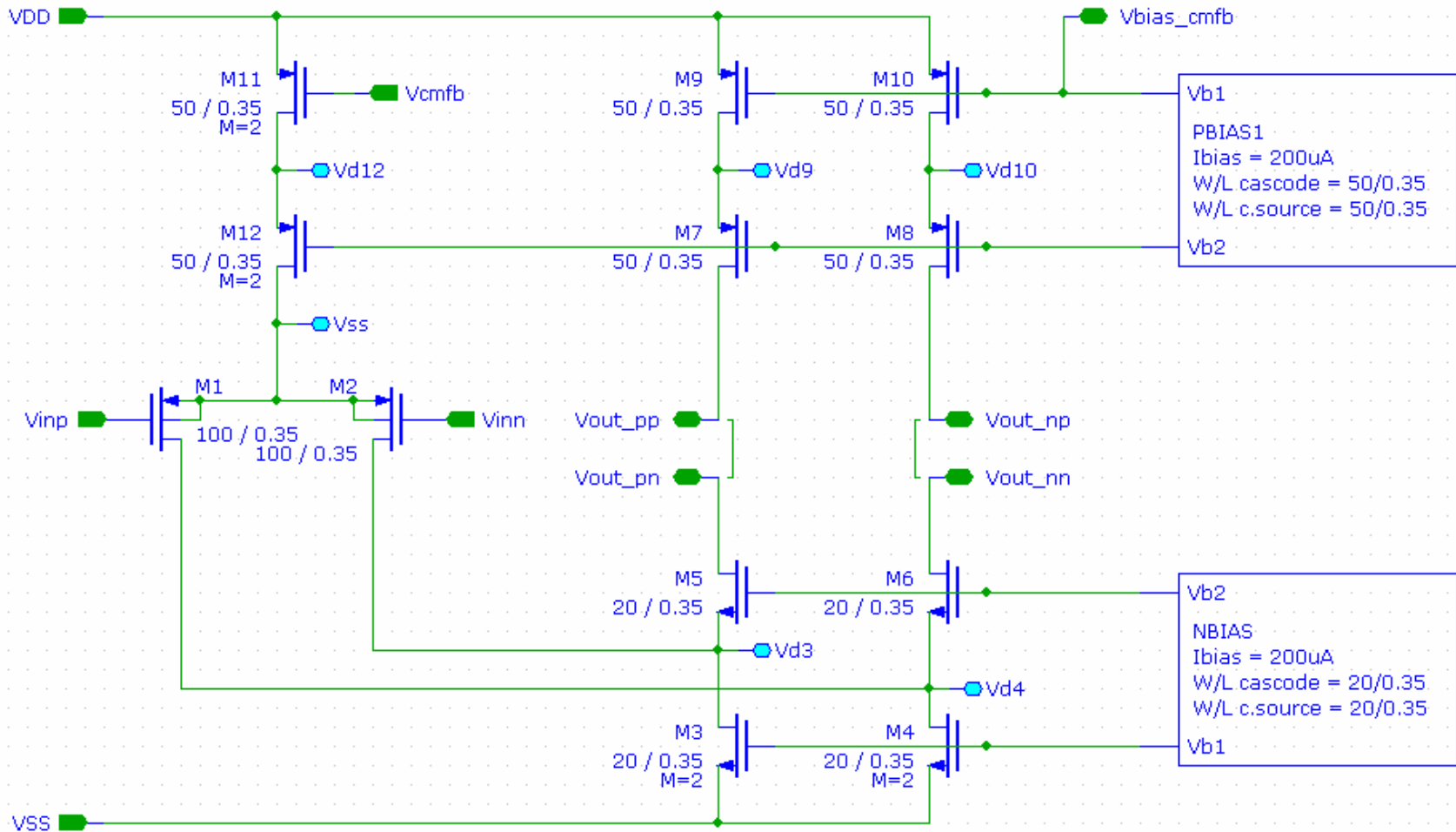

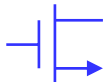
Many more transistors, but overall characteristics very similar to common-source stage.



Bias Subcircuit

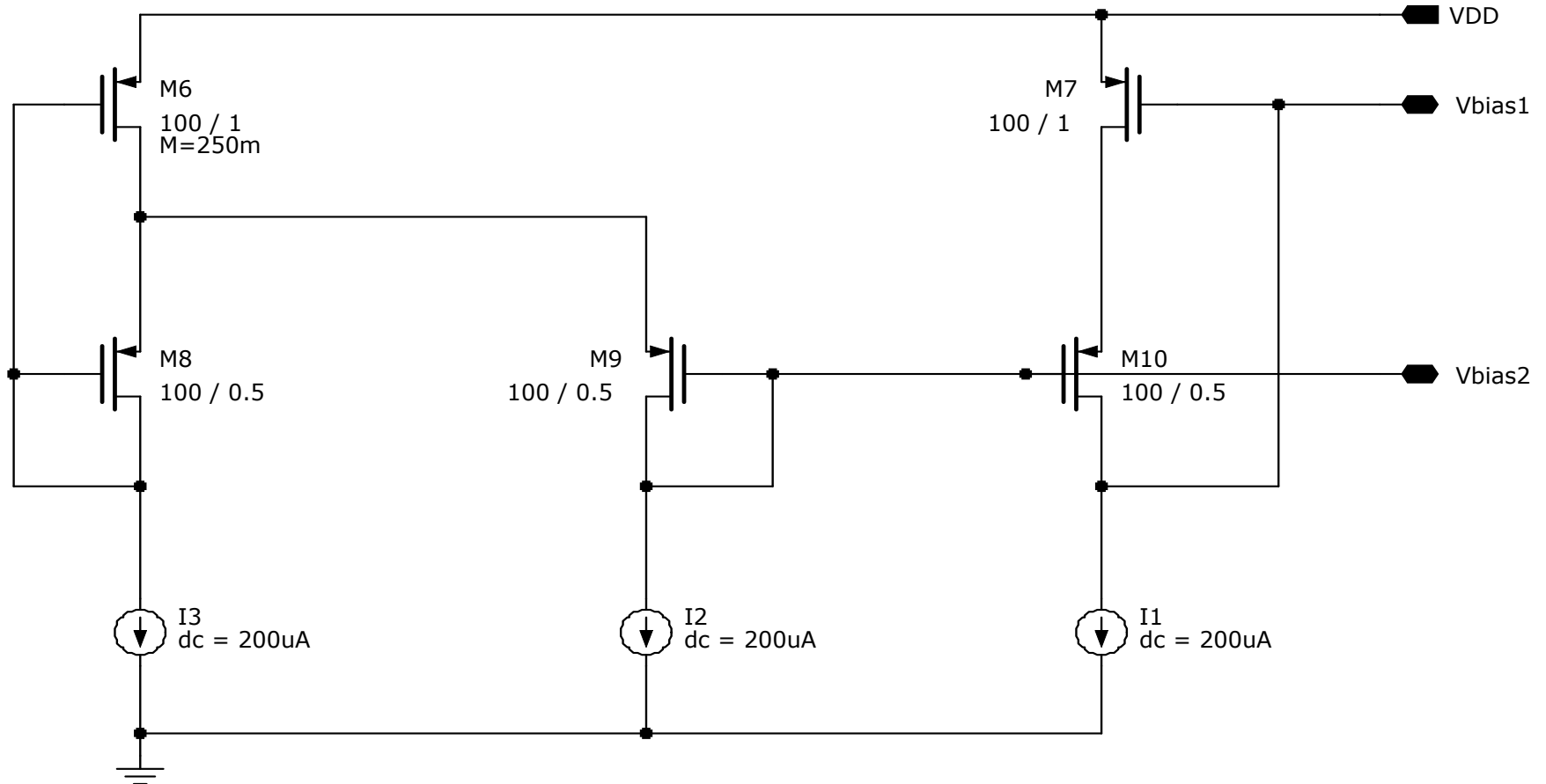

For device sizes on page 7.

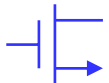



DC Gain, Bias

Folded Cascode: Open-Loop Gain




ISS = 400uA
(W/L)₁ = 100/0.35
(W/L)₃ = 20/0.35
(W/L)₅ = 20/0.35
(W/L)₇ = 50/0.35
(W/L)₉ = 50/0.35

DC Analysis DC_Adm
Device VID
sweep from -50m to 50m (100 steps)

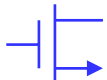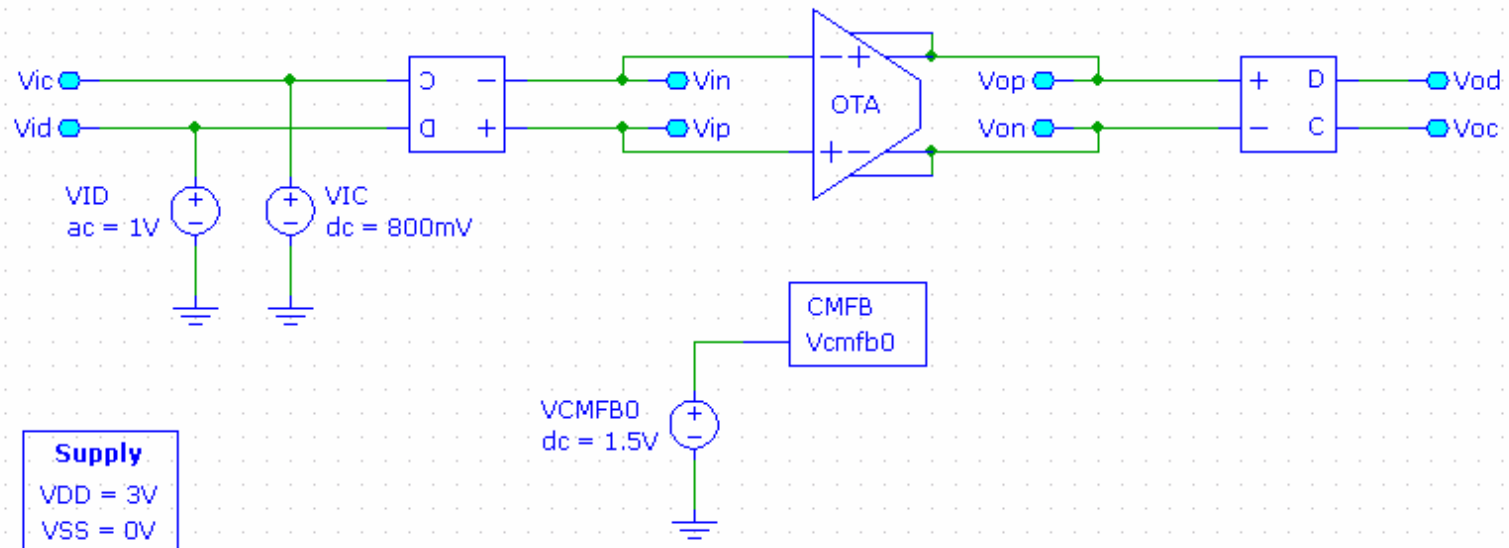
DC Analysis DC_Acm
Device VIC
sweep from 0 to 3 (30 steps)




Bias ... Differential Inputs

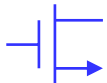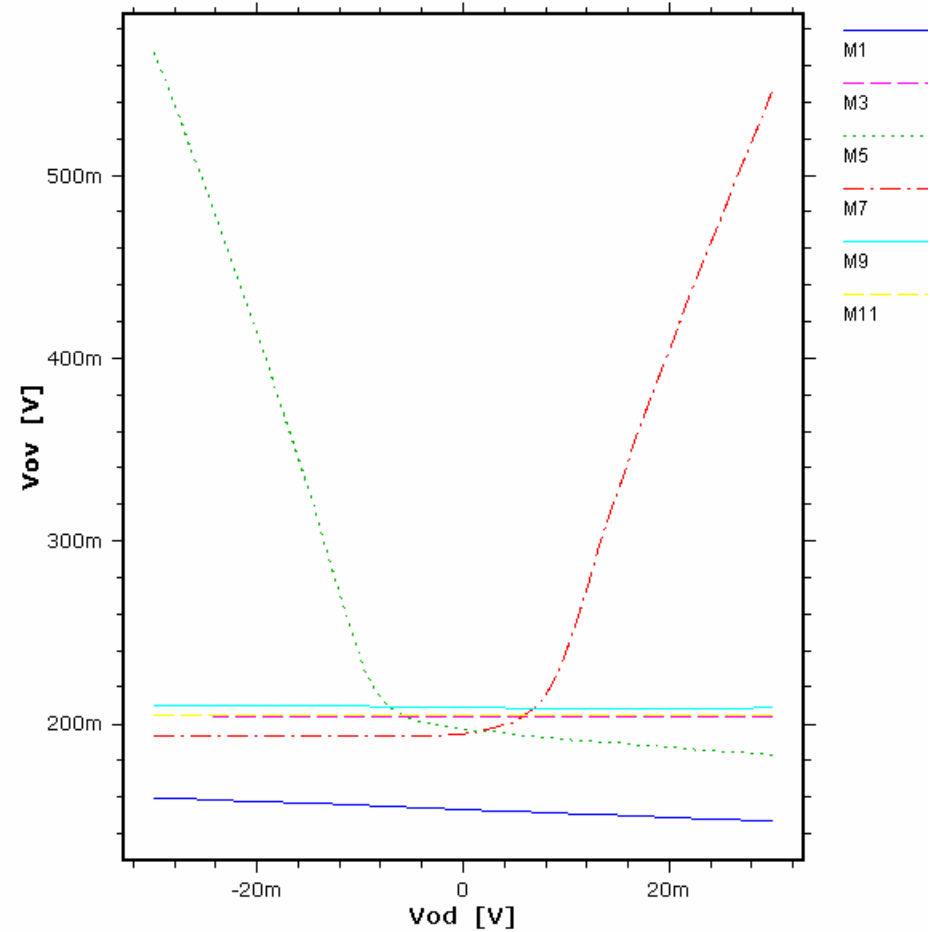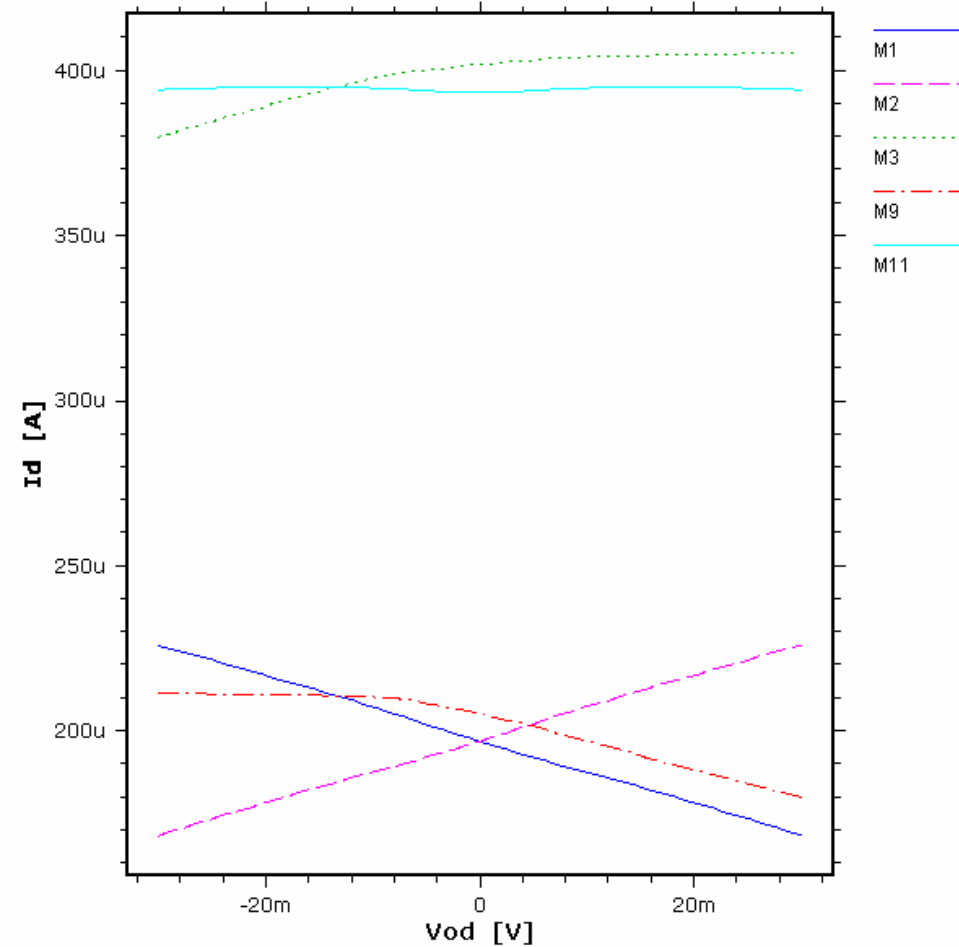




Low Frequency Gain, A_{dm}

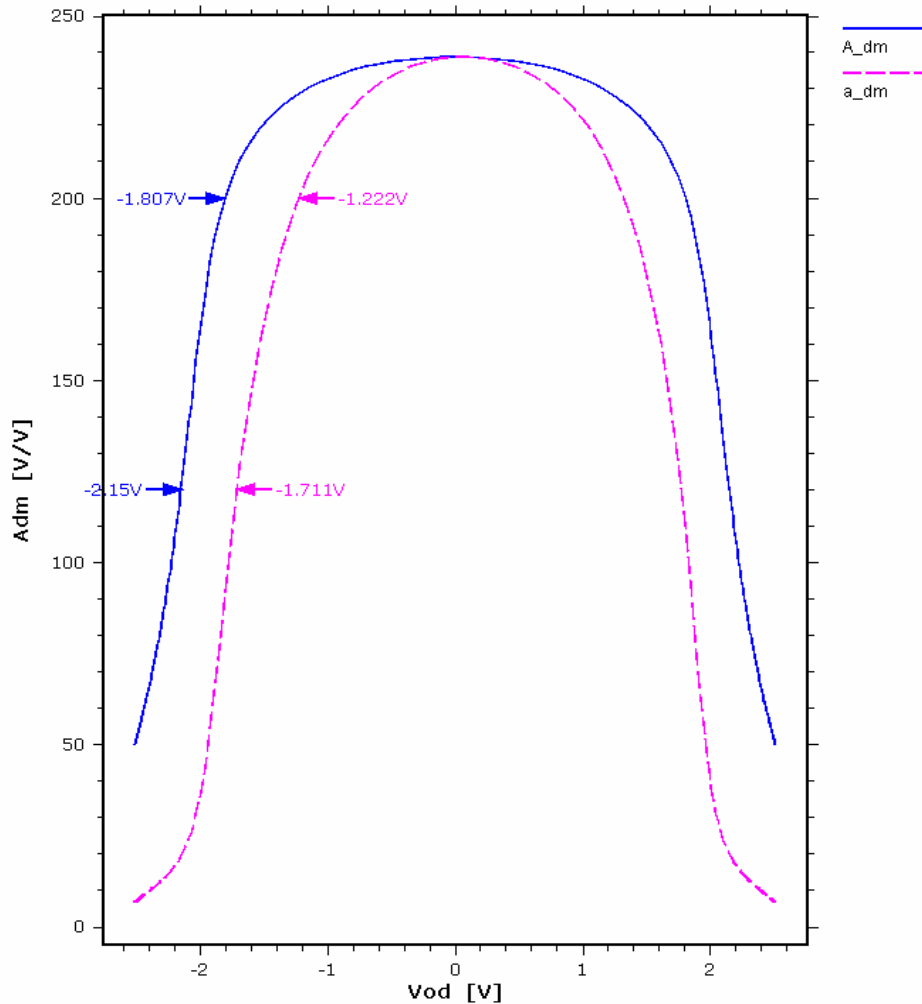

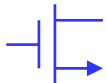
- Gain / Output Range tradeoff
 - $A_{dm}=120 \rightarrow \Delta V_{od} = 4.3V$
 - $A_{dm}=200 \rightarrow \Delta V_{od} = 3.6V$ (nominal parameter)
- Increasing A_{dm} :
 - Moderate:
 - Increase L
 - Affects V^* , phase margin
 - Substantial:
 - Double Cascode
 - Gain boosting
 - Multi-stage amplifier




Increased A_{dm}

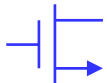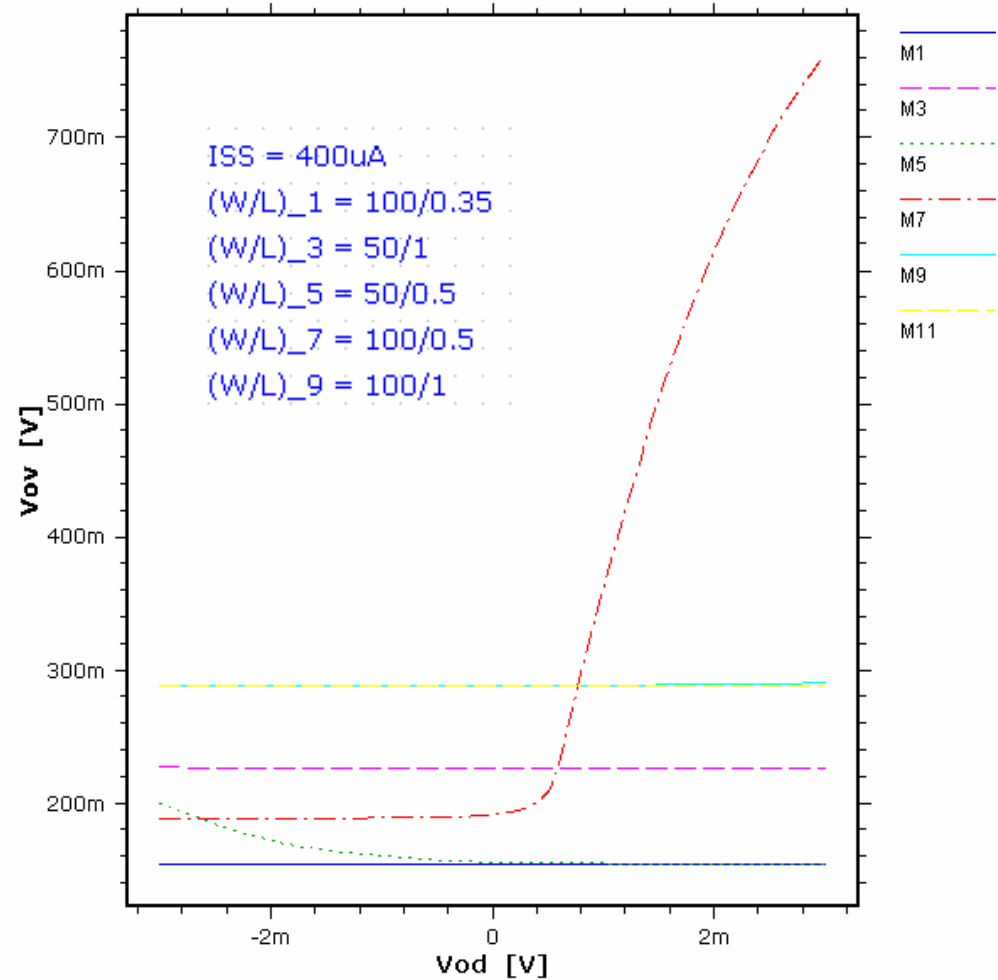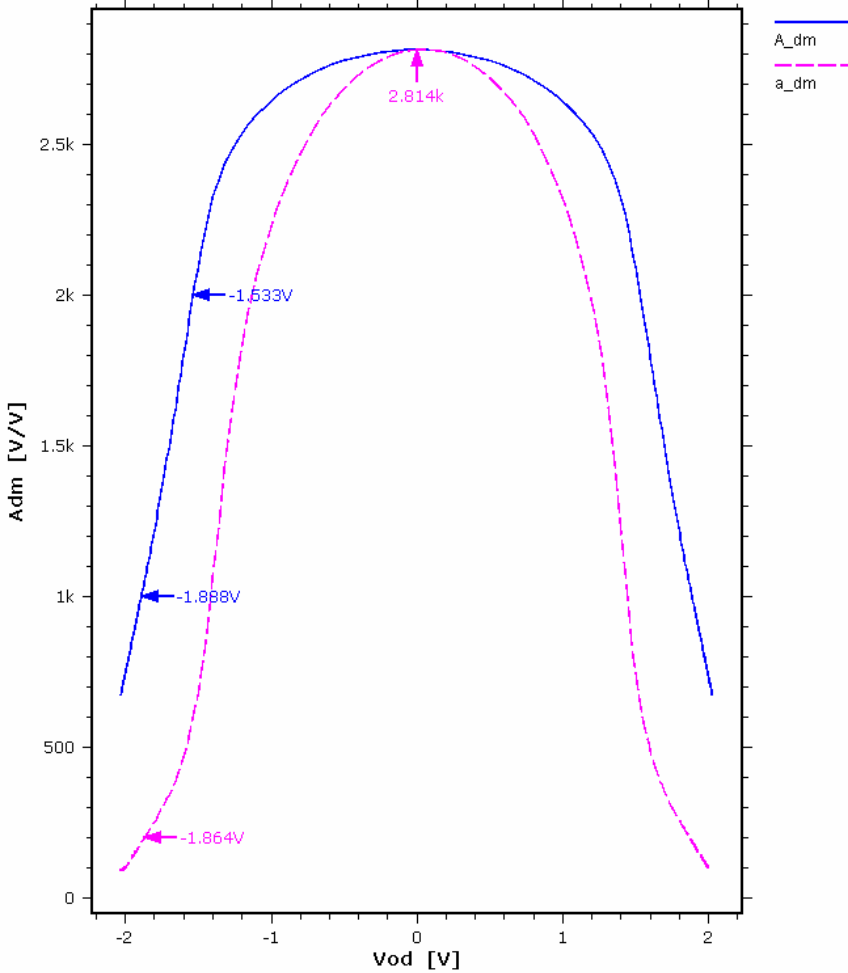

Output Resistance

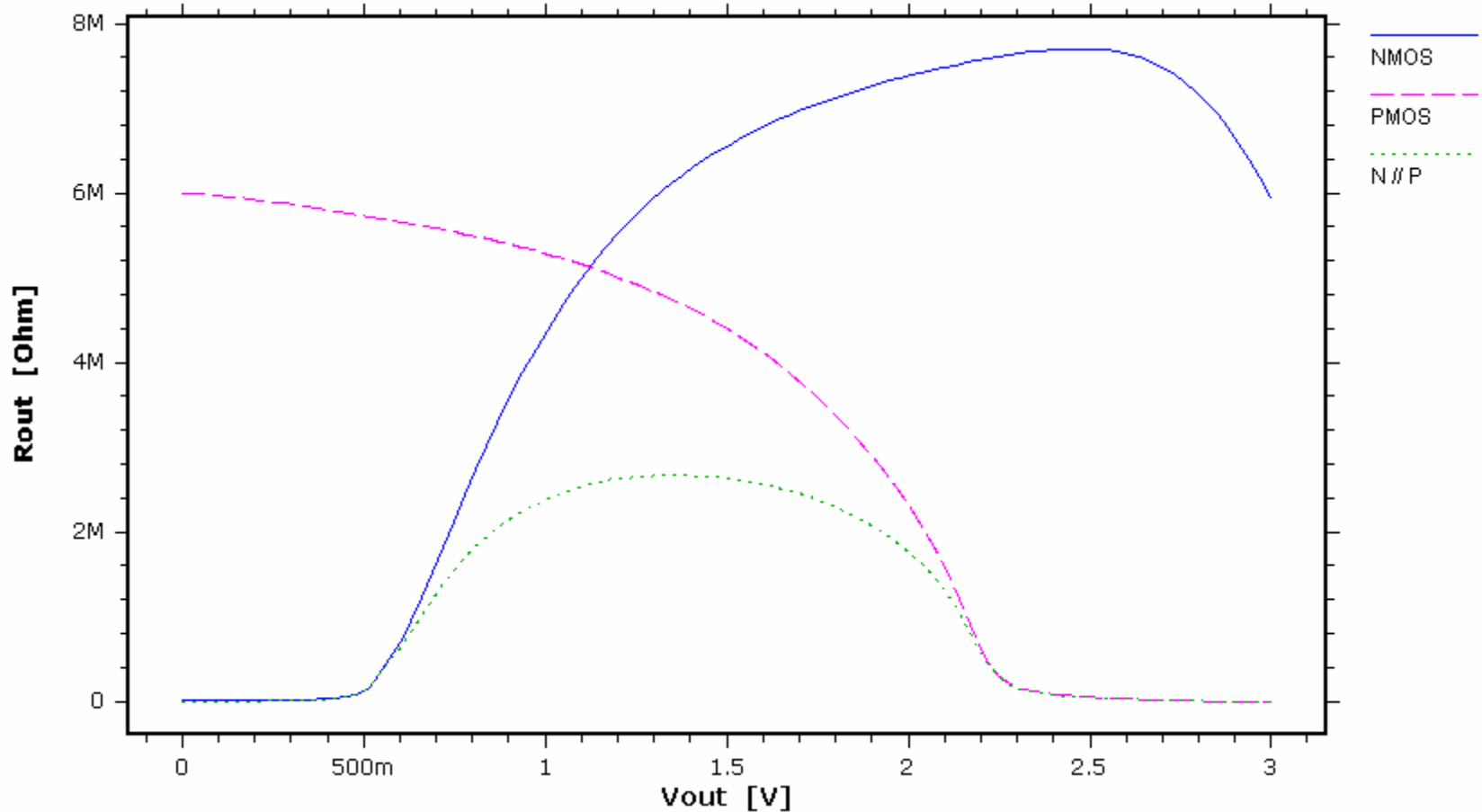

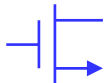Beware of imbalance between NMOS and PMOS current source



G_m , C_{od} Test Circuit

Folded Cascode: G_m

ISS = 400uA

(W/L)₁ = 100/0.35

(W/L)₃ = 50/1

(W/L)₅ = 50/0.5

(W/L)₇ = 100/0.5

(W/L)₉ = 100/1



DC Analysis DC

Device VID



sweep from -500m to 500m (200 steps)

AC Analysis AC1



log sweep from 10k to 10G (101 steps)

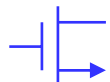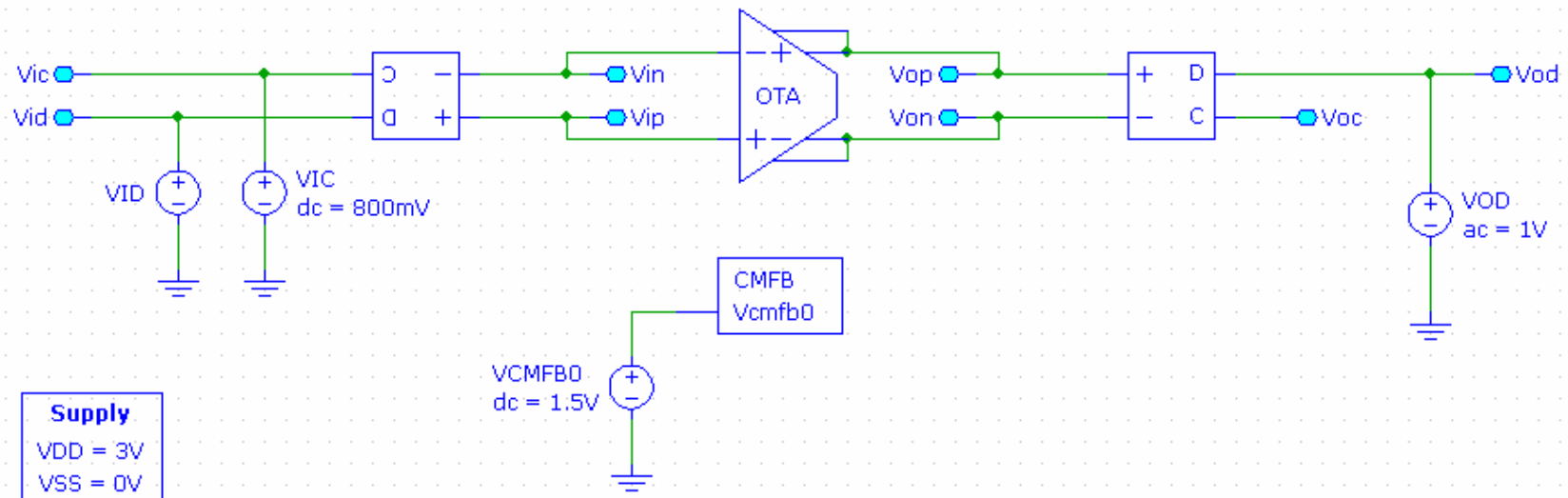


Transconductance

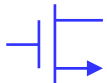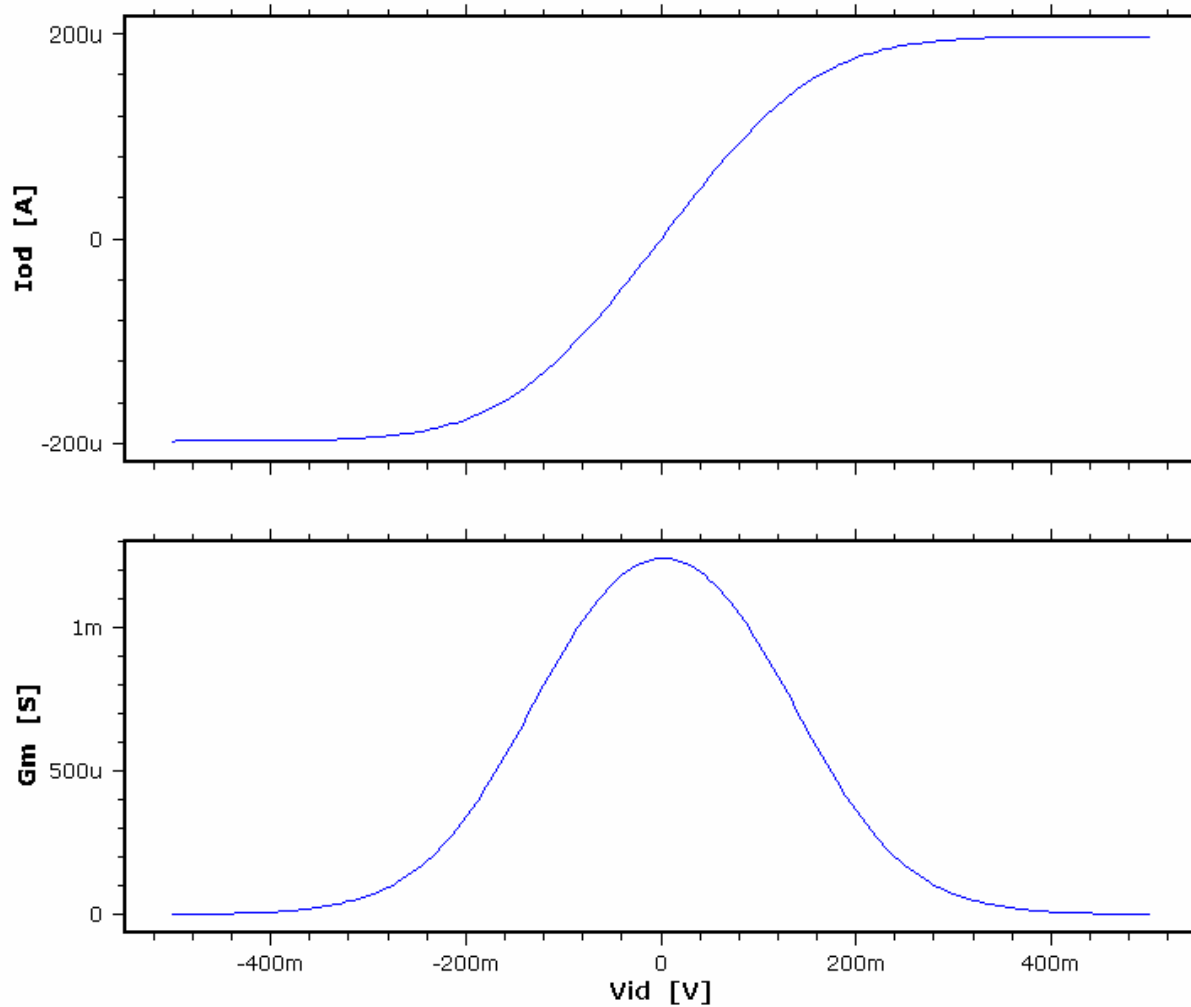

Differential Output Capacitance

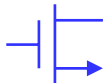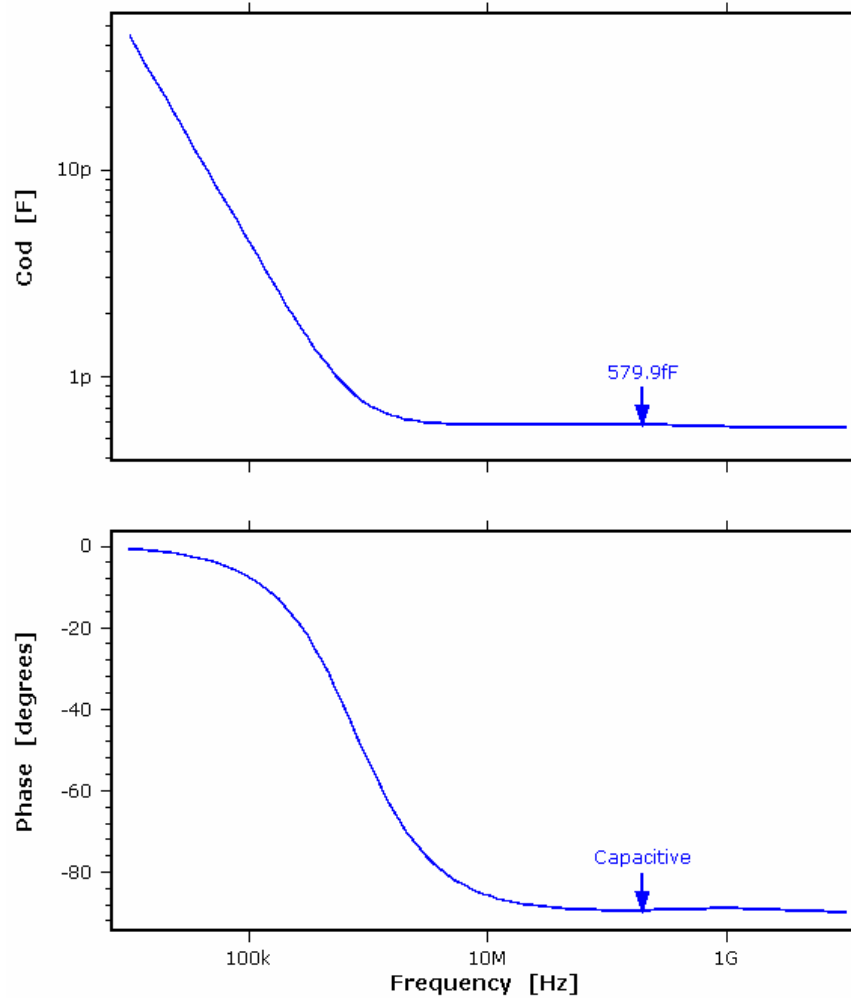


Differential Input Capacitance

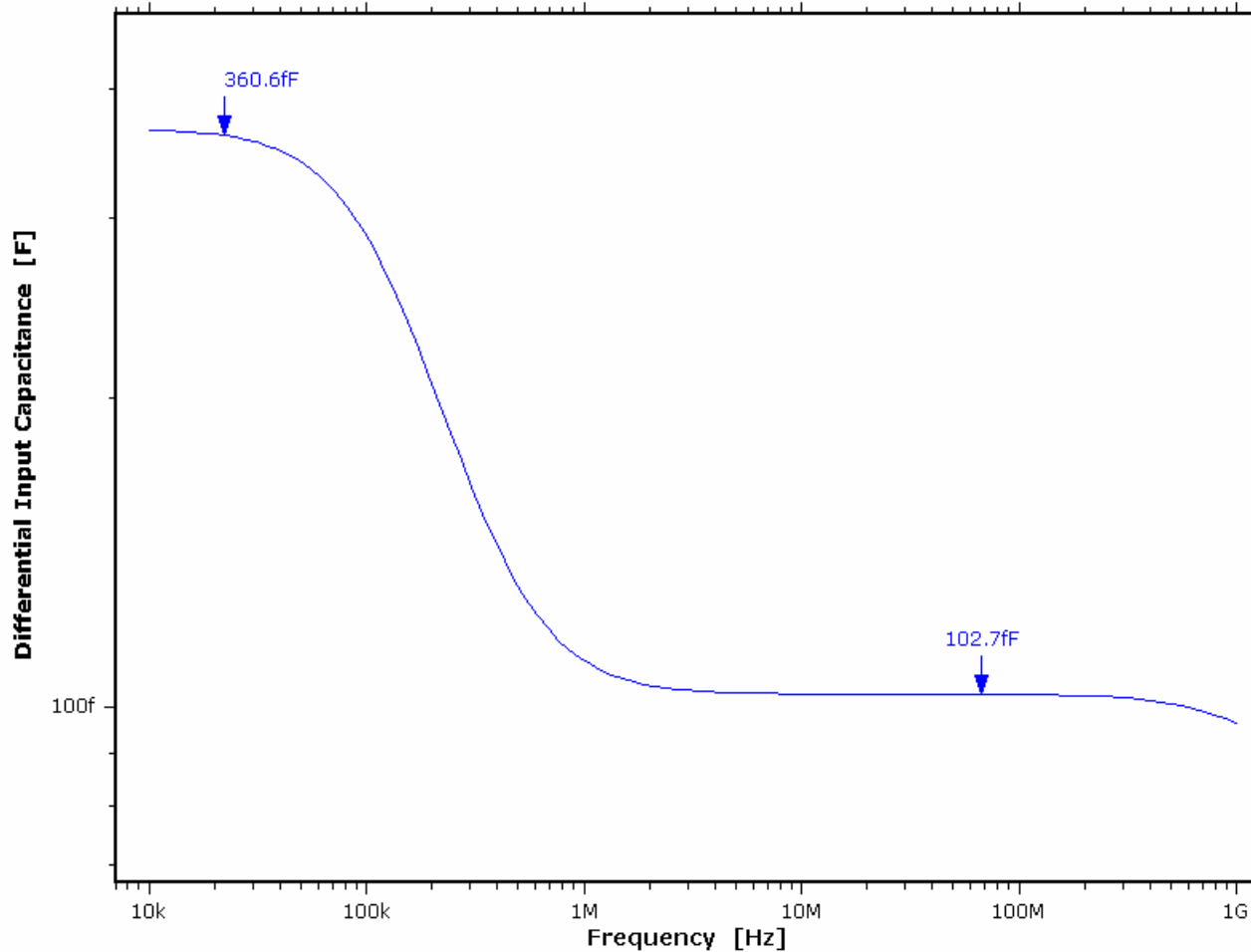


$$\begin{aligned}C_{GS1} &= 2/3 C_{ox} W L \\ &= 117 \text{ fF}\end{aligned}$$

Miller effect significantly increases C_{id} at low frequency

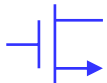Cascoding M1, M2 helps (at the expense of reduced input common-mode range)



Frequency Response (A_{dm})

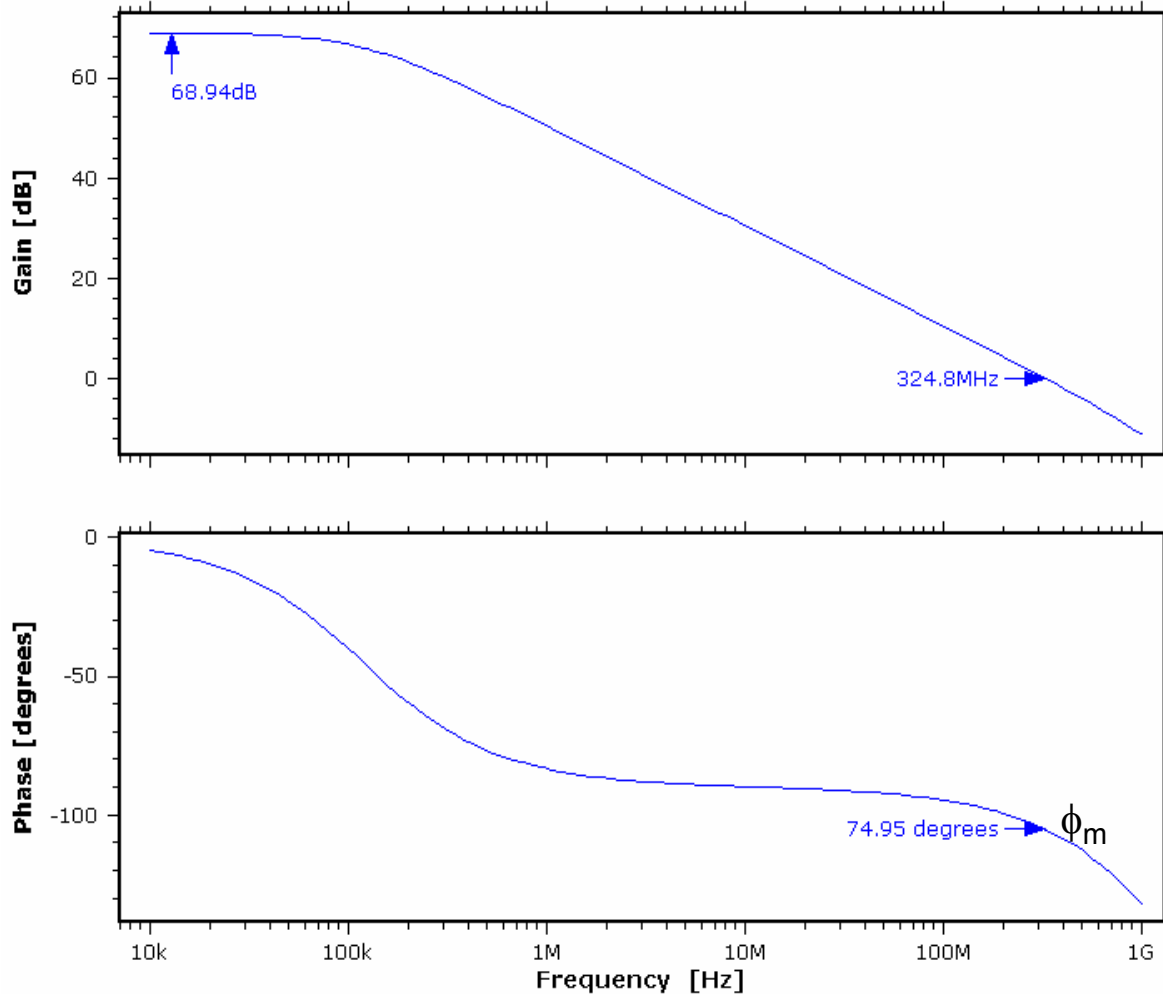

- Bandwidth
 - Strong function of C_L
 - Increasing f_u ?
- Feedback
 - Stability
 - Phase margin
 - Increasing ϕ_m
 - Increasing C_L increases ϕ_m in single-stage amplifier (costly)

