

EECS 240


Analog Integrated Circuits

Topic 13: Two-Stage OTA Design

Ali M. Niknejad and Bernhard E. Boser

© 2006

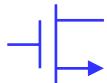Department of Electrical Engineering and Computer Sciences




OTA Realizations

Single stage OTA

- Single high impedance (voltage gain) node
- Near maximum power efficiency
- Limited gain and/or output range
- Can be combined with cascodes, gain boosting
- Examples:
 - Telescopic OTA
 - Maximum power efficiency
 - Limited input common-mode range
 - Folded cascode
 - Large input common-mode range
 - Slightly improved output range
 - Folding adds noise and power penalty

Multi stage OTA

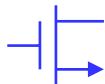- Advantages over single stage OTA
 - Reduced interaction between gain and output range
 - Somewhat higher drive capability for given C_{in}
- Disadvantages
 - Increased power dissipation or reduced speed
 - Need for compensation
- Examples:
 - Miller-compensated 2-stage OTA
 - OTA with preamp (power efficiency?)
 - Nested Miller compensation




Multi-Stage OTAs


- Advantage
 - Higher gain
 - Improved output voltage swing
 - Potentially reduced input capacitance
 - Power dissipation? Noise?
- Challenges
 - Stability: needs compensation (usually)
 - Reduced bandwidth (2 ... 3 times smaller per added stage)
- Approaches
 - 2 high-gain stages with Miller compensation
 - Wide-band preamp (e.g. T. Cho, JSSC 3/95)
 - Nested Miller compensation (e.g. G&M, 4th ed.)




2-Stage OTA Example

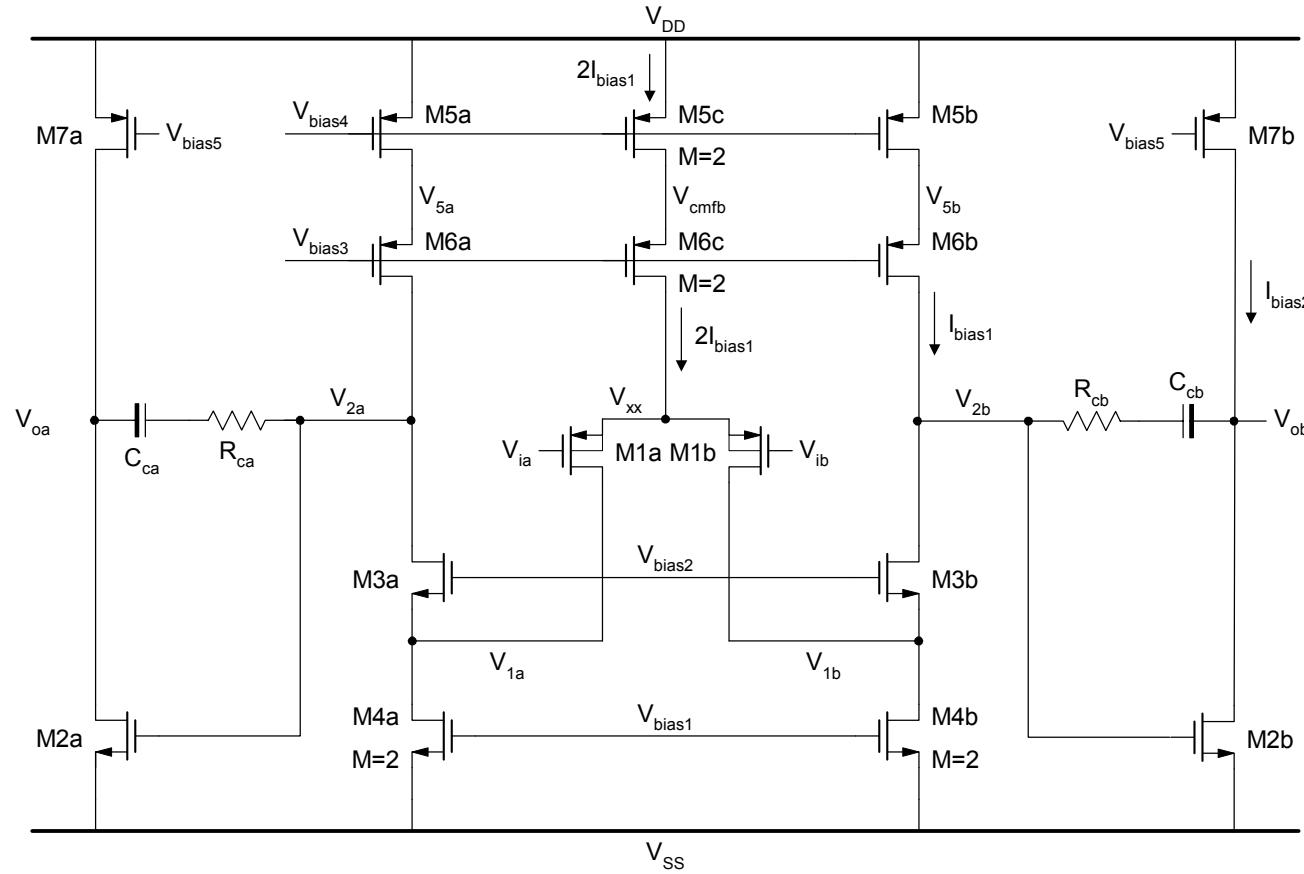


OTA Core

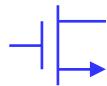

2-Stage CMFB

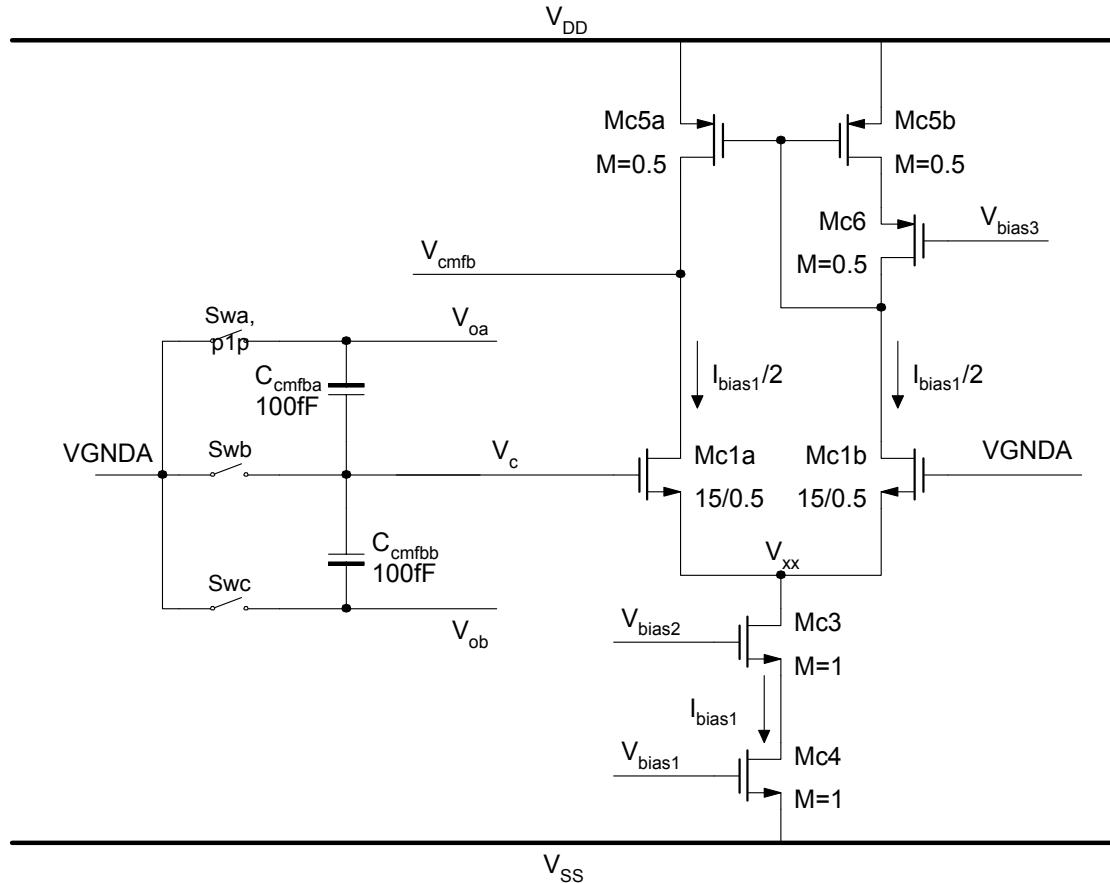


OTA CMFB

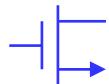

Compensation Techniques

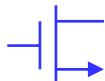- Narrowbanding
 - Very small compensated bandwidth
 - Lower dominant pole or add new dominant pole
 - E.g. offset cancellation loop
- Miller compensation
 - Capacitive feedback splits poles
 - Zero adds phase lag
 - Nulling resistor
 - Cascode compensation




No Compensation

$$p_1 = -\frac{1}{R_1 C_1}$$

$$p_2 = -\frac{1}{R_2 C_2} \quad C_2 = C_L$$

$$a_{v0} = g_{m1} R_1 g_{m2} R_2$$

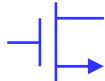
2 dominant poles →
poor phase margin if placed into feedback loop



Miller Compensation

$$p_1 \approx -\frac{1}{(1 + g_{m2}R_2)R_1C_c} \approx -\frac{g_{m1}}{a_{v0}C_c}$$
$$p_2 \approx -\frac{g_{m2}C_c}{C_1C_2 + C_c(C_1 + C_2)}$$
$$\approx -\frac{g_{m2}}{C_2} \quad C_1 \ll C_c, C_2$$
$$z = +\frac{g_{m2}}{C_c}$$
$$a_{v0} = g_{m1}R_1g_{m2}R_2$$

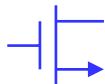- RHP zero
- Caused by capacitive feed-forward
- Often adds significant phase lag (see root locus)



Phase Margin Engineering

$$\omega_u \approx F \frac{g_{m1}}{C_c}$$

$|p_2|, z \gg \omega_u$ of $T(s)$


choose $|p_2| \geq K\omega_u$

$$C_c \geq KFC_2 \frac{g_{m1}}{g_{m2}}$$

$$\frac{z}{\omega_u} = \frac{1}{F} \frac{\underbrace{g_{m2}}_{<1}}{\underbrace{g_{m1}}_{1..10 \text{ (MOS)}}}$$


$$\frac{z}{|p_2|} \approx \frac{C_2}{C_c}$$

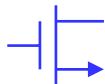- Choose $K > 2$ for reasonable phase margin
- Increasing $C_L = C_2$ *lowers* phase margin
- Zero adds significant phase lag unless $g_{m2} \gg Fg_{m1}$, regardless of C_c




Mitigating Lag from Zero

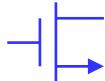- Unilateral Feedback
 - Source Follower
 - Limits output swing
 - Cascode Compensation
 - Ahuja, JSSC 12/1983
 - Ribner, JSSC 12/1984
- Nulling Resistor
 - Zero to infinity
 - Zero cancels p_2




Cascode Compensation (Ahuja)

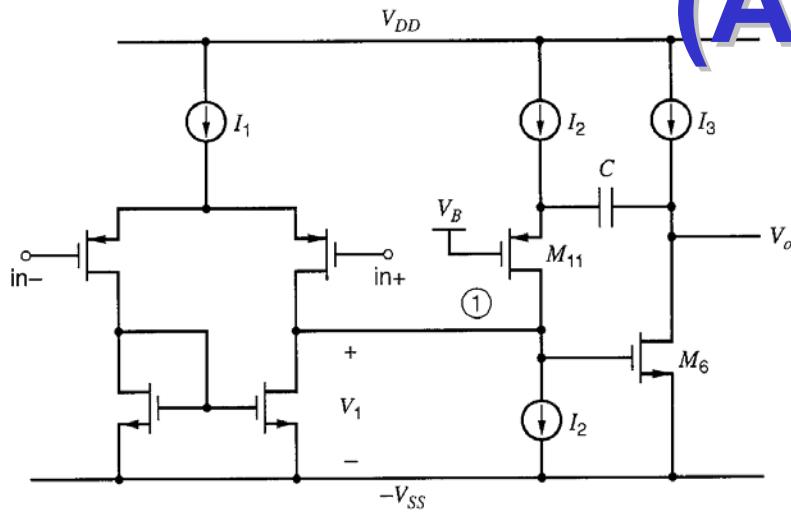

$$p_1 \approx -\frac{1}{(1 + g_{m2}R_2)R_1C_c} \approx -\frac{g_{m1}}{a_{v0}C_c}$$


$$\begin{aligned} p_2 &\approx -\frac{g_{m2}}{C_c + C_2} \frac{C_c}{C_1} \\ &= p_2^* \underbrace{\frac{C_2}{C_c + C_2}}_{\text{usually } >1} \frac{C_c}{C_1} \end{aligned}$$

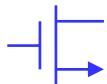- No zero (ideal cascode)
- p_2 at higher frequency
- Translates into smaller C_c for given C_2
- Problems:
 - Current I_2
 - Slewring
 - Mismatch (in I_2) causes offset



Cascode Compensation (Ribner)

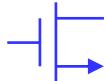- Uses cascode in signal path
- No new current path
- Avoids slewing and matching problem
- 3rd order response
→ very difficult to design



Nulling Resistor R_z

$$z \rightarrow \frac{1}{\left(\frac{1}{g_{m2}} - R_z \right) C_c}$$

p_1, p_2 : no change

$$p_3 \approx -\frac{1}{R_z C_1}$$

- R_z limits feedforward current at high frequency
- Zero moves to higher frequency (and ultimately LHP)
- New pole p_3



Zero to Infinity

$$R_z = \frac{1}{g_{m2}}$$

$z \rightarrow \infty$

$$p_3 \approx -\frac{g_{m2}}{C_1}$$

$$\omega_u \approx F \frac{g_{m1}}{C_c}$$

$$|p_2|, |p_3| \gg \omega_u$$

$$\frac{|p_3|}{\omega_u} = \frac{1}{F} \frac{g_{m2}}{g_{m1}} \frac{C_c}{C_1} \gg \frac{1}{\text{usually}}$$

For $|p_2| \geq K\omega_u$


$$C_c \geq KFC_2 \frac{g_{m1}}{g_{m2}}$$

$$C_2 \leq \frac{C_c}{KF} \frac{g_{m2}}{g_{m1}}$$

- No phase shift from zero

- Phase lag from p_3 decreases as C_c is increased

- Implementation of R_z ?

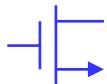

Zero Cancels p₂

$$R_z = \frac{1}{g_{m2}} \left(1 + \frac{C_2}{C_c} \right)$$


$p_3 \approx -\frac{1}{R_z C_1}$ is the new nondominant pole

$$\omega_u \approx F \frac{g_{m1}}{C_c} \quad |p_3| \gg \omega_u$$

For $|p_3| \geq K\omega_u$


$$C_2 \leq \frac{C_c}{KF} \frac{g_{m2}}{g_{m1}} \frac{C_c}{C_1}$$

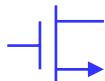- Increased bandwidth
- Smaller C_c for given C₂
- Doublet → not necessarily faster settling



Noise Analysis

Simplified schematic:

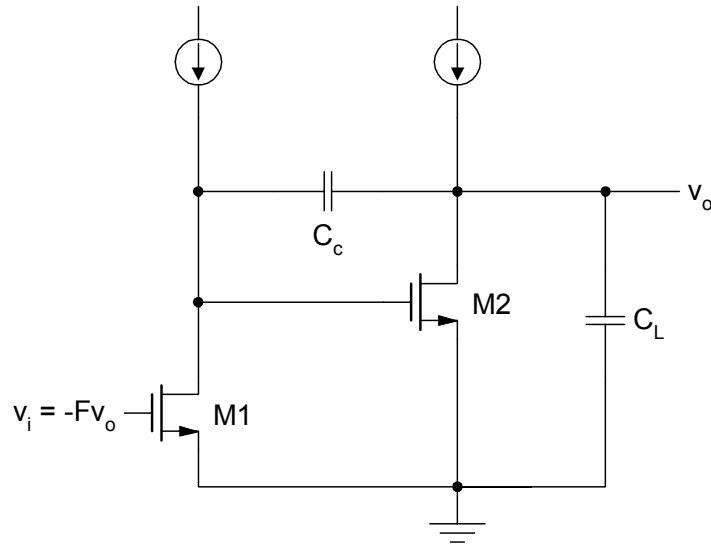

$$sC_c(v_x - v_o) - Fg_{m1}v_o + i_{n1} = 0$$

$$g_{m2}v_x + v_o s(C_L + C_c) + i_{n2} = 0$$


ERROR: 2nd Equation misses $v_x C_c$ term
→

$$v_o = \frac{1}{Fg_{m1}} \frac{1}{1 + \frac{s}{\omega_o Q} + \frac{s^2}{\omega_o^2}} \left(i_{n1} - i_{n2} \frac{sC_c}{g_{m2}} \right)$$

with

$$\omega_o^2 = \frac{Fg_{m1}g_{m2}}{C_c(C_c + C_L)}$$


$$\omega_o Q = \frac{Fg_{m1}}{C_c}$$

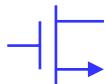

Total Noise at Output

$$\overline{v_{oT}^2} = \frac{k_B T}{C_c} \frac{\gamma}{F} \left(1 + \frac{FC_c}{\underbrace{C_c + C_L}_{<1 \text{ (noise from M2)}}} \right)$$

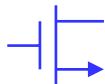- Noise from first stage dominates
- Noise capacitor: C_c , NOT C_L !



Nested Miller Compensation

- >2 gain stages
- Higher order response presents design challenge
- Not (yet?) used much

Ref: R. G. H. Eschauzier and J. H. Huijsing. *Frequency Compensation Techniques for Low-Power Operational Amplifiers*. Kluwer, 1995.

J. Huijsing. *Operational Amplifiers, Theory and Design*. Kluwer, 2001.

